

## Chapter 2 Instructor Notes

Chapter 2 develops the foundations for the first part of the book. Coverage of the entire Chapter would be typical in an introductory course. The first four sections provide the basic definitions and cover Kirchoff's Laws and the passive sign convention; the box *Focus on Methodology: The Passive Sign Convention* (p. 35) and two examples illustrate the latter topic. The sidebars *Make The Connection: Mechanical Analog of Voltage Sources* (p. 20) and *Make The Connection: Hydraulic Analog of Current Sources* (p. 22) present the concept of analogies between electrical and other physical domains; these analogies will continue through the first six chapters.

Sections 2.5 and 2.6 introduce the  $i$ - $v$  characteristic and the resistance element. Tables 2.1 and 2.2 on p. 41 summarize the resistivity of common materials and standard resistor values; Table 2.3 on p. 44 provides the resistance of copper wire for various gauges. The sidebar *Make The Connection: Electric Circuit Analog of Hydraulic Systems – Fluid Resistance* (p. 40) continues the electric-hydraulic system analogy.

Finally, Sections 2.7 and 2.8 introduce some basic but important concepts related to ideal and non-ideal current sources, and measuring instruments.

The Instructor will find that although the material in Chapter 2 is quite basic, it is possible to give an applied flavor to the subject matter by emphasizing a few selected topics in the examples presented in class. In particular, a lecture could be devoted to *resistance devices*, including the resistive displacement transducer of *Focus on Measurements: Resistive throttle position sensor* (pp. 52-54), the resistance strain gauges of *Focus on Measurements: Resistance strain gauges* (pp. 54-55), and *Focus on Measurements: The Wheatstone bridge and force measurements* (pp. 55-56). The instructor wishing to gain a more in-depth understanding of resistance strain gauges will find a detailed analysis in<sup>1</sup>.

Early motivation for the application of circuit analysis to problems of practical interest to the non-electrical engineer can be found in the *Focus on Measurements: The Wheatstone bridge and force measurements*. The Wheatstone bridge material can also serve as an introduction to a laboratory experiment on strain gauges and the measurement of force (see, for example<sup>2</sup>). Finally, the material on practical measuring instruments in Section 2.8b can also motivate a number of useful examples.

The homework problems include a variety of practical examples, with emphasis on instrumentation. Problem 2.36 illustrates analysis related to fuses; problems 2.44-47 are related to wire gauges; problem 2.52 discusses the thermistor; problems 2.54 and 2.55 discuss moving coil meters; problems 2.52 and 2.53 illustrate calculations related to temperature sensors; and problems 2.56-66 present a variety of problems related to practical measuring devices.

It has been the author's experience that providing the students with an early introduction to practical applications of electrical engineering to their own disciplines can increase the interest level in the course significantly.

### Learning Objectives

1. Identify the principal *elements of electrical circuits*: nodes, loops, meshes, branches, and voltage and current sources.
2. Apply *Kirchhoff's Laws* to simple electrical circuits and derive the basic circuit equations.
3. Apply the *passive sign convention* and *compute power* dissipated by circuit elements.
4. Apply the *voltage and current divider laws* to calculate unknown variables in simple series, parallel and series-parallel circuits.
5. Understand the rules for connecting *electrical measuring instruments* to electrical circuits for the measurement of voltage, current, and power.

<sup>1</sup> E. O. Doebelin, *Measurement Systems – Application and Design*, 4<sup>th</sup> Edition, McGraw-Hill, New York, 1990.

<sup>2</sup> G. Rizzoni, *A Practical Introduction to Electronic Instrumentation*, 3<sup>rd</sup> Edition, Kendall-Hunt, 1998.

## Section 2.1: Definitions

### Problem 2.1

#### Solution:

##### Known quantities:

Initial Coulombic potential energy,  $V_i = 17 \text{ kJ} / \text{C}$  ; initial velocity,  $U_i = 93 \text{ M} \frac{\text{m}}{\text{s}}$  ; final Coulombic potential energy,  $V_f = 6 \text{ kJ} / \text{C}$  .

##### Find:

The change in velocity of the electron.

##### Assumptions:

$$\Delta PE_g \ll \Delta PE_c$$

##### Analysis:

Using the first law of thermodynamics, we obtain the final velocity of the electron:

$$Q_{\text{heat}} - W = \Delta KE + \Delta PE_c + \Delta PE_g + \dots$$

Heat is not applicable to a single particle.  $W=0$  since no external forces are applied.

$$\Delta KE = -\Delta PE_c$$

$$\frac{1}{2} m_e (U_f^2 - U_i^2) = -Q_e (V_f - V_i)$$

$$U_f^2 = U_i^2 - \frac{2Q_e}{m_e} (V_f - V_i)$$

$$= \left( 93 \text{ M} \frac{\text{m}}{\text{s}} \right)^2 - \frac{2(-1.6 \times 10^{-19} \text{ C})}{9.11 \times 10^{-37} \text{ g}} (6 \text{ kV} - 17 \text{ kV})$$

$$= 8.649 \times 10^{15} \frac{\text{m}^2}{\text{s}^2} - 3.864 \times 10^{15} \frac{\text{m}^2}{\text{s}^2}$$

$$U_f = 6.917 \times 10^7 \frac{\text{m}}{\text{s}}$$

$$|U_f - U_i| = 93 \text{ M} \frac{\text{m}}{\text{s}} - 69.17 \text{ M} \frac{\text{m}}{\text{s}} = 23.83 \text{ M} \frac{\text{m}}{\text{s}}.$$

### Problem 2.2

#### Solution:

##### Known quantities:

MKSQ units.

##### Find:

Equivalent units of volt, ampere and ohm.

**Analysis:**

$$\text{Voltage} = \text{Volt} = \frac{\text{Joule}}{\text{Coulomb}} \quad V = \frac{J}{C}$$

$$\text{Current} = \text{Ampere} = \frac{\text{Coulomb}}{\text{second}} \quad a = \frac{C}{s}$$

$$\text{Resistance} = \text{Ohm} = \frac{\text{Volt}}{\text{Ampere}} = \frac{\text{Joule} \times \text{second}}{\text{Coulomb}^2} \quad \Omega = \frac{J \cdot s}{C^2}$$

$$\text{Conductance} = \text{Siemen or Mho} = \frac{\text{Ampere}}{\text{Volt}} = \frac{C^2}{J \cdot s}$$

**Problem 2.3****Solution:****Known quantities:**

Battery nominal rate of 100 A-h.

**Find:**

- a) Charge potentially derived from the battery
- b) Electrons contained in that charge.

**Assumptions:**

Battery fully charged.

**Analysis:**

a)

$$\begin{aligned} 100 \text{ A} \times 1 \text{ hr} &= \left( 100 \frac{\text{C}}{\text{s}} \right) (1 \text{ hr}) \left( 3600 \frac{\text{s}}{\text{hr}} \right) \\ &= 360000 \text{ C} \end{aligned}$$

b)

$$\text{charge on electron: } -1.602 \times 10^{-19} \text{ C}$$

no. of electrons =

$$\frac{360 \times 10^3 \text{ C}}{1.602 \times 10^{-19} \text{ C}} = 224.7 \times 10^{22}$$

**Problem 2.4****Solution:****Known quantities:**

Two-rate charge cycle shown in Figure P2.4.

**Find:**

- a) The charge transferred to the battery
- b) The energy transferred to the battery.

**Analysis:**

a) To find the charge delivered to the battery during the charge cycle, we examine the charge-current relationship:

$$i = \frac{dq}{dt} \quad \text{or} \quad dq = i \cdot dt$$

thus:

$$Q = \int_{t_0}^{t_1} i(t) dt$$

$$\begin{aligned} Q &= \int_0^{5\text{hrs}} 50\text{mA} dt + \int_{5\text{hrs}}^{10\text{hrs}} 20\text{mA} dt \\ &= \int_0^{8000\text{s}} 0.05 dt + \int_{8000}^{36000\text{s}} 0.02 dt \\ &= 900 + 360 \\ &= 1260\text{C} \end{aligned}$$

b) To find the energy transferred to the battery, we examine the energy relationship

$$p = \frac{dw}{dt} \quad \text{or} \quad dw = p(t) dt$$

$$w = \int_0^{t_1} p(t) dt = \int_0^{t_1} v(t) i(t) dt$$

observing that the energy delivered to the battery is the integral of the power over the charge cycle. Thus,

$$\begin{aligned} w &= \int_0^{18000} 0.05 \left( 1 + \frac{0.75t}{18000} \right) dt + \int_{18000}^{36000} 0.02 \left( 1 + \frac{0.25t}{18000} \right) dt \\ &= \left( 0.05t + \frac{0.75}{36000} t^2 \right) \Big|_0^{18000} + \left( 0.02t + \frac{0.25}{36000} t^2 \right) \Big|_{18000}^{36000} \end{aligned}$$

$w = 1732.5 \text{ J}$

## Problem 2.5

**Solution:****Known quantities:**

Rated voltage of the battery; rated capacity of the battery.

**Find:**

- a) The rated chemical energy stored in the battery
- b) The total charge that can be supplied at the rated voltage.

**Analysis:**

a)

$$\Delta V \equiv \frac{\Delta PE_c}{\Delta Q} \quad I = \frac{\Delta Q}{\Delta t}$$

$$\text{Chemical energy} = \Delta PE_c$$

$$= \Delta V \cdot \Delta Q$$

$$= \Delta V \cdot (I \cdot \Delta t)$$

$$= 12 \text{ V} \cdot 350 \text{ A} \cdot \text{hr} \cdot 3600 \frac{\text{s}}{\text{hr}}$$

$$= 15.12 \text{ MJ}.$$

As the battery discharges, the voltage will decrease below the rated voltage. The remaining chemical energy stored in the battery is less useful or not useful.

b)  $\Delta Q$  is the total charge passing through the battery and gaining 12 J/C of electrical energy.

$$\Delta Q = I \cdot \Delta t = 350 \text{ A} \cdot \text{hr} = 350 \frac{\text{C}}{\text{s}} \cdot \text{hr} \cdot 3600 \frac{\text{s}}{\text{hr}}$$

$$= 1.26 \text{ MC}.$$

**Problem 2.6****Solution:****Known quantities:**

Resistance of external circuit.

**Find:**

- a) Current supplied by an ideal voltage source
- b) Voltage supplied by an ideal current source.

**Assumptions:**

Ideal voltage and current sources.

**Analysis:**

a) An ideal voltage source produces a constant voltage at or below its rated current. Current is determined by the power required by the external circuit (modeled as R).

$$I = \frac{V_s}{R} \quad P = V_s \cdot I$$

b) An ideal current source produces a constant current at or below its rated voltage. Voltage is determined by the power demanded by the external circuit (modeled as R).

$$V = I_s \cdot R \quad P = V \cdot I_s$$

A real source will overheat and, perhaps, burn up if its rated power is exceeded.

**Sections 2.2, 2.3: KCL, KVL****Problem 2.7****Solution:****Known quantities:**

Circuit shown in Figure P2.7 with currents  $I_0 = -2$  A,  $I_1 = -4$  A,  $I_s = 8$  A, and voltage source  $V_s = 12$  V.

**Find:**

The unknown currents.

**Analysis:**

Applying KCL to node (a) and node (b):

$$\begin{cases} I_0 + I_1 + I_2 = 0 \\ I_0 + I_s + I_1 - I_3 = 0 \end{cases} \Rightarrow \begin{cases} I_2 = -(I_0 + I_1) = 6 \text{ A} \\ I_3 = I_0 + I_s + I_1 = 2 \text{ A} \end{cases}$$

---

## Section 2.4: Sign Convention

### Focus on Methodology: Passive Sign Convention

1. Choose an arbitrary direction of current flow.
2. Label polarities of all active elements (current and voltage sources).
3. Assign polarities to all passive elements (resistors and other loads); for passive elements, current always flows into the positive terminal.
4. Compute the power dissipated by each element according to the following rule: If positive current flows into the positive terminal of an element, then the power dissipated is positive (i.e., the element absorbs power); if the current leaves the positive terminal of an element, then the power dissipated is negative (i.e., the element delivers power).

### Problem 2.8

#### Solution:

##### Known quantities:

Direction and magnitude of the current through the elements in Figure P2.8; voltage at the terminals.

##### Find:

Class of the components A and B.

##### Analysis:

The current enters the negative terminal of element B and leaves the positive terminal: its coulombic potential energy increases.

Element B is a power source. It must be either a voltage source or a current source.

The reverse is true for element A. The current loses energy as it flows through element A.

Element A could be 1. a resistor or 2. a power source through which current is being forced to flow 'backwards'.

### Problem 2.9

#### Solution:

##### Known quantities:

Current absorbed by the heater; voltage at which the current is supplied; cost of the energy.

##### Find:

- a) Power consumption
- b) Energy dissipated in 24 hr.
- c) Cost of the Energy

##### Assumptions:

The heater works for 24 hours continuously.

##### Analysis:

- a)

$$P = VI = 110 \text{ V} (23 \text{ A}) = 2.53 \text{ K} \frac{\text{J}}{\text{A s}} = 2.53 \text{ KW}$$

b)

$$W = Pt = 2.53 \text{ K} \frac{\text{J}}{\text{s}} 24 \text{ hr} 3600 \frac{\text{s}}{\text{hr}} = 218.6 \text{ MJ}$$

c)

$$\text{Cost} = (\text{Rate})W = 6 \frac{\text{cents}}{\text{KW hr}} (2.53 \text{ KW})(24 \text{ hr}) = 364.3 \text{ cents} = \$3.64$$

## Problem 2.10

### **Solution:**

#### **Known quantities:**

Current through elements A, B and C shown in Figure P2.10; voltage across elements A, B and C.

#### **Find:**

Which components are absorbing power, which are supplying power; verify the conservation of power.

#### **Analysis:**

$$\text{A absorbs } (35 \text{ V})(15 \text{ A}) = 525 \text{ W}$$

$$\text{B absorbs } (15 \text{ V})(15 \text{ A}) = 225 \text{ W}$$

$$\text{C supplies } (50 \text{ V})(15 \text{ A}) = 750 \text{ W}$$

$$\text{Total power supplied} = P_C = 750 \text{ W}$$

$$\text{Total power absorbed} = P_B + P_A = 225 \text{ W} + 525 \text{ W} = 750 \text{ W}$$

Total power supplied = Total power absorbed, so conservation of power is satisfied.

## Problem 2.11

### **Solution:**

#### **Known quantities:**

Circuit shown in Figure P2.11 with voltage source,  $V_s = 12\text{V}$ ; internal resistance of the source,  $R_s = 5\text{k}\Omega$ ; and resistance of the load,  $R_L = 7\text{k}\Omega$ .

#### **Find:**

The terminal voltage of the source; the power supplied to the circuit, the efficiency of the circuit.

#### **Assumptions:**

Assume that the only loss is due to the internal resistance of the source.



**Analysis:**

$$KVL: -V_S + I_T R_S + V_T = 0$$

$$OL: V_T = I_T R_L \quad \therefore I_T = \frac{V_T}{R_L}$$

$$-V_S + \frac{V_T}{R_L} R_S + V_T = 0$$

$$V_T = \frac{V_S}{1 + \frac{R_S}{R_L}} = \frac{12 \text{ V}}{1 + \frac{5 \text{ K}\Omega}{7 \text{ K}\Omega}} = 7 \text{ V} \quad \text{or} \quad VD: V_T = \frac{V_S R_L}{R_S + R_L} = \frac{12 \text{ V} \cdot 7 \text{ K}\Omega}{5 \text{ K}\Omega + 7 \text{ K}\Omega} = 7 \text{ V}.$$

$$P_L = \frac{V_R^2}{R_L} = \frac{V_T^2}{R_L} = \frac{(7 \text{ V})^2}{7 \text{ K}\frac{\text{V}}{\text{A}}} = 7 \text{ mW}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{R_L}}{P_{R_S} + P_{R_L}} = \frac{I_T^2 R_L}{I_T^2 R_S + I_T^2 R_L} = \frac{7 \text{ K}\Omega}{5 \text{ K}\Omega + 7 \text{ K}\Omega} = 0.5833 \quad \text{or} \quad 58.33\%.$$

**Problem 2.12****Solution:****Known quantities:**

Circuit shown in Figure P2.12; Current through elements D and E; voltage across elements B, C and E.

**Find:**

- Which components are absorbing power and which are supplying power
- Verify the conservation of power.

**Analysis:**

a)

By KCL, the current through element B is 5 A, to the right. By KVL,

$$v_D = v_E = 10 \text{ V} \quad (\text{positive at the top})$$

$$v_A + 5 - 10 - 10 = 0$$

Therefore the voltage across element A is

$$v_A = 15 \text{ V} \quad (\text{positive on top})$$

$$\text{A supplies } (15 \text{ V})(5 \text{ A}) = 75 \text{ W}$$

$$\text{B supplies } (5 \text{ V})(5 \text{ A}) = 25 \text{ W}$$

$$\text{C absorbs } (10 \text{ V})(5 \text{ A}) = 50 \text{ W}$$

$$\text{D absorbs } (10 \text{ V})(4 \text{ A}) = 40 \text{ W}$$

$$\text{E absorbs } (10 \text{ V})(1 \text{ A}) = 10 \text{ W}$$

b)

$$\text{Total power supplied} = P_A + P_B = 75 \text{ W} + 25 \text{ W} = 100 \text{ W}$$

Total power absorbed =  $P_C + P_D + P_E = 50 \text{ W} + 40 \text{ W} + 10 \text{ W} = 100 \text{ W}$

Total power supplied = Total power absorbed, so conservation of power is satisfied.

## Problem 2.13

### **Solution:**

#### **Known quantities:**

Headlights connected in parallel to a 24-V automotive battery; power absorbed by each headlight.

#### **Find:**

Resistance of each headlight; total resistance seen by the battery.

#### **Analysis:**

Headlight no. 1:

$$P = v \times i = 100 \text{ W} = \frac{v^2}{R} \quad \text{or}$$

$$R = \frac{v^2}{100} = \frac{576}{100} = 5.76\Omega$$

Headlight no. 2:

$$P = v \times i = 75 \text{ W} = \frac{v^2}{R} \quad \text{or}$$

$$R = \frac{v^2}{75} = \frac{576}{75} = 7.68\Omega$$

The total resistance is given by the parallel combination:

$$\frac{1}{R_{TOTAL}} = \frac{1}{5.76\Omega} + \frac{1}{7.68\Omega} \quad \text{or} \quad R_{TOTAL} = 3.29 \Omega$$

## Problem 2.14

### **Solution:**

#### **Known quantities:**

Headlights and 24-V automotive battery of problem 2.13 with 2 15-W taillights added in parallel; power absorbed by each headlight; power absorbed by each taillight.

#### **Find:**

Equivalent resistance seen by the battery.

#### **Analysis:**

The resistance corresponding to a 75-W headlight is:

$$R_{75W} = \frac{v^2}{75} = \frac{576}{75} = 7.68\Omega$$

For each 15-W tail light we compute the resistance:

$$R_{15W} = \frac{v^2}{15} = \frac{576}{15} = 38.4\Omega$$

Therefore, the total resistance is computed as:

$$\frac{1}{R_{TOTAL}} = \frac{1}{7.68\Omega} + \frac{1}{7.68\Omega} + \frac{1}{38.4\Omega} + \frac{1}{38.4\Omega} \text{ or } R_{TOTAL} = 3.2\Omega$$

## Problem 2.15

### **Solution:**

#### **Known quantities:**

Circuit shown in Figure P2.15 with voltage source,  $V_s = 20V$  ; and resistor,  $R_o = 5\Omega$ .

#### **Find:**

The power absorbed by variable resistor R (ranging from 0 to 20  $\Omega$ ).

#### **Analysis:**


The current flowing clockwise in the series circuit is:

$$i = \frac{20}{5 + R}$$

The voltage across the variable resistor R, positive on the left, is:

$$v_R = Ri = \frac{20R}{R + 5}$$
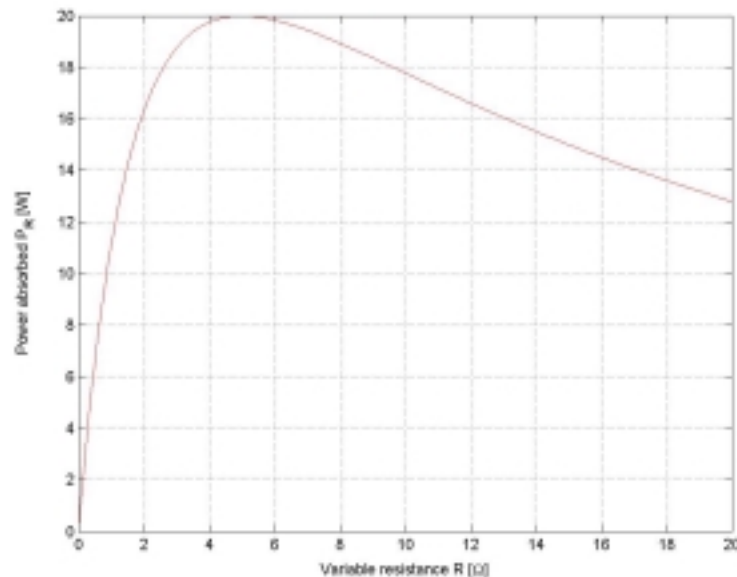
$$\text{Therefore, } P_R = v_R i = \left( \frac{20}{5 + R} \right)^2 R$$



## Problem 2.16

### Solution:

#### Known quantities:

Circuit shown in Figure P2.16 with source voltage,  $V_s = 12V$  ; internal resistance of the source,  $R_s = 0.3\Omega$  . Current,  $I_T = 0, 5, 10, 20, 30$  A.

#### Find:

- The power supplied by the ideal source as a function of current
- The power dissipated by the nonideal source as a function of current
- The power supplied by the source to the circuit
- Plot the terminal voltage and power supplied to the circuit as a function of current

#### Assumptions:

There are no other losses except that on  $R_s$ .

#### Analysis:

a)  $P_s$  = power supplied by the source  $= V_s I_s = V_s I_T$  .

b)  $R_s$  = equivalent resistance for internal losses

$$P_{loss} = I_T^2 R_s$$

c)  $V_T$  = voltage at the battery terminals:



$$VD: V_T = V_s - R_s I_T$$

$P_0$  = power supplied to the circuit ( $R_L$  in this case)  $= I_T V_T$  .

Conservation of energy:

$$P_s = P_{loss} + P_0 .$$

$I_T (A)$	$P_s (W)$	$P_{loss} (W)$	$V_T (V)$	$P_0 (W)$
0	0	0	0	0
2	30	1.875	11.4	28.13
5	60	7.5	10.5	52.5
10	120	30	9	90
20	240	120	6	120
30	360	270	3	90

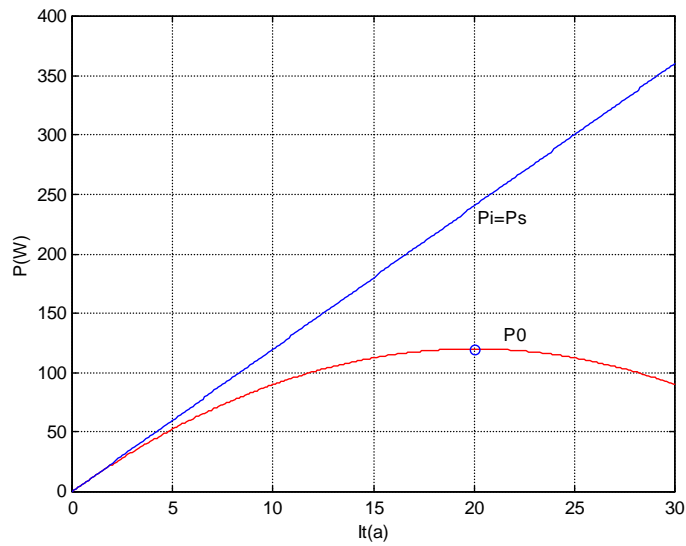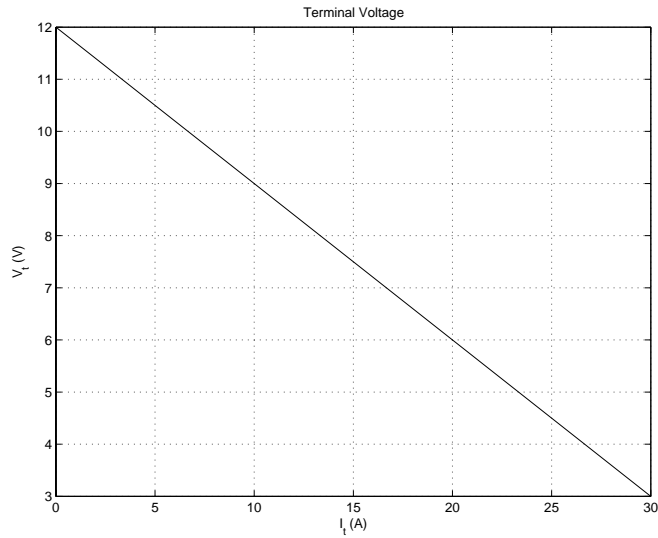

Note that the power supplied to the circuit is maximum when  $I_T = 20a$ .

$$R_L = \frac{P_0}{I_T^2} = \frac{120 Va}{(20 a)^2} = 30 m \frac{V}{a} = 30 m\Omega$$

$$R_S = \frac{P_{loss}}{I_T^2} = \frac{120 Va}{(20 a)^2} = 30 m\Omega$$

$$R_L = R_S$$

## Problem 2.17

### Solution:

#### Known quantities:

Circuit shown in Figure P2.17 if the power delivered by the source is 40 mW; the voltage  $v = v_1/4$ ; and  $R_1 = 8k\Omega$ ,  $R_2 = 10k\Omega$ ,  $R_3 = 12k\Omega$

#### Find:

The resistance  $R$ , the current  $i$  and the two voltages  $v$  and  $v_1$

#### Analysis:

$$P = v \cdot i = 40 \text{ mW} \quad (\text{eq. 1})$$

$$v_1 = R_2 \cdot i = 10000 \cdot i = \frac{v}{4} \quad (\text{eq. 2})$$

From eq.1 and eq.2, we obtain:

$$i = 1.0 \text{ mA} \quad \text{and} \quad v = 40 \text{ V}.$$

Applying KVL for the loop:

$$-v + 8000i + 10000i + Ri + 12000i = 0 \quad \text{or,} \quad 0.001R = 10$$

Therefore,

$$R = 10k\Omega \quad \text{and} \quad v_1 = 10V.$$

## Problem 2.18

### Solution:

#### Known quantities:

Rated power; rated optical power; operating life; rated operating voltage; open-circuit resistance of the filament.

#### Find:

- The resistance of the filament in operation
- The efficiency of the bulb.

#### Analysis:

a)

$$P = VI \quad \therefore I = \frac{P_R}{V_R} = \frac{60 \text{ W}}{115 \text{ V}} = 521.7 \text{ mA}$$

$$\text{OL: } R = \frac{V}{I} = \frac{V_R}{I} = \frac{115 \text{ V}}{521.7 \text{ mA}} = 220.4 \Omega$$

b)

Efficiency is defined as the ratio of the useful power dissipated by or supplied by the load to the total power supplied by the source. In this case, the useful power supplied by the load is the optical power. From any handbook containing equivalent units: 680 lumens=1 W

$$P_{o,out} = \text{Optical Power Out} = 820 \text{ lum} \frac{W}{680 \text{ lum}} = 1.206 W$$

$$\eta = \text{efficiency} = \frac{P_{o,out}}{P_R} = \frac{1.206 W}{60 W} = 0.02009 = 2.009 \% .$$

## Problem 2.19

### Solution:

#### Known quantities:

Rated power; rated voltage of a light bulb.

#### Find:

The power dissipated by a series of three light bulbs connected to the nominal voltage.

#### Assumptions:

The resistance of each bulb doesn't vary when connected in series.

#### Analysis:

When connected in series, the voltage of the source will divide equally across the three bulbs. The across each bulb will be 1/3 what it was when the bulbs were connected individually across the source. Power dissipated in a resistance is a function of the voltage squared, so the power dissipated in each bulb when connected in series will be 1/9 what it was when the bulbs were connected individually, or 11.11 W:

$$\text{Ohm's Law: } P = IV_B = I^2 R_B = \frac{V_B^2}{R_B}$$

$$V_B = V_S = 110 V$$

$$R_B = \frac{V_B^2}{P} = \frac{(110 V)^2}{100 W} = 121 \Omega$$

Connected in series and assuming the resistance of each bulb remains the same as when connected individually:

$$\text{KVL: } -V_S + V_{B1} + V_{B2} + V_{B3} = 0$$

$$\text{OL: } -V_S + IR_{B3} + IR_{B2} + IR_{B1} = 0$$

$$I = \frac{V_S}{R_{B1} + R_{B2} + R_{B3}} = \frac{110 V}{121 + 121 + 121 \frac{V}{a}} = 303 ma$$

$$P_{B1} = I^2 R_{B1} = (303 ma)^2 \left( 121 \frac{V}{a} \right) = 11.11 W = \frac{1}{9} 100 W.$$

## Problem 2.20

### Solution:

#### Known quantities:

Rated power and rated voltage of the two light bulbs.

**Find:**

The power dissipated by the series of the two light bulbs.

**Assumptions:**

The resistance of each bulb doesn't vary when connected in series.

**Analysis:**

When connected in series, the voltage of the source will divide equally across the three bulbs. The across each bulb will be 1/3 what it was when the bulbs were connected individually across the source. Power dissipated in a resistance is a function of the voltage squared, so the power dissipated in each bulb when connected in series will be 1/9 what it was when the bulbs were connected individually, or 11.11 W:

$$\text{Ohm's Law: } P = IV_B = I^2 R_B = \frac{V_B^2}{R_B}$$

$$V_B = V_S = 110 \text{ V}$$

$$R_{60} = \frac{V_B^2}{P_{60}} = \frac{(110 \text{ V})^2}{60 \text{ W}} = 201.7 \Omega$$

$$R_{100} = \frac{V_B^2}{P_{100}} = \frac{(110 \text{ V})^2}{100 \text{ W}} = 121 \Omega$$

When connected in series and assuming the resistance of each bulb remains the same as when connected individually:

$$\text{KVL: } -V_S + V_{B60} + V_{B100} = 0$$

$$\text{OL: } -V_S + IR_{B60} + IR_{B100} = 0$$

$$I = \frac{V_S}{R_{B60} + R_{B100}} = \frac{110 \text{ V}}{201.7 + 121 \frac{\text{V}}{\text{A}}} = 340.9 \text{ mA}$$

$$P_{B60} = I^2 R_{B60} = (340.9 \text{ mA})^2 \left( 201.7 \frac{\text{V}}{\text{A}} \right) = 23.44 \text{ W}$$

$$P_{B100} = I^2 R_{B100} = (340.9 \text{ mA})^2 \left( 121 \frac{\text{V}}{\text{A}} \right) = 14.06 \text{ W}$$

Notes: 1. It's strange but it's true that a 60 W bulb connected in series with a 100 W bulb will dissipate more power than the 100 W bulb. 2. If the power dissipated by the filament in a bulb decreases, the temperature at which the filament operates and therefore its resistance will decrease. This made the assumption about the resistance necessary.

## Problem 2.21

**Solution:****Known quantities:**

Schematic of the circuit shown in Figure P2.21.

**Find:**

The resistor values, including the power rating, necessary to achieve the indicated voltages for:

a)  $V = 30\text{V}, R_1 = 10\text{k}\Omega, v_{out} = 10\text{V}$



b)  $V = 12V, R_1 = 140k\Omega, v_{out} = 8.5V$

**Assumptions:**

Resistors are available in  $\frac{1}{8}$  -  $\frac{1}{4}$  -  $\frac{1}{2}$  -, and 1-W ratings.

**Analysis:**

(a)

$$v_{out} = \left( \frac{R_2}{R_2 + R_1} \right) \cdot V = \frac{R_2}{R_2 + 10000} \cdot (30) = 10$$

$$R_2(30 - 10) = 10 \cdot 10 \cdot 10^3$$

$$R_2 = 5 k\Omega$$

$$P_2 = I^2 R = \left( \frac{30}{15000} \right)^2 \cdot (5000) = 20 mW$$

$$P_{R_2} = \frac{1}{8} W$$

$$P_1 = I^2 R_1 = 40 mW$$

$$P_{R_1} = \frac{1}{8} W.$$

(b)

$$v_{out} = \left( \frac{R_2}{R_2 + R_1} \right) \cdot V = 12 \cdot \left( \frac{140}{140 + R_1} \right) = 8.5$$

$$R_1 = 57\Omega$$

$$I = \frac{V}{R_1 + R_2} = \frac{12 V}{57 \Omega + 140 \Omega} = 61 ma \Rightarrow P_1 = I^2 R_1 = 212.1 mW$$

$$P_2 = I^2 R_2 = 520.9 mW$$

$$P_{R_1} = \frac{1}{4} W$$

$$P_{R_2} = 1 W$$

**Problem 2.22****Solution:****Known quantities:**

Schematic of the circuit shown in Figure P2.22 with resistances,  $R_o = 1.6k\Omega, R_2 = 4.3k\Omega$  ; and voltages,  $V = 110V, v_{out} = 64.3V$  .

**Find:**

The resistor values, including the power rating, necessary to achieve the indicated voltages.

**Assumptions:**

Resistors are available in  $\frac{1}{8}$  -  $\frac{1}{4}$  -  $\frac{1}{2}$ -, and 1-W ratings.

**Analysis:**

$$v_{out} = \frac{R_2}{R_0 + R_1 + R_2} V = 110 \cdot \left( \frac{4300}{1600 + R_1 + 4300} \right) = 64.3$$

$$R_1 = 1.45 k\Omega$$

$$I = \frac{V}{R_0 + R_1 + R_2} = \frac{110 \text{ V}}{1600 \Omega + 1450 \Omega + 4300 \Omega} = 15 \text{ ma}$$

$$P_0 = I^2 R_0 = 360 \text{ mW} \Rightarrow P_{R_0} = \frac{1}{2} \text{ W}$$

$$P_1 = I^2 R_1 = 326.25 \text{ mW} \Rightarrow P_{R_1} = \frac{1}{2} \text{ W}$$

$$P_2 = I^2 R_2 = 967.5 \text{ mW} \Rightarrow P_{R_2} = 1 \text{ W}$$

**Problem 2.23****Solution:****Known quantities:**

Schematic of the circuit shown in Figure P2.23 with source voltage,  $v = 24\text{V}$  ; and resistances,  $R_0 = 8\Omega$ ,  $R_1 = 10\Omega$ ,  $R_2 = 2\Omega$  .

**Find:**

- The equivalent resistance seen by the source
- The current  $i$
- The power delivered by the source
- The voltages  $v_1$  and  $v_2$
- The minimum power rating required for  $R_1$

**Analysis:**

- a) The equivalent resistance seen by the source is

$$R_{eq} = R_0 + R_1 + R_2 = 8 + 10 + 2 = 20\Omega$$

- b) Applying KVL:

$$V - R_{eq} i = 0, \text{ therefore } i = \frac{V}{R_{eq}} = \frac{24\text{V}}{20\Omega} = 1.2\text{A}$$

- c)

$$P_{source} = Vi = 24\text{V} \cdot 1.2\text{A} = 28.8 \text{ W}$$

- d) Applying Ohm's law:

$$v_1 = R_1 i = 10\Omega \cdot 1.2\text{A} = 12 \text{ V}, \text{ and } v_2 = R_2 i = 2\Omega \cdot 1.2\text{A} = 2.4 \text{ V}$$

- e)

$$P_1 = R_1 i^2 = 10\Omega \cdot (1.2\text{A})^2 = 14.4 \text{ W}, \text{ therefore the minimum power rating for } R_1 \text{ is } 16 \text{ W}.$$

## Problem 2.24

### Solution:

#### Known quantities:

Schematic of the circuit shown in Figure P2.24 with resistors,

$$R_1 = 25\Omega, R_2 = 10\Omega, R_3 = 5\Omega, R_4 = 7\Omega.$$

#### Find:

- The currents  $i_1$  and  $i_2$
- The power delivered by the 3-A current source and the 12-V voltage source
- The total power dissipated by the circuit.

#### Analysis:

- a) KCL at node 1 requires that:

$$\frac{v_1}{R_2} + \frac{v_1 - 12 \text{ V}}{R_3} - 3 \text{ A} = 0$$

Solving for  $v_1$  we have

$$v_1 = 3 \frac{(4 + R_3)R_2}{R_2 + R_3} = 18 \text{ V}$$

Therefore,

$$i_1 = -\frac{v_1}{R_2} = -\frac{18}{10} = -1.8 \text{ A}$$

$$i_2 = \frac{12 - v_1}{R_3} = -\frac{6}{5} = -1.2 \text{ A}$$

- b) The power delivered by the 3-A source is:

$$P_{3\text{-A}} = (v_{3\text{-A}})(3)$$

Thus, we can compute the voltage across the 3-A source as

$$v_{3\text{-A}} = 3R_1 + v_1 = 3 \cdot 25 + 18 = 93 \text{ V}$$

Thus,

$$P_{3\text{-A}} = (93)(3) = 279 \text{ W}.$$

Similarly, the power supplied by the 12-V source is:

$$P_{12\text{-V}} = (12)(I_{12\text{-V}})$$

We have  $I_{12\text{-V}} = \frac{12}{R_4} + i_2 = 514.3 \text{ mA}$ , thus:

$$P_{12\text{-V}} = (12)(I_{12\text{-V}}) = 6.17 \text{ W}$$

- c) Since the power dissipated equals the total power supplied:

$$P_{\text{diss}} = P_{3-A} + P_{12-V} = 279 + 6.17 = 285.17 \text{ W}$$

## Problem 2.25

### Solution:

#### Known quantities:

Schematic of the circuit shown in Figure P2.25.

#### Find:

The power delivered by the dependent source.

#### Analysis:

$$i = \frac{24V}{(7+5)\Omega} = \frac{24}{12} \text{ A} = 2 \text{ A}$$

$$i_{\text{source}} = 0.5i^2 = 0.5 \cdot (4) = 2 \text{ A}$$

The voltage across the dependent source (+ ref. taken at the top) can be found by KVL:

$$-v_D + (2A)(15\Omega) + 24V = 0 \Rightarrow v_D = 54 \text{ V}$$

Therefore, the power delivered by the dependent source is

$$P_D = v_D i_{\text{source}} = 54 \cdot 2 = 108 \text{ W}.$$

## Problem 2.26

### Solution:

#### Known quantities:

Schematic of the circuit in Figure P2.26.

#### Find:

- If  $V_1 = 12.0V$ ,  $R_1 = 0.15\Omega$ ,  $R_L = 2.55\Omega$ , the load current and the power dissipated by the load
- If a second battery is connected in parallel with battery 1 with  $V_2 = 12.0V$ ,  $R_2 = 0.28\Omega$ , determine the variations in the load current and in the power dissipated by the load due to the parallel connection with a second battery.

#### Analysis:

a)

$$I_L = \frac{V_1}{R_1 + R_L} = \frac{12}{0.15 + 2.55} = \frac{12}{2.7} = 4.44 \text{ A}$$

$$P_{\text{Load}} = I_L^2 R_L = 50.4 \text{ W}.$$

b) with another source in the circuit we must find the new power dissipated by the load. To do so, we write KVL twice using mesh currents to obtain 2 equations in 2 unknowns:

$$\begin{cases} I_2 R_2 - V_1 + V_2 - I_1 R_1 = 0 \\ (I_1 + I_2) R_L + I_2 R_2 = V_2 \end{cases} \Rightarrow \begin{cases} 0.28 \cdot I_2 - 0.15 \cdot I_1 = 0 \\ 2.55 \cdot (I_1 + I_2) + 0.28 \cdot I_2 = 12 \end{cases}$$

Solving the above equations gives us:

$$I_1 = 2.95 \text{ A}, \quad I_2 = 1.58 \text{ A} \Rightarrow I_L = I_1 + I_2 = 4.53 \text{ A}$$

$$P_{Load} = I_L^2 R_L = 52.33 \text{ W}$$

This is an increase of 1%.

## Problem 2.27

### Solution:

#### Known quantities:

Open-circuit voltage at the terminals of the power source is 50.8 V; voltage drop with a 10-W load attached is to 49 V.

#### Find:

- The voltage and the internal resistance of the source
- The voltage at its terminals with a 15-Ω load resistor attached
- The current that can be derived from the source under short-circuit conditions.

#### Analysis:

(a)

$$\frac{(49V)^2}{R_L} = 10W \Rightarrow R_L = 240\Omega$$

$v_s = 50.8V$ , the open-circuit voltage

$$\frac{R_L}{R_s + R_L} v_s = 49 \Rightarrow \frac{240}{R_s + 240} 50.8 = 49$$

$$R_s = \frac{(240)(50.8)}{49} - 240 = 8.82\Omega$$

(b)

$$v = \frac{R_L}{R_s + R_L} v_s = \frac{15}{8.82 + 15} 50.8 = 32.0V$$

(c)

$$i_{CC}(R_L = 0) = \frac{v_s}{R_s} = \frac{50.8}{8.82} = 5.76 \text{ A}$$

## Problem 2.28

### Solution:

#### Known quantities:

Voltage of the heater, maximum and minimum power dissipation; number of coils, schematics of the configurations.

**Find:**

- a) The resistance of each coil
- b) The power dissipation of each of the other two possible arrangements.

**Analysis:**

(a) For the parallel connection,  $P = 2000$  W. Therefore,

$$\begin{aligned} 2000 &= \frac{(220)^2}{R_1} + \frac{(220)^2}{R_2} \\ &= (220)^2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \end{aligned}$$

or,

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{5}{121}.$$

For the series connection,  $P = 300$  W. Therefore,

$$300 = \frac{(220)^2}{R_1 + R_2}$$

or,

$$\frac{1}{R_1 + R_2} = \frac{3}{484}.$$

Solving, we find that  $R_1 = 131.6\Omega$  and  $R_2 = 29.7\Omega$ .

(b) the power dissipated by  $R_1$  alone is:

$$P_{R_1} = \frac{(220)^2}{R_1} = 368W$$

and the power dissipated by  $R_2$  alone is

$$P_{R_2} = \frac{(220)^2}{R_2} = 1631W.$$

---

## Section 2.5, 2.6: Resistance and Ohm's Law

### Problem 2.29

#### Solution:

##### Known quantities:

Diameter of the cylindrical substrate; length of the substrate; conductivity of the carbon.

##### Find:

The thickness of the carbon film required for a resistance  $R$  of  $33 \text{ K}\Omega$ .

##### Assumptions:

Assume the thickness of the film to be much smaller than the radius  
Neglect the end surface of the cylinder.

##### Analysis:

$$R = \frac{d}{\sigma \cdot A} \cong \frac{d}{\sigma \cdot 2\pi a \cdot \Delta t}$$

$$\Delta t = \frac{d}{R \cdot 2\pi a \cdot \sigma} = \frac{9 \cdot 10^{-3} \text{ m}}{33 \cdot 10^3 \Omega \cdot 2.9 \cdot 10^6 \frac{\text{S}}{\text{m}} \cdot 2\pi \cdot 1 \cdot 10^{-3} \text{ m}}$$


---

### Problem 2.30

#### Solution:

##### Known quantities:

The constants  $A$  and  $k$ ; the open-circuit resistance.

##### Find:

The rated current at which the fuse blows, showing that this happens at:

$$I = \frac{1}{\sqrt{AkR_0}}.$$

##### Assumptions:

Here the resistance of the fuse is given by:

$$R = R_0 [1 + A(T - T_0)]$$

where  $T_0$ , room temperature, is assumed to be  $25^\circ\text{C}$ .

We assume that:

$$T - T_0 = kP$$

where  $P$  is the power dissipated by the resistor (fuse).

##### Analysis:

$$R = R_0 (1 + A \cdot \Delta T) = R_0 (1 + AkP) = R_0 (1 + AkI^2 R)$$

$$R - R_0 AkI^2 R = R_0$$

$$R = \frac{R_0}{1 - R_0 A k I^2} \rightarrow \infty \quad \text{when} \quad I - R_0 A k I^2 \rightarrow 0$$

$$I = \frac{1}{\sqrt{A k R_0}} = (0.7 \frac{m}{^\circ C} 0.35 \frac{^\circ C}{V a} 0.11 \frac{V}{a})^{-\frac{1}{2}} = 6.09 \text{ a.}$$

### Problem 2.31

#### **Solution:**

##### **Known quantities:**

Circuit shown in Figure P2.31 with voltage source,  $V_s = 10V$  and resistors,

$$R_1 = 20\Omega, R_2 = 40\Omega, R_3 = 10\Omega, R_4 = R_5 = R_6 = 15\Omega.$$

##### **Find:**

The current in the  $15\text{-}\Omega$  resistors.

##### **Analysis:**

Since the 3 resistors must have equal currents,

$$I_{15\Omega} = \frac{1}{3} \cdot I$$

and,

$$I = \frac{V_s}{R_1 + R_2 \parallel R_3 + R_4 \parallel R_5 \parallel R_6} = \frac{10}{20 + 8 + 5} = \frac{10}{33} = 303 \text{ mA}$$

$$\text{Therefore, } I_{15\Omega} = \frac{10}{99} = 101 \text{ mA}$$

### Problem 2.32

#### **Solution:**

##### **Known quantities:**

Schematic of the circuit in Figure P2.7 with currents  $I_0 = -2 \text{ A}$ ,  $I_1 = -4 \text{ A}$ ,  $I_s = 8 \text{ A}$ , voltage source  $V_s = 12 \text{ V}$ , and resistance  $R_0 = 2 \Omega$ .

##### **Find:**

The unknown resistances  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$  and  $R_5$ .

##### **Assumption:**

In order to solve the problem we need to make further assumptions on the value of the resistors. For

example, we may assume that  $R_4 = \frac{2}{3}R_1$  and  $R_2 = \frac{1}{3}R_1$ .

##### **Analysis:**

We can express each current in terms of the adjacent node voltages:



$$I_0 = \frac{v_a - v_b}{R_0 + R_4} = \frac{v_a - v_b}{2 + \frac{2}{3}R_1} = -2$$

$$I_1 = \frac{v_a - v_b}{R_1} = -4$$

$$I_2 = \frac{v_a}{R_2} = \frac{v_a}{\frac{1}{3}R_1} = 6$$

$$I_3 = \frac{v_b}{R_3} = 2$$

$$I_S = \frac{V_S - v_b}{R_5} = \frac{12 - v_b}{R_5} = 8$$

Solving the system we obtain:

$$v_a = 3 \text{ V}, \quad v_b = 9 \text{ V}, \quad R_1 = 1.5 \, \Omega, \quad R_2 = 0.5 \, \Omega, \quad R_3 = 4.5 \, \Omega, \quad R_4 = 1 \, \Omega \quad \text{and} \\ R_5 = 0.375 \, \Omega.$$

## Problem 2.33

### **Solution:**

#### **Known quantities:**

Schematic of the circuit in Figure P2.7 with resistors  $R_1 = 2 \, \Omega$ ,  $R_2 = 5 \, \Omega$ ,  $R_3 = 4 \, \Omega$ ,  $R_4 = 1 \, \Omega$ ,  $R_5 = 3 \, \Omega$ , voltage source  $V_S = 54 \text{ V}$ , and current  $I_2 = 4 \text{ A}$ .

#### **Find:**

The unknown currents  $I_0$ ,  $I_1$ ,  $I_3$ ,  $I_S$  and the resistor  $R_0$ .

#### **Analysis:**

We can express each current in terms of the adjacent node voltages:

$$I_0 = \frac{v_a - v_b}{R_0 + R_4}$$

$$I_1 = \frac{v_a - v_b}{R_1}$$

$$I_2 = \frac{v_a}{R_2} = 4 \Rightarrow v_a = 4 \cdot 5 = 20 \text{ V}$$

$$I_3 = \frac{v_b}{R_3}$$

$$I_S = \frac{V_S - v_b}{R_5}$$

Applying KCL to node (a) and (b) :

$$\begin{cases} I_0 + I_1 + I_2 = 0 \\ I_0 + I_S + I_1 - I_3 = 0 \end{cases} \Rightarrow \begin{cases} \frac{20 - v_b}{R_0 + 1} + \frac{20 - v_b}{2} + 4 = 0 \\ \frac{20 - v_b}{R_0 + 1} + \frac{54 - v_b}{3} + \frac{20 - v_b}{2} - \frac{v_b}{4} = 0 \end{cases}$$

Solving the system we obtain:  $v_b = 24 \text{ V}$  and  $R_0 = 1 \Omega$ .

## Problem 2.34

### Solution:

**Known quantities:**

**NOTE:** Typo in Problem Statement for units of  $R_3$

Schematic of the circuit shown in Figure P2.34 with resistors  $R_0 = 2\Omega$ ,  $R_1 = 1\Omega$ ,  $R_2 = 4/3\Omega$ ,  $R_3 = 6\Omega$  and voltage source  $V_S = 12 \text{ V}$ .

**Find:**

- The mesh currents  $i_a$ ,  $i_b$ ,  $i_c$
- The current through each resistor.

**Analysis:**

Applying KVL to mesh (a), mesh (b) and mesh (c):

$$\begin{cases} i_a R_0 + (i_a - i_b) R_1 = 0 \\ (i_a - i_b) R_1 - i_b R_2 + (i_c - i_b) R_3 = 0 \\ V_S = (i_c - i_b) R_3 \end{cases} \Rightarrow \begin{cases} 2i_a + (i_a - i_b) = 0 \\ (i_a - i_b) - \frac{4}{3}i_b + 6(i_c - i_b) = 0 \\ 6(i_c - i_b) = 12 \end{cases}$$

Solving the system we obtain:

$$\begin{cases} i_a = 2 \text{ A} \\ i_b = 6 \text{ A} \\ i_c = 8 \text{ A} \end{cases} \Rightarrow \begin{cases} I_{R_0} = i_a = 2 \text{ A} & \text{(positive in the direction of } i_a) \\ I_{R_1} = i_b - i_a = 4 \text{ A} & \text{(positive in the direction of } i_b) \\ I_{R_2} = i_b = 6 \text{ A} & \text{(positive in the direction of } i_b) \\ I_{R_3} = i_c - i_b = 2 \text{ A} & \text{(positive in the direction of } i_c) \end{cases}$$

## Problem 2.35

### Solution:

#### Known quantities:

**NOTE:** Typo in Problem Statement for units of  $R_3$

Schematic of the circuit shown in Figure P2.34 with resistors  $R_0 = 2\Omega$ ,  $R_1 = 2\Omega$ ,  $R_2 = 5\Omega$ ,  $R_3 = 4\Omega$  and voltage source  $V_s = 24\text{ V}$ .

#### Find:

- The mesh currents  $i_a$ ,  $i_b$ ,  $i_c$
- The current through each resistor.

#### Analysis:

Applying KVL to mesh (a), mesh (b) and mesh (c):

$$\begin{cases} i_a R_0 + (i_a - i_b) R_1 = 0 \\ (i_a - i_b) R_1 - i_b R_2 + (i_c - i_b) R_3 = 0 \\ V_s = (i_c - i_b) R_3 \end{cases} \Rightarrow \begin{cases} 2i_a + 2(i_a - i_b) = 0 \\ 2(i_a - i_b) - 5i_b + 4(i_c - i_b) = 0 \\ 4(i_c - i_b) = 24 \end{cases}$$

Solving the system we obtain:

$$\begin{cases} i_a = 2\text{ A} \\ i_b = 4\text{ A} \\ i_c = 10\text{ A} \end{cases} \Rightarrow \begin{cases} V_{R_0} = R_0 i_a = 4\text{ V} & (\oplus \text{ up}) \\ V_{R_1} = R_1 (i_b - i_a) = 4\text{ V} & (\oplus \text{ down}) \\ V_{R_2} = R_2 i_b = 20\text{ V} & (\oplus \text{ up}) \\ V_{R_3} = R_3 (i_c - i_b) = 24\text{ V} & (\oplus \text{ up}) \end{cases}$$

## Problem 2.36

### Solution:

#### Known quantities:

**NOTE:** Typo in Problem Statement for units of  $R_3$

Schematic of the circuit shown in Figure P2.34 with resistors  $R_0 = 1\Omega$ ,  $R_1 = 3\Omega$ ,  $R_2 = 2\Omega$ ,  $R_3 = 4\Omega$  and of the current source  $I_s = 12\text{ A}$ .

#### Find:

The voltage across each resistance.

#### Analysis:

Applying KVL to mesh (a), mesh (b) and mesh (c):

$$\begin{cases} i_a R_0 + (i_a - i_b) R_1 = 0 \\ (i_a - i_b) R_1 - i_b R_2 + (i_c - i_b) R_3 = 0 \\ i_c = I_s \end{cases} \Rightarrow \begin{cases} i_a + 3(i_a - i_b) = 0 \\ 3(i_a - i_b) - 2i_b - 4i_b + 48 = 0 \\ i_c = 12\text{ A} \end{cases}$$

Solving the system we obtain:

$$\begin{cases} i_a = \frac{16}{3} \text{ A} \\ i_b = \frac{64}{9} \text{ A} \\ i_c = 12 \text{ A} \end{cases} \Rightarrow \begin{cases} V_{R_0} = R_0 i_a = 5.33 \text{ V} & (\oplus \text{ up}) \\ V_{R_1} = R_1 (i_b - i_a) = 5.33 \text{ V} & (\oplus \text{ down}) \\ V_{R_2} = R_2 i_b = 14.22 \text{ V} & (\oplus \text{ up}) \\ V_{R_3} = R_3 (i_c - i_b) = 19.55 \text{ V} & (\oplus \text{ up}) \end{cases}$$

## Problem 2.37

### **Solution:**

#### **Known quantities:**

Schematic of voltage divider network shown of Figure P2.37.

#### **Find:**

- The worst-case output voltages for  $\pm 10$  percent tolerance
- The worst-case output voltages for  $\pm 5$  percent tolerance

#### **Analysis:**

a) 10% worst case: low voltage

$$R_2 = 4500 \, \Omega, R_1 = 5500 \, \Omega$$

$$v_{OUT,MIN} = \frac{4500}{4500 + 5500} 5 = 2.25V$$

10% worst case: high voltage

$$R_2 = 5500 \, \Omega, R_1 = 4500 \, \Omega$$

$$v_{OUT,MAX} = \frac{5500}{4500 + 5500} 5 = 2.75V$$

b) 5% worst case: low voltage

$$R_2 = 4750 \, \Omega, R_1 = 5250 \, \Omega$$

$$v_{OUT,MIN} = \frac{4750}{4750 + 5250} 5 = 2.375V$$

5% worst case: high voltage

$$R_2 = 5250 \, \Omega, R_1 = 4750 \, \Omega$$

$$v_{OUT,MAX} = \frac{5250}{5250 + 4750} 5 = 2.625V$$

## Problem 2.38

### Solution:

#### Known quantities:


Schematic of the circuit shown in figure P2.38 with resistances,  $R_0 = 4\Omega$ ,  $R_1 = 12\Omega$ ,  $R_2 = 8\Omega$ ,  $R_3 = 2\Omega$ ,  $R_4 = 16\Omega$ ,  $R_5 = 5\Omega$ .

#### Find:

The equivalent resistance of the circuit.

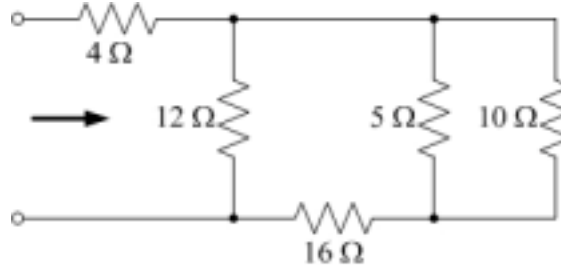
#### Analysis:

Starting from the right side, we combine the two resistors in series:




Then, we can combine the two parallel resistors, namely the 5  $\Omega$  resistor and 10  $\Omega$  resistor:
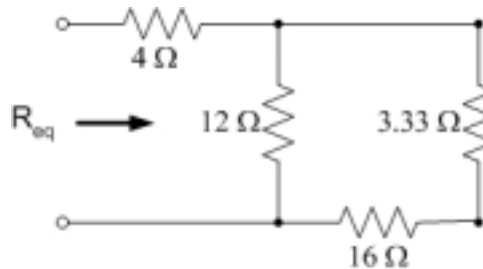
$$\frac{1}{R_{parallel}} = \frac{1}{5} + \frac{1}{10} (\Omega^{-1}) \Rightarrow R_{parallel} = \frac{10}{3} \Omega$$




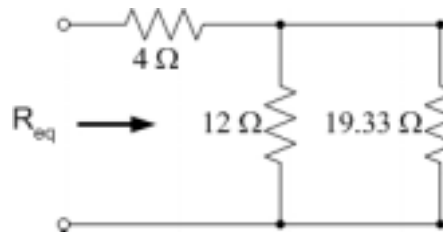Then, we can combine the two resistors in series, namely the 3.33  $\Omega$  and the 16  $\Omega$  resistor:



Then, we can combine the two parallel resistors, namely the 12  $\Omega$  resistor and 19.33  $\Omega$  resistor:
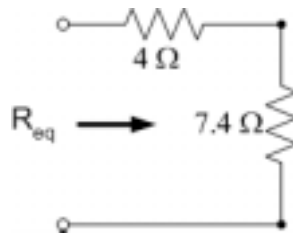
$$\frac{1}{R_{parallel}} = \frac{1}{12} + \frac{1}{19.33} (\Omega^{-1}) \Rightarrow R_{parallel} = 7.4 \Omega$$



Therefore,  $R_{eq} = 4 + 7.4 = 11.4 \, \Omega$ .

### Problem 2.39

#### **Solution:**

##### **Known quantities:**

Schematic of the circuit shown in Figure P2.39 with source voltage,  $V_s = 12V$ ; and resistances,

$$R_0 = 4\Omega, R_1 = 2\Omega, R_2 = 50\Omega, R_3 = 8\Omega, R_4 = 10\Omega, R_5 = 12\Omega, R_6 = 6\Omega.$$


##### **Find:**

The equivalent resistance of the circuit seen by the source; the current  $i$  through the resistance  $R_2$ .

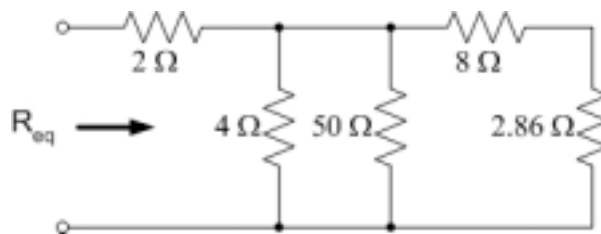
##### **Analysis:**

Starting from the right side, we can combine the three parallel resistors, namely the  $10 \, \Omega$  resistor, the  $12 \, \Omega$  resistor and the  $6 \, \Omega$  resistor:

$$\frac{1}{R_{parallel}} = \frac{1}{10} + \frac{1}{12} + \frac{1}{6} \, (\Omega^{-1}) \Rightarrow R_{parallel} = \frac{20}{7} \, \Omega$$




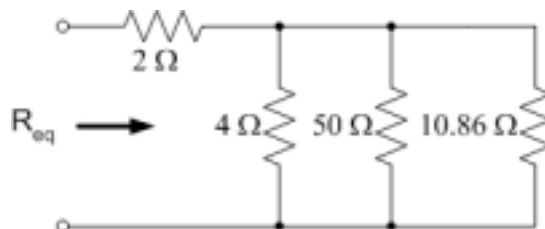Then, we can combine the two resistors in series, namely the  $8 \, \Omega$  and the  $2.86 \, \Omega$  resistor:




Then, we can combine the three parallel resistors, namely the  $4 \, \Omega$  resistor, the  $50 \, \Omega$  resistor and the  $10.86 \, \Omega$  resistor:
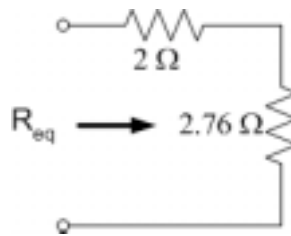
$$\frac{1}{R_{parallel}} = \frac{1}{4} + \frac{1}{50} + \frac{1}{10.86} (\Omega^{-1}) \Rightarrow R_{parallel} = 2.76 \Omega$$



Therefore,  $R_{eq} = 2 + 2.76 = 4.76 \Omega$ .

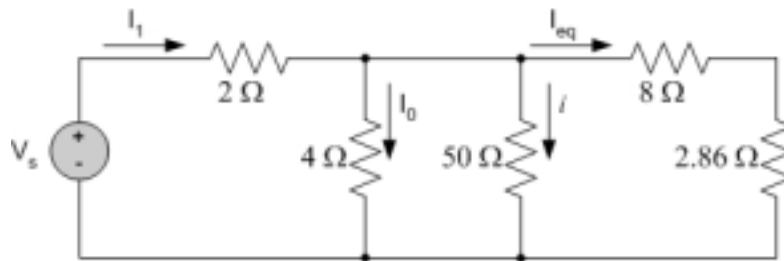Looking at the following equivalent circuit:



We can apply KVL and KCL to the above circuit:

$$\begin{cases} V_s - 2I_1 - 4I_0 = 0 \\ I_1 = I_0 + i + I_{eq} \\ 4I_0 = 50i = 2.86I_{eq} \end{cases} \Rightarrow \begin{cases} I_0 = 12.5i \\ I_1 = 6 - 25i \\ I_{eq} = 17.48i \\ i = I_1 - I_0 - I_{eq} \end{cases} \Rightarrow i = 107 \text{ mA}$$

## Problem 2.40

### Solution:

#### Known quantities:

Schematic of the circuit shown in Figure P2.40 with source voltage,  $V_s = 50V$  ; resistances,

$R_1 = 20\Omega, R_2 = 5\Omega, R_3 = 2\Omega, R_4 = 8\Omega, R_5 = 8\Omega, R_6 = 30\Omega$  ; and power absorbed by the  $20\Omega$  resistor.


#### Find:

The resistance  $R$  .
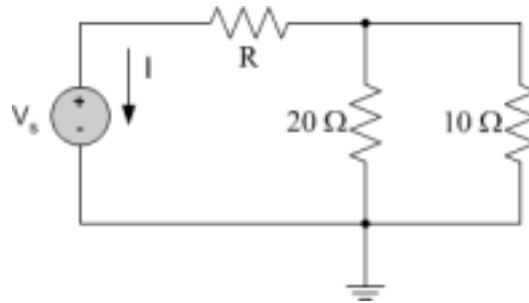
#### Analysis:

Starting from the right side, we can replace resistors  $R_i$  ( $i=2..6$ ) with a single equivalent resistors:

$$R_{eq} = R_2 + (R_3 + (R_4 \parallel R_5)) \parallel R_6 = 10 \Omega$$



The same voltage appears across both  $R_1$  and  $R_{eq}$  and, therefore, these element are in parallel. Applying the voltage divider rule:

$$V_{R_1} = \frac{R_1 \parallel R_{eq}}{R + R_1 \parallel R_{eq}} V_s = \frac{1000}{3R + 20}$$

The power absorbed by the 20-Ω resistor is:

$$P_{20\Omega} = \frac{(V_{R_1})^2}{R_1} = \frac{1}{20} \left( \frac{1000}{3R + 20} \right)^2 = \frac{50000}{(3R + 20)^2} = 20 \Rightarrow R = 10 \Omega$$

## Problem 2.41

### Solution:

#### Known quantities:


Schematic of the circuit shown in Figure P2.41.

#### Find:

The equivalent resistance  $R_{eq}$  of the infinite network of resistors.
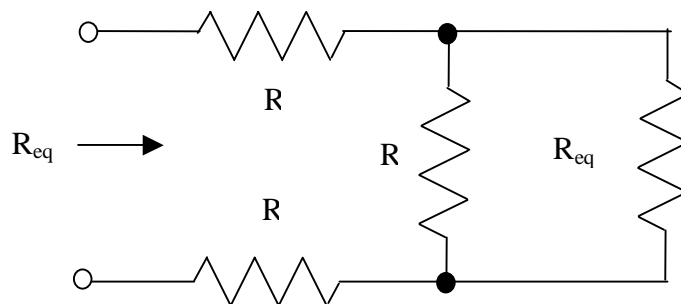
#### Analysis:

We can see the infinite network of resistors as the equivalent to the circuit in the picture:



Therefore,

$$R_{eq} = R + (R \parallel R_{eq}) + R = 2R + \frac{RR_{eq}}{R + R_{eq}} \Rightarrow R_{eq} = (1 + \sqrt{3})R$$



## Problem 2.42

### Solution:

#### Known quantities:

Schematic of the circuit shown in Figure P2.42 with source voltage,  $V_s = 110V$  ; and resistances,

$$R_1 = 90\Omega, R_2 = 50\Omega, R_3 = 40\Omega, R_4 = 20\Omega, R_5 = 30\Omega, R_6 = 10\Omega, R_7 = 60\Omega, R_8 = 80\Omega.$$


#### Find:

- The equivalent resistance of the circuit seen by the source.
- The current through and the power absorbed by the resistance  $90\Omega$  resistance.

#### Analysis:

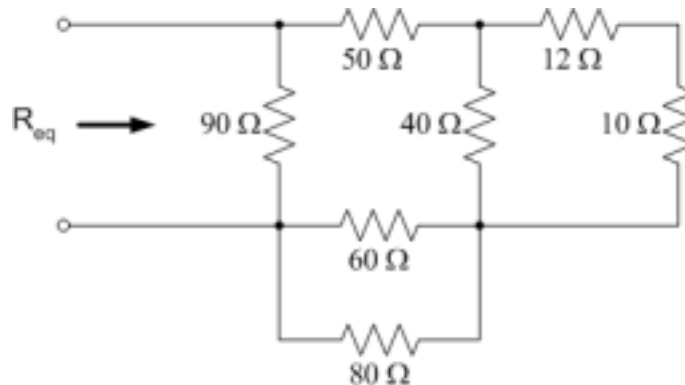
a) Starting from the right side, we can combine the two parallel resistors, namely the  $20\Omega$  resistor and the  $30\Omega$  resistor:

$$\frac{1}{R_{parallel}} = \frac{1}{20} + \frac{1}{30} (\Omega^{-1}) \Rightarrow R_{parallel} = 12\Omega$$




Then we can combine the two parallel resistors in the bottom, namely the  $60\Omega$  resistor and the  $80\Omega$ , and the two resistor in series:
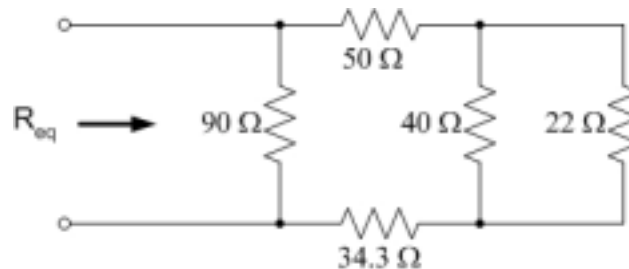
$$\frac{1}{R_{parallel}} = \frac{1}{60} + \frac{1}{80} (\Omega^{-1}) \Rightarrow R_{parallel} = 34.3\Omega$$



Then we can combine the two parallel resistors on the right, namely the  $40\Omega$  resistor and the  $22\Omega$ :
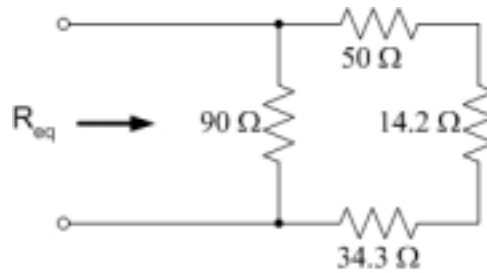
$$\frac{1}{R_{parallel}} = \frac{1}{40} + \frac{1}{22} (\Omega^{-1}) \Rightarrow R_{parallel} = 14.2\Omega$$



Therefore,  $\frac{1}{R_{eq}} = \frac{1}{90} + \frac{1}{(50 + 14.2 + 34.3)} (\Omega^{-1}) \Rightarrow R_{eq} = 47 \Omega$ .

b) The current through and the power absorbed by the 90-Ω resistor are:

$$I_{90\Omega} = \frac{V_s}{R_1} = \frac{110}{90} = 1.22 \text{ A}$$

$$P_{90\Omega} = \frac{(V_s)^2}{R_1} = \frac{110^2}{90} = 134.4 \text{ W}$$

### Problem 2.43

#### **Solution:**

##### **Known quantities:**

Schematic of the circuit shown in Figure P2.43.

##### **Find:**

The equivalent resistance at terminals a,b in the case that terminals c,d are a) open b) shorted; the same for terminals c,d with respect to terminals a,b.

##### **Analysis:**

With terminals c-d open,  $R_{eq} = (360 + 540) \parallel (180 + 540) \Omega = 400 \Omega$ ,

with terminals c-d shorted,  $R_{eq} = (360 \parallel 180) + (540 \parallel 540) \Omega = 390 \Omega$ ,

with terminals a-b open,  $R_{eq} = (540 + 540) \parallel (360 + 180) \Omega = 360 \Omega$ ,

with terminals a-b shorted,  $R_{eq} = (360 \parallel 540) + (180 \parallel 540) \Omega = 351 \Omega$ .

### Problem 2.44

#### **Solution:**

##### **Known quantities:**

Layout of the site shown in Figure P2.44; characteristics of the cables; rated voltage of the generator; range of voltages and currents absorbed by the engine at full load.

##### **Find:**

The minimum AWG gauge conductors which must be used in a rubber insulated cable.

**Analysis:**

The cable must meet two requirements:

1. The conductor current rating must be greater than the rated current of the motor at full load. This requires AWG #14.
2. The voltage drop due to the cable resistance must not reduce the motor voltage below its minimum rated voltage at full load.

$$KVL: -V_G + V_{RC1} + V_{M-Min} + V_{RC2} = 0$$

$$-V_G + I_{M-FL} R_{C1} + V_{M-Min} + I_{M-FL} R_{C2} = 0$$

$$R_{C1} + R_{C2} = \frac{V_G - V_{M-Min}}{I_{M-FL}} =$$

$$= \frac{110 \text{ V} - 105 \text{ V}}{7.103 \text{ A}} = 703.9 \text{ m}\Omega$$

$$R_{Max} = \frac{R_{C1}}{d} = \frac{R_{C2}}{d} = \frac{\frac{1}{2}[703.9 \text{ m}\Omega]}{150 \text{ m}} = 2.346 \text{ m} \frac{\Omega}{m}$$

Therefore, AWG #8 or larger wire must be used.

**Problem 2.45****Solution:****Known quantities:**

Layout of the building shown in Figure P2.45; characteristics of the cables; rated voltage of the generator; total electrical load in the building.

**Find:**

The minimum AWG gauge conductors which must be used in a rubber insulated cable.

**Analysis:**

The cable must meet two requirements:

1. The conductor current rating must be greater than the rated current of the motor at full load. This requires AWG #4.
2. The voltage drop due to the cable resistance must not reduce the motor voltage below its minimum rated voltage at full load.

$$KVL: -V_S + V_{RC1} + V_{L-Min} + V_{RC2} = 0$$

$$-V_S + I_{L-FL} R_{C1} + V_{L-Min} + I_{L-FL} R_{C2} = 0$$

$$R_{C1} + R_{C2} = \frac{V_S - V_{L-Min}}{I_{L-FL}} =$$

$$= \frac{450 \text{ V} - 446 \text{ V}}{51.57 \text{ A}} = 77.6 \text{ m}\Omega$$

$$R_{Max} = \frac{R_{C1}}{d} = \frac{R_{C2}}{d} = \frac{\frac{1}{2}[77.6 \text{ m}\Omega]}{85 \text{ m}} = 0.4565 \text{ m} \frac{\Omega}{m}$$

Therefore, AWG #0 or larger wire must be used.

## Problem 2.46

### Solution:

#### Known quantities:

Layout of the site shown in Figure P2.46; characteristics of the cables; rated voltage of the generator; electrical characteristics of the engine.

#### Find:

The maximum length of a rubber insulated cable with AWG #14 which can be used to connect the motor and the generator.

#### Analysis:

The voltage drop due to the cable resistance must not reduce the motor voltage below its minimum rated voltage at full load.

$$\begin{aligned}
 KVL: \quad & -V_G + V_{RC1} + V_{M-Min} + V_{RC2} = 0 \\
 & -V_G + I_{M-FL} R_{C1} + V_{M-Min} + I_{M-FL} R_{C2} = 0 \\
 & R_{C1} + R_{C2} = \frac{V_G - V_{M-Min}}{I_{M-FL}} = \\
 & = \frac{110 \text{ V} - 105 \text{ V}}{7.103 \text{ A}} = 703.9 \text{ m}\Omega \\
 & d_{Max} = \frac{R_{C1}}{R_{rated}} = \frac{R_{C2}}{R_{rated}} = \frac{\frac{1}{2}[703.9 \text{ m}\Omega]}{8.285 \text{ m} \frac{\Omega}{m}} = 42.48 \text{ m}
 \end{aligned}$$

## Problem 2.47

### Solution:

#### Known quantities:

Layout of the building shown in Figure P2.47; characteristics of the cables; rated voltage of the generator; total electrical load in the building.

#### Find:

The maximum length of a rubber insulated cable with AWG #4 which can be used to connect the source to the load.

#### Analysis:

The voltage drop due to the cable resistance must not reduce the motor voltage below its minimum rated voltage at full load.

$$\begin{aligned}
 KVL: \quad & -V_S + V_{RC1} + V_{L-Min} + V_{RC2} = 0 \\
 & -V_S + I_{L-FL} R_{C1} + V_{L-Min} + I_{L-FL} R_{C2} = 0 \\
 R_{C1} + R_{C2} &= \frac{V_S - V_{L-Min}}{I_{L-FL}} = \\
 &= \frac{450 \text{ V} - 446 \text{ V}}{51.57 \text{ A}} = 77.6 \text{ m}\Omega \\
 d_{Max} &= \frac{R_{C1}}{R_{rated}} = \frac{R_{C2}}{R_{rated}} = \frac{\frac{1}{2}[77.6 \text{ m}\Omega]}{0.8153 \text{ m} \frac{\Omega}{m}} = 47.59 \text{ m}
 \end{aligned}$$


---

## Problem 2.48

### Solution:

#### Known quantities:

Schematic of the circuit shown in Figure P2.48 with resistances,  $R_1 = 2.2 \text{ k}\Omega$ ,  $R_2 = 18 \text{ k}\Omega$ ,  $R_3 = 220 \text{ k}\Omega$ ,  $R_4 = 3.3 \text{ k}\Omega$ .

#### Find:

The equivalent resistance between A and B.

#### Analysis:

Shorting nodes C and D creates a single node to which all four resistors are connected.

$$\begin{aligned}
 R_{eq1} &= R_1 \parallel R_3 = \frac{R_1 R_3}{R_1 + R_3} = \frac{[2.2 \text{ K}\Omega][4.7 \text{ K}\Omega]}{2.2 + 4.7 \text{ K}\Omega} = 1.499 \text{ K}\Omega \\
 R_{eq2} &= R_2 \parallel R_4 = \frac{R_2 R_4}{R_2 + R_4} = \frac{[18 \text{ K}\Omega][3.3 \text{ K}\Omega]}{18 + 3.3 \text{ K}\Omega} = 2.789 \text{ K}\Omega \\
 R_{eq} &= R_{eq1} + R_{eq2} = 1.499 + 2.789 \text{ K}\Omega = 4.288 \text{ K}\Omega
 \end{aligned}$$


---

## Problem 2.49

### Solution:

#### Known quantities:

Schematic of the circuit shown in Figure P2.49 with source voltage,  $V_s = 12 \text{ V}$ ; and resistances,  $R_1 = 11 \text{ k}\Omega$ ,  $R_2 = 220 \text{ k}\Omega$ ,  $R_3 = 6.8 \text{ k}\Omega$ ,  $R_4 = 0.22 \text{ m}\Omega$

#### Find:

The voltage between nodes A and B.

**Analysis:**

The same current flows through R1 and R3. Therefore, they are connected in series. Similarly, R2 and R4 are connected in series.

SPECIFY THE ASSUMED POLARITY OF THE VOLTAGE BETWEEN NODES A AND B. THIS WILL HAVE TO BE A WILD GUESS AT THIS POINT.

Specify the polarities of the voltage across R3 and R4 which will be determined using voltage division. The actual polarities are not difficult to determine. Do so.

$$VD: V_{R3} = \frac{V_S R_3}{R_1 + R_3} = \frac{[12 V][6.8 k\Omega]}{11 + 6.8 k\Omega} = 4.584 V$$

$$VD: V_{R4} = \frac{V_S R_4}{R_2 + R_4} = \frac{[12 V][0.22 \times 10^{-6} k\Omega]}{(220 + 0.22 \times 10^{-6}) k\Omega} = 1.20 \times 10^{-8} V \approx 0$$

$$KVL: -V_{R3} + V_{AB} + V_{R4} = 0 \therefore V_{AB} = V_{R3} - V_{R4} = 4.584 V$$

The voltage is negative indicating that the polarity of  $V_{AB}$  is opposite of that specified.

A solution is not complete unless the assumed positive direction of a current or assumed positive polarity of a voltage IS SPECIFIED ON THE CIRCUIT.

**Problem 2.50****Solution:****Known quantities:**

Schematic of the circuit shown in Figure P2.49 with source voltage,  $V_s = 5V$ ; and resistances,

$$R_1 = 2.2k\Omega, R_2 = 18k\Omega, R_3 = 4.7k\Omega, R_4 = 3.3k\Omega$$

**Find:**

The voltage between nodes A and B.

**Analysis:**

The same current flows through R1 and R3. Therefore, they are connected in series. Similarly, R2 and R4 are connected in series.

SPECIFY THE ASSUMED POLARITY OF THE VOLTAGE BETWEEN NODES A AND B. THIS WILL HAVE TO BE A WILD GUESS AT THIS POINT.

Specify the polarities of the voltage across R3 and R4 which will be determined using voltage division. The actual polarities are not difficult to determine. Do so.

$$VD: V_{R3} = \frac{V_S R_3}{R_1 + R_3} = \frac{[5 V][4.7 K\Omega]}{2.2 K\Omega + 4.7 K\Omega} = 3.406 V$$

$$VD: V_{R4} = \frac{V_S R_4}{R_2 + R_4} = \frac{[5 V][3.3 K\Omega]}{18 K\Omega + 3.3 K\Omega} = 0.917 V$$

$$KVL: -V_{R3} + V_{AB} + V_{R4} = 0 \Rightarrow V_{AB} = V_{R3} - V_{R4} = 2.489 V$$

A solution is not complete unless the assumed positive direction of a current or assumed positive polarity of a voltage IS SPECIFIED ON THE CIRCUIT.

**Problem 2.51****Solution:****Known quantities:**

Schematic of the circuit shown in Figure P2.51 with source voltage,  $V_s = 12V$  ; and resistances,

$$R_1 = 1.7m\Omega, R_2 = 3k\Omega, R_3 = 10k\Omega$$

**Find:**

The voltage across the resistance  $R_3$  .

**Analysis:**

The same voltage appears across both  $R_2$  and  $R_3$  and, therefore, these element are in parallel. Applying the voltage divider rule:

$$V_{R_3} = \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} V_s = \frac{2.3k\Omega}{1.7m\Omega + 2.3k\Omega} 12 \text{ V} = 11.999991 \text{ V } (\oplus \text{ down})$$

Note that since  $R_1 \ll R_2 \parallel R_3$  , then  $V_{R_3} \cong V_s$  .

---

## Sections 2.7, 2.8: Practical Sources and Measuring Devices

### Problem 2.52

#### Solution:

##### Known quantities:

Parameters  $R_0 = 300 \, \Omega$  (resistance at temperature  $T_0 = 298 \, \text{K}$ ), and  $\beta = -0.01 \, \text{K}^{-1}$ , value of the second resistor.

##### Find:

- Plot  $R_{th}(T)$  versus  $T$  in the range  $350 \leq T \leq 750 \, [^\circ\text{K}]$
- The equivalent resistance of the parallel connection with the  $250\text{-}\Omega$  resistor; plot  $R_{eq}(T)$  versus  $T$  in the range  $350 \leq T \leq 750 \, [^\circ\text{K}]$  for this case on the same plot as part a.

##### Assumptions:


$$R_{th}(T) = R_0 e^{-\beta(T-T_0)}.$$

##### Analysis:

$$\text{a) } R_{th}(T) = 300 e^{-0.01(T-298)}$$

$$\text{b) } R_{eq}(T) = R_{th}(T) \parallel 250\Omega = \frac{1500 e^{-0.01(T-298)}}{5 + 6 e^{-0.01(T-298)}}$$

The two plots are shown below.

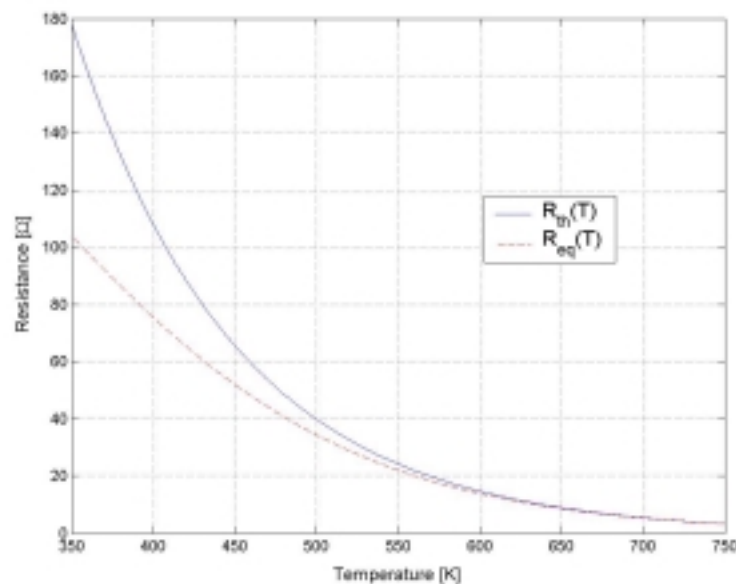

In the above plot, the solid line is for the thermistor alone; the dashed line is for the thermistor-resistor combination.



## Problem 2.53

### Solution:

#### Known quantities:

A potentiometer shown in the circuit of Figure P.253 with The value of the resistance  $R_m$ , the total length of the resistor  $x_T$  and voltage source  $v_S$ .

#### Find:

- The expression for  $v_{out}(x)$ . Plot  $v_{out}/v_S$  versus  $x/x_T$ .
- The distance  $x$  when  $v_{out} = 5\text{ V}$ .
- Assuming the resistance  $R_m$  becomes infinite, repeat parts a and b


#### Assumptions:

$$\frac{v_{out}}{v_S} = \frac{1}{1/(x/x_T) + (R_p/R_m)(1 - x/x_T)}$$

$$R_p(x) = 200e^x$$
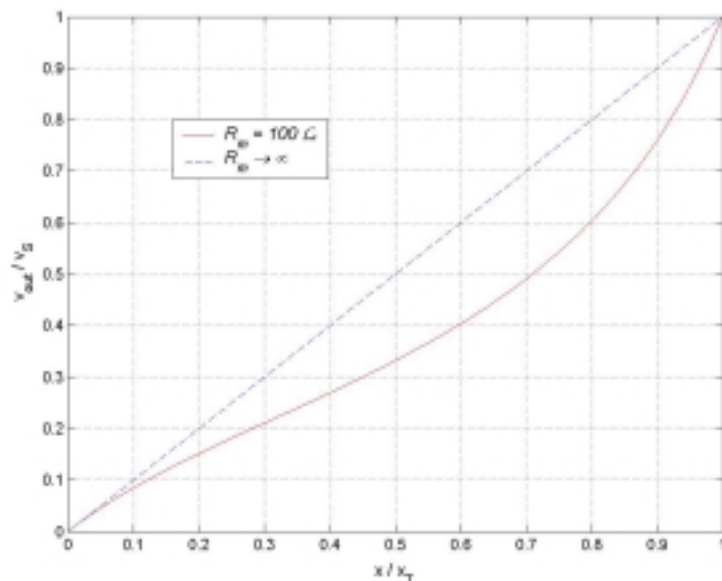
#### Analysis:

$$a) v_{out}(x) = \frac{10}{1/(x/0.02) + (200e^x/100)(1 - x/0.02)} = 500 \frac{x}{1 - 10^2 e^x x + 5 \cdot 10^3 e^x x^2}$$



In the above plot, the solid line is for  $R_m = 100\ \Omega$ ; the dashed line is for  $R_m \rightarrow \infty$ .

$$b) x(v_{out} = 5\text{ V}) = 14.18\text{ cm}$$

$$c) \text{ Now } R_m \rightarrow \infty.$$

$$v_{out}(x) = \frac{10}{1/(x/0.02) + (200e^x/\infty)(1 - x/0.02)} \rightarrow 500x$$

$$x(v_{out} = 5 \text{ V}) = 10 \text{ cm}$$

## Problem 2.54

### Solution:

#### Known quantities:

Meter resistance of the coil; meter current for full scale deflection; max measurable pressure.

#### Find:

- The circuit required to indicate the pressure measured by a sensor
- The value of each component of the circuit; the linear range
- The maximum pressure that can accurately be measured.

#### Assumptions:

Sensor characteristics follow what is shown in Figure P2.54

#### Analysis:

- A series resistor to drop excess voltage is required.
- At full scale, meter:

$$I_{\hat{m}FS} = 10 \mu A$$

$$r_{\hat{m}} = 200 \Omega$$

$$0.L.: V_{\hat{m}FS} = I_{\hat{m}FS} r_{\hat{m}} = 2 \text{ mV}.$$

at full scale, sensor (from characteristics):

$$P_{FS} = 100 \text{ kPa}$$

$$V_{TFS} = 9.5 \text{ mV}$$

$$KVL: -V_{TFS} + V_{RFS} + V_{\hat{m}FS} = 0$$

$$V_{RFS} = V_{TFS} - V_{\hat{m}FS} = 9.5 \text{ mV} - 2 \text{ mV} = 7.5 \text{ mV}$$

$$I_{RFS} = I_{TFS} = I_{\hat{m}FS} = 10 \mu A$$

$$\text{Ohm law: } R = \frac{V_{RFS}}{I_{RFS}} = \frac{7.5 \text{ mV}}{10 \mu A} = 750 \Omega.$$

- from sensor characteristic: 30 kPa – 110 kPa.

## Problem 2.55

### Solution:

#### Known quantities:

Meter resistance of the coil; meter current for full scale deflection; max measurable pressure.

#### Find:

- Redesign the circuit to meet the specification.
- The value of each component of the circuit.
- The linear range of the system.

**Assumptions:**

Sensor characteristics follow what is shown in Figure P2.55

**Analysis:**

a) A series resistor to drop excess voltage is required.

b) At full scale, meter:

$$I_{\hat{m}FS} = 50 \mu A$$

$$r_{\hat{m}} = 1.8 k\Omega$$

$$0.L.: V_{\hat{m}FS} = I_{\hat{m}FS} r_{\hat{m}} = 90 mV.$$

at full scale, sensor (from characteristics):

$$V_{TFS} = 9.5 V$$

$$KVL: -V_{TFS} + V_{RFS} + V_{\hat{m}FS} = 0$$

$$V_{RFS} = V_{TFS} - V_{\hat{m}FS} = 9.5 V - 90 mV = 9.41 V$$

$$I_{RFS} = I_{TFS} = I_{\hat{m}FS} = 50 \mu A$$

$$\text{Ohm law: } R = \frac{V_{RFS}}{I_{RFS}} = \frac{9.41 V}{50 \mu A} = 188.2 k\Omega.$$

c) from sensor characteristic: 20 kPa – 110 kPa.

**Problem 2.56****Solution:****Known quantities:**

Meter resistance of the coil; meter voltage for full scale deflection; max measurable temperature.

**Find:**

- The circuit required to meet the specifications of the new sensor.
- The value of each component of the circuit.
- The linear range of the system.

**Assumptions:**

Sensor characteristics follow what is shown in Figure P2.56

**Analysis:**

a) A parallel resistor is required to shunt (bypass) the excess current.

b) At full scale, meter:

$$V_{\hat{m}FS} = 250 mV$$

$$r_{\hat{m}} = 2.5 k\Omega$$

$$0.L.: I_{\hat{m}FS} = \frac{V_{\hat{m}FS}}{r_{\hat{m}}} = 100 \mu A.$$

at full scale, sensor (from characteristics):

$$T_{FS} = 400 ^\circ C$$

$$I_{TFS} = 8.5 mA$$

$$KCL: -I_{TFS} + I_{RFS} + I_{\hat{m}FS} = 0$$

$$I_{RFS} = I_{TFS} - I_{\hat{m}FS} = 8.5 \text{ mA} - 100 \text{ } \mu\text{A} = 8.4 \text{ mA}$$

$$V_{RFS} = V_{TFS} = V_{\hat{m}FS} = 250 \text{ mV}$$

$$\text{Ohm law: } R = \frac{V_{RFS}}{I_{RFS}} = \frac{250 \text{ mV}}{8.4 \text{ mA}} = 29.76 \text{ } \Omega.$$

c) from sensor characteristic:  $220 \text{ }^{\circ}\text{C} - 410 \text{ }^{\circ}\text{C}$ .

## Problem 2.57

### Solution:

#### Known quantities:

Meter resistance of the coil; meter voltage at full scale; max measurable temperature.

#### Find:

- The circuit required to meet the specifications of the new sensor.
- The value of each component of the circuit
- The linear range of the system.

#### Assumptions:

Sensor characteristics follow what is shown in Figure P2.57

#### Analysis:

- A parallel resistor is required to shunt (bypass) the excess current.
- At full scale, meter:

$$V_{\hat{m}FS} = 250 \text{ mV}$$

$$r_{\hat{m}} = 2.5 \text{ k}\Omega$$

$$\text{O.L.: } I_{\hat{m}FS} = \frac{V_{\hat{m}FS}}{r_{\hat{m}}} = 100 \text{ } \mu\text{A}.$$

at full scale, sensor (from characteristics):

$$T_{FS} = 400 \text{ }^{\circ}\text{C}$$

$$I_{TFS} = 8.5 \text{ mA}$$

$$\text{KCL: } -I_{TFS} + I_{RFS} + I_{\hat{m}FS} = 0$$

$$I_{RFS} = I_{TFS} - I_{\hat{m}FS} = 8.5 \text{ mA} - 100 \text{ } \mu\text{A} = 8.4 \text{ mA}$$

$$V_{RFS} = V_{TFS} = V_{\hat{m}FS} = 250 \text{ mV}$$

$$\text{Ohm law: } R = \frac{V_{RFS}}{I_{RFS}} = \frac{250 \text{ mV}}{8.4 \text{ mA}} = 29.76 \text{ } \Omega.$$

c) from sensor characteristic:  $220 \text{ }^{\circ}\text{C} - 410 \text{ }^{\circ}\text{C}$ .

## Problem 2.58

### Solution:

#### Known quantities:

Schematic of the circuit shown in Figure P2.58; voltage at terminals with switch open and closed for fresh battery; same voltages for the same battery after 1 year.

**Find:**

The internal resistance of the battery in each case.

**Analysis:**

a)

$$V_{out} = \left( \frac{10}{10 + r_B} \right) V_{oc}$$

$$r_B = 10 \left( \frac{V_{oc}}{V_{out}} - 1 \right) = 10 \left( \frac{2.28}{2.27} - 1 \right)$$

$$= 0.044 \Omega$$

b)

$$r_B = 10 \left( \frac{V_{oc}}{V_{out}} - 1 \right) = 10 \left( \frac{2.2}{0.31} - 1 \right)$$

$$= 60.97 \Omega$$

**Problem 2.59****Solution:****Known quantities:**

Ammeter shown in Figure P2.59; Current for full-scale deflection; desired full scale values.

**Find:**

Value of the resistors required for the given full scale ranges.

**Analysis:**

We desire  $R_1$ ,  $R_2$ ,  $R_3$  such that  $I_a = 30 \mu A$  for  $I = 10 \text{ mA}$ ,  $100 \text{ mA}$ , and  $1 \text{ A}$ , respectively. We use conductances to simplify the arithmetic:

$$G_a = \frac{1}{R_a} = \frac{1}{1000} \text{ S}$$

$$G_{1,2,3} = \frac{1}{R_{1,2,3}}$$

By the current divider rule:

$$I_a = \frac{G_a}{G_a + G_x} I$$

or:

$$G_x = G_a \left( \frac{I}{I_a} \right) - G_a \text{ or } \frac{1}{G_x} = \frac{1}{G_a} \left( \frac{I_a}{I - I_a} \right)$$

$$R_x = R_a \left( \frac{I}{I - I_a} \right).$$

We can construct the following table:

x	I	$R_x$ (Approx.)
1	$10^{-2}$ A	$3 \Omega$
2	$10^{-1}$ A	$0.3 \Omega$
3	$10^0$ A	$0.03 \Omega$

## Problem 2.60

### Solution:

#### Known quantities:

Schematic of the circuit shown in Figure P2.60; for part b: value of  $R_p$  and current displayed on the ammeter.

#### Find:

The current  $i$ ; the internal resistance of the meter.

#### Assumptions:

$$r_a \ll 50 \text{ k}\Omega$$

#### Analysis:

a) Assuming that  $r_a \ll 50 \text{ k}\Omega$

$$i \approx \frac{V_s}{R_s} = \frac{12}{50000} = 240 \mu\text{A}$$

b) With the same assumption as in part a)

$$i_{\text{meter}} = 150 \cdot (10)^{-6} = \frac{R_p}{r_a + R_p} i$$

or:

$$150 \cdot (10)^{-6} = \frac{15}{r_a + 15} 240 \cdot 10^{-6} .$$

Therefore,  $r_a = 9 \Omega$ .

## Problem 2.61

### Solution:

#### Known quantities:

Voltage read at the meter; schematic of the circuit shown in Figure P2.61 with source voltage,  $V_s = 12\text{V}$  and source resistance,  $R_s = 25\text{k}\Omega$ .

**Find:**

The internal resistance of the voltmeter.

**Analysis:**

Using the voltage divider rule:

$$V = 11.81 = \frac{r_m}{r_m + R_s} (12)$$

Therefore,  $r_m = 1.55 \text{ M}\Omega$ .

## Problem 2.62

**Solution:****Known quantities:**

Circuit shown in Figure P2.61 with source voltage,  $V_s = 24\text{V}$ ; and ratios between  $R_s$  and  $r_m$ .

**Find:**

The meter reads in the various cases.

**Analysis:**

By voltage division:

$$V = \frac{r_m}{r_m + R_s} (24)$$

$R_s$	V
$0.2 r_m$	20 V
$0.4 r_m$	17.14 V
$0.6 r_m$	15 V
$1.2 r_m$	10.91 V
$4 r_m$	4.8 V
$6 r_m$	3.43 V
$10 r_m$	2.18 V

For a voltmeter, we always desire  $r_m \gg R_s$ .

## Problem 2.63

**Solution:****Known quantities:**

Schematic of the circuit shown in Figure P2.63, values of the components.

**Find:**

The voltage across  $R_4$  with and without the voltmeter for the following values:

- a)  $R_4 = 100\Omega$
- b)  $R_4 = 1k\Omega$
- c)  $R_4 = 10k\Omega$
- d)  $R_4 = 100k\Omega$  .

**Assumptions:**

The voltmeter behavior is modeled as that of an ideal voltmeter in parallel with a 120- k $\Omega$  resistor.

**Analysis:**

We develop first an expression for  $V_{R_4}$  in terms of  $R_4$  . Next, using current division:

$$\begin{cases} I_{R_1} = I_S \left( \frac{R_S}{R_S + R_1 + R_2 \parallel (R_3 + R_4)} \right) \\ I_{R_4} = I_{R_1} \left( \frac{R_2}{R_2 + R_3 + R_4} \right) \end{cases}$$

Therefore,

$$\begin{aligned} I_{R_4} &= I_S \left( \frac{R_S}{R_S + R_1 + R_2 \parallel (R_3 + R_4)} \right) \cdot \left( \frac{R_2}{R_2 + R_3 + R_4} \right) \\ V_{R_4} &= I_{R_4} R_4 \\ &= I_S \left( \frac{R_S R_4}{R_S + R_1 + R_2 \parallel (R_3 + R_4)} \right) \cdot \left( \frac{R_2}{R_2 + R_3 + R_4} \right) \\ &= \frac{66000 \cdot R_4}{R_4 + 2.1352 \cdot 10^6} \end{aligned}$$

Without the voltmeter:

- a)  $V_{R_4} = 3.08 \text{ V}$
- b)  $V_{R_4} = 30.47 \text{ V}$
- c)  $V_{R_4} = 269.91 \text{ V}$
- d)  $V_{R_4} = 1260.7 \text{ V}$ .

Now we must find the voltage drop across  $R_4$  with a 120-k $\Omega$  resistor across  $R_4$  . This is the voltage that the voltmeter will read.

$$\begin{aligned} I_{R_4} &= I_S \left( \frac{R_S}{R_S + R_1 + R_2 \parallel (R_3 + (R_4 \parallel 120k\Omega))} \right) \cdot \left( \frac{R_2}{R_2 + R_3 + (R_4 \parallel 120k\Omega)} \right) \\ V_{R_4} &= I_{R_4} R_4 \\ &= I_S \left( \frac{R_S R_4}{R_S + R_1 + R_2 \parallel (R_3 + (R_4 \parallel 120k\Omega))} \right) \cdot \left( \frac{R_2}{R_2 + R_3 + (R_4 \parallel 120k\Omega)} \right) \\ &= 82.5 \frac{(120000 + R_4) \cdot R_4}{7319R_4 + 320.28 \cdot 10^6} \end{aligned}$$



With the voltmeter:

- a)  $V_{R_4} = 3.08 \text{ V}$
- b)  $V_{R_4} = 30.47 \text{ V}$
- c)  $V_{R_4} = 272.57 \text{ V}$
- d)  $V_{R_4} = 1724.99 \text{ V}$ .

## Problem 2.64

### **Solution:**

#### **Known quantities:**

Schematic of the circuit shown in Figure P2.64, value of the components.

#### **Find:**

The current through  $R_5$  both with and without the ammeter, for the following values of the resistor  $R_5$  :

- a)  $R_5 = 1k\Omega$
- b)  $R_5 = 100\Omega$
- c)  $R_5 = 10\Omega$
- d)  $R_5 = 1\Omega$ .

#### **Analysis:**

First we should find an expression for the current through  $R_5$  in terms of  $R_5$  and the meter resistance,  $R_m$ . By the voltage divider rule we have:

$$V_{R_3} = \frac{R_3 \parallel (R_4 + R_5 + R_m) V_s}{R_3 \parallel (R_4 + R_5 + R_m) + R_2 + (R_1 \parallel R_s)}$$

and

$$I_{R_3} = \frac{V_{R_3}}{R_4 + R_5 + R_m}$$

Therefore,

$$\begin{aligned} I_{R_3} &= \frac{R_3 \parallel (R_4 + R_5 + R_m) V_s}{R_3 \parallel (R_4 + R_5 + R_m) + R_2 + (R_1 \parallel R_s)} \cdot \frac{1}{R_4 + R_5 + R_m} \\ &= \frac{5904}{208350 + 373 \cdot (R_m + R_s)} \end{aligned}$$

Using the above equation will give us the following table:

	with meter in circuit	without meter in circuit
a	10.15 mA	9.99 mA
b	24.03 mA	23.15 mA
c	27.84 mA	26.67 mA
d	28.29 mA	27.08 mA

## Problem 2.65

### Solution:

#### Known quantities:

Schematic of the circuit and geometry of the beam shown in Figure P2.65, characteristics of the material, reads on the bridge.

#### Find:

The force applied on the beam.

#### Assumptions:

Gage Factor for Strain gauge is 2

#### Analysis:

$R_1$  and  $R_2$  are in series;  $R_3$  and  $R_4$  are in series.

$$\text{Voltage Division: } V_{R_2} = \frac{V_S R_2}{R_1 + R_2} = \frac{V_S (R_0 - \Delta R)}{R_0 + \Delta R + R_0 - \Delta R} = \frac{V_S (R_0 - \Delta R)}{2R_0}$$

$$\text{Voltage Division: } V_{R_4} = \frac{V_S R_4}{R_3 + R_4} = \frac{V_S (R_0 + \Delta R)}{R_0 - \Delta R + R_0 + \Delta R} = \frac{V_S (R_0 + \Delta R)}{2R_0}$$

$$\text{KVL: } -V_{R_2} - V_{BA} + V_{R_4} = 0$$

$$V_{BA} = V_{R_4} - V_{R_2} = \frac{V_S (R_0 + \Delta R)}{2R_0} - \frac{V_S (R_0 - \Delta R)}{2R_0} = \frac{V_S 2\Delta R}{2R_0} = V_S GF \epsilon = \frac{V_S (2)(6)LF}{wh^2 Y}$$

$$F = \frac{V_{BA} wh^2 Y}{V_S 12L} = \frac{0.050 \text{ V} (0.025 \text{ m})(0.100 \text{ m})^2 69 \times 10^9 \frac{\text{N}}{\text{m}^2}}{12 \text{ V}(12) 0.3 \text{ m}} = 19.97 \text{ kN}.$$

## Problem 2.66

### Solution:

#### Known quantities:

Schematic of the circuit and geometry of the beam shown in Figure P2.65, characteristics of the material, reads on the bridge.

#### Find:

The force applied on the beam.

**Assumptions:**

Gage Factor for Strain gauge is 2

**Analysis:**

$R_1$  and  $R_2$  are in series;  $R_3$  and  $R_4$  are in series.

$$\text{VD: } V_{R_2} = \frac{V_S R_2}{R_1 + R_2} = \frac{V_S (R_0 - \Delta R)}{R_0 + \Delta R + R_0 - \Delta R} = \frac{V_S (R_0 - \Delta R)}{2R_0}$$

$$\text{VD: } V_{R_4} = \frac{V_S R_4}{R_3 + R_4} = \frac{V_S (R_0 + \Delta R)}{R_0 - \Delta R + R_0 + \Delta R} = \frac{V_S (R_0 + \Delta R)}{2R_0}$$

$$\text{KVL: } -V_{R_2} - V_{BA} + V_{R_4} = 0$$

$$V_{BA} = V_{R_4} - V_{R_2} = \frac{V_S (R_0 + \Delta R)}{2R_0} - \frac{V_S (R_0 - \Delta R)}{2R_0} = \frac{V_S 2\Delta R}{2R_0} = V_S GF \epsilon = \frac{V_S (2)(6)LF}{wh^2 y}$$

$$F = 1.3 \times 10^6 \text{ N} = \frac{V_{BA} wh^2 y}{V_S 12L} = \frac{V_{BA} (0.03 \text{ m})(0.07 \text{ m})^2 200 \times 10^9 \frac{\text{N}}{\text{m}^2}}{24V(12)1.7m}$$

$$V_{BA} = \frac{1.3 \times 10^6 \text{ N} \times 24V(12)1.7m}{(0.03 \text{ m})(0.07 \text{ m})^2 200 \times 10^9 \frac{\text{N}}{\text{m}^2}} = 21.6 \text{ V}$$


---