

Chapter 17 Instructor Notes

The objective of Chapter 17 is to introduce the foundations for the analysis of rotating electric machines. In Section 17.1, rotating electric machines are classified on the basis of their energy conversion characteristics and of the nature of the electric power they absorb (or generate). Section 17.2 reviews the physical structure of a DC machine and presents a simple general circuit model that is valid for both motors and generators, including dynamic equations. Section 17.3 contains a brief discussion of DC generators. Section 17.4 describes the characteristics of the various configurations of DC motors, both of the wound stator and permanent magnet types. The torque speed characteristics of the different configurations are compared, and the dynamic equations are given for each type of motor. The section ends with a brief qualitative discussion of speed control in DC motors.

The second half of the chapter is devoted to the analysis of AC machines. In Section 17.5, we introduce the concept of a rotating magnetic field. The next two sections describe synchronous generators and motors; the discussion is brief, but includes the analysis of circuit models of synchronous machines and a few examples. Circuit models for the induction motor, as well as general performance characteristics of this class of machines are discussed in Section 17.8, including a brief treatment of AC machine speed and torque control. Although the discussion of the AC machines is not particularly detailed, all of the important concepts that a non-electrical engineer would be interested in to evaluate the performance characteristics of these machines are introduced in the chapter, and reinforced in the homework problem set. The homework problems include a mix of traditional electric machinery problems based on circuit models and of more system-oriented problems. Problems 17.24-36 deal with the performance and dynamics of systems including DC motors. These problems are derived from the author's experience in teaching a Mechanical Engineering System Dynamics course with emphasis on electromechanics, and are somewhat unusual (although relevant and useful for non-electrical engineers) in this type of textbook. These problems are well suited to a more mature audience that has already been exposed to a first course in system dynamics. Problem 17.39 provides a link to the power electronics topics covered in Chapter 12. All other problems are based on the content of the chapter.

Learning Objectives

1. Understand the basic principles of operation of rotating electric machines, their classification, and basic efficiency and performance characteristics. [Section 1.](#)
2. Understand the operation and basic configurations of separately-excited, permanent-magnet, shunt and series DC machines. [Section 2.](#)
3. Analyze DC generators at steady-state. [Section 3.](#)
4. Analyze DC motors under steady-state and dynamic operation. [Section 4.](#)
5. Understand the operation and basic configuration of AC machines, including the synchronous motor and generator, and the induction machine. [Sections 5, 6, 7, 8.](#)

Section 17.1: Rotating Electric Machines

Problem 17.1

Solution:

Known quantities:

The relationship of the power rating and the ambient temperature is shown in the table. A motor with $P_e = 10\text{ kW}$ is rated up to 85°C .

Find:

The actual power for the following conditions.

- Ambient temperature is 50°C .
- Ambient temperature is 25°C .

Assumptions:

None.

Analysis:

a)

The power at ambient temperature 50°C :

$$P_e' = 10 - 10 \times 0.125 = 8.75\text{ kW}$$

b)

The power at ambient temperature 30°C :

$$P_e' = 10 + 10 \times 0.08 = 10.8\text{ kW}$$

Problem 17.2

Solution:

Known quantities:

The speed-torque characteristic of an induction motor is shown in the table. The load requires a starting torque of $4\text{ N} \cdot \text{m}$ and increase linearly with speed to $8\text{ N} \cdot \text{m}$ at 1500 rev/min .

Find:


- The steady state operating point of the motor.
- The change in voltage if the load torque increases to $10\text{ N} \cdot \text{m}$.

Assumptions:

None.

Analysis:

The characteristic is shown below:

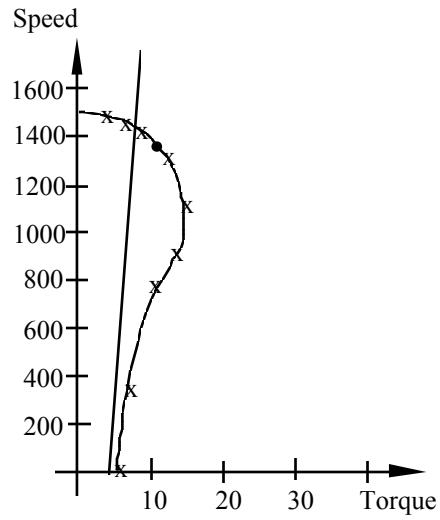

a)

The operating point is:

$$n_m = 1425 \text{ rev/min}, \quad T = 7 \text{ N} \cdot \text{m}$$

b)

From the following equation:

$$\frac{T_{new}}{T_{old}} = \left| \frac{V_{s,new}}{V_{s,old}} \right|^2$$

$$\Rightarrow \frac{10}{7} = \left| \frac{KV_s}{V_s} \right|^2 = K^2$$

$$\Rightarrow K = 1.195$$

$$\therefore V_{s,new} = 1.195 V_{s,old}$$

Section 17.2: Direct Current Machines

Problem 17.3

Solution:

Known quantities:

Each conductor of the DC motor is 6 in. long. The current is 90 A. The field density is $5.2 \times 10^{-4}\text{ Wb/in}^2$.

Find:

The force exerted by each conductor on the armature.

Assumptions:

None.

Analysis:

$$F = BI \times l = 5.2 \times 10^{-4} \frac{\text{Wb}}{\text{in}^2} \times \frac{\text{in}^2}{(0.0254\text{ m})^2} \times 90 \times 6\text{ in} \times \frac{0.0254\text{ m}}{\text{in}}$$

$$= 11.06\text{ Nt}$$

Problem 17.4

Solution:

Known quantities:

The air-gap flux density of the DC machine is 4 Wb/m^2 . The area of the pole face is $2\text{ cm} \times 4\text{ cm}$.

Find:

The flux per pole in the machine.

Assumptions:

None.

Analysis:

With $B = 4\text{ kG} = 0.4\text{ T} = 0.4\text{ Wb/m}^2$, we can compute the flux to be:

$$\phi = BA = 0.4 \times 0.02 \times 0.04 = 0.32\text{ mWb}$$

Section 17.3: Direct Current Generators

Problem 17.5

Solution:

Known quantities:

A 120V, 10A shunt motor. The armature resistance is 0.6Ω . The shunt field current is 2A.

Find:

The LVDT equations.

Assumptions:

None.

Analysis:

V_L at full load is 120V and

$$E_b = 120 + (2 + 10) \times 0.6 = 127.2V$$

$$R_f = \frac{120}{2} = 60\Omega$$

Assuming E_b to be constant, we have:

$$i_a = i_f = \frac{127.2}{0.6 + 60} = 2.1A$$

Therefore:

$$V_L = 127.2 - 2.1 \times 0.6 = 125.9V$$

$$\text{Voltage reg.} = \frac{125.9 - 120}{120} = 0.049 = 4.9\%$$

Problem 17.6

Solution:

Known quantities:

A 20kW, 230V separately excited generator. The armature resistance is 0.2Ω . The load current is 100A.

Find:

- The generated voltage when the terminal voltage is 230V.
- The output power.

Assumptions:

None.

Analysis:

If we assume rated output voltage, that is $V_L = 230V$, we have

a)

The generated voltage is 230V.

b)

The output power is 23kW.

If we assume rated output power, that is $P_{out} = 20kW$, we have

a)

The generated voltage is $200V$.

b)

The output power is $20kW$.If we assume $E_b = 230V$, and compute the output voltage to be:

$$V_L = 230 - 100 \times 0.2 = 210V$$

We have:

a)

The generated voltage is $210V$.

b)

The output power is $21kW$.

Problem 17.7

Solution:

Known quantities:

A $10kW, 120VDC$ series generator. The armature resistance is 0.1Ω and a series field resistance is 0.05Ω .

Find:

a) The armature current.


b) The generated voltage.

Assumptions:

The generator is delivering rated current at rated speed.

Analysis:

The circuit is shown below:

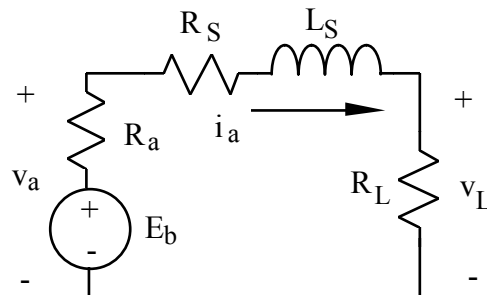

a)

$$i_a = \frac{P}{V_L} = \frac{10 \times 10^3}{120} = 83.33 A$$

b)

$$V_a = 120 + i_a R_s = 124.17V$$

Problem 17.8**Solution:****Known quantities:**

A 30 kW , 440 V shunt generator. The armature resistance is $0.1\ \Omega$ and a series field resistance is $200\ \Omega$.

Find:


- The power developed at rated load.
- The load, field, and armature currents.
- The electrical power loss.

Assumptions:

None.

Analysis:

The circuit is shown below:

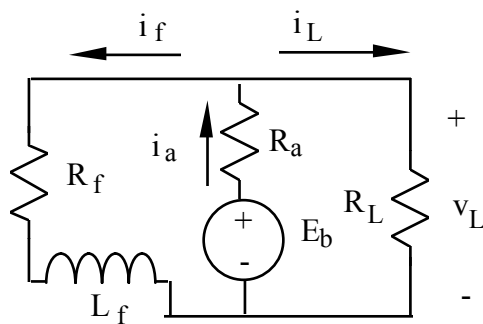

$$i_L = \frac{30 \times 10^3}{440} = 68.2\text{ A}$$

$$i_f = \frac{440}{200} = 2.2\text{ A}$$

$$i_a = 70.4\text{ A}$$

a)

$$E_b = V_L + i_a R_a = 440 + 70.4 \times 0.1 = 447.04\text{ V}$$

$$P = E_b i_a = 31.471\text{ kW}$$

b)

$$i_L = 62.8\text{ A}$$

$$i_f = 2.2\text{ A}$$

$$i_a = 70.4\text{ A}$$

c)

$$P_{\text{loss}} = i_a^2 R_a + i_f^2 R_f = 1464\text{ W}$$

Problem 17.9**Solution:****Known quantities:**

A four-pole 450 kW , 4.6 kV shunt generator. The armature resistance is $2\ \Omega$ and a series field resistance is $333\ \Omega$. The generator is operating at the rated speed of 3600 rev/min .

Find:

The no-load voltage of the generator and terminal voltage at half load.

Assumptions:

None.

Analysis:

For $n = 3600\text{ rev/min}$, $\omega_m = 377\text{ rad/sec}$:

$$i_L = \frac{450 \times 10^3}{4.6 \times 10^3} = 97.8\text{ A}$$

$$i_f = \frac{4.6 \times 10^3}{333} = 13.8\text{ A}$$

$$i_a = i_f + i_L = 111.6\text{ A}$$

Using the relation:

$$E_b = V_L + i_a R_a = 4823.2\text{ V}$$

At no-load,

$$V_L = E_b - i_a R_a = 4820.4\text{ V}$$

At half load,

$$i_L = 48.9\text{ A}$$

$$i_a = i_f + i_L = 62.7\text{ A}$$

$$V_L = E_b - i_a R_a = 4810.7\text{ V}$$

Problem 17.10**Solution:****Known quantities:**

A 30 kW , 240 V generator is running at half load at 1800 rev/min with efficiency of 85 percent.

Find:

The total losses and input power.

Assumptions:

None.

Analysis:

$$P_{out} = \frac{1}{2} \text{ rated load} = 15\text{ kW}$$

At an efficiency of 0.85, the input power can be computed to be:

$$P_{in} = \frac{15 \times 10^3}{0.85} = 17.647\text{ kW}$$

The total loss is:

$$P_{loss} = P_{in} - P_{out} = 2.647 \text{ kW}$$

Problem 17.11

Solution:

Known quantities:

A self excited DC shunt generator. At 200 rev/min , it delivers 20 A to a 100 V line. The armature resistance is 1.0Ω and a series field resistance is 100Ω . The magnetization characteristic is shown in Figure P17.11. When the generator is disconnected from the line, the drive motor speed up to 220 rad/s .

Find:

The terminal voltage.

Assumptions:

None.

Analysis:

From the figure, for $I_f > 0.5 \text{ A}$, $\omega = 200 \text{ rad/sec}$

$$E_b = 40I_f + 100$$

For $\omega = 220 \text{ rad/sec}$, we have:

$$\frac{E'_b}{220} = \frac{100 + 40I_f}{200}$$

Therefore,

$$E'_b = \frac{220}{200}(100 + 40I_f) = 110 + 44I_f$$

For no load, $I_a = I_f$. Therefore,

$$110 + 44I_f = 101I_f$$

$$\therefore I_f = 1.93 \text{ A}$$

The terminal voltage is:

$$V = I_f R_f = 193 \text{ V}$$

Section 17.4: Direct Current Motors

Problem 17.12

Solution:

Known quantities:

A 220V shunt motor. The armature resistance is $0.32\ \Omega$. A field resistance is $110\ \Omega$. At no load the armature current is $6\ A$ and the speed is $1800\ rpm$.

Find:

- The speed of the motor when the line current is $62\ A$.
- The speed regulation of the motor.

Assumptions:

The flux does not vary with load. Assume a $8\ N \cdot m$ brush drop.

Analysis:

a)

$$1800 = \frac{220 - 2 - 6(0.32)}{K_a \phi}$$

$$\Rightarrow K_a \phi = 0.12$$

$$\therefore n = \frac{220 - 2 - 6(0.32)}{K_a \phi} = 1657\ rpm$$

b)

$$\%reg = \frac{1800 - 1657}{1657} \times 100 = 8.65\%$$

Problem 17.13

Solution:

Known quantities:

A 50 hp, 550 volt shunt generator. The armature resistance including brushes is $0.36\ \Omega$. Operating at rated load and speed, the armature current is $75\ A$.

Find:

What resistance should be inserted in the armature circuit to get a 20 percent speed reduction when the motor is developing 70 percent of rated torque.

Assumptions:

There is no flux change.

Analysis:

$$T = K_a \phi I_a \Rightarrow I_a = 0.7(75) = 52.5\ A$$

$$n_R = \frac{550 - 75(0.36)}{K_a \phi} \Rightarrow K_a \phi n_R = 523$$

$$0.8n_R = \frac{550 - 52.5R_T}{K_a \phi} \Rightarrow 0.8 \times 523 = 550 - 52.5R_T$$

$$\therefore R_T = 2.51\ \Omega$$

$$R_{add} = 2.51 - 0.36 = 2.15\ \Omega$$

Problem 17.14
Solution:**Known quantities:**

A 100 kW , 440 V shunt DC motor. The armature resistance is $0.2\ \Omega$ and a series field resistance is $400\ \Omega$. The generator is operating at the rated speed of 1200 rev/min . The full-load efficiency is 90 percent.

Find:

- The motor line current.
- The field and armature currents.
- The counter emf at rated speed.
- The output torque.

Assumptions:

None.

Analysis:

At $n = 1200\text{ rev/min}$, $\omega_m = 125.7\text{ rad/sec}$, the output power is $100\text{ hp} = 74.6\text{ kW}$.

From full-load efficiency of 0.9, we have:

$$P_{in} = \frac{74.6}{0.9} = 82.9\text{ kW}$$

a)

From $P_{in} = i_s V_s = 82.9\text{ kW}$, we have:

$$i_s = \frac{82.9 \times 10^3}{440} = 188.4\text{ A}$$

b)

$$i_f = \frac{440}{400} = 1.1\text{ A}$$

$$i_a = 187.3\text{ A}$$

c)

$$E_b = V_L - i_a R_a = 402.5\text{ V}$$

d)

$$T_{out} = \frac{P_{out}}{\omega_m} = 593.5\text{ N} \cdot \text{m}$$

Problem 17.15**Solution:****Known quantities:**

A 240 V series motor. The armature resistance is $0.42\ \Omega$ and a series field resistance is $0.18\ \Omega$. The speed is 500 rev/min when the current is 36 A .

Find:

What is the motor speed when the load reduces the line current to 21 A .

Assumptions:

A 3 volts brush drop and the flux is proportional to the current.

Analysis:

$$500 = \frac{240 - 3 - 36(0.6)}{K_a \phi} \Rightarrow K_a \phi = 0.431$$

$$n = \frac{240 - 3 - 21(0.6)}{\left(\frac{21}{36}\right)(0.431)} = 893 \text{ rpm}$$

Problem 17.16**Solution:****Known quantities:**

A 220VDC shunt motor. The armature resistance is 0.2Ω . The rated armature current is 50 A.

Find:

- The voltage generated in the armature.
- The power developed.

Assumptions:

None.

Analysis:

a)

$$E_b = V_L - i_a R_a = 220 - 50 \times 0.2 = 210 \text{ V}$$

b)

$$P = E_b i_a = 210 \times 50 = 10.5 \text{ kW} = 14.07 \text{ hp}$$

Problem 17.17**Solution:****Known quantities:**

A 550V series motor. The armature resistance is 0.15Ω . The speed is 820 rev/min when the current is 112 A and the load is 75 hp.

Find:

The horsepower output of the motor when the current drops to 84 A.

Assumptions:

The flux is reduced by 15 percent.

Analysis:

$$HP = \frac{2\pi \cdot n \cdot T}{33,000}$$

$$75 = \frac{2\pi(820)T}{33,000} \Rightarrow T = 480.4 \text{ lb} \cdot \text{ft}$$

$$T = K_a \phi I_a \Rightarrow 480.4 = K_a \phi (112) \Rightarrow K_a \phi = 4.29$$

$$T_n = 4.29(0.85)(84) = 306.2 \text{ lb} \cdot \text{ft}$$

$$n_n = \frac{550 - 84(0.15)}{0.85(0.65)} = 973 \text{ rpm}$$

$$HP_n = \frac{2\pi(973)(306.2)}{33,000} = 56.7 \text{ hp}$$

Problem 17.18**Solution:****Known quantities:**

A 220VDC shunt motor. The armature resistance is 0.1Ω and a series field resistance is 100Ω .

The speed is 1100 rev/min when the current is 4 A and there is no load.

Find:

E and the rotational losses at 1100 rev/min .

Assumptions:

The stray-load losses can be neglected.

Analysis:

Since $n = 1100 \text{ rev/min}$ corresponds to $\omega = 115.2 \text{ rad/sec}$, we have:

$$i_s = 4 \text{ A}$$

$$i_f = \frac{200}{100} = 2 \text{ A}$$

$$i_a = i_s - i_f = 2 \text{ A}$$

Also,

$$E_b = 200 - 2 \times 0.1 = 199.8 \text{ V}$$

The power developed by the motor is:

$$\begin{aligned} P &= P_{in} - P_{copper_loss} \\ &= 200 \times 4 - (2^2 \times 100 + 2^2 \times 0.1) \\ &= 399.6 \text{ W} \end{aligned}$$

Problem 17.19**Solution:****Known quantities:**

A 230VDC shunt motor. The armature resistance is 0.5Ω and a series field resistance is 75Ω . At 1100 rev/min , $P_{rot} = 500\text{ W}$. When loaded, the current is 46 A .

Find:

- a) The speed P_{dev} and T_{sh} .
 b) $i_a(t)$ and $\omega_m(t)$ if $L_f = 25\text{ H}$, $L_a = 0.008\text{ H}$ and the terminal voltage has a 115 V change.

Assumptions:

None.

Analysis:

$$i_f = \frac{230}{75} = 3.07\text{ A}$$

$$i_a = i_L - i_f = 42.93\text{ A}$$

$$\omega_m = 117.3\text{ rad/sec}$$

At no load, $117.3 = \frac{230}{K_a\phi}$, therefore,

$$K_a\phi = 1.96$$

At full load,

$$\omega_m = \frac{230 - 0.5 \times 42.93}{K_a\phi}$$

The back emf is:

$$E_b = 230 - 0.5 \times 42.93 = 208.5\text{ V}$$

The power developed is:

$$P_{dev} = E_b I_a = 8.952\text{ kW}$$

The power available at the shaft is:

$$P_o = P_{dev} - P_{rot} = 8952 - 500 = 8452\text{ W}$$

The torque available at the shaft is:

$$T_{sh} = \frac{P_o}{\omega_m} = 72.1\text{ N} \cdot \text{m}$$

Problem 17.20**Solution:****Known quantities:**

A 200VDC shunt motor. The armature resistance is 0.1Ω and a series field resistance is 100Ω . At 955 rev/min with no load, $P_{rot} = 500W$, the line current is 5 A.

Find:

The motor speed, the motor efficiency, total losses, and the load torque when the motor draws 40 A from the line.

Assumptions:

Rotational power losses are proportional to the square of shaft speed.

Analysis:

$$i_s = 5 A$$

$$i_f = \frac{200}{100} = 2 A$$

$$i_a = i_s - i_f = 3 A$$

The copper loss is:

$$P_{copper} = i_f^2 R_f + i_a^2 R_a = 400.9 W$$

The input power is:

$$P_{in} = 5 \times 200 = 1 kW$$

Therefore,

$$P_{rot} + P_{SL} = 1000 - 409 = 599.1 W$$

$$\text{at } \omega_m = 2\pi \frac{955}{60} = 100 \text{ rad/sec}.$$

Also, E_b at no load is:

$$E_b = 200 - 3 \times 0.1 = 199.7 V$$

$$K_a \phi = 1.997$$

When $i_s = 40 A$ with $i_f = 2 A$ and $i_a = 38 A$,

$$E_b = 200 - 38 \times 0.1 = 196.2 V$$

$$\omega_m = \frac{E_b}{K_a \phi} = 98.25 \text{ rad/sec} = 938.2 \text{ rev/min}$$

The power developed is:

$$P = E_b I_a = 196.2 \times 38 = 7456 W$$

The copper loss is:

$$P_{copper} = i_f^2 R_f + i_a^2 R_a = 544.4 W$$

The input power is:

$$P_{in} = 40 \times 200 = 8 kW$$

And

$$P_{SH} = 7456 - \frac{98.25}{100} \times 599.1 = 6867.4 \text{ W}$$

$$T_{SH} = \frac{6867.4}{98.25} = 69.9 \text{ N} \cdot \text{m}$$

Finally, the efficiency is:

$$eff = \frac{P_{SH}}{P_{in}} = 85.84\%$$

Problem 17.21

Solution:

Known quantities:

A 50 hp, 230V shunt motor operates at full load when the line current is 181 A at 1350 rev/min. The field resistance is 17.7 Ω. To increase the speed to 1600 rev/min, a resistance of 5.3 Ω is cut in via the field rheostat. The line current is increased to 190 A.

Find:

- The power loss in the field and its percentage of the total power input for the 1350 rev/min speed.
- The power losses in the field and the field rheostat for the 1600 rev/min speed.
- The percent losses in the field and in the field rheostat at 1600 rev/min speed.

Assumptions:

None.

Analysis:

a)

$$I_f = \frac{230}{17.7} = 13.0 \text{ A}$$

$$P_f = (230)(13.0) = 2988.7 \text{ W}$$

$$\frac{P_f}{P_m} = \frac{2988.7}{(230)(181)} = 0.072 = 7.2\%$$

b)

$$I_f = \frac{230}{(17.7 + 5.3)} = 10 \text{ A}$$

$$P_f = 10^2(17.7) = 1770 \text{ W}$$

$$P_R = 10^2(5.3) = 530 \text{ W}$$

c)

$$P_{in} = (230)(190) = 43,700 \text{ W}$$

$$\%P_f = \frac{1770}{43700} \times 100 = 4.05\%$$

$$\%P_R = \frac{530}{43700} \times 100 = 1.21\%$$

Problem 17.22**Solution:****Known quantities:**

A 10 hp, 230 V shunt-wound motor. The armature resistance is 0.26Ω and a series field resistance is 225Ω . The rated speed is 1000 rev/min . The full-load efficiency is 86 percent.

Find:

The effect on counter emf, armature current and torque when the motor is operating under rated load and the field flux is very quickly reduced to 50 percent of its normal value. The effect on the operation of the motor and its speed when stable operating conditions have been regained.

Assumptions:

None.

Analysis:

$E_C = K\phi n$; counter emf will decrease.

$I_a = \frac{V - E_C}{r_a}$; armature current will increase.

$T = K\phi I_a$; effect on torque is indeterminate.

Operation of a dc motor under weakened field conditions is frequently done when speed control is an important factor and where decreased efficiency and less than rated torque output are lesser considerations.

$$n = \frac{V - I_a r_a}{K\phi} \Rightarrow 1000 = \frac{V - I_a r_a}{K\phi}$$

$$n_{new} = \frac{V - I_a r_a}{0.5K\phi}$$

Assume small change in the steady-state value of I_a . Then:

$$\frac{1000}{n_{new}} = \frac{0.5}{1} \Rightarrow n_{new} = 2000 \text{ rpm}$$

Problem 17.23**Solution:****Known quantities:**

The machine is the same as that in Example 17.7. The circuit is shown in Figure P17.23. The armature resistance is 0.2Ω and the field resistance is negligible. $n = 120 \text{ rev/min}$, $I_a = 8 \text{ A}$. In the operating region, $\phi = kI_f$, $k = 200$.

Find:

- The number of field winding turns necessary for full-load operation.
- The torque output for the following speeds:

$$1. \ n' = 2n \quad 3. \ n' = n/2$$

$$2. \ n' = 3n \quad 4. \ n' = n/4$$

- Plot the speed-torque characteristic for the conditions of part b.

Assumptions:

None.

Analysis:

in Example 17.7, $i_f = 0.6 \text{ A}$, the mmf F is:

$$F = 200 \times 0.6 = 120 \text{ At}$$

For a series field winding with:

a)

$i_{series} = i_a = 8 \text{ A}$, we have:

$$N_{series} = \frac{120}{8} = 15 \text{ turns}$$

b)

$$n_m = 120 \text{ rev/min}$$

$$\omega_m = 12.57 \text{ rad/sec}$$

$$E_b = V_s - i_a(R_a + R_s)$$

Neglecting R_s , we have

$$E_b = 7.2 - 8 \times 0.2 = 5.6 \text{ V} = k_a \phi \omega_m$$

$$k_a \phi = \frac{5.6}{12.57} = 0.446$$

From $T = k_T \phi i_a$ and $k_T = k_a$,

$$T = 0.446 \times 8 = 3.56 \text{ N} \cdot \text{m}$$

By using $\phi = k i_a$, we have:

$$E_b = k_a k i_a \omega_m = V_s - i_a R_a$$

$$T = k_T (k i_a) i_a = k_a k i_a^2$$

From $i_a = \frac{V_s}{R_a + K \omega_m}$, where $K = k_a k = \frac{5.6}{8 \times 12.57} = 0.056$

And $T \propto \left(\frac{1}{R_a + K \omega_m} \right)^2$, we have:

$$\frac{T_x}{T} = \left(\frac{R_a + K \omega_m}{R_a + K \omega_x} \right)^2 = \left(\frac{\frac{R_a}{K} + \omega_m}{\frac{R_a}{K} + \omega_x} \right)^2$$

$$\therefore \frac{R_a}{K} = 3.59$$

$$\therefore T_x = 3.56 \left(\frac{3.59 + \omega_m}{3.59 + \omega_x} \right)^2$$

1. at $\omega_x = 2\omega_m = 25.12 \text{ rad/sec}$,

$$T_x = 1.13 \text{ N} \cdot \text{m}$$

2. at $\omega_x = 3\omega_m = 37.71 \text{ rad/sec}$,

$$T_x = 0.55 \text{ N} \cdot \text{m}$$

3. at $\omega_x = 0.5\omega_m = 6.28 \text{ rad/sec}$,


$$T_x = 9.54 \text{ N} \cdot \text{m}$$

$$4. \text{ at } \omega_x = 0.25\omega_m = 3.14 \text{ rad/sec},$$

$$T_x = 20.53 \text{ N} \cdot \text{m}$$

c)

The diagram is shown below:

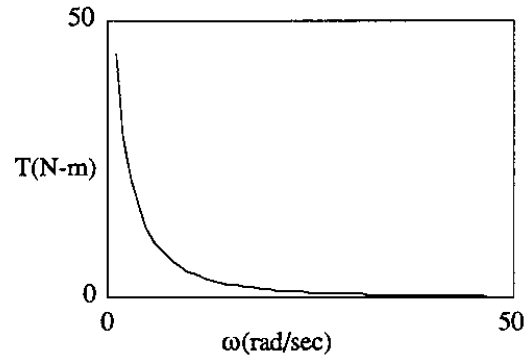

Problem 17.24

Solution:

Known quantities:

PM DC motor circuit model; mechanical load model. Example 17.9.

Find:

Voltage-step response of motor.

Assumptions:

None.

Analysis:

Applying KVL and equation 17.47 to the electrical circuit we obtain:

$$V_L(t) - R_a I_a(t) - L_a \frac{dI_a(t)}{dt} - E_b(t) = 0$$

or

$$L_a \frac{dI_a(t)}{dt} + R_a I_a(t) - K_{aPM} \omega_m(t) = V_L(t)$$

Applying Newton's Second Law and equation 17.46 to the load inertia, we obtain:

$$J \frac{d\omega_m(t)}{dt} + T(t) - T_{Load}(t) = b \omega_m(t)$$

or

$$K_{TPM} I_a(t) - J \frac{d\omega_m(t)}{dt} - b \omega_m(t) = 0$$

since the load torque is assumed to be zero. To derive the transfer function from voltage to speed, we use the result of Example 17.9 with $T_{load} = 0$:

$$m(s) = \frac{K_{TPM}}{sL_a + R_a + (sJ + b) K_{aPM} K_{TPM}} V_L(s)$$

The step response of the system can be computed by assuming a unit step input in voltage:

$$m(s) = \frac{K_{TPM}}{sL_a + R_a + (sJ + b) K_{aPM} K_{TPM}} \frac{1}{s}$$

$$F(s) = \frac{K_{TPM}}{(sL_a + R_a)(sJ + b) + K_{aPM}K_{TPM}} \frac{1}{s}$$

$$F(s) = \frac{K_{TPM}}{s[JL_a s^2 + (L_a b + R_a J)s + R_a b + K_a K_T]}$$

$$F(s) = \frac{K_{TPM}}{s \left[s^2 + \frac{(L_a b + R_a J)}{JL_a} s + \frac{(R_a b + K_a K_T)}{JL_a} \right]}$$

Set:

$$m = \frac{(L_a b + R_a J)}{JL_a} \quad n = \frac{(R_a b + K_a K_T)}{JL_a}$$

$$F(s) = \frac{K_{TPM}}{s[s^2 + ms + n]} = \frac{K_{TPM}}{s \left[\left(s^2 + ms + \frac{m^2}{4} \right) + n - \frac{m^2}{4} \right]} = \frac{K_{TPM}}{s \left[\left(s + \frac{m}{2} \right)^2 + \left(n - \frac{m^2}{4} \right) \right]}$$

For

$$F(s) = \frac{1}{s[(s-a)^2 + b^2]} \quad f(t) = \frac{1}{b_o} \frac{1}{bb_o} e^{-at} \sin(bt)$$

$$\text{where : } a = \tan^{-1} \frac{b}{a} \quad \text{and } b_o = \sqrt{b^2 - a^2}$$

Therefore:

$$a = \frac{m}{2} = \frac{(L_a b + R_a J)}{2JL_a} \quad b = \sqrt{n - \frac{m^2}{4}} = \sqrt{\frac{R_a b + K_a K_T}{JL_a} - \left(\frac{L_a b + R_a J}{JL_a} \right)^2 \frac{1}{4}}$$

$$b_o^2 = \left[\frac{(L_a b + R_a J)}{2JL_a} \right]^2 + \frac{R_a b + K_a K_T}{JL_a} - \left(\frac{L_a b + R_a J}{JL_a} \right)^2 \frac{1}{4} = \frac{R_a b + K_a K_T}{JL_a}$$

$$\phi = \tan^{-1} \frac{\sqrt{\frac{R_a b + K_a K_T}{JL_a} - \left(\frac{L_a b + R_a J}{JL_a} \right)^2 \frac{1}{4}}}{-\frac{(L_a b + R_a J)}{2JL_a}}$$

Thus giving the step response:

$$\Omega_m(t) = \frac{JL_a}{R_a b + K_a K_T} + \frac{1}{\left(\sqrt{\frac{R_a b + K_a K_T}{JL_a} - \left(\frac{L_a b + R_a J}{JL_a} \right)^2 \frac{1}{4}} \right) \left(\sqrt{\frac{R_a b + K_a K_T}{JL_a}} \right)} e^{-\left[\frac{(L_a b + R_a J)}{2JL_a} \right] t} * \sin \left[\left(\sqrt{\frac{R_a b + K_a K_T}{JL_a} - \left(\frac{L_a b + R_a J}{JL_a} \right)^2 \frac{1}{4}} \right) t - \tan^{-1} \frac{\sqrt{\frac{R_a b + K_a K_T}{JL_a} - \left(\frac{L_a b + R_a J}{JL_a} \right)^2 \frac{1}{4}}}{-\frac{(L_a b + R_a J)}{2JL_a}} \right]$$

Expressions for the natural frequency and damping ratio of the second-order system may be derived by comparing the motor voltage-speed transfer function to a standard second-order system transfer function:

$$H(s) = \frac{K_S}{s^2 \frac{1}{2\zeta\omega_n s} \omega_n^2}$$

The motor transfer function is:

$$\frac{\omega_m(s)}{V_L(s)} = \frac{K_{TPM}}{sL_a R_a (sJ + b) K_{aPM} K_{TPM}} = \frac{K_{TPM}}{JL_a s^2 + JR_a bL_a s + R_a b K_{aPM} K_{TPM}}$$

$$\frac{K_{TPM}}{JL_a s^2 + \frac{JR_a bL_a}{JL_a} s + \frac{R_a b K_{aPM} K_{TPM}}{JL_a}}$$

Comparing terms, we determine that:

$$\omega_n^2 = \frac{R_a b K_{aPM} K_{TPM}}{JL_a}$$

$$2\zeta\omega_n = \frac{JR_a bL_a}{JL_a}$$

or

$$\omega_n = \sqrt{\frac{R_a b K_{aPM} K_{TPM}}{JL_a}}$$

$$\zeta = \frac{1}{2} \frac{JR_a bL_a}{JL_a} \sqrt{\frac{JL_a}{R_a b K_{aPM} K_{TPM}}}$$

From these expressions, we can see that both natural frequency and damping ratio are affected by each of the parameters of the system, and that one cannot predict the nature of the damping without knowing numerical values of the parameters.

Problem 17.25

Solution:

Known quantities:

Torque-speed curves of motor and load: $T_m = a\omega + b$ (motor), $T_L = c\omega^2 + d$ (load),

Find:

Equilibrium speeds and their stability.

Assumptions:

All coefficients of torque-speed curve functions are positive constants

Analysis:

The first consideration is that the motor static torque, $T_{0,m} = b$ must exceed the load static torque, $T_{0,L} = d$; thus, the first condition is $b > d$.

The next step is to determine the steady state speed of the motor-load pair. If we set the motor torque equal to the load torque, the resulting angular velocities will be the desired solutions.

$$T_m = T_L \quad a\omega + b = c\omega^2 + d$$


resulting in the quadratic equation

$$c\omega^2 + a\omega + d - b = 0$$

with solution

$$\omega = \frac{-a \pm \sqrt{a^2 - 4c(b-d)}}{2c}$$

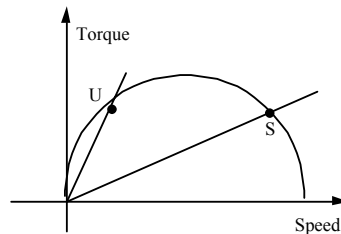Both solutions are positive, and therefore physically acceptable. The question of stability can be addressed by considering the following sketch.



In the figure, we see that the intersection of a line with a quadratic function when both solutions are positive leads to two possible situations: the line intersecting the parabola when the rate of change of both curves is positive, and the line intersecting the parabola when the rate of change of torque w.r. to speed of the latter is negative. The first case leads to an unstable operating point; the second case to a stable operating point (you can argue each case qualitatively by assuming a small increase in load torque and evaluating the consequences). We can state this condition mathematically by requiring that the following steady-state stability condition hold:

$$\frac{dT_L}{d\omega} > \frac{dT_m}{d\omega}$$

Evaluating this for our case, we see that

$$\frac{dT_L}{d\omega} = 0 > \frac{dT_m}{d\omega} = 2c\omega + a$$

From the expression we obtained earlier,

$$\omega = \frac{-a \pm \sqrt{a^2 - 4c(b-d)}}{2c}$$

it is clear that $2c\omega + a > 0$ always holds, since the term under the square root is a positive constant. Thus, this motor-load pair always leads to stable solutions. To verify this conclusion intuitively, you might wish to plot the motor and load torque-speed curves and confirm that the condition $\frac{dT_L}{d\omega} > \frac{dT_m}{d\omega}$ is always satisfied (note that the sketch above is **not** an accurate graphical representation of the two curves).

Problem 17.26**Solution:****Known quantities:**

Expression for friction and windage torque, T_{FW} , functional form of motor torque, T , or load torque, T_L .

Find:


Sketch torque-speed curve

Assumptions:

None.

Analysis:

The sketches are shown below.

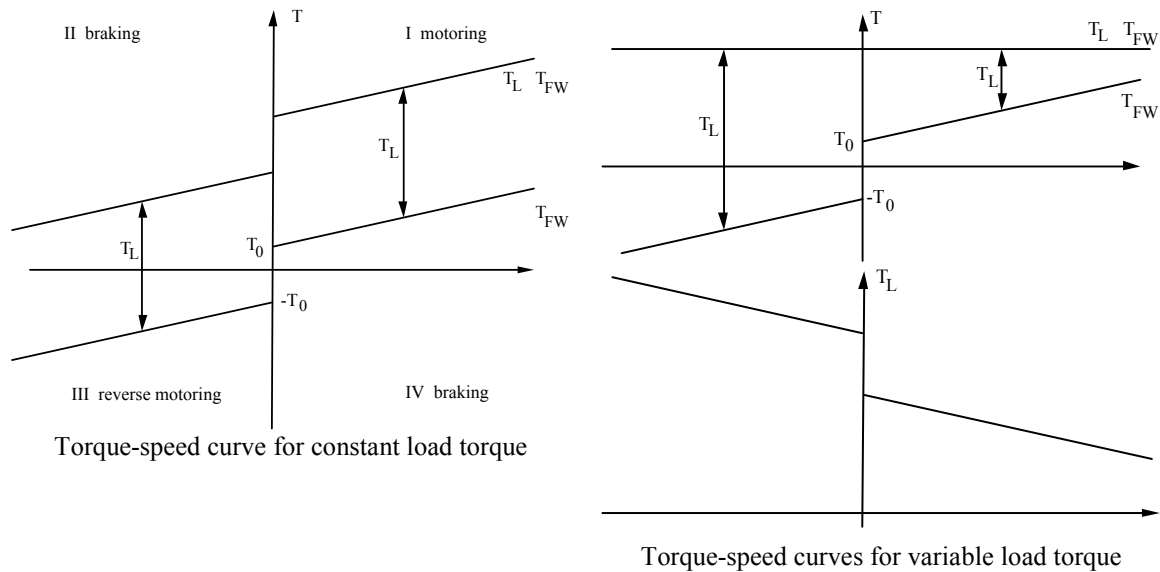**Problem 17.27****Solution:****Known Quantities:**

A PM DC motor and parameters when 1) in steady-state, no load conditions, and 2) connected to a pump

Find:

- A damping coefficient, sketch of the motor, the dynamic equations, the transfer function, and 3 dB bandwidth.
- A sketch of the motor, dynamic equations, transfer function, and 3 dB bandwidth.

Assumptions: k_t k_a k_{PM} **Analysis:**


a)

The magnetic torque balanced the damping torque gives s:

$$k_t * i_a - b * \omega_m$$

or

$$b = \frac{k_{PM} * i_a}{\omega_m} = \frac{7 * 10^{-3} \frac{\text{N} \cdot \text{m}}{\text{A}} * .15 \text{ A}}{\frac{3350 \text{ rev}}{\text{min}} * \frac{2 \text{ rad}}{\text{rev}} * \frac{1 \text{ min}}{60 \text{ sec}}} = 2.993 * 10^{-6} \text{ N} \cdot \text{m} \cdot \text{sec}$$

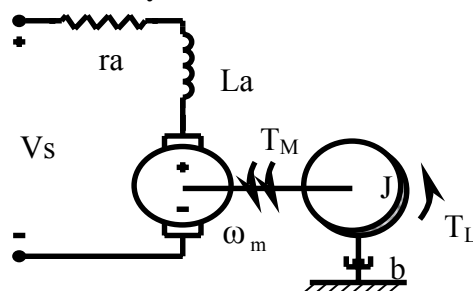Sketch: **PM DC Motor-Load System**

Dynamic equations:

$$\begin{aligned}
 V_s &= L_a \frac{di_a}{dt} + r_a i_a + E_b \\
 E_b &= k_{PM} \omega_m \\
 V_s &= L_a \frac{di_a}{dt} + r_a i_a + k_{PM} \omega_m \\
 J \frac{d\omega_m}{dt} &= T_m - T_L - b \omega_m \\
 T_m &= k_{PM} i_a \\
 T_L &= J \frac{d\omega_m}{dt} + b \omega_m + k_{PM} i_a
 \end{aligned}$$

To get the transfer function:


$$\begin{bmatrix} (L_a s + r_a) & k_{PM} \\ -k_{PM} & (J s + b) \end{bmatrix} \begin{bmatrix} i_a \\ \omega_m \end{bmatrix} = \begin{bmatrix} V_s \\ -T_L \end{bmatrix}$$

$$\omega_m(s) = \frac{\det \begin{bmatrix} (L_a s + r_a) & V_s \\ -k_{PM} & -T_L \end{bmatrix}}{\det \begin{bmatrix} (L_a s + r_a) & k_{PM} \\ -k_{PM} & (J s + b) \end{bmatrix}}$$

$$\left. \frac{\omega_m(s)}{V_s} \right|_{T_L=0} = \frac{k_{PM}}{(J * L_a) s^2 + (r_a * J + L_a * b) s + r_a * b + k_{PM}^2}$$

b)

Sketch:

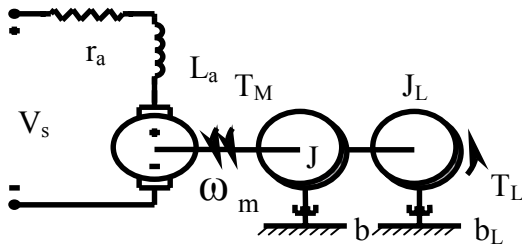

Dynamic Equations:

$$\begin{aligned}
 V_s &= L_a \frac{di_a}{dt} + r_a i_a + E_b \\
 E_b &= k_{PM} \omega_m \\
 V_s &= L_a \frac{di_a}{dt} + r_a i_a + k_{PM} \omega_m \\
 (J + J_L) \frac{d\omega_m}{dt} &= T_m - T_L - (b + b_L) \omega_m \\
 T_m &= k_{PM} i_a \\
 T_L &= (J + J_L) \frac{d\omega_m}{dt} + (b + b_L) \omega_m + k_{PM} i_a
 \end{aligned}$$


To get the transfer function:

$$\begin{bmatrix} (L_a s + r_a) & k_{PM} \\ -k_{PM} & ((J + J_L)s + (b + b_L)) \end{bmatrix} \begin{bmatrix} i_a \\ \omega_m \end{bmatrix} = \begin{bmatrix} V_s \\ -T_L \end{bmatrix}$$

$$\omega_m(s) = \frac{\det \begin{bmatrix} (L_a s + r_a) & V_s \\ -k_{PM} & -T_L \end{bmatrix}}{\det \begin{bmatrix} (L_a s + r_a) & k_{PM} \\ -k_{PM} & ((J + J_L)s + (b + b_L)) \end{bmatrix}}$$

$$\left. \frac{\omega_m(s)}{V_s} \right|_{T_L=0} = \frac{k_{PM}}{((J + J_L) * L_a) s^2 + (r_a * (J + J_L) + L_a * (b + b_L)) s + r_a * (b + b_L) + k_{PM}^2}$$

Frequency Response:

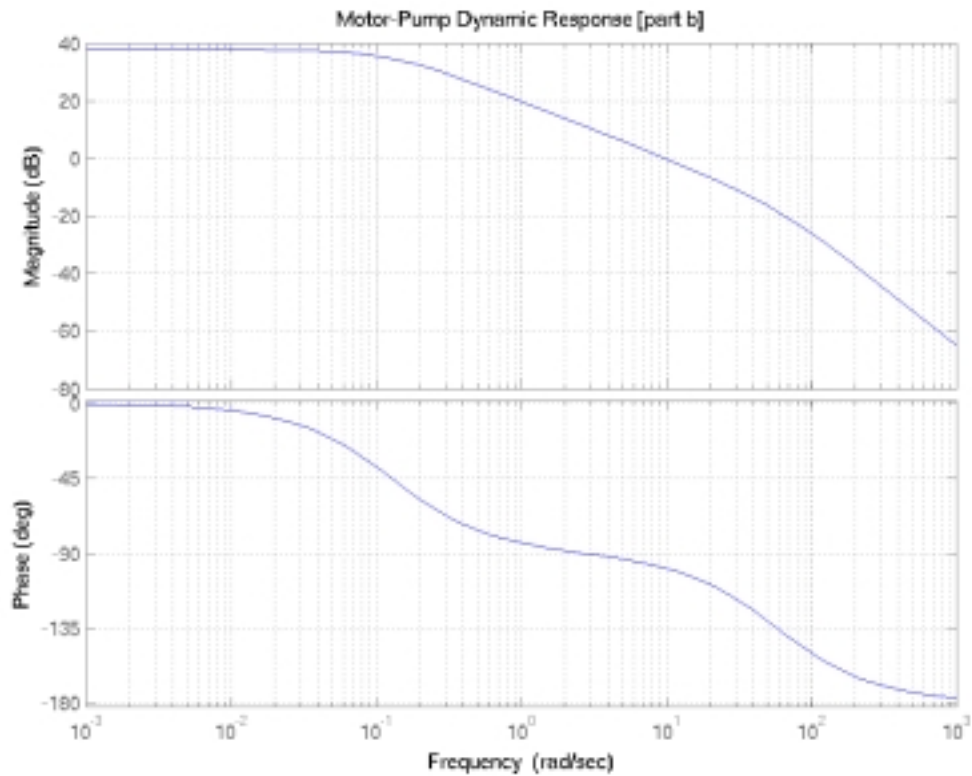

Problem 17.28

Solution:

Known Quantities:

A PM DC motor is used to power a pump

Find:


The dynamic equations of the system and the transfer function between the motor voltage and pressure.

Assumptions:

The inertia and damping of the motor and pump can be lumped together.

Analysis:

Sketch:

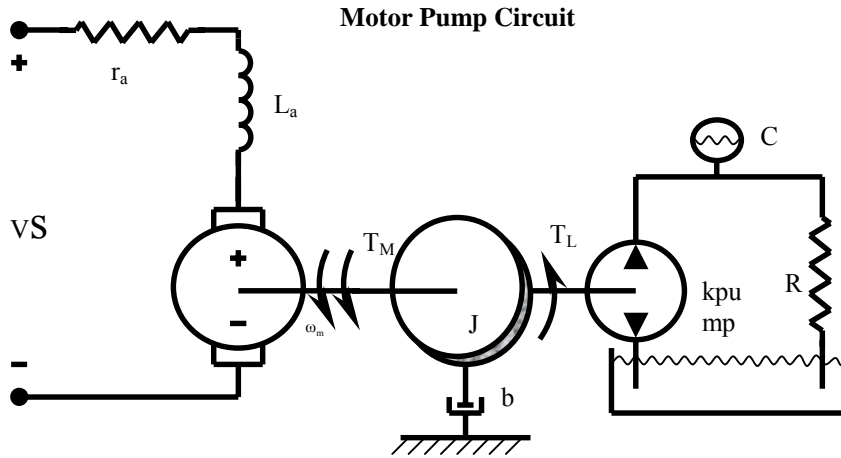

$$V_s = L_a \frac{di_a}{dt} + r_a i_a + E_b$$

$$V_s = L_a \frac{di_a}{dt} + r_a i_a + k_{PM} \omega_m$$

$$J \frac{d\omega_m}{dt} = T_M - T_L - b \omega_m$$

$$T_L = J \frac{d\omega_m}{dt} + b \omega_m + k_{PM} \omega_m$$

$$k_p \omega_m = \frac{p - 0}{R} = C_{acc} \frac{dp}{dt}$$

$$C_{acc} \frac{dp}{dt} = \frac{p}{R} - k_p \omega_m = 0$$

To get the transfer function:

$$\begin{bmatrix} L_a s + r_a & k_{PM} & 0 \\ -k_{PM} & Js + b & k_p \\ 0 & -Rk_p & RC_{acc}s + 1 \end{bmatrix} \begin{bmatrix} i_a \\ \omega_m \\ p \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \\ 0 \end{bmatrix}$$

$$p(s) = \frac{\det \begin{bmatrix} L_a s + r_a & k_{PM} & V_s \\ -k_{PM} & Js + b & 0 \\ 0 & -Rk_p & 0 \end{bmatrix}}{\det \begin{bmatrix} L_a s + r_a & k_{PM} & 0 \\ -k_{PM} & Js + b & k_p \\ 0 & -Rk_p & RC_{acc}s + 1 \end{bmatrix}}$$

$$\frac{p}{V_s}(s) = \frac{k_{PM} R k_p}{(L_a s + r_a)(Js + b)(RC_{acc}s + 1) + k_{PM}^2 (RC_{acc}s + 1) + R k_p^2 (L_a s + r_a)}$$

Problem 17.29**Solution:****Known quantities:**

Motor circuit shown in Figure P17.29 and magnetization parameters, load parameters. Operating point.

Note correction to the operating point: $I_{a0} = 186.67$ A;

Note correction to the parameter: $k_f = 0.12$ V-s/A-rad

Find:

- a) System differential equations in symbolic form
- b) Linearized equations

Assumptions:

The dynamics of the field circuit are negligible.

Analysis:

- a) Differential equations

Applying KVL and equation 17.47 to the electrical circuit we obtain:

$$L_f \frac{dI_f(t)}{dt} + R_f I_f(t) = V_S(t) \quad \text{field circuit}$$

or

$$L_a \frac{dI_a(t)}{dt} + R_a I_a(t) - k_f I_f(t) = m(t) \quad \text{armature circuit}$$

Applying Newton's Second Law and equation 17.46 to the load inertia, we obtain:

$$J \frac{d\omega_m(t)}{dt} + T_m(t) - T_L(t) = b \omega_m(t)$$

or

$$k_f I_f(t) I_a(t) - J \frac{d\omega_m(t)}{dt} - b \omega_m(t) = T_L(t)$$

Since the dynamics of the field circuit are much faster than those of the armature circuit (time constant

$\frac{L_f}{R_f}$ vs $\frac{L_a}{R_a}$), we can write $I_f = \frac{V_S}{R_f}$ and the system of equations is now:

$$L_a \frac{dI_a(t)}{dt} + R_a I_a(t) - k_f \frac{V_S(t)}{R_f} = m(t)$$

$$k_f \frac{V_S(t)}{R_f} I_a(t) - J \frac{d\omega_m(t)}{dt} - b \omega_m(t) = T_L(t)$$

- b) Linearization

Define perturbation variables:

$$I_a(t) = \bar{I}_a + \tilde{I}_a(t)$$

$$\omega_m(t) = \bar{\omega}_m + \tilde{\omega}_m(t)$$

$$V_S(t) = \bar{V}_S + \tilde{V}_S(t)$$

Next, we write the steady-state equations (all derivatives equal to zero):

$$R_a \bar{I}_a - k_f \frac{\bar{V}_S}{R_f} = \bar{m}$$

$$k_f \frac{\bar{V}_S}{R_f} \bar{I}_a - b \bar{\omega}_m = \bar{T}_L$$

These equations must be satisfied at the operating point. We can verify this using numerical values:

$$0.75 \quad \bar{I}_a \quad 0.12 \frac{150}{60} 200 \quad 200$$

resulting in

$$\bar{I}_a \quad \frac{1}{0.75} 200 \quad 0.12 \frac{150}{60} 200 \quad 186.67$$

$$0.12 \frac{150}{60} 186.67 \quad 0.6 \quad 200 \quad \bar{T}_L$$

resulting in

$$\bar{T}_L \quad 56 \quad 120 \quad 64 \text{ N} \cdot \text{m}$$

Now, given that the system is operating at the stated operating point, we can linearize the differential equation for the perturbation variables around the operating point. To linearize the equation we recognize

the nonlinear terms: $k_f \frac{V_S(t)}{R_f} m(t)$ and $k_f \frac{V_S(t)}{R_f} I_a(t)$.

To linearize these terms, we use the first-order term in the Taylor series expansion:

$$k_f \frac{V_S(t)}{R_f} m(t) \approx \left. \frac{k_f}{R_f} \frac{V_S(t)}{V_S} m(t) \right|_{\bar{V}_S, \bar{m}} V_S(t) \frac{k_f}{R_f} \frac{V_S(t)}{m} m(t) \Big|_{\bar{V}_S, \bar{m}} m(t)$$

$$\frac{k_f}{R_f} \bar{m} V_S(t) - \bar{V}_S m(t)$$

$$k_f \frac{V_S(t)}{R_f} I_a(t) \approx \left. \frac{k_f}{R_f} \frac{V_S(t) I_a(t)}{V_S} \right|_{\bar{V}_S, \bar{I}_a} V_S(t) \frac{k_f}{R_f} \frac{V_S(t) I_a(t)}{I_a} \Big|_{\bar{V}_S, \bar{I}_a} \bar{I}_a(t)$$

$$\frac{k_f}{R_f} \bar{I}_a V_S(t) - \bar{V}_S I_a(t)$$

Now we can write the linearized differential equations in the perturbation variables:

$$L_a \frac{d I_a(t)}{dt} = R_a I_a(t) - \frac{k_f}{R_f} \bar{V}_S m(t) - V_S(t) \frac{k_f}{R_f} \bar{m} V_S(t)$$

$$\frac{k_f}{R_f} \bar{V}_S I_a(t) - J \frac{d m(t)}{dt} = b m(t) - \bar{I}_a V_S(t) - T_L(t)$$

This set of equations is now linear, and numerical values can be substituted to obtain a numerical answer, valid in the neighborhood of the operating point, for given voltage and load torque inputs to the system.

Problem 17.30

Solution:

Known Quantities:

$$T_L = 5 + 0.05 \omega + 0.001 \omega^2$$

$$k_{TPM} = k_{APM} = 2.42$$

$$R_a = 0.2$$

$$V_S = 50V$$

Find:

What will the speed of rotation be of the fan?

Assumptions:

The fan is operating at constant speed.

Analysis:

Applying KVL for a PM DC motor (note at constant current short inductor)

$$V_s = i_a R_a + E_b \quad (\text{eqn. 17.48})$$

$$i_a = \frac{T}{k_{TPM}}$$

$$E_b = k_{aPM} \omega_m$$

$$V_s = \frac{T}{k_{TPM}} R_a + k_{aPM} \omega_m$$

$$T = T_L = 5 \text{ N} \cdot \text{m} = 0.001 \text{ m}^2$$

$$V_s = \frac{5 \text{ N} \cdot \text{m} \cdot 0.001 \text{ m}^2}{k_{TPM}} R_a + k_{aPM} \omega_m$$

Plug in the known variables and solving for ω_m .

$$50 \text{ V} = 5 \text{ N} \cdot \text{m} \cdot 0.001 \text{ m}^2 \cdot \frac{0.02}{2.42 \text{ N} \cdot \text{m/Amp}} + 2.42 \text{ V} \cdot \text{sec/rad} \cdot \omega_m$$

$$8.26 \times 10^{-5} \text{ m}^2 = 2.42 \cdot 4.13 \times 10^{-3} \text{ m} \cdot (\omega_m - 50 \cdot 0.413) \cdot 0$$

$$\omega_m = 20.5, \text{ or } -29318 \text{ rad/sec}$$

$$\omega_m = 20.5 \text{ rad/sec}$$

$$N_m = 20.5 \text{ rad/sec} \cdot \frac{60 \text{ sec}}{\text{min}} \cdot \frac{\text{rev}}{2} = 196 \text{ RPM}$$

Problem 17.31

Solution:

Known Quantities:

A separately excited DC motor

$$R_a = 0.1 \Omega, R_f = 100 \Omega, L_a = 0.2 \text{ H}, L_f = 0.02 \text{ H}, K_a = 0.8, K_f = 0.9$$

$$J = 0.5 \text{ kg} \cdot \text{m}^2, b = 2 \text{ N} \cdot \text{m} \cdot \text{rad} / \text{s}$$

Find:

- A sketch of the system and its three differential equations
- Sketch a simulation block diagram
- Put the diagram into Simulink
- Run the simulation with *Armature Control* with a constant field voltage $V_f = 100 \text{ V}$
Plot the current and angular speed responses
Run the simulation with *Field Control* with a constant armature voltage $V_a = 100 \text{ V}$
Plot the current and angular speed responses


Assumptions:

No external load torque is applied

Analysis:

- Sketch:

Separately Excited DC Motor

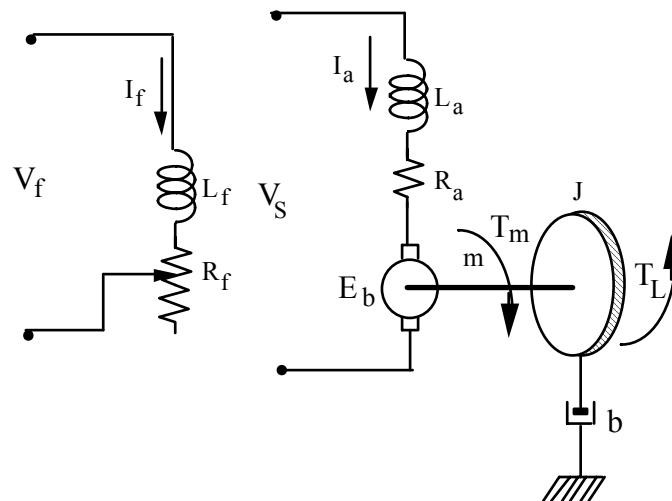


The three dynamic equations are:

$$V_f - L_f \frac{dI_f}{dt} - R_f I_f = 0$$


$$V_a - L_a \frac{dI_a}{dt} - R_a I_a - E_b = 0$$

$$J \frac{d\omega}{dt} + b \omega = T_m - T_L = k_a I_a - k_a I_a k_f I_f$$


b) Simulink block diagram

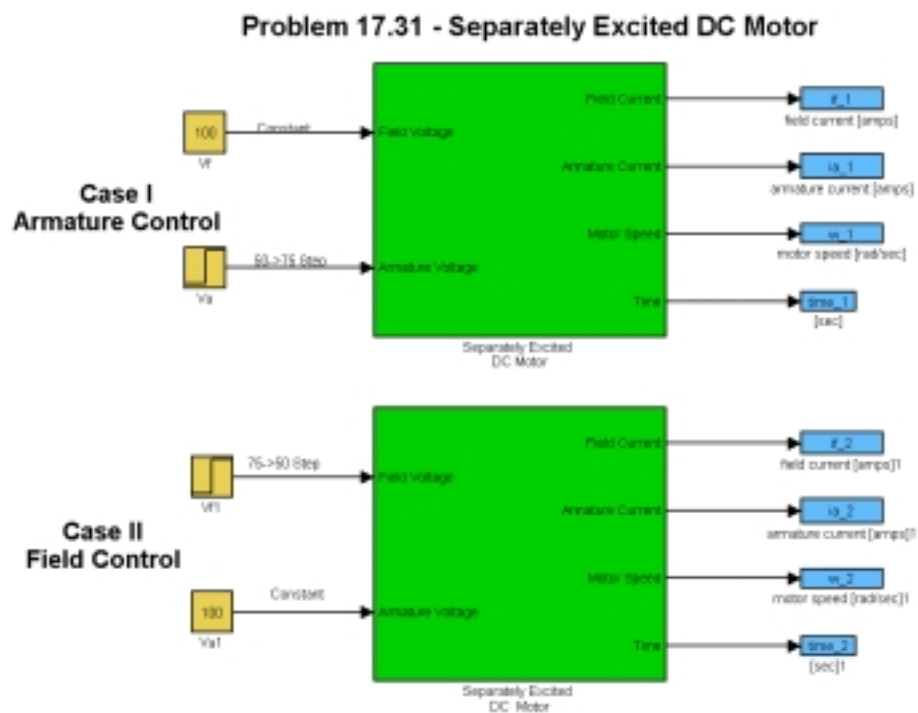


Simulink DC Motor Subsystem

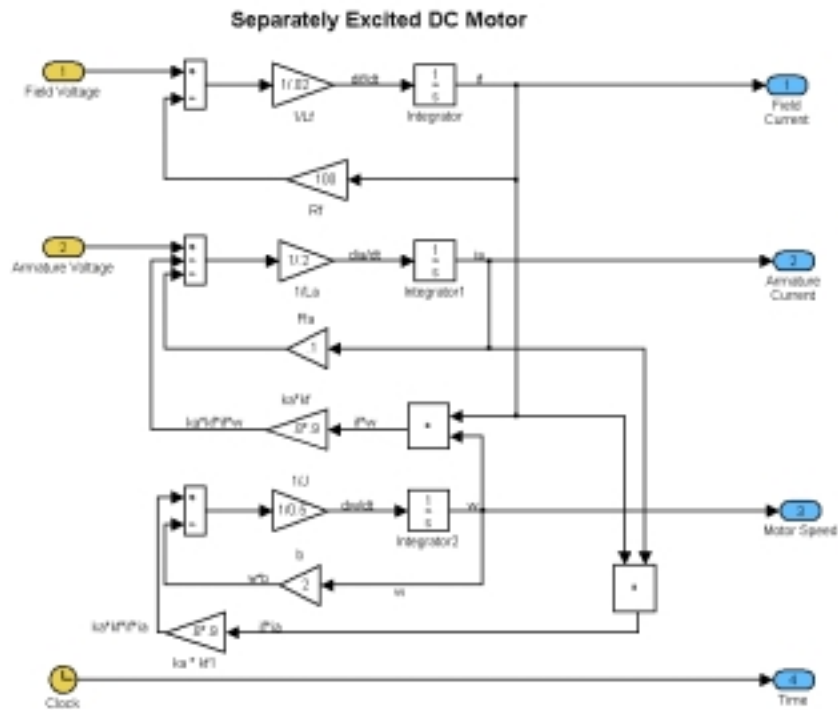

d) Simulink Responses:
Armature Control:

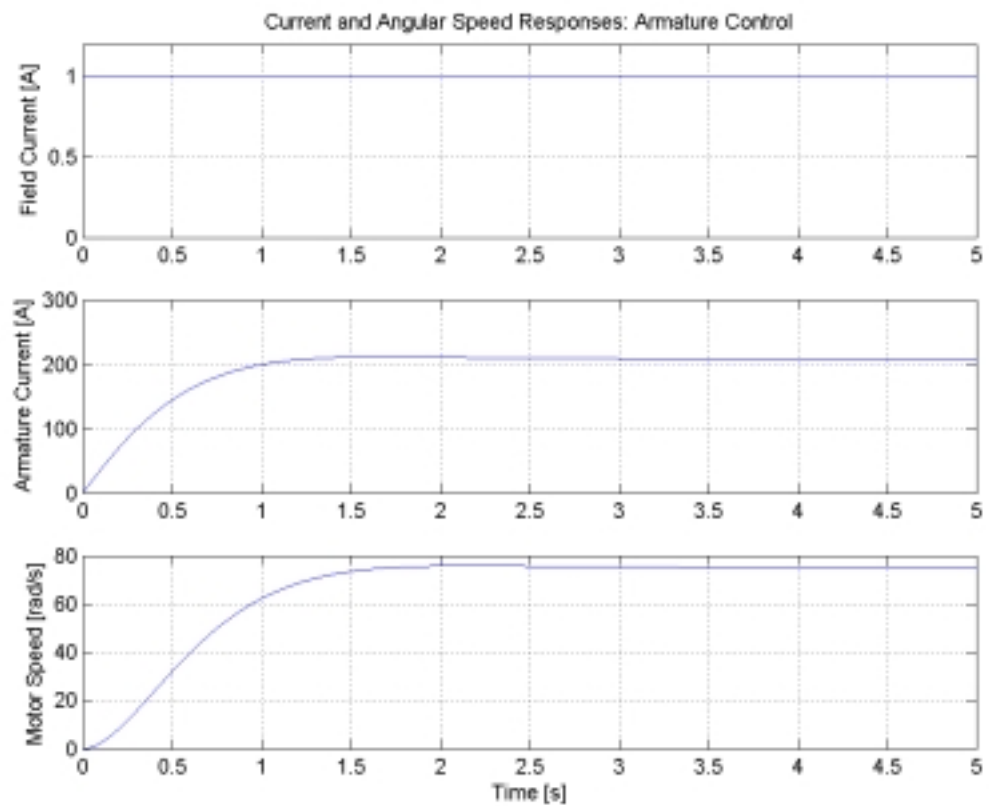

Field Control:

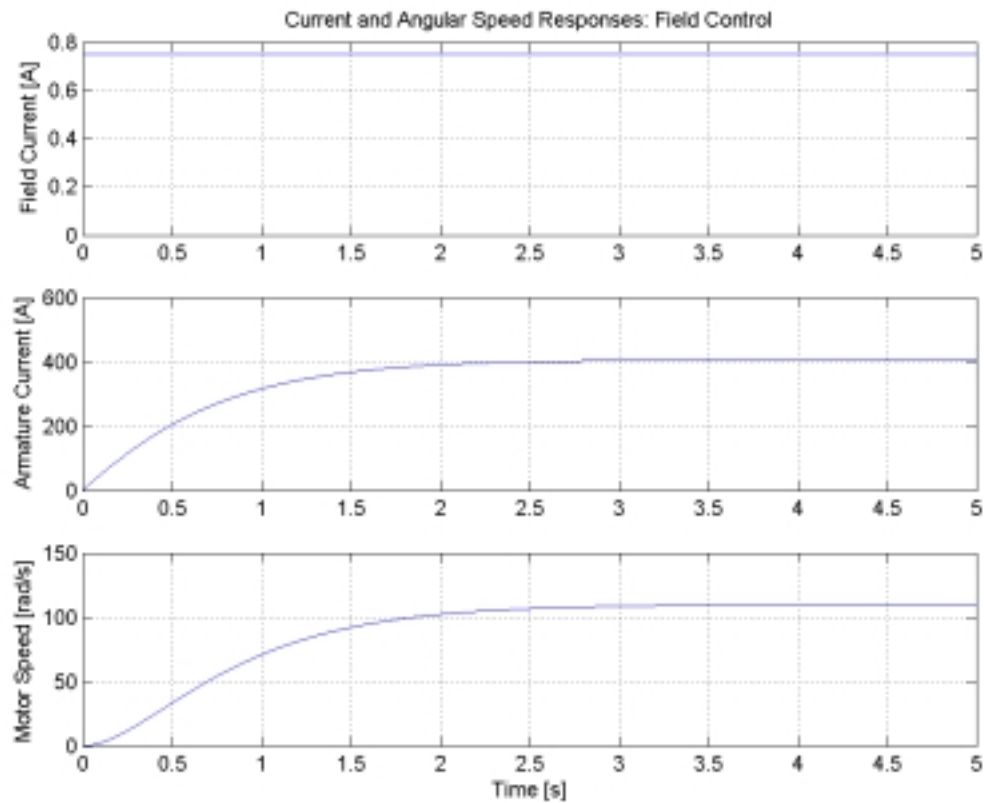

Problem 17.32

Solution:

Known quantities:

$$R_a, L_a, k_a = k_T, J_m, b_m, J, b, T_L.$$

Find:

Transfer functions from armature voltage to angular velocity and from load torque to angular velocity.

Schematics, diagrams, circuits and given data.

See equations 17.16-18 and Figure 17.20.

Assumptions:

Analysis:

Applying KVL and equation 17.47 to the electrical circuit we obtain:

$$V_a(t) - R_a I_a(t) - L_a \frac{dI_a(t)}{dt} - E_b(t) = 0$$

or

$$L_a \frac{dI_a(t)}{dt} + R_a I_a(t) - k_a \omega_m(t) = V_a(t)$$

Applying Newton's Second Law and equation 17.46 to the load inertia, we obtain:

$$J_m \frac{d}{dt} T_m(t) = T_L(t) - b_m \dot{\theta}(t)$$

or

$$k_T I_a(t) - J_m \frac{d}{dt} T_m(t) = b_m \dot{\theta}(t) - T_L(t)$$

To derive the transfer function, we Laplace transform the two equations to obtain:

$$sL_a I_a(s) - R_a I_a(s) - k_a V_a(s) = 0$$

$$k_a I_a(s) - s J_m T_m(s) - J T_L(s) = b_m \dot{\theta}(s)$$

We can write the above equations in matrix form and resort to Cramer's rule to solve for $\Omega_m(s)$ as a function of $V_a(s)$ and $T_L(s)$.

$$\begin{bmatrix} sL_a & R_a & k_a \\ k_a & sJ_m & J \end{bmatrix} \begin{bmatrix} I_a(s) \\ T_m(s) \end{bmatrix} = \begin{bmatrix} V_a(s) \\ T_L(s) \end{bmatrix}$$

with solution

$$T_m(s) = \frac{\det \begin{bmatrix} sL_a & R_a & V_a(s) \\ k_a & T_L(s) & \end{bmatrix}}{\det \begin{bmatrix} sL_a & R_a & k_a \\ k_a & sJ_m & J \end{bmatrix}}$$

or

$$T_m(s) = \frac{sL_a R_a - k_a^2}{sL_a R_a - sJ_m J - b_m b} T_L(s) + \frac{k_a}{sL_a R_a - sJ_m J - b_m b} V_a(s)$$

and finally

$$\left. \frac{T_m(s)}{T_L(s)} \right|_{V_a(s)=0} = \frac{sL_a R_a - k_a^2}{sL_a R_a - sJ_m J - b_m b} \quad \left. \frac{T_m(s)}{V_a(s)} \right|_{T_L(s)=0} = \frac{k_a}{sL_a R_a - sJ_m J - b_m b}$$

Problem 17.33

Solution:

Known Quantities:

A PM DC motor that is coupled to a pump with a long shaft.

Find:

The dynamic equations of the system and the transfer function from input voltage to load inertia speed.


Assumptions:

The energy conversion is ideal.

Analysis:

Sketch:

PM DC Motor-Load Coupling

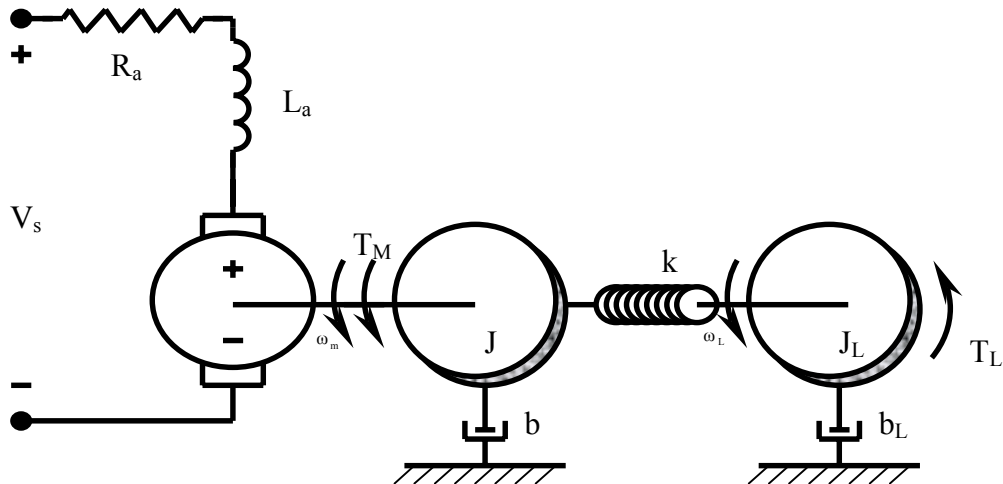

Knowing:

$$\frac{d}{dt} \quad \frac{1}{s}$$

Then the three dynamic equations for the system are:

$$V_a - L_a \frac{di_a}{dt} - R_a i_a = E_a = L_a \frac{di_a}{dt} + R_a i_a + k_a \omega_m$$

$$J_m \frac{d\omega_m}{dt} + b_m \omega_m + K \frac{\omega_m}{s} - k_a i_a = K \frac{\omega_L}{s} - T_L$$

$$J_L \frac{d\omega_L}{dt} + b_L \omega_L + K \frac{\omega_L}{s} - K \frac{\omega_m}{s} = T_L$$

Putting them in matrix form:

$$\begin{bmatrix} L_a s + R_a & k_a & 0 \\ -k_a & J_m s^2 + b_m s + K/s & -K/s \\ 0 & -K/s & J_L s^2 + b_L s + K/s \end{bmatrix} \begin{bmatrix} i_a \\ \omega_m \\ \omega_L \end{bmatrix} = \begin{bmatrix} V_a \\ 0 \\ -T_L \end{bmatrix}$$

$$\left. \frac{\omega_L}{V_a}(s) \right|_{T_L=0} = \frac{k_a K/s}{(L_a s + R_a)(J_m s + b_m + K/s)(J_L s + b_L + K/s) - (-K/s)^2 (L_a s + R_a) + (J_L s + b_L + K/s)(-k_a)(k_a)}$$

Problem 17.34

Solution:

Known quantities:


Field and armature circuit parameters; magnetization and armature constants; motor and load inertia and damping coefficients.

Find:

- sketch system diagrams for shunt and series configuration
- write expression for torque-speed curves for each configuration
- write the differential equations for each configuration
- determine whether equations are linear or nonlinear and how they could be linearized

Assumptions:**Analysis:**

a) System diagrams

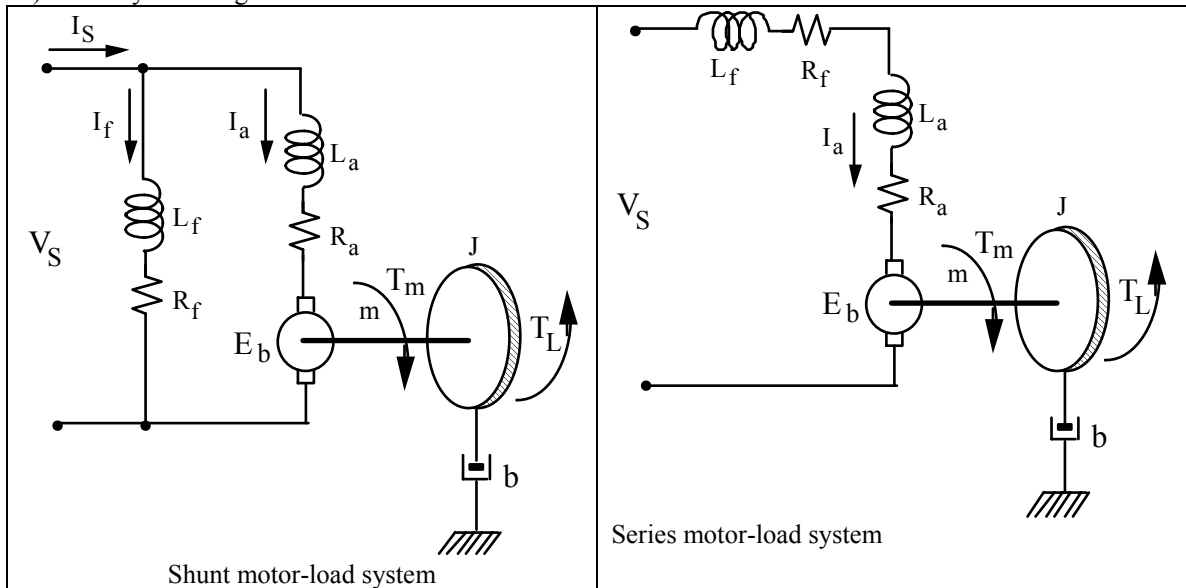

b) Write expressions for the torque-speed curves

Shunt configuration

Applying KVL and Newton's Second Law for the steady-state system we write:

$$V_S = R_f I_f \quad \text{field circuit}$$

and

$$V_S = R_a I_a + k_f I_f \omega_m \quad \text{armature circuit}$$

or

$$V_S = R_a I_a + k_f \frac{V_S}{R_f} \omega_m$$

$$T_m = k_f I_f I_a = k_f \frac{V_S}{R_f} I_a \quad \omega_m = T_L$$

To obtain the torque-speed curve of the motor (there will also be a load torque-speed equation, but we do not have any information on the nature of the load), we write:

$$T_m = k_f I_f I_a$$

$$I_a = \frac{T_m}{k_f I_f} = \frac{T_m R_f}{k_f V_S}$$

and substitute the expression for I_a in the electrical circuit equation:

$$V_S = R_a I_a + k_f \frac{V_S}{R_f} \omega_m = \frac{R_a R_f}{k_f V_S} T_m + k_f \frac{V_S}{R_f} \omega_m$$

or

$$T_m = \frac{k_f V_S}{R_a R_f} V_S - k_f \frac{V_S}{R_f} \omega_m = \frac{k_f V_S^2}{R_a R_f} - \frac{k_f^2 V_S^2}{R_a R_f^2} \omega_m$$

Series configuration

Applying KVL and Newton's Second Law for the steady-state system we write:

$$V_S = R_a I_a + R_f I_a + k_f I_a^2 \omega_m$$

$$T_m = k_f I_a^2 \omega_m - b \omega_m - T_L$$

To obtain the torque-speed curve of the motor (there will also be a load torque-speed equation, but we do not have any information on the nature of the load), we write:

$$I_a = \sqrt{\frac{T_m}{k_f}}$$

$$V_S = R_a I_a + R_f I_a + k_f I_a^2 \omega_m = R_a I_a + R_f \sqrt{\frac{T_m}{k_f}} + T_m \omega_m$$

which leads to a quadratic equation in T_m and ω_m .

c) Write the differential equations

Shunt configuration

Applying KVL and equation 17.47 to the electrical circuit we obtain:

$$L_f \frac{dI_f(t)}{dt} + R_f I_f(t) = V_S(t) \quad \text{field circuit}$$

or

$$L_a \frac{dI_a(t)}{dt} + R_a I_a(t) + k_f I_f(t) \omega_m(t) = V_S(t) \quad \text{armature circuit}$$

Applying Newton's Second Law and equation 17.46 to the load inertia, we obtain:

$$J \frac{d\omega_m(t)}{dt} = T_m(t) - T_L(t) - b \omega_m(t)$$

or

$$k_f I_f(t) I_a(t) - J \frac{d\omega_m(t)}{dt} - b \omega_m(t) = T_L(t)$$

Note that we have three differential equations that must be solved simultaneously. If the dynamics of the field circuit are much faster than those of the armature circuit (time constant $\frac{L_f}{R_f} \ll \frac{L_a}{R_a}$, as is often the

case) one can assume that the field current varies instantaneously with the supply voltage, leading to

$$I_f = \frac{V_S}{R_f} \quad \text{and to the equations:}$$

$$L_a \frac{dI_a(t)}{dt} + R_a I_a(t) + k_f \frac{V_S(t)}{R_f} \omega_m(t) = V_S(t)$$

$$k_f \frac{V_S(t)}{R_f} I_a(t) - J \frac{d\omega_m(t)}{dt} - b \omega_m(t) = T_L(t)$$

Series configuration

Applying KVL and equation 17.47 to the electrical circuit we obtain:

$$L_a \frac{dI_a(t)}{dt} + (R_a + R_f) I_a(t) + k_f I_a(t) \omega_m(t) = V_S(t)$$

Applying Newton's Second Law and equation 17.46 to the load inertia, we obtain:

$$J \frac{d\omega_m(t)}{dt} = T_m(t) - T_L(t) - b \omega_m(t)$$

or

$$k_f I_a^2(t) - J \frac{d\omega_m(t)}{dt} - b \omega_m(t) = T_L(t)$$

d) Determine whether the equations are nonlinear

Both systems of equations are nonlinear. In the shunt case, we have product terms in I_f and ω_m , and in I_f and I_a (or in V_S and ω_m and in V_S and I_a if we use the simplified system of two equations). In the series case, we have a quadratic term in I_a^2 and a product term in I_f and ω_m . In either case, no simple assumption leads

to a linear set of equations; thus either linearization or nonlinear solution methods (e.g.: numerical simulation) must be employed.

Problem 17.35

Solution:

Known quantities:

A shunt-connected DC motor shown in Figure P17.35

Motor parameters: k_a, k_T = armature and torque reluctance constant and k_f = field flux constant

Find:

Derive the differential equations describing the electrical and mechanical dynamics of the motor

Draw a simulation block diagram of the system

Assumptions:

None

Analysis:

Electrical subsystem


$$V_S(t) = L_f \frac{dI_f(t)}{dt} + R_f I_f(t) \quad \text{field}$$

$$V_S(t) = L_a \frac{dI_a(t)}{dt} + R_a I_a(t) + k_a \phi \omega_m(t) = L_a \frac{dI_a(t)}{dt} + R_a I_a(t) + k_a k_f I_f(t) \omega_m(t) \quad \text{armature}$$

Mechanical subsystem

$$J \frac{d\omega_m(t)}{dt} = T_m(t) - T_L(t) - b\omega_m(t) = k_a \phi I_a(t) - T_L(t) - b\omega_m(t) = k_a k_f I_f(t) I_a(t) - T_L(t) - b\omega_m(t)$$

Simulation block diagram:

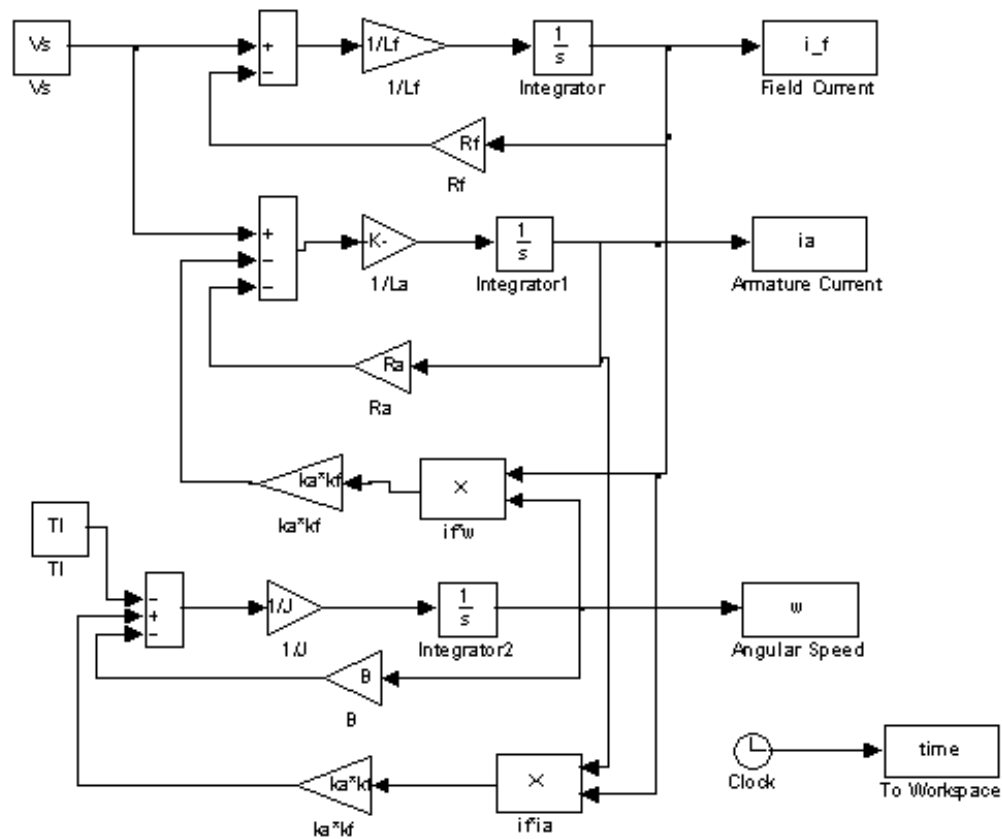

Problem 17.36

Solution:

Known quantities:

A series-connected DC motor shown in Figure P17.36

Motor parameters: k_a, k_T = armature and torque reluctance constant and k_f = field flux constant

Find:

Derive the differential equations describing the electrical and mechanical dynamics of the motor
Draw a simulation block diagram of the system

Assumptions:

None

Analysis:

Electrical subsystem

$$V_S(t) = L_a \frac{dI_a(t)}{dt} + R_a I_a(t) + k_a \omega_m(t)$$

$$V_S(t) = L \frac{dI_a(t)}{dt} + R I_a(t) + k_a k_f I_a(t) \omega_m(t)$$


$$\frac{dI_a(t)}{dt} = \frac{1}{L} V_S(t) - \frac{R}{L} I_a(t) - \frac{k_a k_f}{L} I_a(t) \omega_m(t)$$

Mechanical subsystem

$$J \frac{d\omega_m(t)}{dt} = T_m(t) - T_L(t) - b \omega_m(t) - k_T I_a(t) \omega_m(t) - k_T k_f I_a^2(t) \omega_m(t) - T_L(t) - b \omega_m(t)$$

$$\frac{d\omega_m(t)}{dt} = \frac{k_T k_f}{J} I_a^2(t) \omega_m(t) - \frac{1}{J} T_L(t) - \frac{b}{J} \omega_m(t)$$

Simulation block diagram:

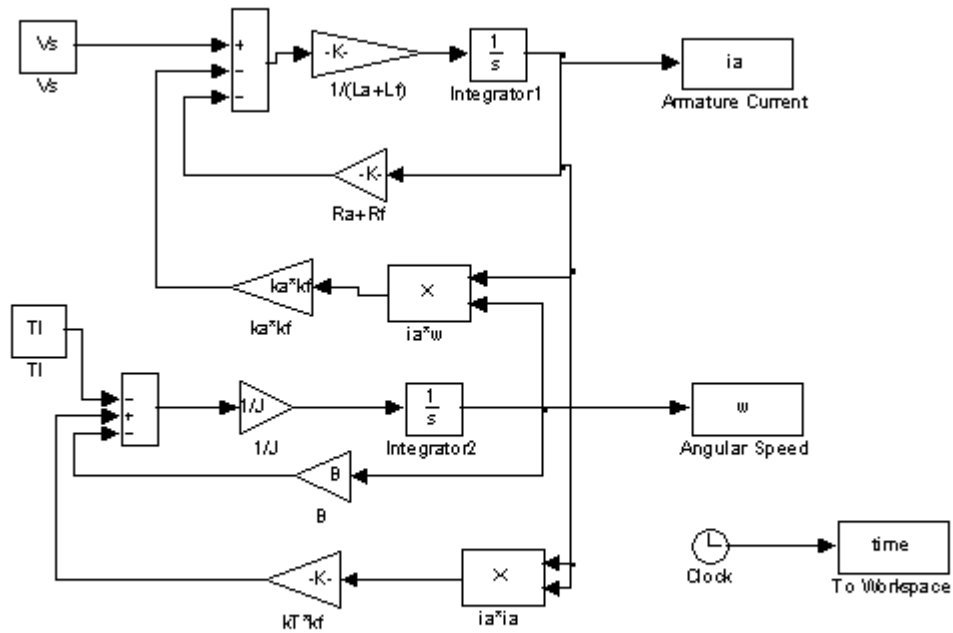

Section 17.6: The Alternator (Synchronous Generator)

Problem 17.37

Solution:

Known quantities:

A $550V \cdot A, 20V$ rated automotive alternator. At rated $V \cdot A$, the power factor is 0.85 . The resistance per phase is 0.05Ω . The field takes $2A$ at $12V$. The friction and windage loss is $25W$ and core loss is $30W$.

Find:

The percent efficiency under rated conditions.

Assumptions:

None.

Analysis:

$$I_a = \frac{500}{20} = 25A$$

$$P_a = I_a^2 R_a = 31.25W$$

$$P_{out} = 500(0.85) = 425W$$

$$P_f = 2(12) = 24W$$

$$P_{in} = P_{out} + P_a + 25 + 30 + 24 = 535.25W$$

$$\% = \frac{425}{535.25} \times 100 = 79.4\%$$

Problem 17.38

Solution:

Known quantities:

A three-phase $2300V, 500kV \cdot A$ synchronous generator. $X_s = 8.0\Omega, r_a = 0.1\Omega$. The machine is operating at rated load and voltage at a power factor of 0.867 lagging.

Find:

The generated voltage per phase and the torque angle.

Assumptions:

None.

Analysis:

$$\begin{aligned}
 I &= \frac{500k}{\sqrt{3}(2300)} = 125.5 \text{ A} \\
 E &= \frac{2300}{\sqrt{3}} \angle 0^\circ + 125.5 \angle -30^\circ (0.1 + j0.8) \\
 &= 1327.9 + 101.2 \angle 52.9^\circ \\
 &= 1389 + j80.7 \\
 &= 1391.3 \angle 3.3^\circ \text{ V} \\
 \therefore E &= 1391.3 \text{ V} \\
 \delta &= 3.3^\circ
 \end{aligned}$$

Problem 17.39**Solution:****Known quantities:**

As shown in Figure P17.39.

Find:

Explain the function of Q , D , Z , and SCR .

Assumptions:

None.

Analysis:

Q : The setting of R_1 determines the biasing of Q . When Q conducts, the SCR will fire, energizing the alternator's field.

D : This diode serves as a "free-wheeling" element, allowing the field current to circulate without interfering with the commutation of the SCR .

Z : The Zener diode provides a fixed reference voltage at the emitter of transistor Q ; i.e., determination of when Q conducts is controlled solely by the setting of R_1 .

SCR : The SCR acts as a half-wave rectifier, providing field excitation for the alternator. Without the field, of course, the alternator cannot generate.

Section 17.7: The Synchronous Motor

Problem 17.40

Solution:

Known quantities:

A non-salient pole, Y-connected, three phase, two-pole synchronous machine. The synchronous reactance is $7\ \Omega$ and the resistance and rotational losses are negligible. One point on the open-circuit characteristic is given by $V_0 = 400\text{ V}$ (phase voltage) for a field current of 3.32 A . The machine operates as a motor, with a terminal voltage of 400 V (phase voltage). The armature current is 50 A , with power factor 0.85 leading.

Find:


E_b , field current, torque developed, and power angle δ .

Assumptions:

None.

Analysis:

The per phase circuit is shown below:

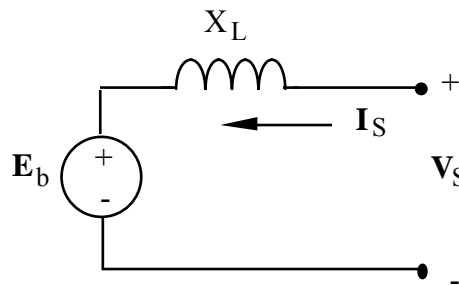

Since the power factor is 0.85 , we have:

$$\theta = 31.79^\circ$$

$$\omega_m = \frac{2\pi}{60} 3600 = 377\text{ rad/sec}$$

From $V_{OC} = 400\text{ V}$, we have

$$E_b = 400\text{ V (open circuit)} = k\omega_m i_f$$

$$\text{Therefore } k = \frac{400}{377 \times 3.32} = 0.3196$$

$$\begin{aligned} E_b &= 400\angle 0^\circ - 50\angle 31.79^\circ \times 7\angle 90^\circ \\ &= 400 + 184.38 - j297.49 \\ &= 655.74\angle -26.98^\circ\text{ V} \end{aligned}$$

$$i_f = \frac{E_b}{120.48} = 5.44\text{ A}$$

$$\theta_T = 31.79^\circ + 26.98^\circ = 58.77^\circ$$


The torque developed is:

$$T = \frac{3}{377} |E_b| |I_s| \cos \theta_T = 135.27\text{ N} \cdot \text{m}$$

δ is the angle from V to E_b :

$$\delta = -26.98^\circ$$

The phase diagram is shown below:

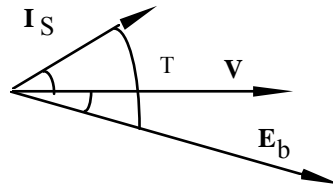

Problem 17.41

Solution:

Known quantities:

A factory load of 900 kW at 0.6 power factor lagging is increased by adding a 450 kW synchronous motor.

Find:

The power factor this motor operates at and the KVA input if the overall power factor is 0.9 lagging.

Assumptions:

None.

Analysis:

$$P_{old} = 900\text{ kW} \quad Q_{old} = 1200\text{ kVAR}$$

$$P_m = 450\text{ kW}$$

$$P_T = 1350\text{ kW} \quad Q_T = 653.8\text{ kVAR}$$

$$Q_m = 653.8 - 1200 = -546.2\text{ kVAR}$$

$$pf_m = \cos(\tan^{-1} \frac{Q_m}{P_m}) = 0.636 \text{ leading}$$

$$S_m = \frac{P_m}{pf_m} = 708\text{ kVA}$$

Problem 17.42

Solution:

Known quantities:

A non-salient pole, Y-connected, three phase, two-pole synchronous generator is connected to a 400 V (line to line), 60 Hz , three-phase line. The stator impedance is $0.5 + j1.6$ (per phase). The generator is delivering rated current 36 A at unity power factor to the line.

Find:

The power angle for this load and the value of E_b for this condition. Sketch the phasor diagram, showing E_b , I_S , and V_S .

Assumptions:

None.

Analysis:


$$V_L = \frac{400}{\sqrt{3}} \angle 0^\circ = 230.9 \angle 0^\circ \text{ V}$$

$$I_L = 36 \angle 0^\circ \text{ A}$$

$$Z_S = 0.5 + j1.6 = 1.676 \angle 72.65^\circ \Omega$$

$$\begin{aligned} E_b = V_L + I_L Z_S &= 248.9 + j57.6 \\ &= 255.5 \angle 13.03^\circ \text{ V} \end{aligned}$$

The power angle is 13.03° .

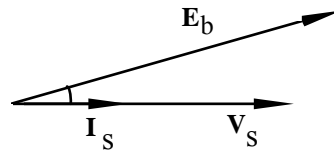**Problem 17.43****Solution:****Known quantities:**

A non-salient pole, three phase, two-pole synchronous generator is connected in parallel with a three-phase, Y-connected load. The equivalent circuit is shown in Figure P17.43. The parallel combination is connected to a 220V (line to line), three-phase line. The load current is 25 A at a power factor of 0.866 inductive. $X_S = 2 \Omega$. The motor is operating with $I_f = 1 \text{ A}$, $T = 50 \text{ N} \cdot \text{m}$ at a power angle of -30° .

Find:

I_S, P_{in} (to the motor), the overall power factor and the total power drawn from the line.

Assumptions:

Neglect all losses for the motor.

Analysis:

The phasor per-phase voltage is:

$$V_S = 127 \angle 0^\circ \text{ V}$$

$$T_{dev} = 50 \text{ N} \cdot \text{m} = -\frac{3}{377} \frac{|E_b| |V_S|}{X_S} \sin \delta$$

Therefore,

$$|E_b| = -\frac{50(377)2}{3(127) \sin(-30^\circ)} = 197.9 \text{ V}$$

$$E_b = 197.9 \angle -30^\circ \text{ V}$$

For $i_f = 1 \text{ A}$,

$$I_S = 49.47 + j22.2 = 54.23 \angle 24.16^\circ \text{ A}$$

The load current is:

$$I_L = 25 \angle -\cos^{-1} 0.866 = 21.65 - j12.5$$

and

$$I_1 = I_L + I_S = 71.12 + j9.7 = 71.78 \angle 7.77^\circ \text{ A}$$

$$P_{in_motor} = 3 \times 54.23 \times 127 \times \cos 24.16^\circ = 18.85 \text{ kW}$$

$$P_{in_total} = 3 \times 71.78 \times 127 \times \cos 7.77^\circ = 27.10 \text{ kW}$$

The power factor is:

$$pf = \cos 7.77^\circ = 0.991 \text{ leading}$$

Problem 17.44

Solution:

Known quantities:

A non-salient pole, Y-connected, three phase, four-pole synchronous machine. The synchronous reactance is 10Ω . It is connected to a $230\sqrt{3} \text{ V}$ (line to line), 60 Hz , three-phase line. The load requires a torque of $T_{shaft} = 30 \text{ N} \cdot \text{m}$. The line current is 15 A leading the phase voltage.

Find:

The power angle δ and E for this condition. The line current when the load is removed. Is it leading or lagging the voltage.

Assumptions:

All losses can be neglected.

Analysis:

At $\omega_m = 188.5 \text{ rad/sec}$, we can calculate

$$P_{out} = 30 \times 188.5 = 5655 \text{ W}$$

Since $P_{in} = P_{out}$ and $P'_{in} (\text{per phase}) = 1885 \text{ W} = 230 \times 15 \cos \theta$, we calculate

$$\theta = \cos^{-1} 0.5464 = 56.88^\circ$$

Since $V_S = 230 \angle 0^\circ \text{ V}$, $I_S = 15 \angle 56.88^\circ \text{ A}$

$$E_b = 355.6 - j81.96 = 364.92 \angle -12.98^\circ \text{ V}$$

The power angle is:

$$\delta = -12.98^\circ$$

If the load is removed, the power angle is 0° and from

$$364.92 \angle 0^\circ = 230 \angle 0^\circ - 10 \angle 90^\circ$$

$$\Rightarrow I = 13.495 \angle 90^\circ \text{ A}$$

The current is leading the voltage.

Problem 17.45**Solution:****Known quantities:**

A 10 hp , 230 V , 60 Hz Y-connected, three phase synchronous motor delivers full load at a power factor of 0.8 leading. The synchronous reactance is 6Ω . The rotational loss is 230 W , and the field loss is 50 W .

Find:

- The armature current.
- The motor efficiency.
- The power angle.

Assumptions:

Neglect the stator winding resistance.

Analysis:

$$P_{out} = 10\text{ hp} = 7460\text{ W}$$

$$P_{in} = P_{out} + P_r + P_{copper} = 7740$$

$$\therefore P_{in} (\text{per phase}) = 2580 = V_s I_s 0.8$$

$$V_s = \frac{230}{\sqrt{3}} = 132.8\text{ V}$$

$$\therefore I_s = \frac{2580}{132.8 \times 0.8} = 24.3\text{ A}$$

That is:

$$V_s = 132.8 \angle 0^\circ \text{ V}, \quad I_s = 24.3 \angle 36.87^\circ \text{ A}$$

$$E_b = V_s - I_s (6 \angle 90^\circ) = 249.2 \angle -27.9^\circ \text{ V}$$

a)

$$I_s = 24.3 \angle 36.87^\circ \text{ A}$$

b)

$$\text{efficiency} = \frac{7460}{7740} = 0.964 = 96.4\%$$

c)

$$\text{power angle} = -27.9^\circ$$

Problem 17.46**Solution:****Known quantities:**

A three-phase 2300 V , 60 Hz , 30 poles , 2000 hp , unity power factor synchronous motor.

$X_s = 1.95\Omega$ per phase.

Find:

The maximum power and torque.

Assumptions:

Neglect all losses.

Analysis:

$$n_s = \frac{3600}{15} = 240 \text{ rev/min}$$

$$\omega_s = 25.13 \text{ rad/sec}$$

At full load,

$$P_{in} = 746 \times 2000 = 1.492 \text{ MW}$$

$$V_s = \frac{2300}{\sqrt{3}} = 1327.9 \angle 0^\circ \text{ V}$$

For unity power factor,

$$I_s = 374.5 \angle 0^\circ \text{ A}$$

$$\begin{aligned} E_b &= V_s - I_s jX_s = 1327.9 - j730.3 \\ &= 1515.5 \angle -28.2^\circ \text{ V} \end{aligned}$$

The maximum power and torque are:

$$P_{\max} = 3 \frac{|E_b| |V_s|}{X_s} = 3.096 \text{ MW}$$

$$T_{\max} = \frac{P_{\max}}{\omega_s} = 123.2 \text{ kN} \cdot \text{m}$$

Problem 17.47**Solution:****Known quantities:**

A 1200V Y-connected, three phase synchronous motor takes 110kW when operated under a certain load at 1200 rev/min. The back emf of the motor is 2000V. The synchronous reactance is 10Ω per phase.

Find:

The line current and the torque developed by the motor.

Assumptions:

Winding resistance is negligible.

Analysis:

$$V_s = \frac{1200}{\sqrt{3}} = 692.8 \angle 0^\circ$$

The input power per phase is:

$$L = \frac{N^2}{\Re_T} = \frac{100^2}{12.51 \times 10^3} = 0.8 \text{ H}$$

The power developed is:

$$P = -3 \frac{|E_b| |V_s|}{X_s} \sin \delta$$

$$\therefore \sin \delta = -0.2646$$

$$\delta = -15.34^\circ$$

The torque developed is:

$$T = \frac{P}{\omega_s} = 875.1 \text{ N} \cdot \text{m}$$

Problem 17.48

Solution:

Known quantities:

A 600V Y-connected, three phase synchronous motor takes 24 kW at a leading power factor of 0.707. The per-phase impedance is $5 + j50 \Omega$.

Find:

The induced voltage and the power angle of the motor.

Assumptions:

None.

Analysis:

$$V_s = \frac{600}{\sqrt{3}} = 346.4 \angle 0^\circ \text{ V}$$

$$Z_s = 5 + j50 = 50.25 \angle 84.29^\circ \Omega$$

From $pf = 0.707$, we have $\theta = 45^\circ$.

From $P_{in} = 3|V_s||I_s| \cos \theta$, we have

$$|I_s| = \frac{24 \times 10^3}{3 \times 346.4} \times 0.707 = 32.67 \text{ A}$$

$$I_s = 32.67 \angle 45^\circ \text{ A}$$

$$\begin{aligned} E_b = V_s - I_s Z_s &= 1385 - j1270.6 \\ &= 1880.3 \angle -42.51^\circ \text{ V} \end{aligned}$$

The power angle is:

$$\delta = -42.51^\circ$$

The power developed and the copper loss are:

$$P_{dev} = 3|E_b||I_s| \cos 87.51^\circ = 8.006 \text{ kW}$$

$$P_{loss} = 3|I_s|^2 R_s = 16.01 \text{ kW}$$

Section 17.8: The Induction Motor

Problem 17.49

Solution:

Known quantities:

A 74.6 kW three-phase, 440 V (line to line), four-pole, 60 Hz induction motor. The equivalent circuit parameters are:

$$\begin{aligned} R_s &= 0.06\ \Omega & R_r &= 0.08\ \Omega \\ X_s &= 0.3\ \Omega & X_r &= 0.3\ \Omega & X_m &= 5\ \Omega \end{aligned}$$

The no-load power input is 3240 W at a current of 45 A .

Find:

The line current, the input power, the developed torque, the shaft torque, and the efficiency at $s = 0.02$.

Assumptions:

None.

Analysis:

$$V_s = \frac{400}{\sqrt{3}} = 254\angle 0^\circ\text{ V}$$

$$\begin{aligned} Z_{in} &= 0.06 + j0.3 + \frac{j5(4 + j0.3)}{4 + j5.3} \\ &= 2.328 + j2.294 = 3.268\angle 44.59^\circ\ \Omega \end{aligned}$$

$$I_s = 77.7\angle -44.59^\circ\text{ A}$$

$$P_{in} = 3 \times 254 \times 77.7 \cos(-44.59^\circ) = 42.16\text{ kW}$$

$$I_2 = \frac{j5}{4 + j5.3} I_s = 58.51\angle -7.55^\circ\text{ A}$$

The total power transferred to the rotor is:

$$P_T = 3 \frac{R_s}{s} |I_2|^2 = 41.1\text{ kW}$$

$$\begin{aligned} P_m &= P_T - P_{\text{copper_loss_in_rotor}} \\ &= 41.1 \times 10^3 (1 - s) = 40.25\text{ kW} \end{aligned}$$

$$\omega_m = (1 - s)\omega_s = 0.98 \times 188.5 = 184.7\text{ rad/sec}$$

Therefore, the torque developed is:

$$\begin{aligned} T_{dev} &= \frac{P_m}{184.7} = 218\text{ N} \cdot \text{m} \\ &= 1880.3\angle -42.51^\circ\text{ V} \end{aligned}$$

The rotational power and torque losses are:

$$P_{rot} = 3240 - 3 \times 45^2 \times 0.06 = 2875.5 W$$

$$T_{rot} = 15.56 N \cdot m$$

The shaft torque is:

$$T_{sh} = 218 - 15.56 = 202.4 N \cdot m$$

Efficiency is:

$$T_{sh} = \frac{P_{out}}{P_{in}} = \frac{202.4 \times 184.7}{42.16 \times 10^3} = 0.887$$

Problem 17.50

Solution:

Known quantities:

A 60 Hz , four-pole, Y-connected induction motor is connected to a three-phase, 400 V (line to line), 60 Hz line. The equivalent circuit parameters are:

$$\begin{aligned} R_S &= 0.2\ \Omega & R_R &= 0.1\ \Omega \\ X_S &= 0.5\ \Omega & X_R &= 0.2\ \Omega & X_m &= 20\ \Omega \end{aligned}$$

When the machine is running at 1755 rev/min , the total rotational and stray-load losses are 800 W .

Find:

The slip, input current, total input power, mechanical power developed, shaft torque and efficiency.

Assumptions:

None.

Analysis:

From $n_s = 1800\text{ rev/min}$, we have

$$s = 0.025$$

$$\frac{R_R}{s} = 4$$

$$\begin{aligned} Z_{in} &= 0.2 + j0.5 + \frac{j20(4 + j0.2)}{4 + j20.2} \\ &= 3.972 + j1.444 = 4.226 \angle 19.98^\circ\ \Omega \end{aligned}$$

Therefore,

$$I_s = 54.6 \angle -19.98^\circ \text{ A}$$

$$P_{in} = 3(54.6) \left(\frac{400}{\sqrt{3}} \cos(-19.98^\circ) \right) = 35.6 \text{ kW}$$

$$P_t = P_{in} = 3|I_s|^2 R_s$$

$$= 35.6 \times 10^3 - 3(54.6)^2 \times 0.2 = 33.81 \text{ kW}$$

$$P_m = (1 - s)P_t = 32.97 \text{ kW}$$

$$P_{sh} = P_{out} = P_m - 800 = 32.17 \text{ kW}$$

$$\omega_m = 183.8 \text{ rad/sec}$$

$$T_{sh} = 175 \text{ N} \cdot \text{m}$$

$$\text{efficiency} = \frac{32.17}{35.6} = 0.904$$

Problem 17.51

Solution:

Known quantities:

A three-phase, 60 Hz , eight-pole induction motor operates with a slip of 0.05 for a certain load.

Find:

- The speed of the rotor with respect to the stator.
- The speed of the rotor with respect to the stator magnetic field.
- The speed of the rotor magnetic field with respect to the rotor.
- The speed of the rotor magnetic field with respect to the stator magnetic field.

Assumptions:

None.

Analysis:

$$n_s = 900 \text{ rev/min}, \quad \omega_s = 94.25 \text{ rad/sec}$$

a)

$$n_m = (1 - s)n_s = 855 \text{ rev/min}$$

b)

The speed of the stator field is 900 rev/min , the rotor speed relative to the stator field is -45 rev/min .

c)

$$45 \text{ rev/min}$$

d)

$$0 \text{ rev/min}$$

Problem 17.52**Solution:****Known quantities:**

A three-phase, 60 Hz , 400 V (per phase), two-pole induction motor develops $P_m = 37\text{ kW}$ at a certain speed.

The rotational loss at this speed is 800 W .

Find:

- a) The slip and the output torque if the total power transferred to the rotor is 40 kW .
 b) I_s and the power factor if $P_m = 45\text{ kW}$, $R_s = 0.5\Omega$.

Assumptions:

Stray-load loss is negligible.

Analysis:

a)

$$P_m = 3(1-s)P_t = 37\text{ kW}$$

$$1-s = 0.925 \Rightarrow s = 0.075$$

$$n_s = 3600\text{ rev/min}, \quad \omega_s = 377\text{ rad/sec}$$

$$\omega_m = (1-s)\omega_s = 348.7\text{ rad/sec}$$

$$P_{sh} = P_{out} = 37 - 0.8 = 36.2\text{ kW}$$

$$T_{sh} = \frac{P_{sh}}{\omega_m} = 103.8\text{ N} \cdot \text{m}$$

b)

$$P_{in} = 3|I_s|^2 R_s + P_t$$

$$3|I_s|^2 R_s = 5\text{ kW}$$

$$\therefore |I_s| = 57.7\text{ A}$$

$$P_{in} = 3|V_s||I_s|\cos\theta = 45\text{ kW}$$

The power factor is:

$$\cos\theta = 0.65\text{ lagging}$$

Problem 17.53**Solution:****Known quantities:**

The nameplate speed of a 25 Hz induction motor is 720 rev/min . The speed at no load is 745 rev/min .

Find:

- a) The slip.
 b) The percent regulation.

Assumptions:

None.

Analysis:

a)

$$p \approx \frac{120(25)}{720} = 4.17 \Rightarrow p = 4$$

$$n_{sync} = \frac{120(25)}{4} = 750 \text{ rpm}$$

$$slip = \frac{750 - 720}{750} = 0.04 = 4\%$$

b)

$$reg = \frac{745 - 720}{720} = 0.035 = 3.5\%$$

Problem 17.54**Solution:****Known quantities:**

The name plate of a squirrel-cage four-pole induction motor has 25 hp , 220 V , 60 Hz , 830 rev/min , 64 A , three-phase line current. The motor draws $20,800 \text{ W}$ when operating at a full load.

Find:

- a) slip.
- b) Percent regulation if the no-load speed is 895 rpm .
- c) Power factor.
- d) Torque.
- e) Efficiency.

Assumptions:

None.

Analysis:

a)

$$n_{sync} = 900 \text{ rpm}$$

$$slip = \frac{900 - 830}{900} = 0.078 = 7.8\%$$

b)

$$reg = \frac{895 - 830}{830} = 0.078 = 7.8\%$$

c)

$$pf = \frac{20,800}{\sqrt{3}(220)(64)} = 0.853 \text{ lagging}$$

d)

$$T = \frac{7.04(25 \times 746)}{830} = 158.2 \text{ lb} \cdot \text{ft}$$

e)

$$eff = \frac{25 \times 746}{20,800} = 0.897 = 89.7\%$$

Problem 17.55**Solution:****Known quantities:**

A 60 Hz , four-pole, Y-connected induction motor is connected to a 200 V (line to line), three-phase, 60 Hz line. The equivalent circuit parameters are:

$$\begin{aligned} R_s &= 0.48\ \Omega & \text{Rotational loss torque} &= 3.5\text{ N} \cdot \text{m} \\ X_s &= 0.8\ \Omega & R_r &= 0.42\ \Omega \text{ (referred to the stator)} \\ X_m &= 30\ \Omega & X_r &= 0.8\ \Omega \text{ (referred to the stator)} \end{aligned}$$

The motor is operating at slip $s = 0.04$.

Find:

The input current, input power, mechanical power, and shaft torque.

Assumptions:

Stray-load losses are negligible.

Analysis:

$$\begin{aligned} V_s &= 115.5\text{ V} \\ \omega_m &= (1 - s)188.5 = 181\text{ rad/sec} \\ Z_{in} &= 0.48 + j0.8 + \frac{j30(10.5 + j0.8)}{10.5 + j30.8} \\ &= 9.404 + j4.63 = 10.48\angle 26.2^\circ \\ \therefore I_s &= 11.02\angle -26.2^\circ\text{ A} \\ P_{in}(\text{per phase}) &= 115.5 \times 11.02 \times \cos(-26.2^\circ) \\ P_{in}(\text{total}) &= 3426\text{ W} \\ P_t &= P_{in}(\text{total}) - 3R_s|I_s|^2 = 3251\text{ W} \\ \therefore P_m &= (1 - s)P_t = 3121\text{ W} \\ T_{sh} &= \frac{3121}{181} = 17.24\text{ N} \cdot \text{m} \end{aligned}$$

Problem 17.56**Solution:****Known quantities:**

- a) A three-phase, 220 V , 60 Hz induction motor runs at 1140 rev/min .
 b) A three-phase squirrel-cage induction motor is started by reducing the line voltage to $V_s/2$ in order to reduce the starting current.

Find:

- a) The number of poles (for minimum slip), the slip, and the frequency of the rotor currents.
 b) The factor the starting torque and the starting current reduced.

Assumptions:

None.

Analysis:

a)

For minimum slip, the synchronous speed, $\frac{3600}{p/2}$, should be as close as possible to 1140 rev/min ,

therefore,

$$n_s = 1200, \quad p = 6 \text{ poles}$$

$$s = \frac{1200 - 1140}{1200} = 0.05$$

$$f_{\text{rotor}} = 3 \text{ Hz}$$

b)

If the line voltage is reduced to half, the starting current is reduced by a factor of 2. The developed torque is proportional to $|I_s|^2$. Therefore, the starting torque is reduced by a factor of 4.

Problem 17.57**Solution:****Known quantities:**

A six-pole induction machine has a 50 kW rating and is 85 percent efficient. If the supply is 220 V at 60 Hz .

6 poles

60 Hz

50 kW

85% efficient

220 Volt

4% slip

Find:

The motor speed and torque at a slip $s = 0.04$.

Assumptions:

None.

Analysis:

$$a) \quad n_s = \frac{120f}{p} = \frac{120 \cdot 60}{6} = 1200 \text{ rev/min}$$

@ slip of 4%

$$n = n_s (1 - s) = 1200 \text{ rev/min} (1 - 0.04) = 1152 \text{ rev/min}$$

$$P_{\text{out}} = P_{\text{in}} \times \text{efficiency} = (50 \text{ kW})(0.85) = 42.5 \text{ kW}$$

$$b) \quad T_{\text{out}} = \frac{P_{\text{out}}}{\omega} = \frac{42500 \text{ W}}{1152 \text{ rev/min}} * \frac{1 \text{ rev}}{2\pi \text{ rad}} \frac{60 \text{ sec}}{\text{min}} = 352.3 \text{ N} \cdot \text{m}$$

Problem 17.58**Solution:**

Known quantities:

6 poles

60 Hz
 240 Volt rms
 10% slip
 Torque = 60 N-m

Find:

- a) The speed and the slip of the induction machine if a load torque of 50 N-m opposes the motor.
 b) The rms current when the induction machine is operating under the load conditions of part a.

Assumptions:

The speed torque curve is linear in the region of our interests.


Analysis:

a)

$$n_s = \frac{120f}{p} = \frac{120}{6} \frac{60}{1} = 1200 \text{ rev/min}$$

@ slip of 4%
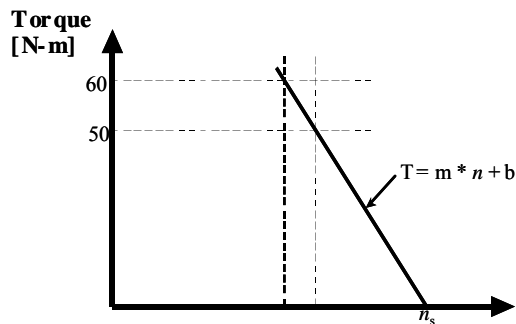
$$n = n_s (1 - s) = 1200 \text{ rev/min} (1 - 0.04) = 1152 \text{ rev/min}$$



torque

$$T = m n + b$$

$$m = \frac{60 - 0 \text{ N-m}}{1080 - 1200 \text{ rev/min}} = 0.5 \frac{\text{N-m}}{\text{rev/min}}$$

$$b = T - m n = 60 \text{ N-m} - 0.5 \frac{\text{N-m}}{\text{rev/min}} (1080 \text{ rev/min}) = 600 \text{ N-m}$$

motor speed (@ 50 N-m)

$$n = \frac{T - b}{m} = \frac{50 \text{ N-m} - 600 \text{ N-m}}{0.5 \text{ N-m/rev/min}} = 1000 \text{ rev/min}$$

slip (@ 50 N-m)

$$s = \frac{n_s - n}{n_s} = \frac{1200 - 1100}{1200} = 0.0833 = 8.33\%$$

b)

Output Power

$$P_{out} = T \omega = 50 \text{ N-m} \cdot 1100 \frac{\text{rev}}{\text{min}} \cdot \frac{2\pi \text{ rad}}{\text{rev}} \cdot \frac{1 \text{ min}}{60 \text{ sec}} = 5760 \text{ W}$$

Input Power

$$P_{in} = \frac{P_{out}}{\text{efficiency}} = I_{rms} V_{rms}$$

Current

$$I_{rms} = \frac{P_{out}}{\text{efficiency} \cdot V_{rms}} = \frac{5760 \text{ W}}{0.92 \cdot 240 \text{ volts}} = 26.1 \text{ amps}$$

Problem 17.59**Solution:****Known quantities:**A three-phase, 5 hp, 220 V, 60 Hz induction motor. $V = 8V$, $I = 18 A$, $P = 610 W$.**Find:**

- a) The equivalent stator resistance per phase, R_S .
- b) The equivalent rotor resistance per phase, R_R .
- c) The equivalent blocked-rotor reactance per phase, X_R .

Assumptions:

None.

Analysis:

a)

$$R_S = \frac{1}{2} \frac{P_{BR}}{3I_{BR}^2} = 0.314 \Omega$$

b)

$$R_R = 0.314 \Omega$$

c)

$$Z_S = \frac{V_{BR}/\sqrt{3}}{I_{BR}} = \frac{48/\sqrt{3}}{18} = 1.54 \Omega$$

$$X_R = \sqrt{Z_S^2 - R^2} = \sqrt{(1.54)^2 - (0.628)^2} = 1.4 \Omega$$

Problem 17.60**Solution:****Known quantities:**

The starting torque equation is:

$$T = \frac{m}{\omega_e} \cdot V_s^2 \cdot \frac{R_R}{(R_R + R_S)^2 + (X_R + X_S)^2}$$

Find:

- a) The starting torque when it is started at 220 V.
- b) The starting torque when it is started at 110 V.

Assumptions:

None.

Analysis:

a)

$$T = \frac{1}{\omega_s} \frac{q_1 V_1^2 (R_R/s)}{R^2 + X^2}; \quad s = 1$$

$$\therefore T = \frac{1}{377} \frac{3(127)^2 (0.314)}{(0.628)^2 + (1.4)^2} = 17.1 \text{ N} \cdot \text{m}$$

b)

$$T = \frac{1}{377} \frac{3(63.5)^2 (0.314)}{(0.628)^2 + (1.4)^2} = 4.28 \text{ N} \cdot \text{m}$$

Problem 17.61**Solution:****Known quantities:**

A four-pole, three-phase induction motor drives a turbine load with torque-speed characteristic given by

$$T_L = 20 + 0.006\omega^2$$

At a certain operating point, the machine has 4% slip and 87% efficiency.

Find:

Torque at the motor-turbine shaft

Total power delivered to the turbine

Total power consumed by the motor

Assumptions:

Motor run by 60-Hz power supply

Analysis:

Synchronous speed of four-pole induction motor at 60-Hz:

$$n_s = \frac{120f}{P} = \frac{60s/\text{min} \times 60r/s}{4/2} = 1800r/\text{min}$$

$$\omega_s = 1800\text{rev}/\text{min} \times \frac{2\pi\text{rad}/\text{rev}}{60s/\text{min}} = 188.5\text{rad}/s$$

Rotor mechanical speed at 4% slip:

$$\omega_m = (1-s)\omega_s = (1-0.04)(188.5\text{rad}/s) = 181.0\text{rad}/s$$

Load torque at the shaft:

$$T_L = 20 + 0.006(181.0\text{rad}/s)^2 = 216\text{N} \cdot \text{m}$$

Total power delivered to the turbine:

$$P = T_L \omega_m = (216\text{N} \cdot \text{m})(181.0\text{rad}/s) = 39.1\text{kW}$$

Total power consumed by the motor:

$$P_m = \frac{P}{\eta} = \frac{39.1\text{kW}}{0.87} = 44.9\text{kW}$$

Problem 17.62**Solution:****Known quantities:**

A four-pole, three-phase induction motor rotates at 1700 r/min when the load is 100 N-m.

The motor is 88% efficient.

Find:

- a) Slip
- b) For a constant-power, 10-kW load, the operating speed of the machine
- c) Total power consumed by the motor
- d) Sketch the motor and load torque-speed curves on the same graph. Show numerical values.

Assumptions:

Motor run by 60-Hz power supply

Analysis:

- a) Synchronous speed of four-pole induction motor at 60-Hz:

$$n_s = \frac{120f}{P} = \frac{60s/\min \times 60r/s}{4/2} = 1800r/\min$$

Slip:

$$s = \frac{n_s - n}{n_s} = \frac{1800r/\min - 1700r/\min}{1800r/\min} = 0.056 = 5.6\%$$

- b) Operating speed of machine for a constant-power load of 10-kW


$$\omega = \frac{P}{T_L} = \frac{10000W}{100N-m} = 100rad/sec$$

$$n = \omega \frac{60s/\min}{2\pi rad/rev} = 955r/\min$$

- c) Total power consumed by the motor

$$P_m = \frac{P}{\eta} = \frac{10kW}{0.88} = 11.4kW$$

- d) Sketch of motor and load torque-speed curves on the same graph, with the operating point at the first intersection:

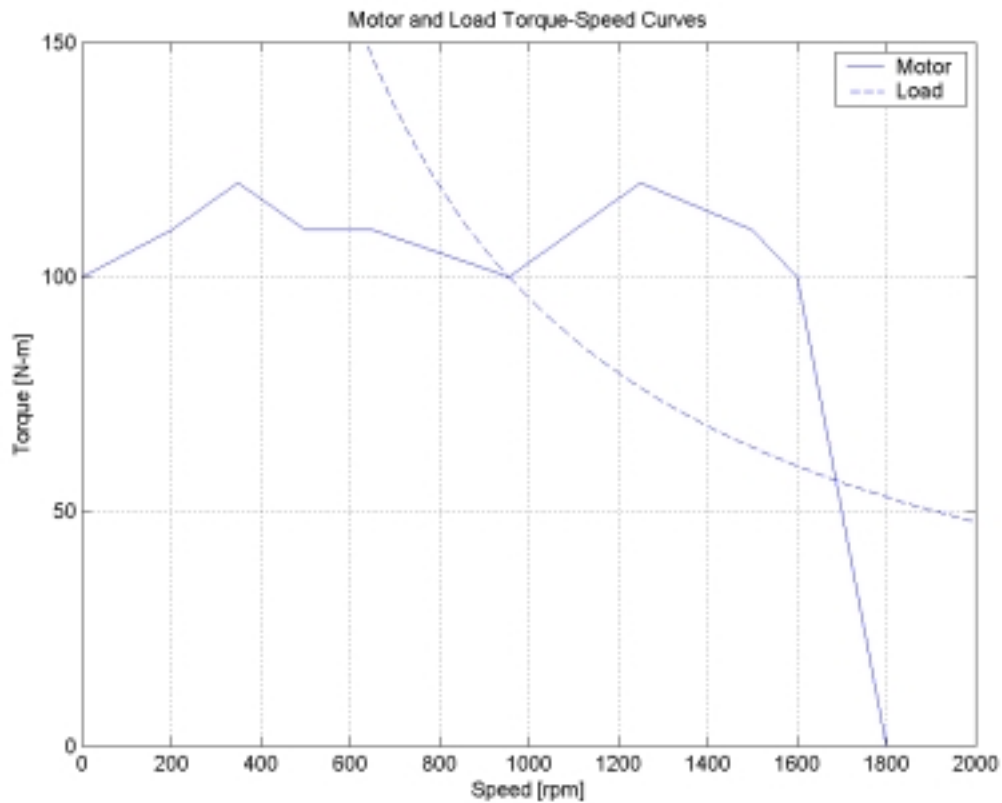

Problem 17.63

Solution:

Known quantities:

A six-pole, three-phase motor.

Find:

The speed of the rotating field when the motor is connected to:

a) a 60 Hz line.

b) a 50 Hz line.

Assumptions:

None.

Analysis:

a)

$$\text{For } 60\text{ Hz}, \omega_m = \frac{4\pi f}{P} = 125.7\text{ rad/sec}, \quad n_m = 1200\text{ rev/min}$$

b)

$$\text{For } 50\text{ Hz}, \omega_m = 104.72\text{ rad/sec}, \quad n_m = 1000\text{ rev/min}$$

Problem 17.64**Solution:****Known quantities:**

A six-pole, three-phase, 440V, 60 Hz induction motor. The model impedances are:

$$R_S = 0.8 \Omega \quad X_S = 0.7 \Omega$$

$$R_R = 0.3 \Omega \quad X_R = 0.7 \Omega$$

$$X_m = 35 \Omega$$

Find:

The input current and power factor of the motor for a speed of 1200 rev/min.

Assumptions:

None.

Analysis:

$$V_S = \frac{440}{\sqrt{3}} = 254 \angle 0^\circ \text{ V}$$

For $n_m = n_s = 1200 \text{ rev/min}$, $s = 0$ (no load).

$$\begin{aligned} Z_{in} &= R_S + j(X_S + X_m) = 0.8 + j35.7 \\ &= 35.71 \angle 88.7^\circ \Omega \end{aligned}$$

$$I_S = 7.11 \angle -88.7^\circ \text{ A}$$

The power factor is:

$$\cos 88.7^\circ = 0.0224 \text{ lagging}$$

$$P_{in} = 3|I_S||V_S|\cos\theta = 121.4 \text{ W}$$

Problem 17.65**Solution:****Known quantities:**

A eight-pole, three-phase, 220V, 60 Hz induction motor. The model impedances are:

$$R_S = 0.78 \Omega \quad X_S = 0.56 \Omega$$

$$R_R = 0.28 \Omega \quad X_R = 0.84 \Omega$$

$$X_m = 32 \Omega$$

Find:

The input current and power factor of the motor for $s = 0.02$.

Assumptions:

None.

Analysis:

For 8 poles,

$$n_s = \frac{3600}{4} = 900 \text{ rev/min}$$

$$\omega_s = 94.25 \text{ rad/sec}$$

$$\omega_m = (1 - s)\omega_s = 92.4 \text{ rad/sec}$$

By using the equivalent circuit, we have:

$$Z_{in} = 0.78 + j0.56 + \frac{j32(\frac{0.28}{0.02} + j0.84)}{14 + j32.84}$$

$$= 12.03 + j6.17 = 13.52 \angle 27.15^\circ \Omega$$

$$V_s = 127 \angle 0^\circ \text{ V}$$

$$I_s = 9.39 \angle -27.15^\circ \text{ A}$$

$$pf = \cos(-27.15^\circ) = 0.8898 \text{ lagging}$$

Problem 17.66

Solution:

Known quantities:

The nameplate is as given in Example 17.2.

Find:

The rated torque, rated volt amperes, and maximum continuous output power for this motor.

Assumptions:

None.

Analysis:

The speed is:

$$n_m = 3565 \text{ rev/min}$$

$$\omega_m = \frac{2\pi \times 3565}{60} = 373.3 \text{ rad/sec}$$

The rated *volt · amperes* is:

$$\sqrt{3} \times (230 \text{ V}) \times (106 \text{ A}) = 42.23 \text{ kVA}$$

$$\text{or } \sqrt{3} \times (460 \text{ V}) \times (53 \text{ A}) = 42.23 \text{ kVA}$$

The maximum continuous output power is:

$$P_o = 40 \times 746 = 29840 \text{ W}$$

The rated output torque is:

$$T = \frac{P_o}{\omega_m} = 79.93 \text{ N} \cdot \text{m}$$

Problem 17.67**Solution:****Known quantities:**

At rated voltage and frequency, the 3-phase induction machine has a starting torque of 140 percent and a maximum torque of 210 percent of full-load torque.

Find:

- a) The slip at full load.
- b) The slip at maximum torque.
- c) The rotor current at starting as a percent of a full-load rotor current.

Assumptions:

Neglect stator resistance and rotational losses. Assume constant rotor resistance.

Analysis:

a)

$$T_R = \frac{KV^2(R_2/s_R)}{(R_2/s_R)^2 + X^2}$$

$$T_{ST} = 1.4T_R \quad s_{ST} = 1.0$$

$$T_{MT} = 2.1T_R \quad s_{MT} = \frac{R_2}{X}$$

The above leads to 3 equations in 3 unknowns:

$$(1) \quad 4.2XR_2 = 1.4R_2^2 + 1.4X^2$$

$$(2) \quad \frac{R_2^2}{s_R} + s_R X^2 = 1.4R_2^2 + 1.4X^2$$

$$(3) \quad 4.2 \frac{XR_2}{s_R} = \left(\frac{R_2}{s_R}\right)^2 + X^2$$

Solving the equations, we have:

$$\frac{R_2}{X} = 0.382$$

$$s_R = 0.097$$

b)

$$s_{MT} = \frac{R_2}{X} = 0.382$$

c)

$$I_R = \frac{KV}{4.06}, \quad I_{ST} = \frac{KV}{1.07}$$

$$\frac{I_{ST}}{I_R} \times 100 = 379\%$$