

Q1: In the circuit shown, prove that $\sum P = 0$.

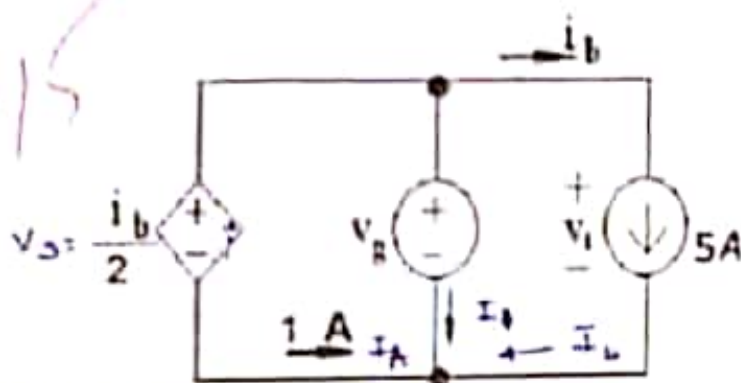


Fig. 1

$$i_b = 5A$$

$$v_s = \frac{i_b}{2} = \frac{5}{2} = 2.5V$$

$$v_b = 2.5V$$

$$v_i = -2.5V$$

$$I_A + I_b + I_i = 0$$

$$I_A + 5 + 1 = 0$$

$$I_A = -6$$

$$P_s = -V_s I_s$$

$$= -(2.5)(1)$$

$$= -2.5 \text{ Watt}$$

$$P_b = -V_b I_b$$

$$= -(2.5)(-4)$$

$$= +10 \text{ Watt}$$

$$P_i = V_i I_i$$


$$= 2.5 \times 5$$

$$= 12.5 \text{ Watt}$$

$$\sum P = 0$$

$$-2.5 + 10 + 12.5 = 0$$

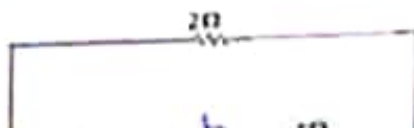Q2: In the circuit shown in Fig. 2, use nodal analysis method to find the current I_L



using KCL :-

at node a :-

$$V_a - V_b - I_L = 0$$

Q.

$$i_b = 5A$$

$$V_s = 25V$$

$$V_g = 25V$$

$$V_i = 25V$$

$$i_A + i + i_b = 0$$

$$i_A + 5 + 1 = 0$$

$$i_A = -6A$$


$$\begin{aligned} P_s &= V I \\ &= (25)(-6) \\ &= -15 \text{ Watt} \end{aligned}$$

$$\begin{aligned} P_{V_s} &= V I \\ &= 25(1) \\ &= 25 \text{ watt} \end{aligned}$$

$$\begin{aligned} P_{V_g} &= V I \\ &= 25(5) \\ &= 125 \text{ watt} \end{aligned}$$

$$\begin{aligned} \Sigma P &= -15 + 25 + 125 \\ &= 0 \end{aligned}$$

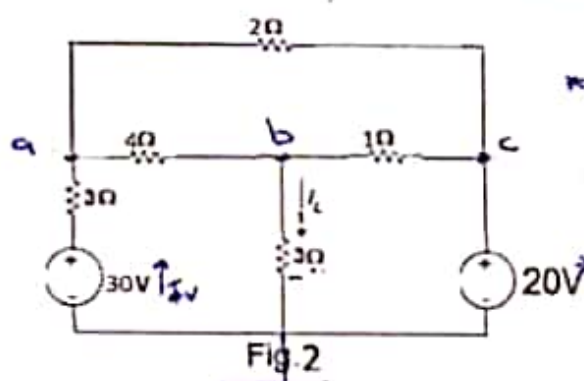Q2: In the circuit shown in Fig. 2, use nodal analysis method to find the current I_L



using KCL :-

* KCL at node a :-

$$\frac{V_a - V_c}{2} + \frac{V_a - V_b}{4} - I_V = 0$$

* KCL at node b :-

$$\frac{V_b - V_c}{1} + \frac{V_b - V_a}{4} + \frac{V_b}{3} = 0$$

$$\frac{3}{4}V_a - \frac{V_b}{4} - I_V = 10 \quad \text{--- (1)}$$

$$-\frac{V_a}{4} + \frac{19}{12}V_b = 20 \quad \text{--- (2)}$$

$$V_a + 3I_V = 30 \quad \text{--- (3)}$$



$$\begin{aligned} V_a &= 2640/119 \\ V_b &= 1920/119 \\ I_V &= 310/119 \end{aligned} \quad \left| \quad \begin{aligned} I_L &= \frac{V_b}{3} \\ &= \frac{640}{119} \text{ A} \\ &= 5.378 \text{ A} \end{aligned} \right|$$

$$\rightarrow V_c - 0 = 20 \text{ V} \rightarrow V_c = 20 \text{ V}$$

$$\rightarrow V_a - 0 = 30 - 3I_V$$

$$V_a + 3I_V = 30$$

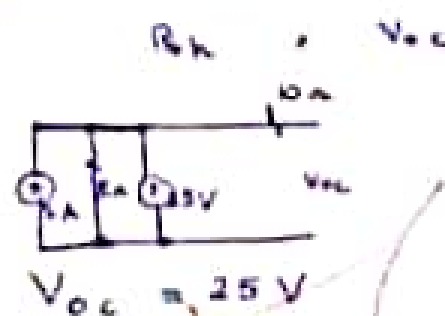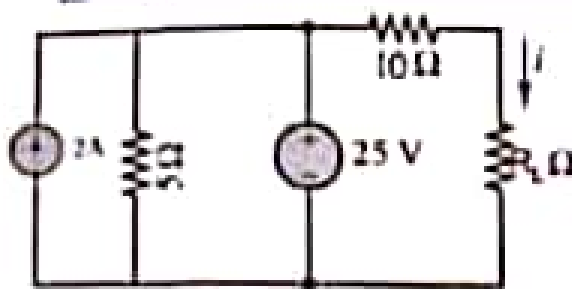
Q3: Find R_L to transfer the maximum power and the power in the Fig.3.



$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$


$$= \frac{25^2}{4 \times 10}$$

$$= \frac{125}{8} \text{ Watt}$$


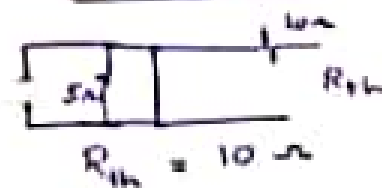


$R_L = R_{th}$ to transfer the max. power
 $R_L = 10\Omega$

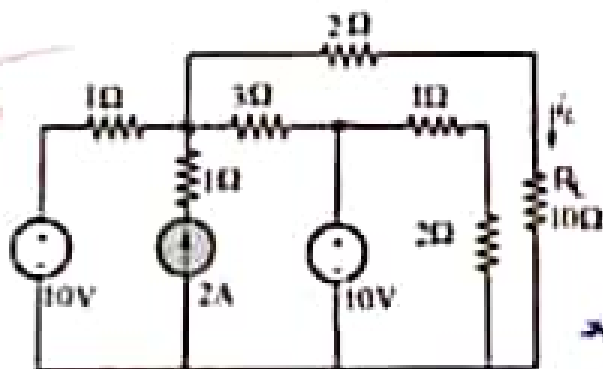Q4: In the circuit shown in Fig.4, using mesh analysis method to find the current i_L .




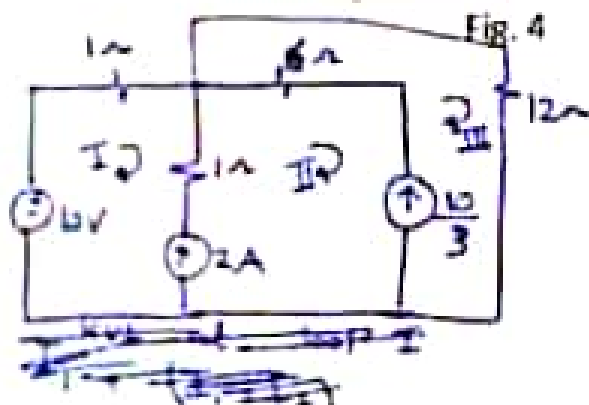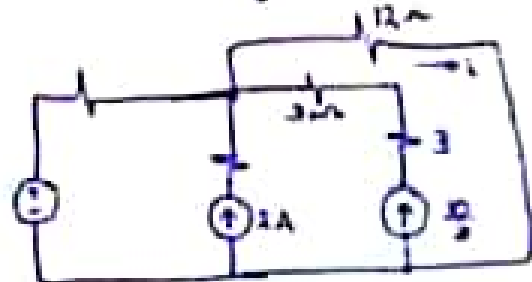Using source transformation
 $I = \frac{10}{3} \text{ A}$



Q4

Just = 15

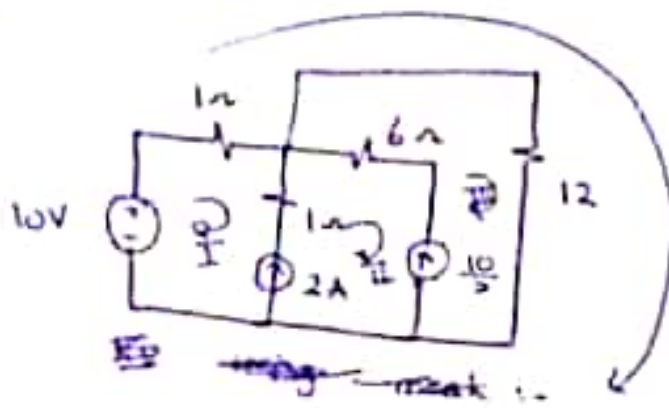

Eq. ~~using~~ mesh

~~using~~

supermesh

$$-10 + I_1 + 12 I_2 = 0 \quad \text{--- (1)}$$

$$I_2 - I_1 = 2 \quad \text{--- (2)}$$

$$I_3 - I_2 = \frac{10}{2} \quad \text{--- (3)}$$

$$I_1 + 12 I_2 = 10$$

$$-I_1 + I_2 = 2$$

$$-I_2 + I_3 = \frac{10}{2}$$

$$I_1 = -\frac{54}{13} A$$

$$I_2 = -\frac{28}{13} A$$

$$I_3 = \frac{46}{39} A$$

$$I_3 = I_1 = \frac{46}{39} A$$

Q5: In the Fig. 5, find I_x by using superposition Principle.

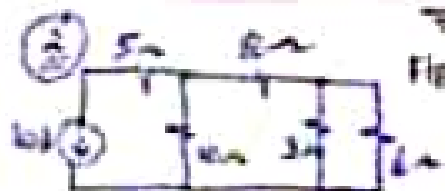
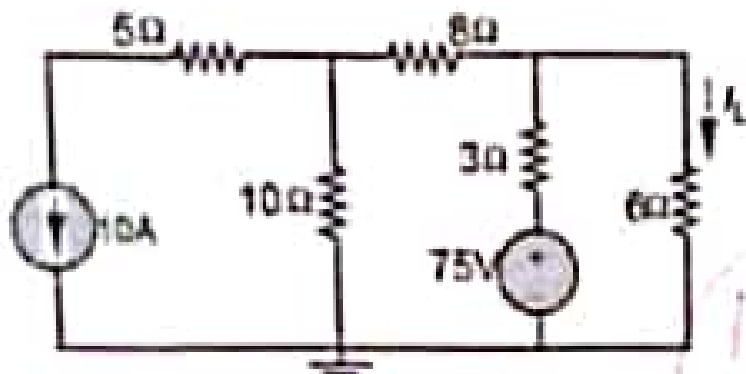


Fig. 5


$$R_{eq} = 5 + 10 = 15 \Omega$$

$$I_x = \frac{10A}{15} = 0.67A$$

$$R_{eq} = 5 + 5 = 10 \Omega$$

$$I_x = \frac{10A}{10} = 1A$$

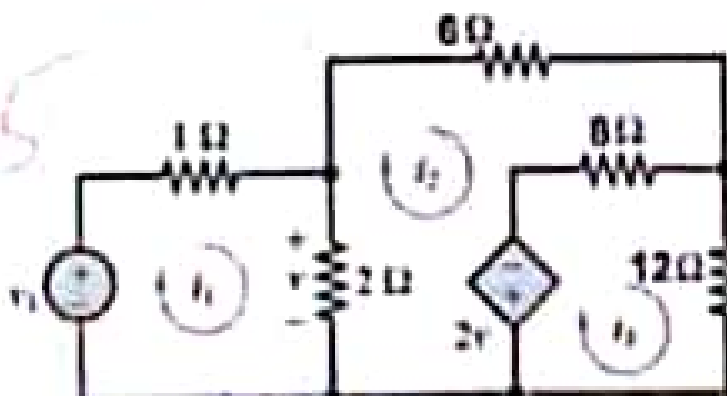Q6: In the circuit shown in Fig. 6, write a set of equations according to mesh current method to solve the unknown currents.




then set of equations are:-

$$10I_1 - 2I_2 = 10$$

$$-6I_1 + 20I_2 - 8I_3 = 0$$

$$-4I_1 - 4I_2 + 20I_3 = 0$$

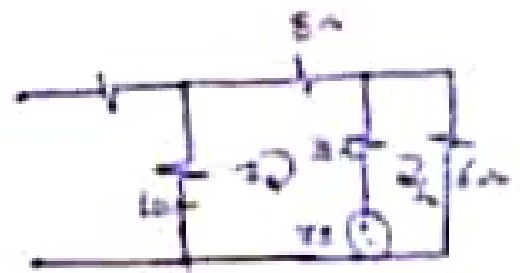

any vrl 1.
vrl at loop I

$$10I_1 + 10I_1 + 2I_1 - I_2 = 75$$

$$6I_1 + 2(I_1 - I_2) - 75 = 0$$

$$2I_1 - 2I_2 = -75$$

$$-3I_1 + 9I_2 = 75$$

$$I_1 = -\frac{25}{3}$$

$$I_2 = \frac{15}{2}$$

$$I_x = I_1 + I_2 = -\frac{25}{3} + \frac{15}{2} = -\frac{10}{6} = -1.67A$$

$$1I_1 + 2(I_1 - I_2) - V_1 = 0$$

$$3I_1 - 2I_2 - V_1 = 0 \quad \text{--- (1)}$$

any vrl 1. (loop II).

$$6I_2 + 8(I_2 - I_3) - 2V = 0$$

$$+ 2(I_2 - I_1) = 0$$

$$-V = 2(I_1 - I_2)$$

$$\rightarrow 14I_2 - 8I_3 + 2(I_1 - I_2) - 4(I_1 - I_2) = 0$$

$$20I_2 - 8I_3 - 6I_1 = 0$$

any vrl at loop III.

$$8(I_3 - I_1) - 12I_3 + 2(2I_1 - I_2) = 0$$

$$20I_3 - 4I_1 - 8I_2 = 0 \quad \text{--- (2)}$$