


Jordan University
Faculty of Engineering and Technology
Electrical Engineering Department
Spring 2005

EE203


First Exam

Time: 60 minutes

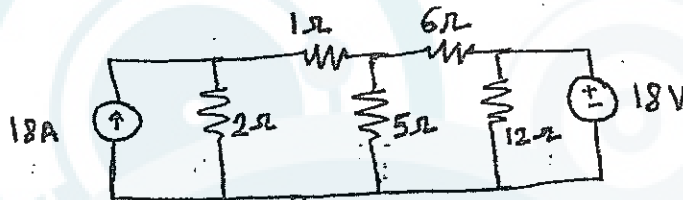
Q1- Calculate the current passing through $R=5\ \Omega$ Using Thevenin's Theorem. (30 Marks)



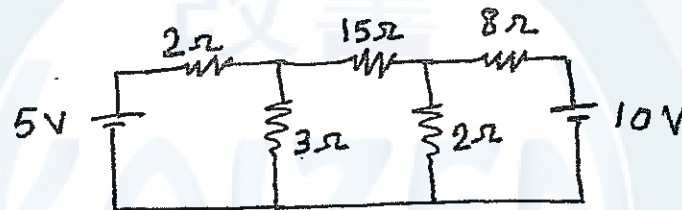
Q2- Calculate the Voltage across $R=15\ \Omega$ Using Superposition Principle. (30 Marks)



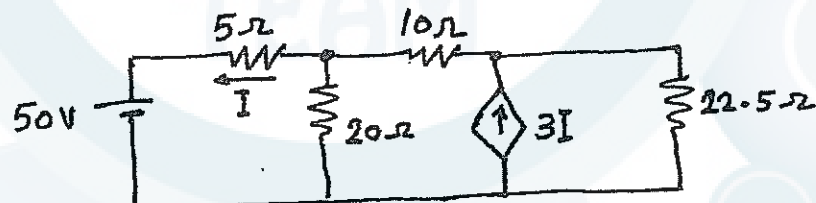Q3- Using Nodal analysis technique to find the Voltage across $R=22.5\ \Omega$ (30 Marks)



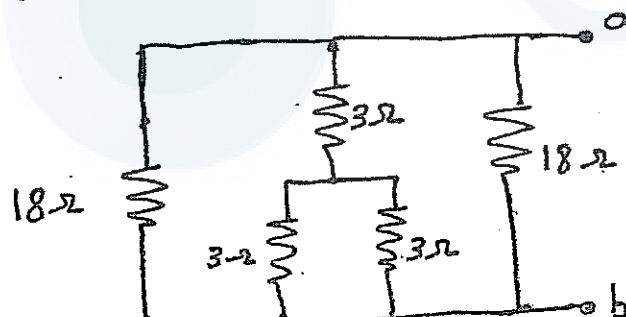Q4- Find the Equivalent Resistance between the two Terminals (a,b) (10 Marks)



Jordan University
Faculty of Engineering and Technology
Electrical Engineering Department
Spring 2005


EE206

First Exam

Time: 60 minutes


Q1- Calculate the current passing through $R=2\ \Omega$ Using Sources Transformation Technique.

(25 Marks)

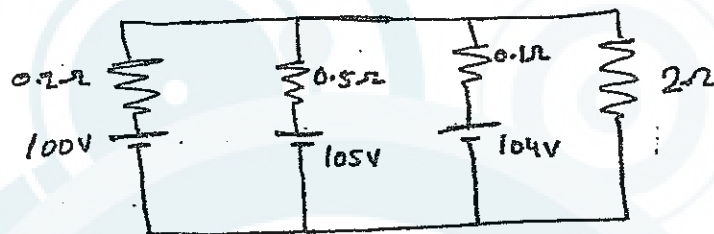


Q2- Calculate the Voltage across $R=3\ \Omega$ Using Superposition Principle.

(25 Marks)

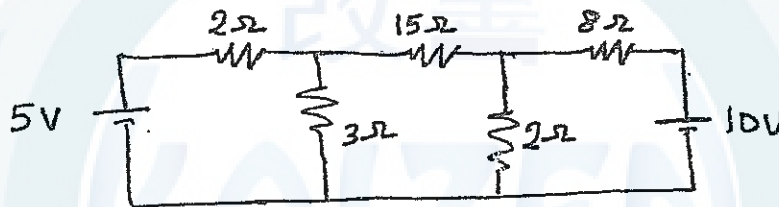

Q3- Using Nodal analysis technique to find the Voltage across $R=10\ k\ \Omega$

(25 Marks)

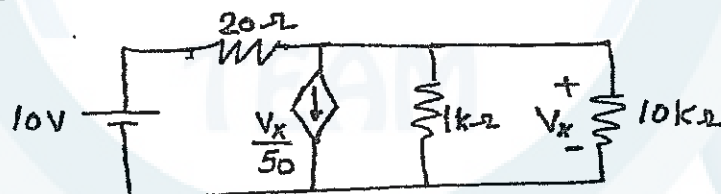

Q4- The voltage across and the current through a capacitor are shown in the following figure; determine the value of the capacitor.

(25 Marks)

