

University of Jordan  
Electrical Engineering Department  
First Exam.  
Electrical Engineering (0903203)

first

Student Name (Arabic): عزالسليم العيسى

Student Number: 008 4469

Section:

① 12.00 – 1.00      2 11.00 – 12.00      3 1.00 – 2.00      4 9.30 – 11.00

Date: Nov. 9<sup>th</sup>, 2009

Time allowed: 60 Min.

|           | point    |    |
|-----------|----------|----|
| Problem 1 | 20       | 20 |
| Problem 2 | 40       | 33 |
| Problem 3 | 40       | 40 |
| Total     | 100 Pts. | 93 |

### Problem 1:

Find  $R_{in}$  for the circuit of Fig. (1)

$R_{eq}$

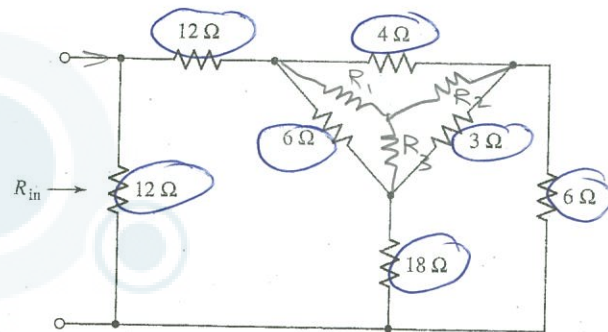


Fig. (1)

### Solution

→  $\Delta \rightarrow Y$

$$R_1 = \frac{(4)(6)}{4+3+6} = 1.85 \Omega$$

$$R_2 = \frac{(4)(3)}{4+3+6} = 0.92 \Omega$$

$$R_3 = \frac{(3)(6)}{4+3+6} = 1.38 \Omega$$

$$\rightarrow 12 + R_1 = 12 + 1.85 = 13.85$$




$$\rightarrow 6 + R_2 = 6.92 \Omega$$

$$\rightarrow R_3 + 18 = 19.38 \Omega$$

$$\rightarrow (19.38 / 6.92) = 5.09 \Omega$$

$$\rightarrow 5.09 + 13.85 = 18.94 \Omega$$

$$\rightarrow R_{eq} = 7.349 \Omega$$

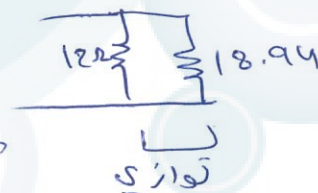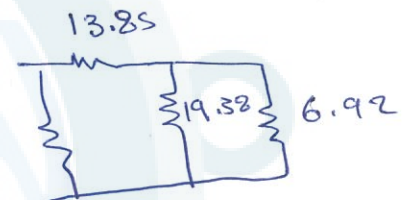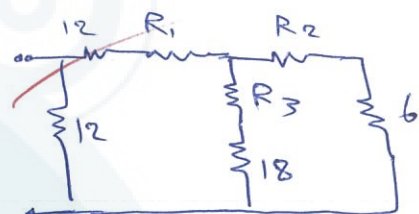

## Problem 2:

The variable resistor in the circuit in Fig. (2) is adjusted for maximum power transfer to  $R_o$ .

What is the value of this max. power?


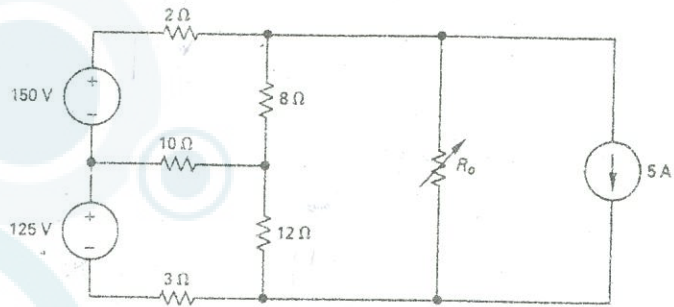


Fig. (2)

$$R_1 = \frac{(8)(2)}{20} = 0.8 \Omega$$

$$R_2 = \frac{(8)(10)}{20} = 4 \Omega$$

$$R_3 = \frac{(2)(10)}{20} = 1 \Omega$$

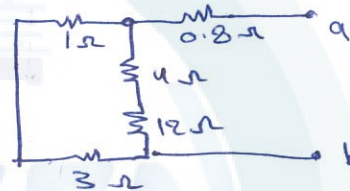

$$R_{th} = (4 \parallel 12) + 0.8 = 4 \Omega$$


to have max Power  
 $R_L = R_{th} = 4 \Omega$

KVL →

$$-(12)(9.65) + (8)(14.32) + V_{ab} = 0$$

$$V_{ab} = 230.36 \text{ V}$$



$V_{th} = 230.36 \text{ V}$

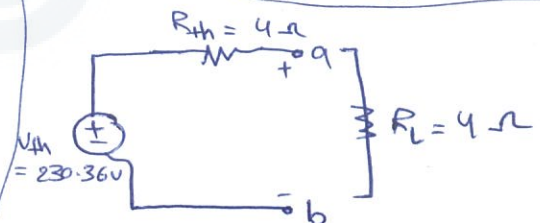

$$P_{max} = \frac{(V_{th})^2}{4(R_{th})} = \frac{(230.36)^2}{4(4)}$$

$$= 3316.6 \text{ W}$$

## Solution

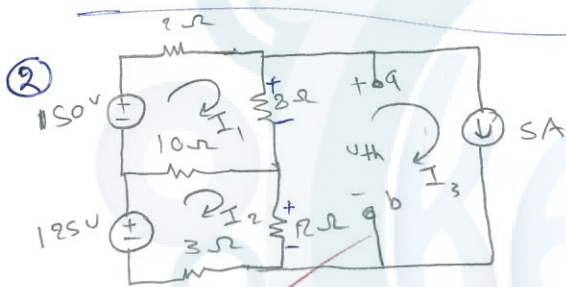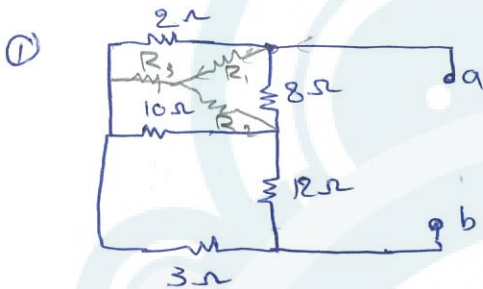

mesh →

$$I_3 = 5 \text{ A}$$

mesh ①

$$-150 + 2I_1 + 8[I_1 - 5] + 10[I_1 - I_2] = 0$$

$$-150 + 2I_1 + 8I_1 - 40 + 10I_1 - 10I_2 = 0$$

$$20I_1 - 10I_2 = 190 \quad \text{--- (1)}$$

mesh ②

$$-125 + 10[I_2 - I_1] + 12[I_2 - 5] + 3I_2 = 0$$

$$-125 + 10I_2 - 10I_1 + 12I_2 - 60 + 3I_2 = 0$$

$$-10I_1 + 34I_2 = 185 \quad \text{--- (2)}$$

$$20I_1 - 10I_2 = 190$$

$$-20I_1 + 68I_2 = 370$$

$$58I_2 = 560$$

$$I_2 = 9.65 \text{ A}$$

$$I_1 = 14.32 \text{ A}$$

رأيت آية  
كان هذا الخط  
من أخطاء  
الطلاب

### Problem 3:

Use the principle of superposition to find the voltage  $v_o$  in the circuit in Fig. (3).

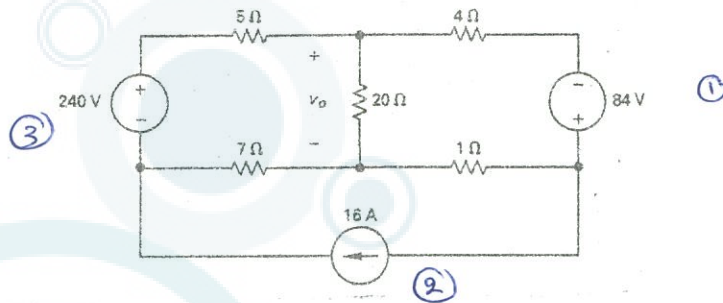


Fig. (3)

40  
40

### Solution

→ Kill ① + ③





$$5 + 7 = 12 \text{ } \Omega$$


$$7.5 \text{ } \Omega = \frac{(5+7) \parallel 20}{1} = 7.5 \text{ } \Omega$$

$$V_{7.5 \text{ } \Omega} = \frac{(7.5)(84)}{(7.5)+5} = 50.4 \text{ V}$$
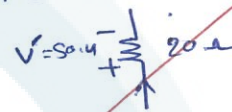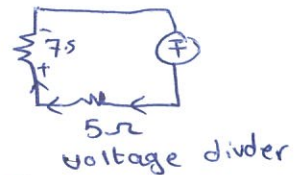
$$V_{20 \text{ } \Omega} = 50.4 \text{ V}$$



→ Kill ② + ③


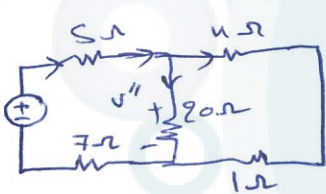


$$4 + 1 = 5 \text{ } \Omega$$


$$4 \text{ } \Omega = \frac{(4+1) \parallel 20}{1} = 4 \text{ } \Omega$$

$$V_{4 \text{ } \Omega} = \frac{(4)(240)}{4+12} = 60 \text{ V}$$
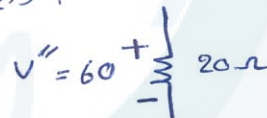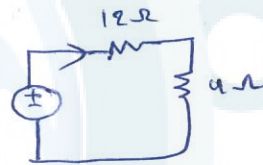
$$V_{4 \text{ } \Omega} = 60 \text{ V} = V_{20 \text{ } \Omega}$$



→ Kill ① + ②

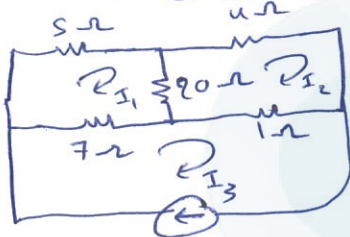

$$I_3 = 16 \text{ A}$$

mesh ①:

$$5I_1 + 20[I_1 - I_2] + 7[I_1 - 16] = 0$$

$$5I_1 + 20I_1 - 20I_2 + 7I_1 - 112 = 0$$

$$32I_1 - 20I_2 = 112 \quad \dots \text{①}$$

mesh ②:

$$20[I_2 - I_1] + 4I_2 + 1[I_2 - 16] = 0$$

$$20I_2 - 20I_1 + 4I_2 + I_2 - 16 = 0$$

$$-20I_1 + 25I_2 = 16 \quad \dots \text{②}$$

$$640I_1 - 400I_2 = 2240$$

$$-640I_1 + 800I_2 = 512$$

$$400I_2 = 2752$$

$$I_2 = 6.88 \text{ A}$$

$$I_1 = 7.8 \text{ A}$$

على الصفحة البع

م