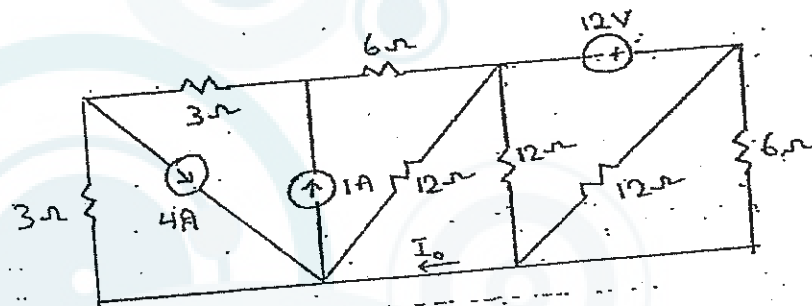


Problem (1)
Using Source Transformation find the current I_o in the circuit
Of Fig (1).




Solution:

Fig (1)


Starting from R.H.S. we have:

$$6 \parallel 12 = \frac{6 \times 12}{18} = 4\Omega$$

By source transformation we get:

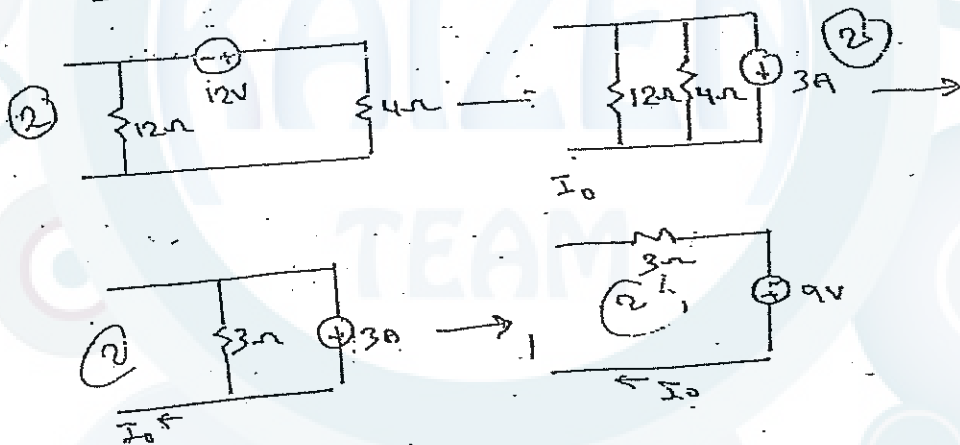

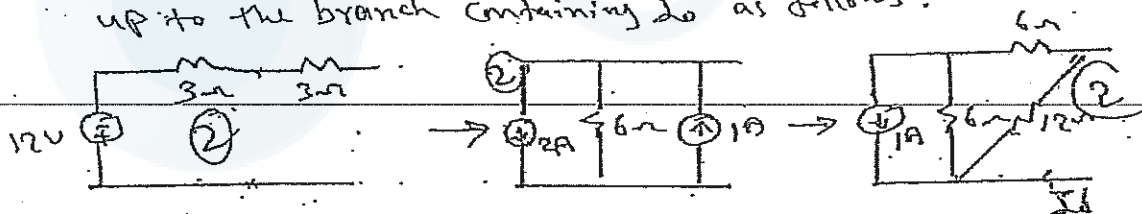Then we perform source transformation from L.H.S.
up to the branch containing I_o as follows:



Continue next page:

Problem (2)

In the circuit of Fig (2), find the following:

- R_L Which will receive maximum power.
- The value of the maximum power transferred to R_L .
- Norton equivalent circuit between terminals of resistor R_L .

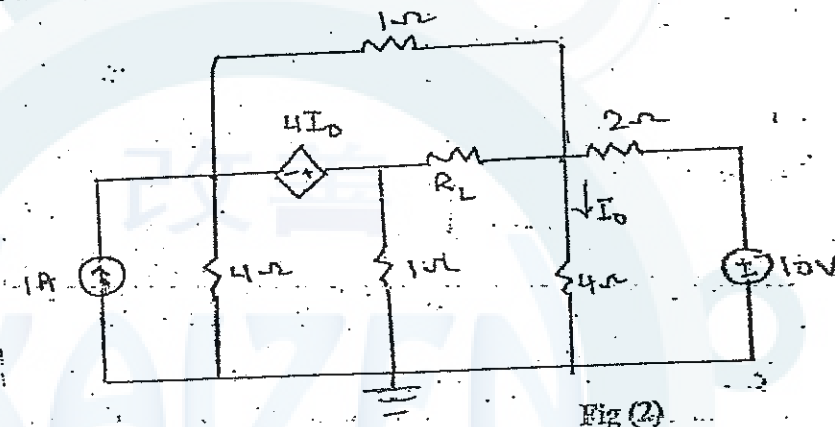


Fig (2)


Solution:

(a) $R_L = R_{TH}$ to receive max. power

Since the circuit contains independent and dependent

sources $R_{TH} = \frac{V_{o.c.}}{I_{s.c.}}$ (2)

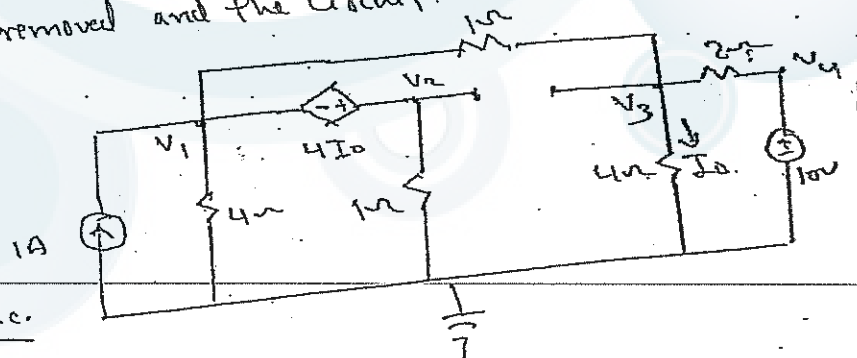is removed and the circuit becomes as follows:



Calculation of $V_{o.c.}$

$$(1) V_{o.c.} = V_{TH} = V_2 - V_3$$


Applying nodal analysis we have:

at node-3 we have:

$$0 = V_3 \left(\frac{1}{1} + \frac{1}{2} + \frac{1}{2} \right) - \frac{V_1}{1} - \frac{10}{2} \quad (3)$$

$$\text{or } -4V_1 + 7V_3 = 20 \quad (1)$$

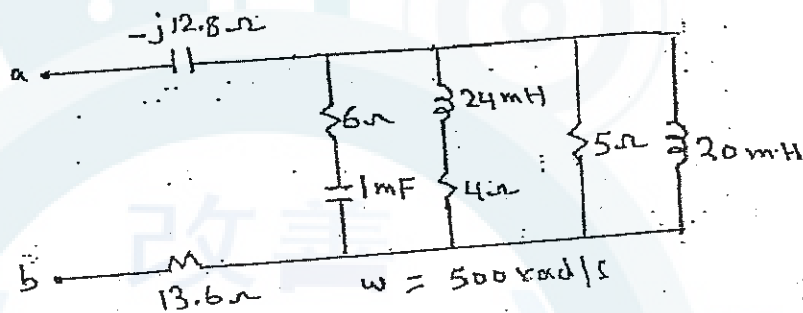Problem (3)
In the circuit shown in Fig (3), find the admittance Y_{ab} in millimhos and in both Rectangular and Polar forms where $\omega = 500 \text{ rad/sec}$



Solution:

Fig (3)

$$20 \text{ mH} \rightarrow j \times 500 \times 20 \times 10^{-3} = j10 \Omega \quad (1)$$

$$24 \text{ mH} \rightarrow j 500 \times 24 \times 10^{-3} = j12 \Omega \quad (1)$$

$$1 \text{ mF} \rightarrow -j \frac{1}{500 \times 1 \times 10^{-3}} = -j2 \Omega \quad (1)$$

We find the admittance for the four branches in parallel in the R.H.S. of Fig.(3) and call it Y_1 :

$$Y_1 = \frac{1}{6-j2} + \frac{1}{4+j12} + \frac{1}{5} + \frac{1}{j10} \quad (1)$$

$$= \frac{6+j2}{40} + \frac{4-j12}{160} + \frac{32}{160} - j0.1 \quad (2)$$

$$= \frac{60-j20}{160} = \frac{3-j1}{8} \quad (2)$$

$$Z_1 = \frac{1}{Y_1} = \frac{8}{3-j1} = 2.4 + j0.8 \quad (2)$$

$$Z_{ab} = 13.6 - j12.8 + 2.4 + j0.8 = 16 - j12 \quad (2)$$

$$= 20 \angle -36.87^\circ \quad (1)$$

$$Y_{ab} = \frac{1}{Z_{ab}} = \frac{1}{20 \angle -36.87^\circ} \text{ mS} = 50 \angle 36.87^\circ \text{ mS} = 40 + j30 \text{ mS} \quad (1)$$

Problem (4)

In the circuit shown in Fig (4) and using Mesh Analysis find:

- The currents $I_a, I_b, I_c,$ and I_d in rectangular form and in time domain.
- Phase shift between each current in part (a) above and the relevant voltage across each element these currents are passing through.

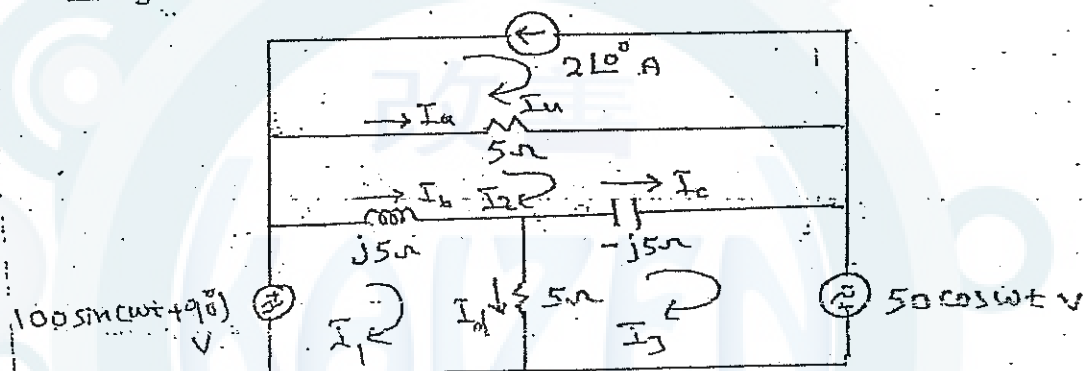


Fig (4)

Solution:

(a) In phasor domain voltage sources become:

$$\textcircled{1} 100\angle 0^\circ \text{ V} \text{ \& } 50\angle 0^\circ \text{ V} \textcircled{1}$$

mesh #1:

$$100 = I_1(5+j5) - I_2 j5 - I_3 \times 5 \quad \text{--- (1)} \quad \textcircled{2}$$

mesh #2:

$$0 = -I_1 j5 + I_2(5+j5-j5) - I_4 \times 5 + I_3 j5$$

$$\text{But } I_4 = -2\angle 0^\circ \text{ A}$$

above eqn. becomes:

$$\textcircled{2} -10 = -j5I_1 + 5I_2 + j5I_3 \quad \text{--- (2)}$$

mesh #3:

$$50\angle 0^\circ = -5I_1 + j5I_2 + (5-j5)I_3 \quad \text{--- (3)}$$

Solving above 3 equations we get:

Q1. Write one equation only to determine V_a in the circuit shown in Fig.1.

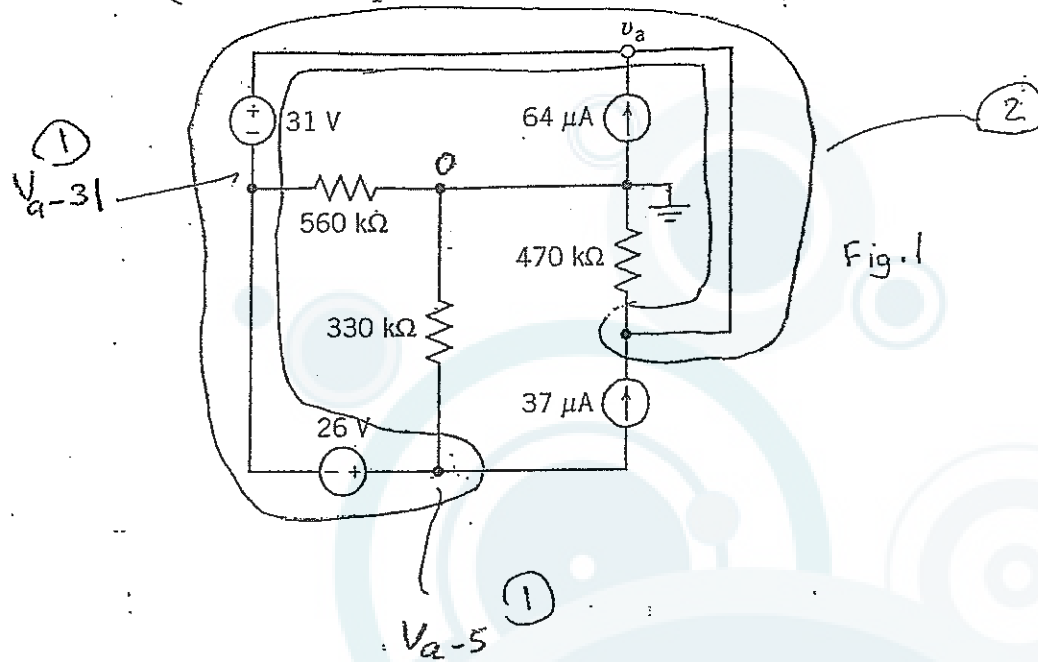


Fig.1

$$\left[-64 \times 10^{-6} + \frac{V_a}{470 \times 10^3} + \frac{V_a - 31}{560 \times 10^3} + \frac{V_a - 5}{330} = 0 \right]$$

$$-64 + 2.12766 V_a + 1.785 V_a - 55.357 + 3.03 V_a - 15.15 = 0$$

$$6.94336 V_a = 134.508$$

$$V_a = 19.37 \text{ V}$$

Problem 2:

Use mesh analysis method to find the two currents i_{10} and i_3 in the circuit of Fig. (2).

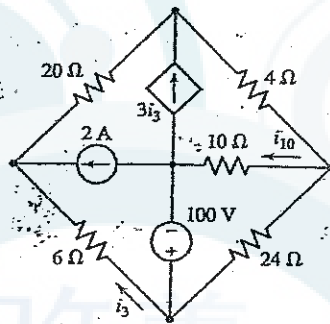


Fig. (2)

Solution

* on Supermesh:



$$0 = 20(i_1) + 4(i_2) + 10(i_2 - i_4) - 100 + 6(i_3)$$

$$20i_1 + 4i_2 + 10i_2 - 10i_4 + 6i_3 = 100$$

$$100 = 20i_1 + 14i_2 + 6i_3 - 10i_4 \quad (1)$$

* on the other mesh:

$$100 + 10(i_4 - i_2) + 24(i_4) = 0$$

$$-100 = 10i_4 - 10i_2 + 24i_4 \quad (2)$$


$$-100 = 34i_4 - 10i_2 \quad (2)$$

* relations between currents:

$$3i_3 = i_2 - i_1 \quad (3) \quad i_2 = i_1 - i_3 \quad (4)$$

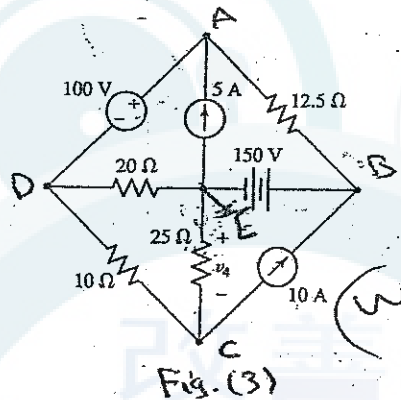Problem 3:

Use nodal analysis method to find v_4 in the circuit shown in Fig. (3).



$$v_4 = -v_c$$

Solution

$$v_E = 0V \quad v_B = 150V \quad (2)$$

* Super node at B and A:

$$v_A - v_D = 100 \quad (5)$$

$$\frac{v_A - v_B}{12.5} + \frac{v_D - v_C}{10} + \frac{v_D}{20} = 5 \quad (6)$$

$$0.08v_A = 0.08v_B + 0.1v_D - 0.1v_C + 0.05v_D = 5$$

$$0.08v_A + 0.15v_D - 0.1v_C = 5 + 12$$

$$0.08v_A + 0.15v_D - 0.1v_C = 17 \quad (7)$$


* at node C:

$$\frac{v_C - v_D}{10} + \frac{v_C}{25} = -10 \quad (8)$$

$$0.1v_C - 0.1v_D + 0.04v_C = -10 \Rightarrow 0.14v_C - 0.1v_D = -10 \quad (9)$$

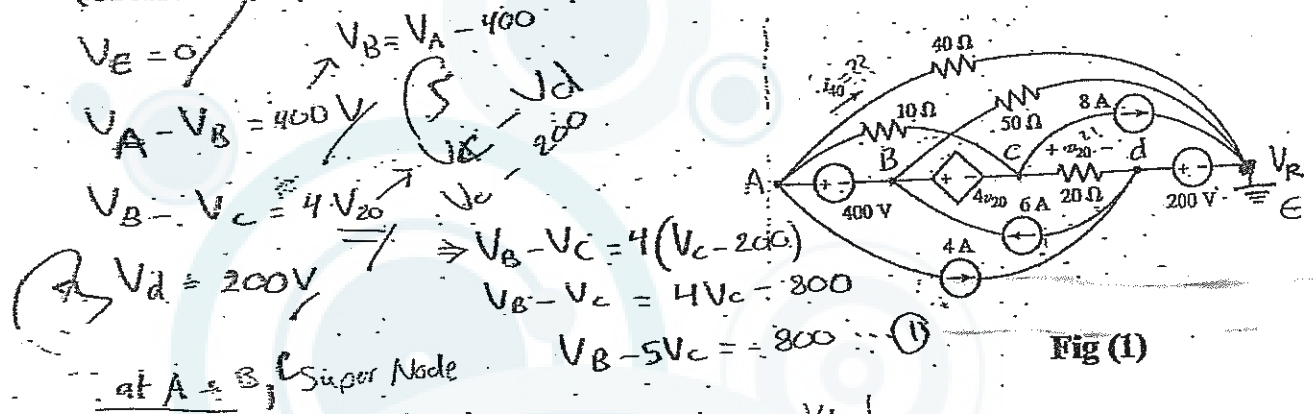Problem (1)

Use Nodal Analysis method to find i_{40} and v_{20} in the circuit of Fig (1).
(Crossed wires not marked by a solid dot are not in physical contact).



$$+6 - 4 = V_A \left(\frac{1}{10} + \frac{1}{40} \right) - V_C \frac{1}{10} \Rightarrow 2 = \frac{1}{8} V_A + \frac{1}{50} V_B - \frac{1}{10} V_C \quad (2)$$

at B & C $\Rightarrow$ Super Node

$$-8 + 6 = V_B \left(\frac{1}{50} \right) + V_C \left(\frac{1}{20} + \frac{1}{10} \right) - V_d \frac{1}{20} - V_A \frac{1}{10}$$

$$\Rightarrow -2 = -\frac{1}{10} V_A + \frac{1}{50} V_B + \frac{3}{20} V_C - \frac{200}{20} \cdot \frac{1}{10}$$

$$8 = -\frac{1}{10} V_A + \frac{1}{50} V_B + \frac{3}{20} V_C$$


at d

$$+4 - 6 = V_d \left(\frac{1}{20} \right) - V_C \left(\frac{1}{20} \right)$$

$$-\frac{2}{20} = \frac{1}{20} (200) - \frac{1}{20} V_C$$

$$i_{40} = \frac{V_A}{40}$$

In the circuit of Fig (2), use Mesh Analysis method to determine the power associated with the (2.2V) voltage source and state whether this source is delivering or absorbing power.

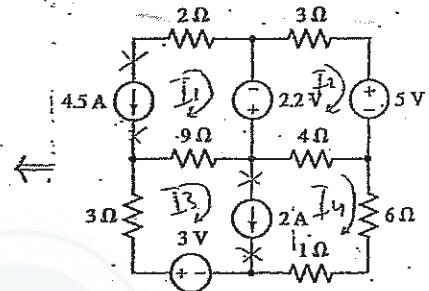
$$\begin{aligned} I_1 &= -4.5 \text{ A} \dots (*) \\ I_3 - I_4 &= 2 \text{ A} \dots (1) \end{aligned}$$

$$-4.5$$
$$= -1.5$$

$$-5 - 2 \cdot 2 = \cancel{I_2(3+4)} - \cancel{I_4(4)} \dots \textcircled{3} w$$

$$I_3 - I_4 = 2 \quad \text{--- (1)}$$

$$-4I_2 + 12I_3 + 11I_4 = -1.5 \quad \text{--- (2)}$$

$$7I_2 + 0 - 4I_4 = -7.2 \quad (3)$$

$$I_2 = \begin{vmatrix} 2 & 1 & -1 \\ -1.5 & 12 & 11 \\ -7.2 & 0 & 4 \end{vmatrix}$$

0	1	-1
-4	12	11
7	6	-4

$$\vec{I}_3 = \begin{pmatrix} 0 \\ -4 \\ -7.2 \end{pmatrix} \begin{pmatrix} 2 \\ 1.5 \\ 11 \\ 4 \end{pmatrix}$$

$$I_4 = \begin{vmatrix} 0 & 1 & 1 \\ -4 & 12 & 2 \\ 7 & 0 & -15 \\ & & -7.5 \end{vmatrix}$$

0	1
-4	12
7	0

$$P = \frac{(I_2 - I_1) \cdot 2 \cdot z}{(2 \cdot \text{Absy})}$$

Problem 2:

The variable resistor in the circuit in Fig. (2) is adjusted for maximum power transfer to R_o .

What is the value of this max. power?

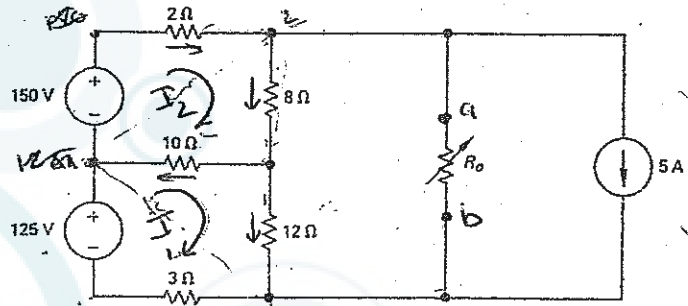


Fig. (2)




Solution R_{th}

to calculate R_{th} :

$$R_1 = \frac{10 \times 12 + 8 \times 12 + 8 \times 10}{10} = 19.6 \Omega$$

$$R_2 = \frac{19.6}{8} = 2.45 \Omega$$

$$R_3 = \frac{19.6}{12} = 1.63 \Omega$$

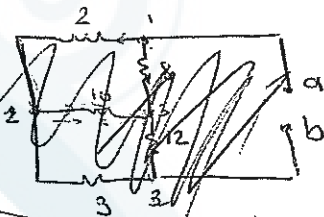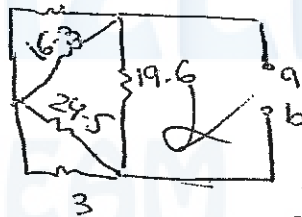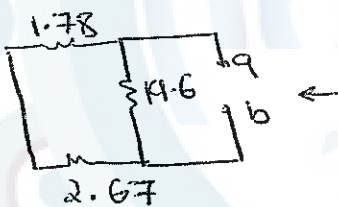

$$R_1 = \frac{2 \times 8}{2 + 8} = 0.8 \Omega$$

$$R_2 = \frac{2 \times 10}{2 + 10} = 1 \Omega$$

$$R_3 = \frac{10 \times 8}{10 + 8} = 4 \Omega$$

$$R_{th} = \frac{(1.78 + 2.67) \times 19.6}{(1.78 + 2.67) + 19.6} = 3.63 \Omega$$

$$150 - 2I_2 - 8I_2 - 10(I_2 - I_1) = 0$$

$$I_1(10) + I_2(-2-8-10) = -150 \quad \text{--- (1)}$$


$$125 + 10(I_2 - I_1) - 12I_1 - 3I_1 = 0$$

$$I_1(-10-12-3) + I_2(10) = -125 \quad \text{--- (2)}$$

$$I_1 = 10 \text{ A}, \quad I_2 = 12.5 \text{ A}$$

$$V_{th} = -3(10) + 125 + 150 - 2(12.5) = 220 \text{ V}$$

$$\text{max Power} = \left[\frac{220}{2 \times 3.63} \right]^2 \times 3.63 = 252.97 \text{ W}$$

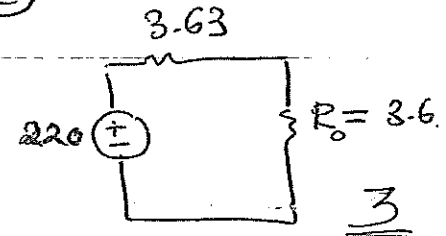3

Problem (3)

In the circuit shown in Fig (3), use Superposition Principle to find the current i_A and the power developed in the dependent voltage source.

i_A due to $30V$ only

Mesh

$$-53i_2 + 8i_1 = 8I_1 - 3I_2 - 5I_3$$

$$0 = -45I_1 + 50I_2 - 5I_3$$

$$-53i_A = I_1(3+5) - 3I_2 - 5I_3$$

$$30 = I_3(20+2+5) - 5I_1 - 20I_2$$

$$0 = I_2(7+3+20) - 20I_3 - 5I_1$$

$$\Rightarrow 0 = -45I_1 + 50I_2 - 5I_3$$

$$30 = -5I_1 - 20I_2 + 27I_3$$

$$0 = -3I_1 + 27I_2 - 20I_3$$

$$\begin{bmatrix} -45 & 50 & -5 \\ -5 & -20 & 25 \\ -3 & 20 & -20 \end{bmatrix} \begin{bmatrix} 0 \\ 30 \\ 0 \end{bmatrix} \quad I_1 = \frac{\begin{vmatrix} 0 & 50 & -5 \\ 30 & -20 & 25 \\ 0 & 20 & -20 \end{vmatrix}}{\begin{vmatrix} -45 & 50 & -5 \\ -5 & -20 & 25 \\ -3 & 20 & -20 \end{vmatrix}}$$

$$I_2 = \frac{\begin{vmatrix} -45 & 0 & -5 \\ -5 & 30 & 25 \\ -3 & 0 & -20 \end{vmatrix}}{\begin{vmatrix} -45 & 50 & -5 \\ -5 & -20 & 25 \\ -3 & 20 & -20 \end{vmatrix}} \quad I_3 = \frac{\begin{vmatrix} -45 & 50 & 0 \\ -5 & -20 & 30 \\ -3 & 20 & 0 \end{vmatrix}}{\begin{vmatrix} -45 & 50 & -5 \\ -5 & -20 & 25 \\ -3 & 20 & -20 \end{vmatrix}}$$

i_A due to $30V$ only


Mesh

$$-53(I_2 - I_3) = I_1(8) - 3I_2 - 5I_3 \quad \text{--- (1)}$$

$$30 = I_2(20) - 20I_3 - 3I_1 \quad \text{--- (2)}$$

$$0 = I_3(27) - 5I_1 - 20I_2 \quad \text{--- (3)}$$

$$\begin{bmatrix} -45 & 50 & -5 \\ -3 & 20 & -20 \\ -5 & -20 & 27 \end{bmatrix} \quad I_2 = \frac{\begin{vmatrix} -45 & 0 & -5 \\ -3 & 30 & 25 \\ -5 & 0 & -20 \end{vmatrix}}{\begin{vmatrix} -45 & 50 & -5 \\ -3 & 20 & -20 \\ -5 & -20 & 27 \end{vmatrix}} \quad I_3 = \frac{\begin{vmatrix} -45 & 50 & 0 \\ -3 & -20 & 30 \\ -5 & 20 & 0 \end{vmatrix}}{\begin{vmatrix} -45 & 50 & -5 \\ -3 & 20 & -20 \\ -5 & -20 & 27 \end{vmatrix}}$$

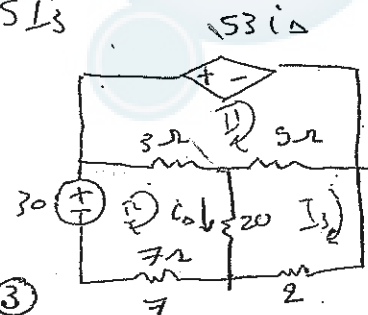

$$I_1 = -\frac{250}{13}$$

$$I_2 = -\frac{240}{13}$$

$$I_3 = -\frac{230}{13}$$