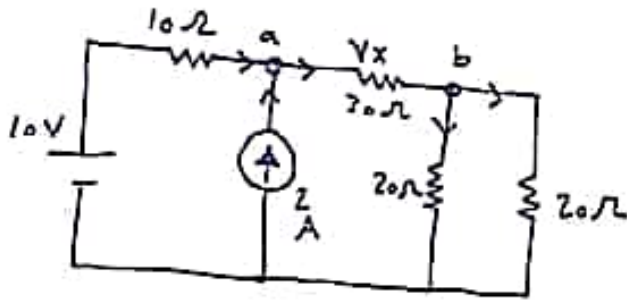


Q1) by using nodal method find V_x and power by current source



node a

$$\frac{10 - V_a}{10} + 2 = \frac{V_a - V_b}{30} \dots (1)$$

node b

$$\frac{V_a - V_b}{30} = \frac{V_b}{20} + \frac{V_b}{20} \dots (2)$$


$$V_a = 24V$$

$$V_b = 6V$$


$$V_x = V_a - V_b = 18V$$

Power by current source = $P = I V = -24 \times 2 = -48W$ (delivered)

Q2) find i_L by using superposition

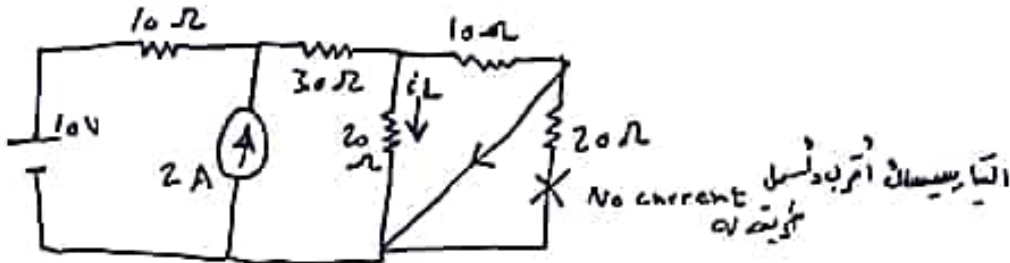

* Kill voltage source

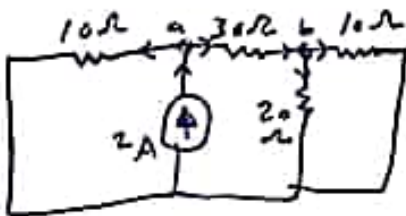

node a

$$2 = \frac{V_a}{10} + \frac{V_a - V_b}{30} \dots (1)$$

node b


$$\frac{V_a - V_b}{30} = \frac{V_b}{20} + \frac{V_b}{10} \dots (2)$$

$$V_a = 1.566V$$

$$V_b = 0.2739V$$

$$i_L' = \frac{V_b}{20} = \frac{0.273}{20} = 0.0137A$$


* Kill current source

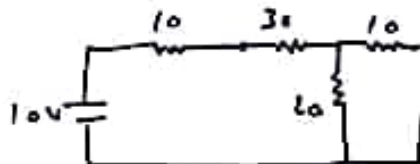

$$i_L'' = \frac{1.43}{20} = 0.071$$

$$i_L = i_L' + i_L'' = 0.0851A$$

Q3) by using mesh current method solve unknown current

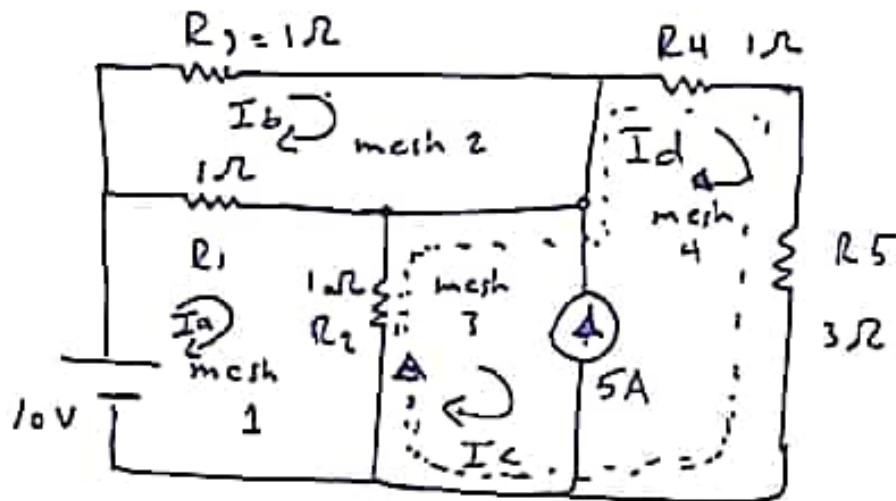

mesh 1

$$-10 + I_a(1 + 1) - I_b - I_c = 0 \quad \dots \textcircled{1}$$

mesh 2

$$I_b(2) - I_a = 0 \quad \dots \textcircled{2}$$

mesh 3 and 4 super mesh

$$I_c(1) - I_a(1) + I_d(3 + 1) = 0 \quad \dots \textcircled{3}$$

$$I_d - I_c = 5 \quad \dots \textcircled{4}$$

4 equations and 4 unknowns

by solving equations


$$I_a \approx 4.6 \text{ A}$$

$$I_b \approx 2.3 \text{ A}$$



$$I_c = -3 \text{ A}$$

$$I_d = 1.9 \text{ A}$$

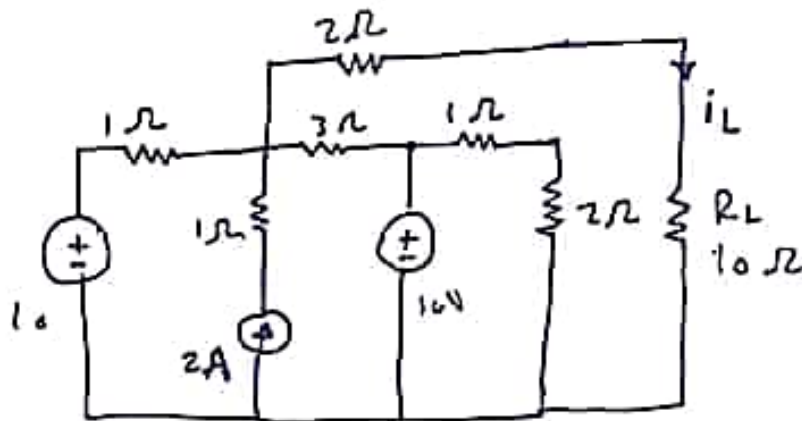Q4) using thevenin equivalent circuit Find i_L




Kill all sources and Remove R_L

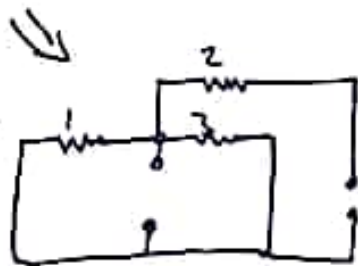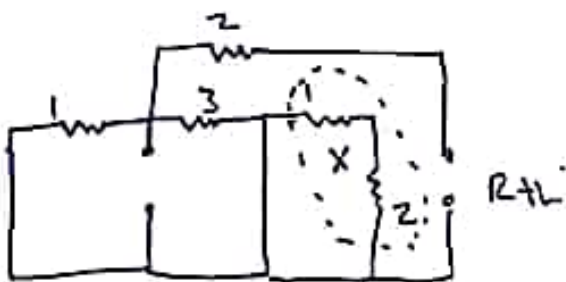


$$(3 \parallel 2) + 2 = 2.75 \Omega = R_{th}$$

Draw thevenin equivalent

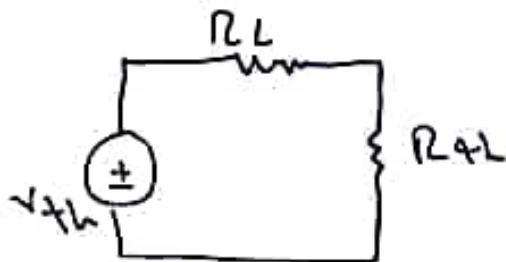

Find V_{th}

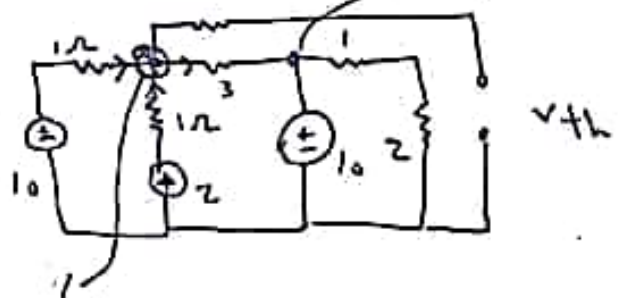

$$V_a = V_{th}$$


by using nodal method

$$\frac{10 - V_a}{1} + 2 = \frac{V_a - 10}{3}$$


$$V_a = 11.5 = V_{th}$$

$$i_L = \frac{V_{th}}{R_{th} + R_L} = \frac{11.5}{10 + 2.75} = 0.90196 A$$

Q5) Find i_L by using superposition

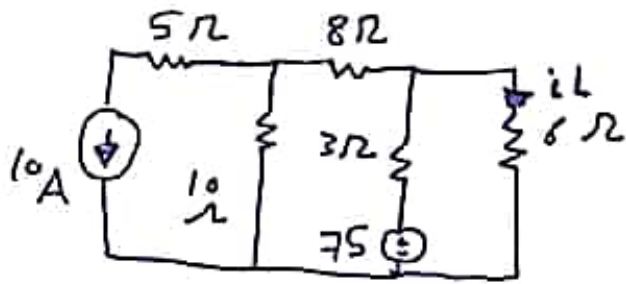

1) Kill V_s

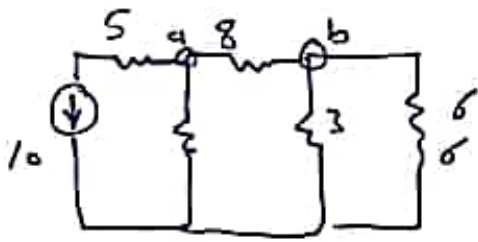

by using nodal

nodal

$$\frac{V_b - V_a}{8} = 10 + \frac{V_a}{10}$$

node b


$$-\frac{V_b}{3} = \frac{V_b}{6} + \frac{V_b - 9}{8}$$

$$V_a = 50V$$


$$V_b = 10V$$

$$i_L = \frac{V_b}{6} = \frac{10}{6} A = \frac{5}{3} A$$


2) Kill current source

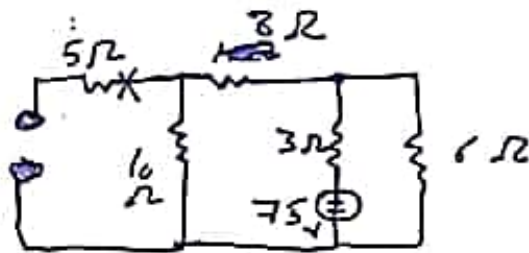

node

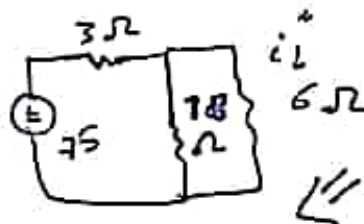

$$\frac{18 \times 6}{24} + 3$$

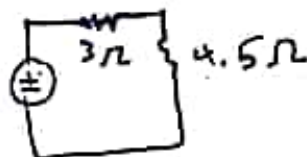


$$V = 75 \times \frac{4.5}{7.5} = 45$$

$$I_L = \frac{45}{6} = 7.5$$

$$I_L'' = 7.5 + \frac{5}{3} = 9.16 A$$

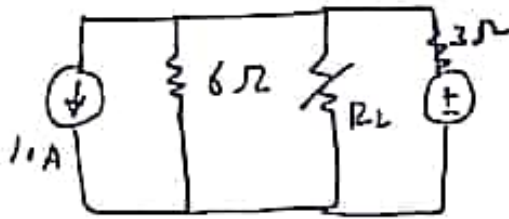Q6) Find R_L to transfer max Power of P_{R_L} and power



$$R_L = R_{th}$$




$$R_{th} = \frac{3 \times 6}{3 + 6} = 2\Omega$$

draw thevenin equivalent



Find V_{th}

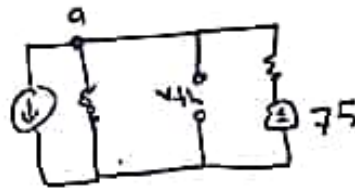


$$\frac{75 - V_a}{3} = \frac{10 + V_a}{6} \Rightarrow V_a = V_{th} = 30$$

use

$$P_L = \frac{V_{th}^2}{4R_{th}} = \frac{30^2}{4 \times 2} = 112.5W$$

$$P_L = I_L^2 R_L = \left(\frac{30}{4}\right)^2 \times 2 = 112.5W$$

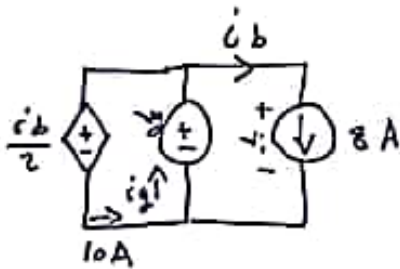Q7) Find Power by each source (~~delivered~~ / supplied) and Prove $\sum P = 0$



$$i_g = 8 + 10 = 18 \uparrow A$$

$$\frac{i_b}{2} = V_g = V_i = 4V$$



$$P_g = -4 \times 18 = -72 \text{ supplied}$$

$$P_2 = 4 \times 18 = 72 \text{ consumed}$$


$$P_1 = 8 \times 4 = 32 \text{ consumed}$$

$$\{ P = -72 + 72 + 32 = 0 \}$$

Q8) using superposition to find i_L

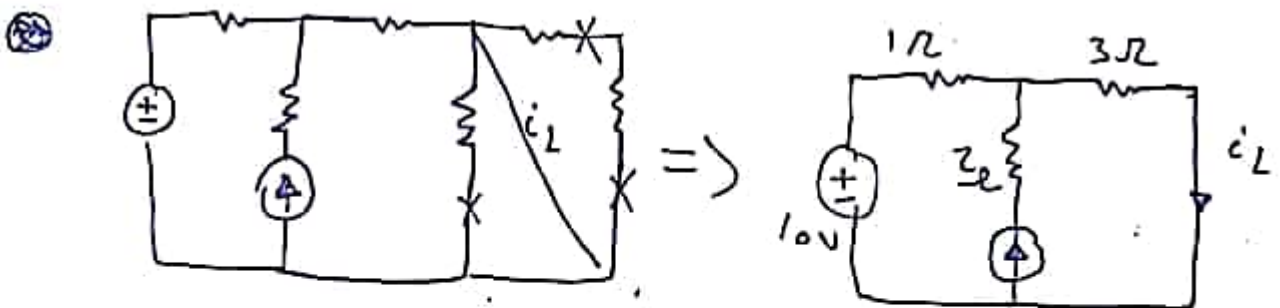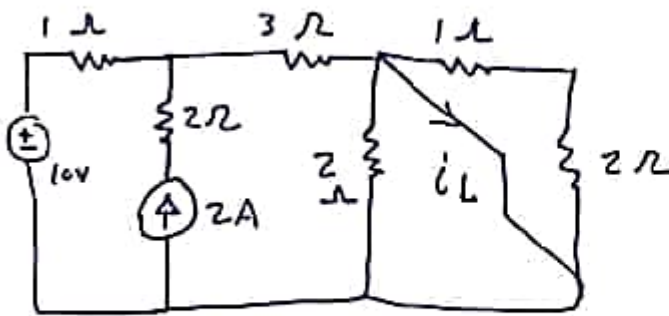


* Kill V_s

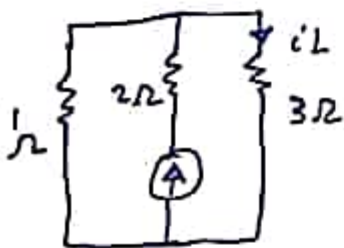

$$i'_L = 2 \times \frac{1}{3+1} = 0.5 \text{ A}$$

* Kill i_s

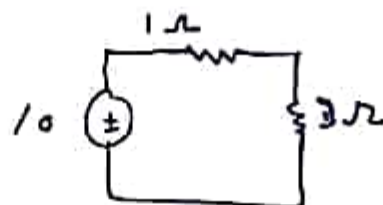

$$i''_L = \frac{10}{4} = 2.5$$



$$i_L = i'_L + i''_L = 3 \text{ A}$$

Σw


14

St. Name: Sama Obeid
me law

St. #: 0143721 ; Seat / Section

Aug. 2nd, 2017; Exam lasts 1 ⁰/₆₀ h

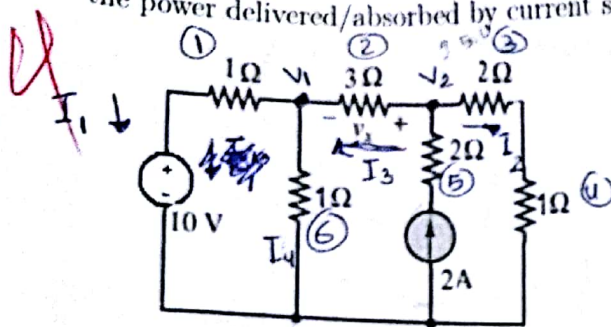Problem 1: In the circuit shown, find the voltage v_x by using nodal voltage analysis, then determine the power delivered/absorbed by current source.



$$\frac{v_2 - 0}{2+1} + \frac{v_2 - v_1}{3} - 2 = 0 \quad \text{--- (1)}$$

$$\frac{v_1 - 10}{1} + \frac{v_1 - v_2}{3} + \frac{v_1 - 0}{1} = 0 \quad \text{--- (2)}$$

$$v_2 \left[\frac{1}{3} + \frac{1}{3} \right] - \frac{1}{3} v_1 = 2 \quad \text{--- (1)}$$

$$v_2 \left[-\frac{1}{3} \right] + v_1 \left[1 + \frac{1}{3} + 1 \right] = 10 \quad \text{--- (2)}$$

$$v_2 = 5.54 \text{ V}$$

$$v_1 = 5.1 \text{ V}$$

$$v_x = v_2 - v_1 = 5.54 - 5.1 = 0.44 \text{ V}$$

$$I_1 = \frac{v_1 - 10}{1} = -4.9 \text{ A}$$

$$I_4 = \frac{v_1 - 0}{1} = 5.1 \text{ A}$$

$$I_3 = \frac{v_2 - v_3}{3} = 0.147 \text{ A}$$

$$I_2 = \frac{v_2 - 0}{3} = 1.85 \text{ A}$$

$$P_{10V} = IV = -4.9 \times 10 = -49 \text{ W}$$

$$P_{2A} = IV_2 = 2 \times 5.54 = 11.08 \text{ W}$$

$$\Sigma P_{\text{absorbed}} = 68.34 \text{ W}$$

$$P_{R1} = I^2 R = (4.9)^2 \times 1 = 24.01 \text{ W}$$

$$P_{R3} = (1.85)^2 \times 2 = 6.845 \text{ W}$$

$$P_{R4} = (1.85)^2 \times 1 = 3.42 \text{ W}$$

$$P_{R2} = I_3^2 \times 3 = (0.147)^2 \times 3 = 0.065 \text{ W}$$



$$P_{R5} = (2)^2 \times 2 = 8 \text{ W}$$

$$P_{R6} = (I_u)^2 \times 1 = (5.1)^2 \times 1 = 26 \text{ W}$$


$$P_{\text{delivered}} = 49 + 11.08 = 60.08 \text{ W}$$

$$\Sigma P_{\text{absorbed}} = 24.01 + 0.065 + 6.845 + 8 + 26 + 3.42 = 68.34 \text{ W}$$

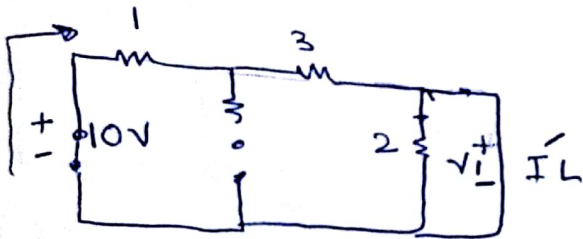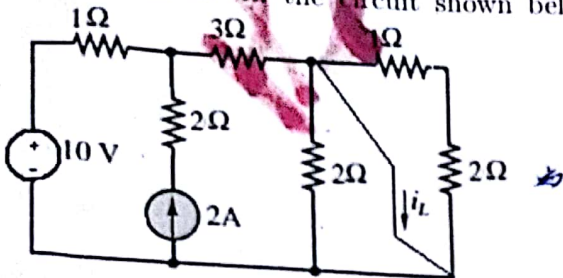
Problem 2: In the circuit shown below find the value of i_L , by using principle of superposition.



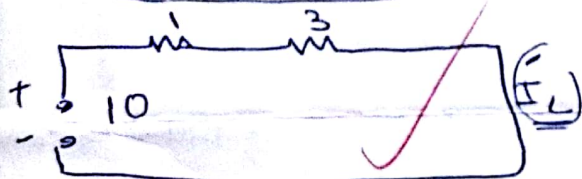~~$$i_L' = \frac{10}{1+3} = 2.5 \text{ A}$$~~


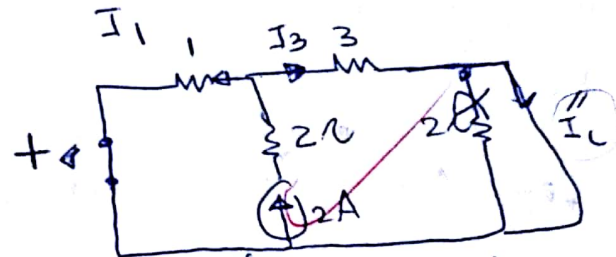
$$i_L'' = \frac{10}{1+3} \Rightarrow 2.5 \text{ A}$$





$$I_3 = i_L'' = I_{2A} \times \frac{1}{1+3}$$

~~$$I_3 = 2.05 \text{ A}$$~~

$$i_L'' = 0.5 \text{ A}$$

$$\therefore i_L = i_L' + i_L'' \Rightarrow 0.5 \text{ A} + 2.5 \text{ A} = 3 \text{ A}$$

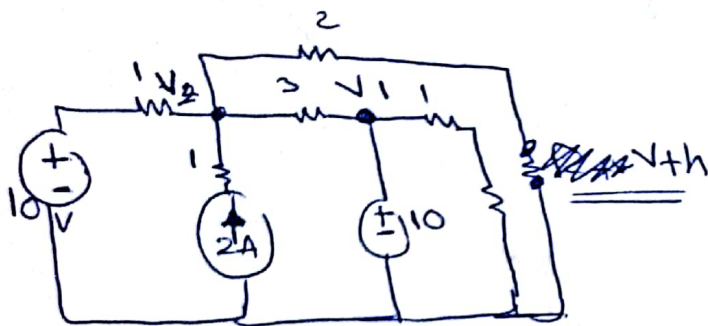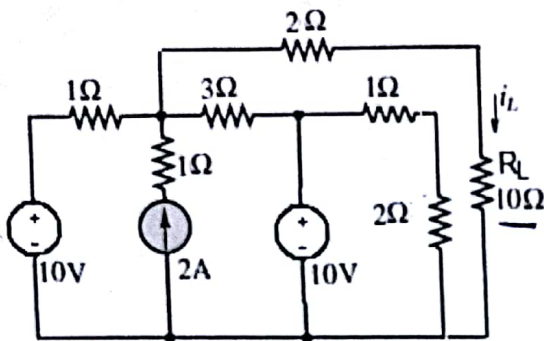Problem 3 : For the circuit shown below find the current i_L , flown through the resistance of R_L , by using thevenin equivalent circuit.




~~$V_1 + V_2 + V_3 = 0$~~

$V_1 = 10 \text{ V}$


$$\frac{V_2 - 10}{3} + \frac{V_2 - 10}{1} - 2 = 0 \quad \text{--- (1)}$$

$$V_2 \left[\frac{1}{3} + 1 \right] = 2 + 10 + \frac{10}{3}$$

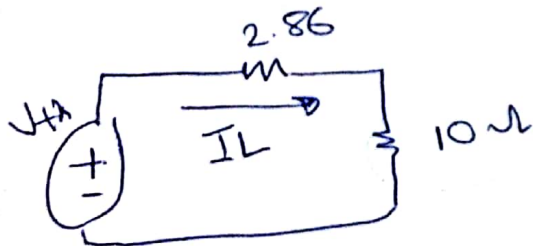$V_2 = 11.5 \text{ V} \Rightarrow V_{th} = 11.5 \text{ V}$


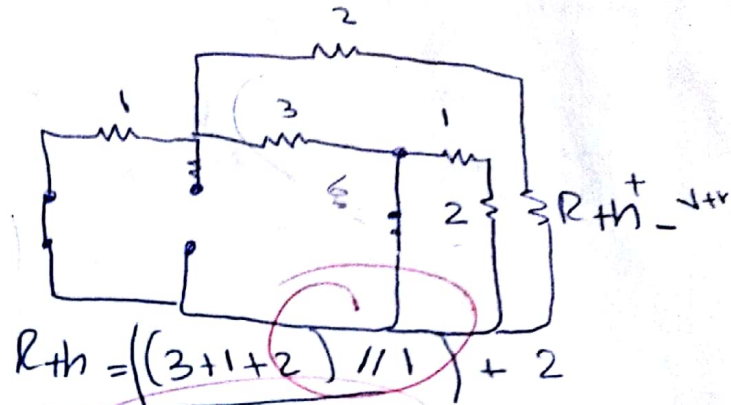
$$I_L = \frac{V_{th}}{R_{th} + R_L} = 0.894 \text{ A}$$




$$R_{th} = ((3 + 1 + 2) // 1) + 2$$

$R_{th} = 2.86 \Omega$

$V_{th} = V_2 - 0$

$R_{th} = 2.86$

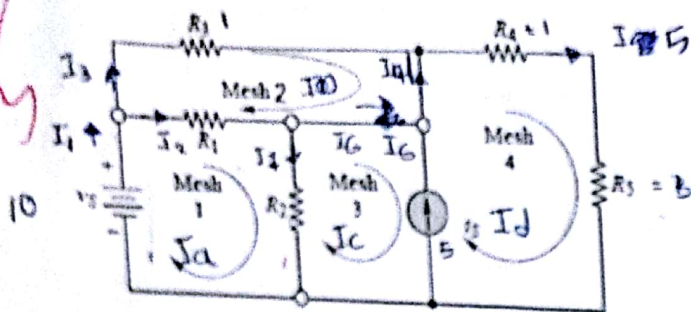Problem 4 : In the circuit shown, use mesh current method to solve for the unknown currents.
 Data: $R_1 = R_2 = R_3 = R_4 = 1\Omega$, $R_5 = 3\Omega$, $v_s = 10V$, & $i_s = 5A$



$$\begin{aligned} \text{KCL: } (5 + I_c) + I_c - I_a &= 0 \\ 20 + 1I_c + 1 \cdot I_a &= 0 \\ 5I_c - I_a &= -20 \end{aligned}$$

$$2I_a - I_b - I_c = 10 \dots (1) \quad \checkmark$$

$$2I_b - I_a = 0 \dots (2) \quad \checkmark$$

$$(1+3)I_d + 1I_c - I_a = 0 \dots (3)$$

$$5 + I_c = I_d \dots (4)$$



$$(1+3)(5 + I_c) + I_c - I_a = 0 \quad \Rightarrow \quad 5I_c - I_a = -20 \quad (3')$$

$$I_a = 4.62A \quad \checkmark$$

$$I_b = 2.31A \quad \checkmark$$

$$I_c = -3.07A \quad \checkmark$$

$$I_d = -3.07 + 5 = 1.93A$$

$$I_1 = I_a = 4.62A$$

$$I_2 = I_a - I_b = 2.3A$$

$$I_3 = I_b = 2.31A$$

$$I_4 = I_d - I_b = -0.38A$$

$$I_5 = I_d = 1.93A$$

$$I_6 = I_c - I_b = -5.38A$$

$$I_7 = I_a - I_c = 7.69A$$