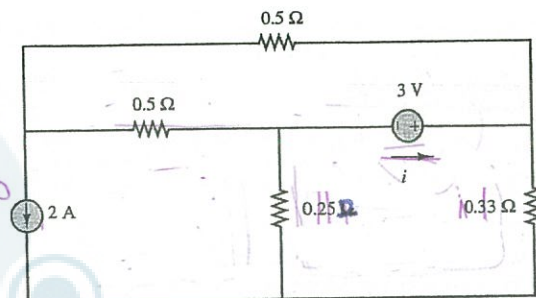


« أسئلة المراجعة : ربيح الدّيبس »

Q8- Use Mesh Analysis to find the value of i in the shown circuit.



$$0.5I_2 + 3 + 0.5(I_2 - \frac{I_1}{2}) = 0$$

$$I_1 = 2A$$

$$0.25(i_3 - I_1) + 0.33i = 0$$

$$0.25(i - 2) + 0.33i - 3 = 0$$

$$0.58i = 3 + (2 \times 0.25)$$

$$i = 6.03A$$


$$0.25(i + 2) - 3 + 0.33i = 0$$

$$0.58i + 0.5 - 3 = 0$$

$$0.58i = 2.5$$

$$i = 4.3A$$

$$i = 4.3A$$

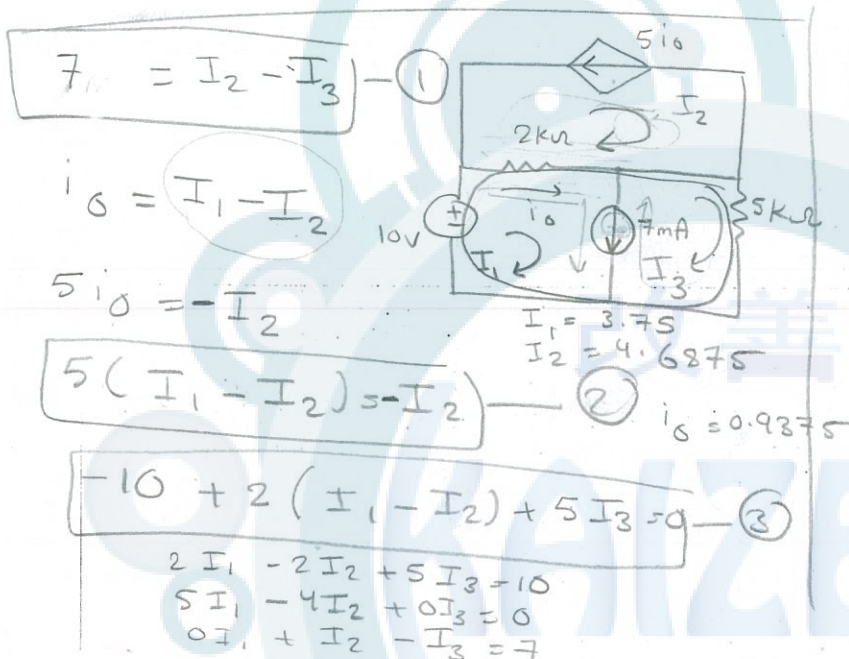

$$7I_0 = I_2 - I_3 \quad \text{--- (1)}$$

$$I_0 = I_1 - I_2$$

$$5I_0 = -I_2$$

$$5(I_1 - I_2) = -I_2 \quad \text{--- (2)}$$

$$I_0 = 0.9375$$


$$-10 + 2(I_1 - I_2) + 5I_3 = 0 \quad \text{--- (3)}$$

$$2I_1 - 2I_2 + 5I_3 = 10$$

$$5I_1 - 4I_2 + 0I_3 = 0$$

$$0I_1 + I_2 - I_3 = 7$$

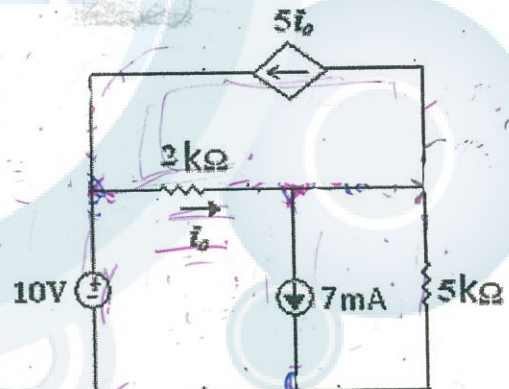Q9- Find i_0 in the shown circuit with an appropriate method (Mesh or Nodal analysis).



$$i_0 =$$


Good Luck

Don't cry ☹, Just try ☺ ...


Student Name: محمد ابو زيد ID#: 004411

- This exam is *closed book* and notes.
- Read *all* of the questions before starting (Total of 100 points).
- *Don't* write anything on this exam sheet. Solutions *must be* on the answer sheet.

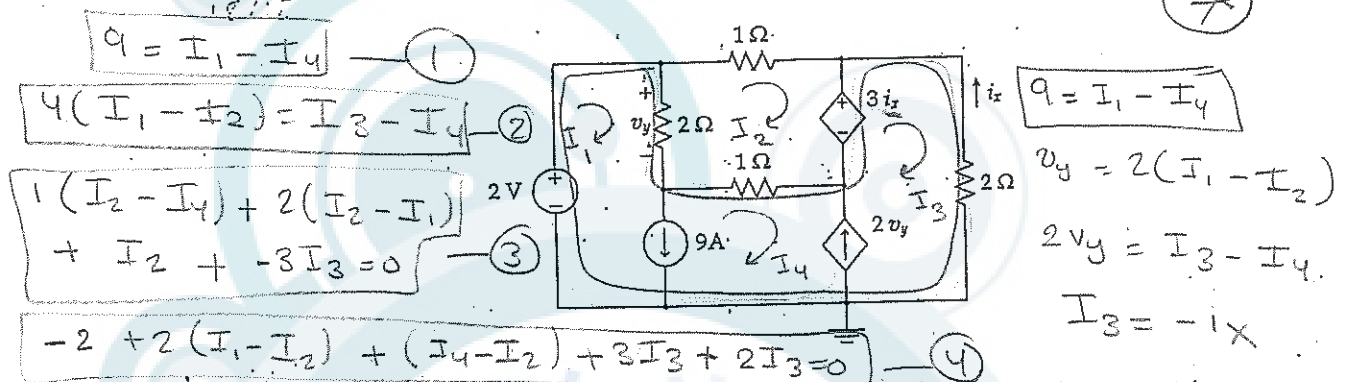
Q1. [18 points] Use mesh analysis in the circuit below to calculate v_y . **DON'T** solve the equations you obtain; just write them in their *final form*.



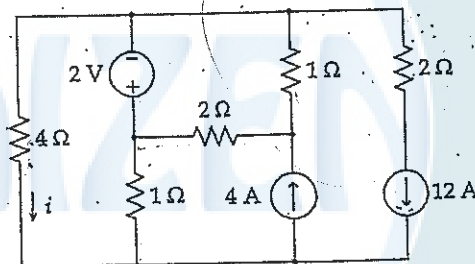Q2. [18 points] Use superposition in the circuit below to calculate the current i . **IMPORTANT:** During your solution, you can only use current division, voltage division, Ohm's law, KCL and KVL, parallel and series combinations.




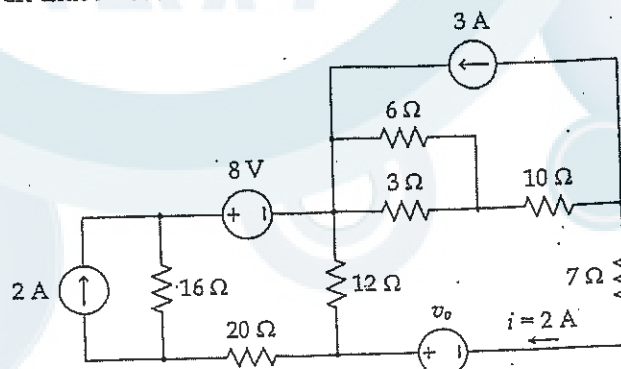Q3. [18 points] Use source transformation in the circuit below to find the value of the voltage v_o given that $i = 2$ A.




Q4. [28 points]

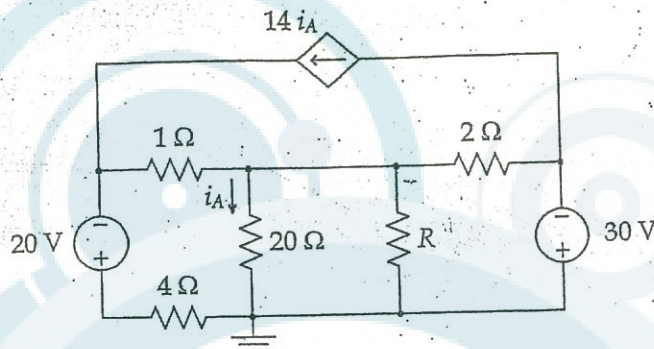- (a) Find the Thevenin Equivalent of the circuit below as seen by the resistor R .
IMPORTANT: You must use nodal analysis to analyze the circuit as you evaluate the Thevenin Equivalent. Use the provided reference point.
 (b) Calculate the *maximum* power that can be delivered from the circuit to R .





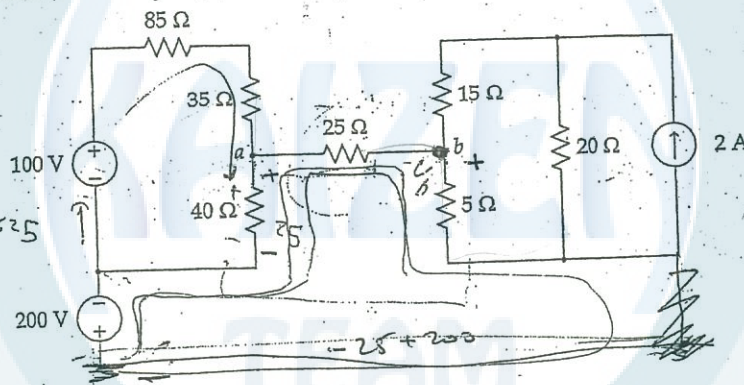Q5. [8 points]

- Use only current division, voltage division, Ohm's law, KCL and KVL, parallel and series combinations to find the voltage between node b and the ground. (Do NOT use nodal analysis, mesh analysis, superposition or source transformation).



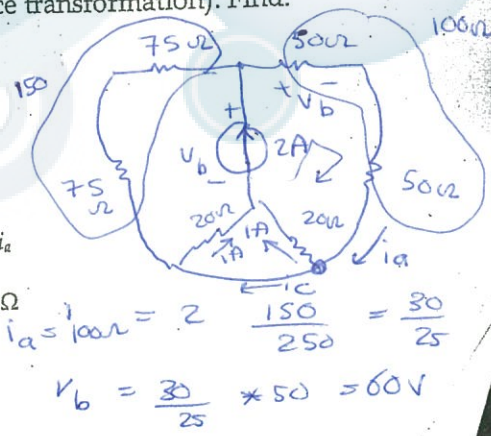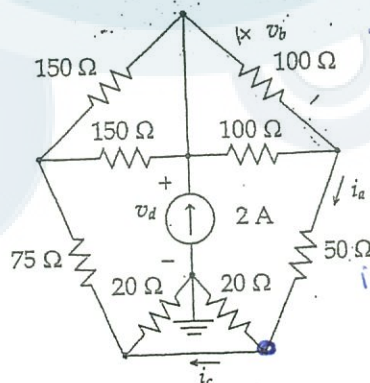- Q6. [10 points] Use only current division, voltage division, Ohm's law, KCL and KVL, parallel and series combinations to analyze the following circuit (i.e., do NOT use nodal analysis, mesh analysis, superposition or source transformation). Find:
 (a) i_a (b) v_b (c) i_c (d) v_d



$$i_a = 100\Omega = 2 \quad \frac{150}{250} = \frac{30}{25}$$

$$v_b = \frac{30}{25} \times 50 = 60V$$

$$\frac{30}{25} = 1 + i_c$$

$$-v_d + \frac{30}{25} \times 100 + 1 \times 25 = 0$$

Midterm Exam

Time 90 Minutes

University of Jordan
Electrical Engineering Department
Circuit Analysis

Dr. Hisham Hamdan
Dr. Ghasan Halasa
Dr. Mahmoud Al-Husari

Total Marks: 100

17/11/2007

Name (Arabic): راشد الحميد مصطفى ابو حجلة
Section Number: 01

Reg. Number: 0066897
Instructor name: علاء حلة

Question Number	Marks
Q1 (24 Marks)	2.5 + 12.5
Q2 (17 Marks)	13
Q3 (17 Marks)	17
Q4 (24 Marks)	14
Q5 (18 Marks)	15

63.5


+ 12.5

76


23

19
30

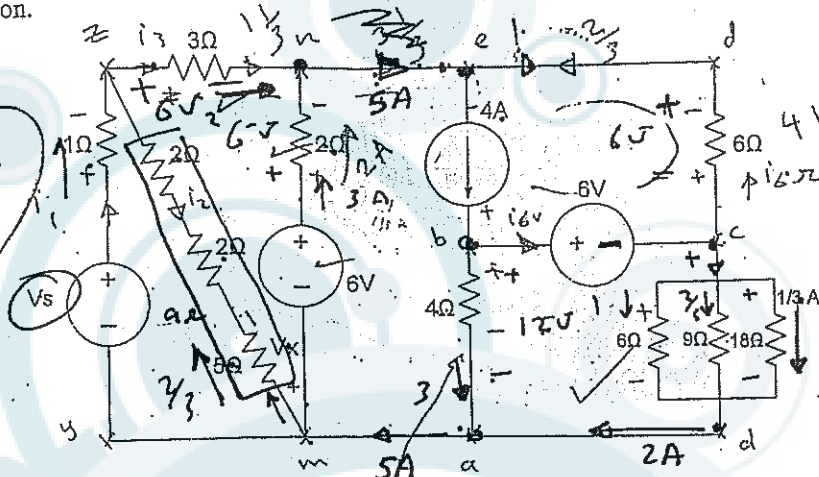Question 1. (24 marks) In the circuit shown below find the source voltage V_s and the voltage V_x across the 5Ω resistor using only simple KCL, KVL, voltage and current division.



2.5/24

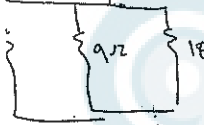

$$V_{18\Omega} = R_{18} \cdot I_{18} = \frac{18}{3} = 6 \text{ Volts}$$

Since they (9Ω, 6Ω, 18Ω) parallel

$$V_{9\Omega} = V_{6\Omega} = V_{18\Omega} = 6 \text{ Volts}$$

KVL abcd

$$-V_{4\Omega} + 6 + V_{9\Omega} = 0$$

$$V_{4\Omega} = 6 + V_{9\Omega} = 6 + 6 = 12 \text{ Volts}$$

$$I_{4\Omega} = \frac{V_{4\Omega}}{R_{4\Omega}} = \frac{12}{4} = 3 \text{ A}$$

Applying KCL at Node (b)

$$-4 + 3 + i_{6V} = 0$$

$$i_{6V} = 1 \text{ A}$$

KCL at Node (c)

$$-i_3 - 1 + i_{6\Omega} = 0$$

$$i_{6\Omega} = 0.666 \text{ A}$$

direction polarity

KVL [mncam]

$$-6 + V_{2\Omega} - V_{4\Omega} + V_{4\Omega} = 0$$

$$V_{2\Omega} = 6 + V_{4\Omega} - V_{4\Omega}$$

$$V_{2\Omega} = 6 + 10 - 12$$

$$V_{2\Omega} = 4 \text{ Volts}$$

$$I_{2\Omega}$$

KVL (yzmj)

$$-V_s + V_{1\Omega} + V_{2\Omega} + V_{2\Omega} + V_{5\Omega} = 0$$

$$-V_s + i_1 + 2i_2 + 2i_2 + 5i_2 = 0$$

$$V_s = i_1 + 9i_2$$

KVL (mnm)

$$-6 + V_{2\Omega} - V_{3\Omega} + V_{2\Omega} + V_{2\Omega} + V_{5\Omega} = 0$$

$$-6 + 4 - 3i_3 + 2i_2 + 2i_2 + 5i_2 = 0$$

$$9i_2 - 3i_3 = 2$$

applying KCL at Node (ned)

$$-i_3 + i_{2\Omega} + 4 - i_{6\Omega} = 0$$

$$i_3 = -i_{2\Omega} + 4 - i_{6\Omega}$$

$$i_3 = -2 + 4 = 0.666$$

$$i_3 = 0.334 \text{ A}$$

$$i_2 = \frac{2 + 3i_3}{9} = 0.666$$

$$V_x = -12 * 0.5 = -6.666 * 5 = -3.333 \text{ Volts}$$

$$i_1 = 1.334 + 0.666$$

$$i_1 = 1.999 \text{ A}$$


$$V_s = 1.999 + 9 * 0.666$$

$$V_s = 7.999 \text{ Volts}$$

$$6i_b + 3(i_c - i_a) + 6(i_c - i_b) + 6i_d = 0 \quad (3)$$

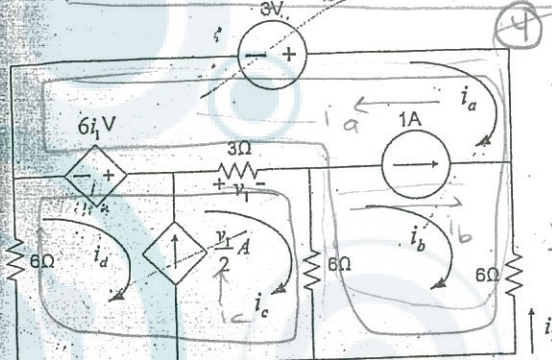Question 2. (17 Marks) Write the mesh equations in their final form as a function of the labeled mesh currents for the circuit shown below. (Don't attempt to solve the equations).

$$-3 + 6i_b + 6(i_b - i_c) + 3(i_a - i_c) + -6i_b = 0 \quad (2)$$



$$1 = i_a - i_b$$

$$V_1 = 3(i_c - i_a)$$

$$i_b = -i_1$$

$$i_d = +i_2$$

$$\frac{V_1}{2} = i_c - i_d$$

$$\frac{3}{2}(i_a - i_c) = i_c - i_d \quad (1)$$

at the dependent current source

$$-6i_1 + 3 + 6i_b + 6(i_b - i_c) + 3(i_a - i_c) = 0$$

$$3i_a + 12i_b - 9i_c + 6i_1 = 3$$

$$\text{but } i_1 = -i_b$$

$$3i_a + 12i_b - 9i_c - 6i_b = 3$$

$$3i_a + 6i_b - 9i_c = 3 \quad (1)$$

Mesh c & d

$$6i_d - 6i_1 + 3(i_c - i_a) + 6(i_c - i_b) = 0$$

$$-3i_a - 6i_b + 9i_c + 6i_d - 6i_1 = 0$$

$$i_1 = -i_b \quad \checkmark$$

$$-3i_a - 6i_b + 9i_c + 6i_d + 6i_b = 0$$

$$-3i_a + 9i_c + 6i_d = 0 \quad (2)$$

at the 1A source

$$i_b - i_a = 1 \quad (3)$$

$$i_c - i_d = \frac{V_1}{2}$$

$$V_1 = 3(i_c - i_a)$$

ok

$$i_c - i_d = \frac{3(i_c - i_a)}{2}$$

$$2i_c - 2i_d = 3i_c - 3i_a$$

$$-3i_a + i_c + 2i_d = 0 \quad (4)$$

$$1 = i_a - i_b \quad (3)$$

$$V_1 = 3(i_c - i_a)$$

$$\frac{V_1}{2} = i_c - i_d$$

$$\frac{3}{2}(i_a - i_c) = i_c - i_d \quad (1)$$

$$-6i_1 + (i_c - i_d) + 6(i_d - i_2) = 0$$

$$3(i_c - i_a) + 6(i_c - i_b) + (i_c - i_d) = 0$$


$$-3 + 6(i_b - i_1) + 6(i_b - i_c) + 3(i_a - i_c)$$

$$+ 6i_1 = 0 \quad (5)$$

$$i_b = -i_1 ; i_2 = -i_d \quad (6)$$

Question 3 (17 Marks) Find the current I_o using superposition. In the process of your solution use only Ohm's law and current division.


due to 2mA

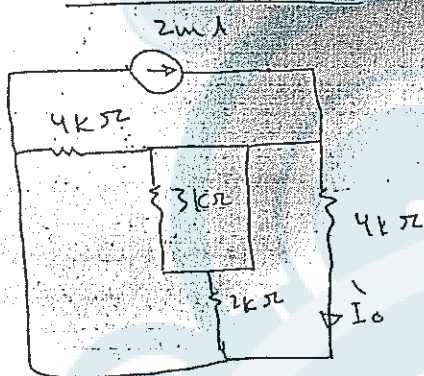

$$I_o = I \cdot \frac{\frac{1}{R_o}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$I_o = 2 \times 10^{-3} \cdot \frac{\frac{1}{4k}}{\frac{1}{4k} + \frac{1}{2k} + \frac{1}{4k}} = 590 \times 10^{-6} \text{ A}$$

due to (9V)

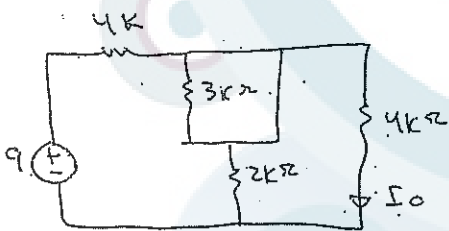


(4kΩ, 2kΩ) parallel


$$R_o = \left(\frac{1}{2k} + \frac{1}{4k} \right)^{-1} = 1.33k\Omega$$

$$I = \frac{9}{4k + 1.33k} = 1.6975 \times 10^{-3} \text{ A}$$
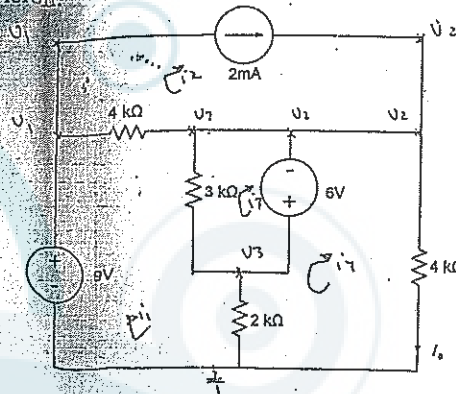
$$I_o = 1.6975 \times 10^{-3} \cdot \frac{2k}{4k + 1.33k} = 562.5 \times 10^{-6} \text{ A}$$



due to 6V

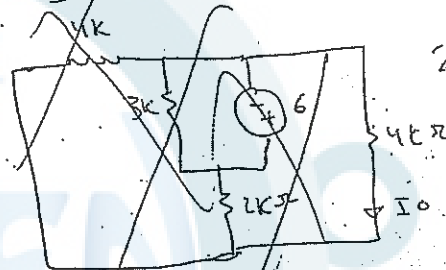


$$I_o = \frac{6}{4k} = 1.5 \times 10^{-3} \text{ A}$$

$$I_o = \frac{6}{4k} \cdot \frac{\frac{1}{4k}}{\frac{1}{4k} + \frac{1}{5k} + \frac{1}{4k}} = -535.7 \times 10^{-6} \text{ A}$$

$$I_o = I_o' + I_o'' + I_o''' = 590 \times 10^{-6} + 562.5 \times 10^{-6} - 535.7 \times 10^{-6} = 616.8 \times 10^{-6} \text{ A}$$

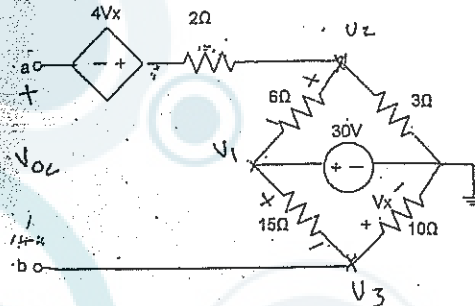Question 4. (24 Marks) Use nodal analysis to find the Norton equivalent circuit with respect to terminals a and b of the circuit shown below.



at Node (V_1)

$$V_1 = 30 \text{ Volts}$$

at Node (V_2)

$$\frac{V_2}{3} + \frac{V_2 - V_1}{6} = 0$$

$$V_2 + \frac{V_2 - V_1}{2} = 0$$

$$2V_2 + V_2 - V_1 = 0$$

$$3V_2 - V_1 = 0$$

$$3V_2 = 30$$

$$V_2 = 10 \text{ Volts}$$

at Node (V_3)

$$\frac{V_3}{15} + \frac{V_3 - V_1}{15} = 0$$

$$\frac{V_3}{2} + \frac{V_3 - V_1}{3} = 0$$

$$3V_3 + 2V_3 - 2V_1 = 0$$

$$5V_3 = 60$$


$$V_3 = 12$$

KVL [ba V_2 V_1 V_3 b]

$$-V_{oc} - 4V_x + 2(0) + (V_2 - V_1) + (V_1 - V_3) = 0$$

$$V_{oc} = -4 \times 12 + 0 + 10 - 12 = -28 \text{ Volts}$$

$$V_1 = 30 \text{ Volts}$$

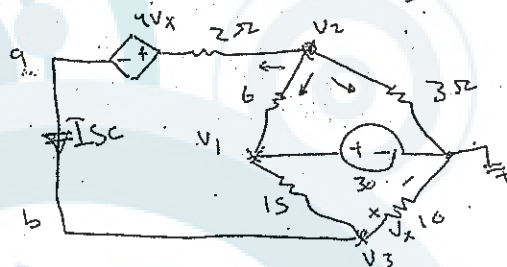

at Node (V_1)

$$V_1 = 30 \text{ Volts} \quad \text{--- (1)}$$

at Node V_2

$$\frac{V_2 - 4V_x}{2} + \frac{V_2}{3} + \frac{V_2 - V_1}{6} = 0$$

$$3V_2 - 12V_x + 2V_2 + V_2 - V_1 = 0$$

$$6V_2 - 12V_x = V_1$$

$$6V_2 - 12V_3 = 30$$

$$V_2 - 2V_3 = 5 \quad \text{--- (2)}$$

at Node (V_3)

$$\frac{V_3}{10} + \frac{V_3 - V_1}{15} = 0$$

$$\frac{V_3}{2} + \frac{V_3 - V_1}{3} = 0$$

$$3V_3 + 2V_3 - 2V_1 = 0$$

$$5V_3 = 60 \Rightarrow V_3 = 12 \text{ Volts}$$

$$I_{sc} = 5 + 2V_3 = 29 \text{ Volts}$$


$$I_{sc} = \frac{V_2 - 4V_x}{2}$$

$$I_{sc} = \frac{29 - 4 \times 12}{2}$$


$$I_{sc} = -9.5 \text{ A}$$

$$R_{th} = R_{No} = 5.263 \Omega$$

Norton Eq.

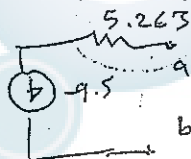

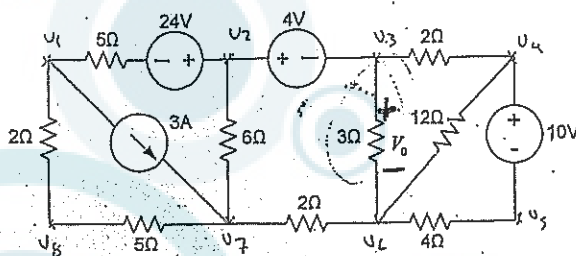Question 5. (18 Marks) Use source transformation as many times as needed to find V_0



(10V, 4Ω) series

$$I_s = \frac{10}{4} = 2.5 \text{ A}$$

(3A, 6Ω) series parallel

$$R_{eq} = 2 + 5 = 7 \Omega$$



$$V = I R = 3 \times 7 = 21 \text{ Volts}$$

(3V, 12) series

$$I = \frac{3}{12} = 0.25 \text{ A}$$

(2.5A, 3) parallel

$$V = 2.5 \times 3 = 7.5$$

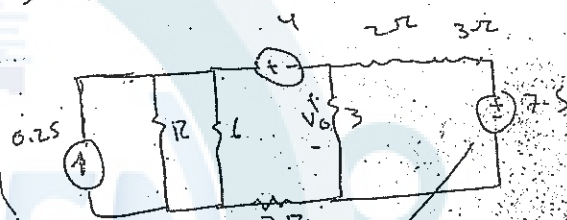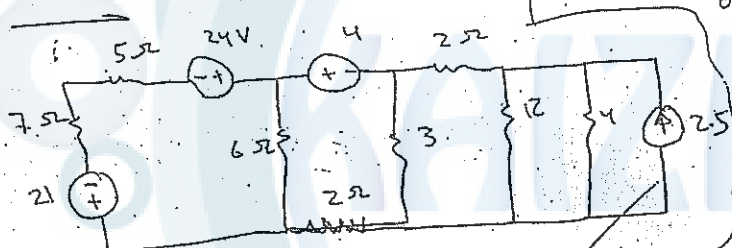

(7.5V, 5Ω) series


$$R_{eq} = 7 + 5 = 12 \Omega$$

(21V, 24V) series

$$V_{eq} = -21 + 24 = 3$$

(4, 12) parallel
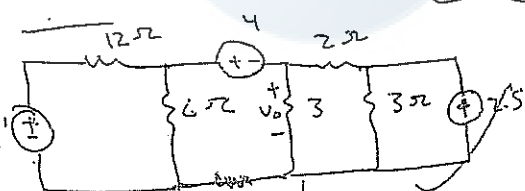
$$R_{eq} = \left(\frac{1}{12} + \frac{1}{4} \right)^{-1} = 3 \Omega$$



(2, 3) series


$$R_{eq} = 2 + 3 = 5 \Omega$$

(0.25A, 4Ω) parallel

$$V = 0.25 \times 4 = 1 \text{ V}$$

(7.5V, 5Ω)

$$I = \frac{7.5}{5} = 1.5 \text{ A}$$

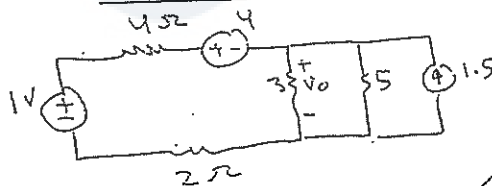

(2V, 4Ω) series $\Rightarrow R_{eq} = 6 \Omega$

(4V, 1V) series $\Rightarrow V_0 = -1 + 4 = 3 \text{ V}$

* أرجو مراجعة السؤال
* أرجو مراجعة السؤال

Electrical Circuits
EE 221
Mid Exam


Time: 90 mins

Reg. No: 0057345

Name (Arabic):

منذر علي حسن كوي

Q1) In the following circuit, $V_1 = 3V$

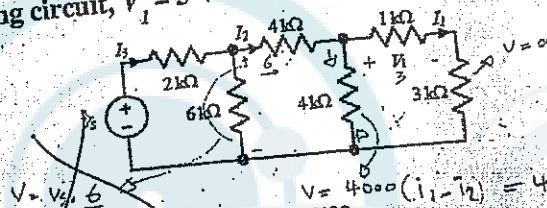

a) Find V_S

b) Determine the power supplied by the source.

$$I_1 = \frac{3}{10^3} = 3 \times 10^{-3}$$

KVL

$$\Rightarrow 4000(I_1 - I_2) + 3 \times 10^{-3} = 0$$

KVL

$$-\frac{6V_S}{8} + 4000(6 \times 10^{-3}) + 4000(6 \times 10^{-3} - 3 \times 10^{-3}) = 0$$

$$-\frac{6V_S}{8} + 24 + 24 - 12 = 0$$

$$-\frac{6V_S}{8} + 48 = 12 \Rightarrow -\frac{6V_S}{8} = -36 \Rightarrow -6V_S = -288 \Rightarrow V_S = 48V$$


b) Power

$P = IV$

$$I_1 = 48 \times \frac{2000}{8000} = \frac{1}{2000}$$

$$P = 6 \times 10^{-3}$$

$$P = 288W$$

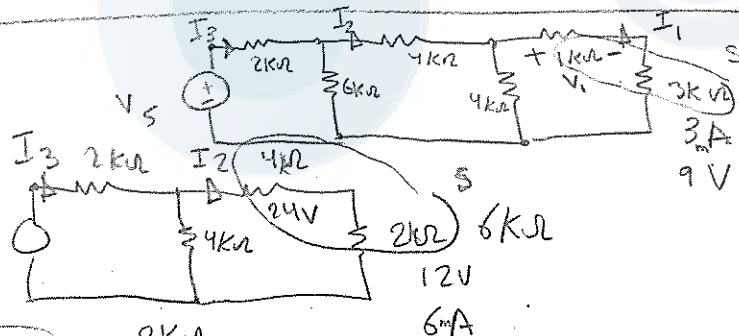

$$V_1 = 3V$$


$$V_S = ?$$

$$I = 3mA$$

$$I_2 = 6mA$$


$$V_S = 66V$$

$$P = 990mW$$

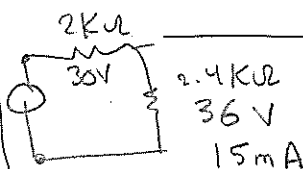

$$I_1 = 15mA$$

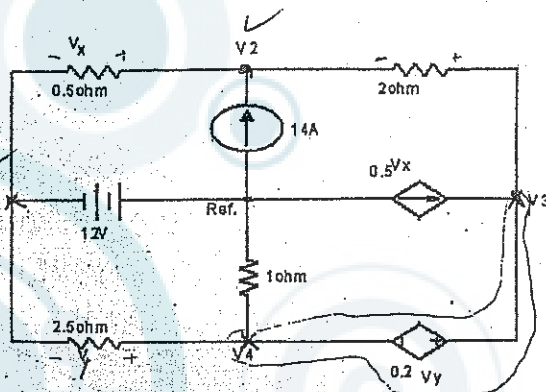Q2. Using nodal analysis technique to Determine the values of the unknowns node to reference voltage in the following circuit..



$$V_1 = -12$$

$$2: -14 + \frac{V_2}{0.5} - \frac{V_3}{2} + \frac{V_4}{1} = 0$$

$$10 = 2.5V_2 - 0.5V_3$$

1 per node:


$$-0.5V_x + \frac{V_3}{2} - \frac{V_4}{2.5} = 0$$

$$-0.5V_x + 0.5V_4 + 0.5V_3 - 0.05V_2 - 0.4V_1 = 0$$

$$V_3 - V_4 = 12V_y$$

$$-0.5 \left(\frac{V_2 - 12}{0.5} \right) + 0.5V_4 + 0.5V_3 - 0.05V_2 - 0.4V_1 = 0$$

Missing equation

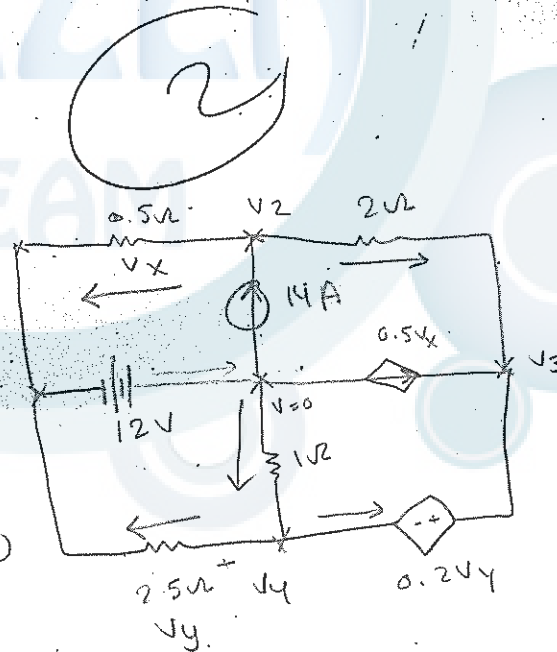

$$V_1 = 12V \quad (1)$$

$$14 = \frac{V_2 - V_1}{0.5} + \frac{V_2 - V_3}{2} \quad (2)$$

$$\frac{V_2 - V_3}{2} + 0.5(V_2 - V_1) + 0.2(V_4 - V_1) = 0 \quad (3)$$

$$-V_4 = 0.2(V_4 - V_1) + \frac{V_4 - V_1}{2.5} \quad (4)$$


$$V_x = V_2 - V_1$$

$$V_y = V_4 - V_1$$

$$V_1 = 12V, V_2 = 20.3V$$

$$V_3 = 25.7V, V_4 = 4.5V$$

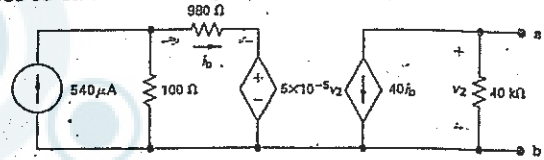Q3 Determine the Thevenin equivalent with respect to the terminals a,b for the circuit shown.



$$V = 5 \times 10^{-5} \frac{980}{1080} \times 42 \text{ V}$$

$$i_b = 540 \times 10^{-6} \times \frac{100}{1080} - \frac{5 \times 10^{-5} v_2}{1080}$$

$$i_b = .05 - 4.629 \times 10^{-8} v_2$$

$$i_2 = 40 \times 10^{-3} = 40 i_b \text{ OK}$$




$$i_2 = 40 \times 10^{-3} = 40 (.05 - 4.629 \times 10^{-8} v_2)$$

$$2 = 40 \times 10^{-3} (2 - 1.851 \times 10^{-6} v_2)$$

$$2 = 80 \times 10^{-3}$$

$$i_b = .05 - 3.2032 \times 10^{-3}$$





$$i_b = .496$$

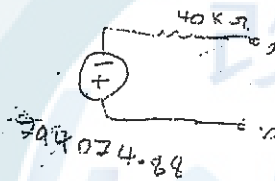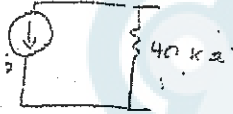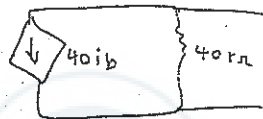

KAIZEN
TEAM

Q4- Use a series of source transformations to find i_0 in the following circuit.

3

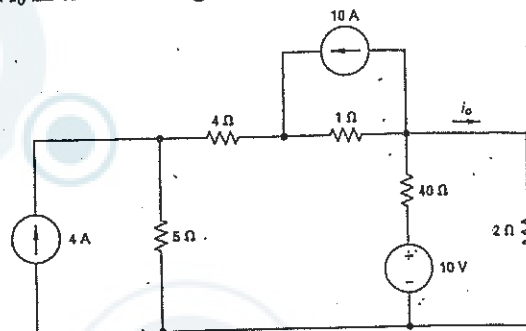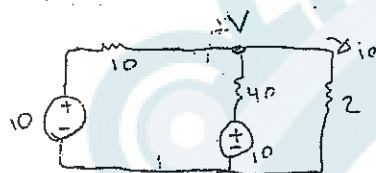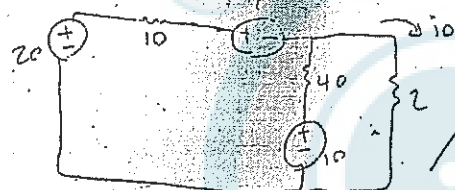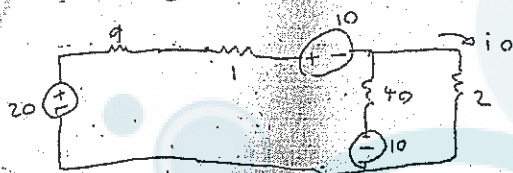

$$V_{10\Omega} = 10 \times \frac{10}{50} = 2$$

$$V_L = -10 + 2 + 2i_0 = 0 \Rightarrow -8 + 2i_0 = 0 \Rightarrow 8 = 2i_0 \Rightarrow i_0 = 4A$$



$$\frac{V}{10} - \frac{10}{10} + \frac{V}{40} - \frac{10}{40} + \frac{V}{2} = 0$$

$$1V - 1 + 0.025V - 0.25 + 0.5V = 0$$

$$1.525V - 1.25 = 0 \Rightarrow 1.525V = 1.25 \Rightarrow V = 0.8196V$$

$$i_0 = \frac{V}{2} = 0.409A$$

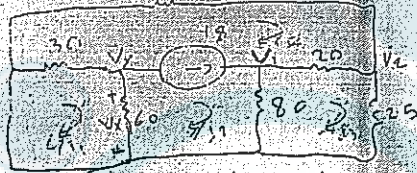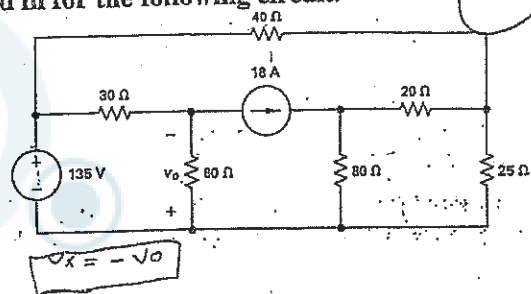Q5- Find the voltage V_o using superposition method in for the following circuit.



$V_x = -V_o$


Nodal:

$$1) \frac{V_x}{30} + \frac{V_x}{60} + \frac{V_x}{40} - \frac{V_2}{40} = \frac{V_x}{30} = 0 \quad || \quad -0.75 V_x - 0.25 V_2 + 0.333 V_x = 0$$

$$2) \frac{V_2}{20} - \frac{V_1}{20} + \frac{V_2}{40} - \frac{V_x}{40} - \frac{V_2}{25} = 0 \quad || \quad 0.115 V_2 - 0.05 V_1 - 0.025 V_x = 0$$

$$3) \frac{V_1}{20} - \frac{V_2}{20} + \frac{V_1}{80} = 18 \quad || \quad 0.0625 V_1 - 0.05 V_2 = 18$$

~~$0.1083 V_x - 0.025 V_2 = 0$~~

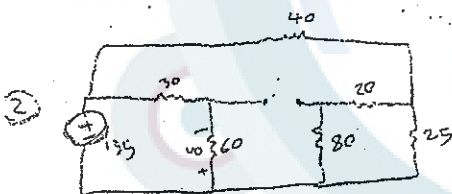

KVL: $-135 + 30i + 60i = 0 \quad || \quad 90i = 135 \quad i = 1.5$

$V_o = 90V$

$$V_o = V_o' + V_o'' \\ = V_o + 90$$