



Madarju.com

Electrical



Dr Hassan farahneh




$$I = \frac{dQ}{dt}$$

No:-

Date: 24/9/2019

Power Supplies (Power Sources)

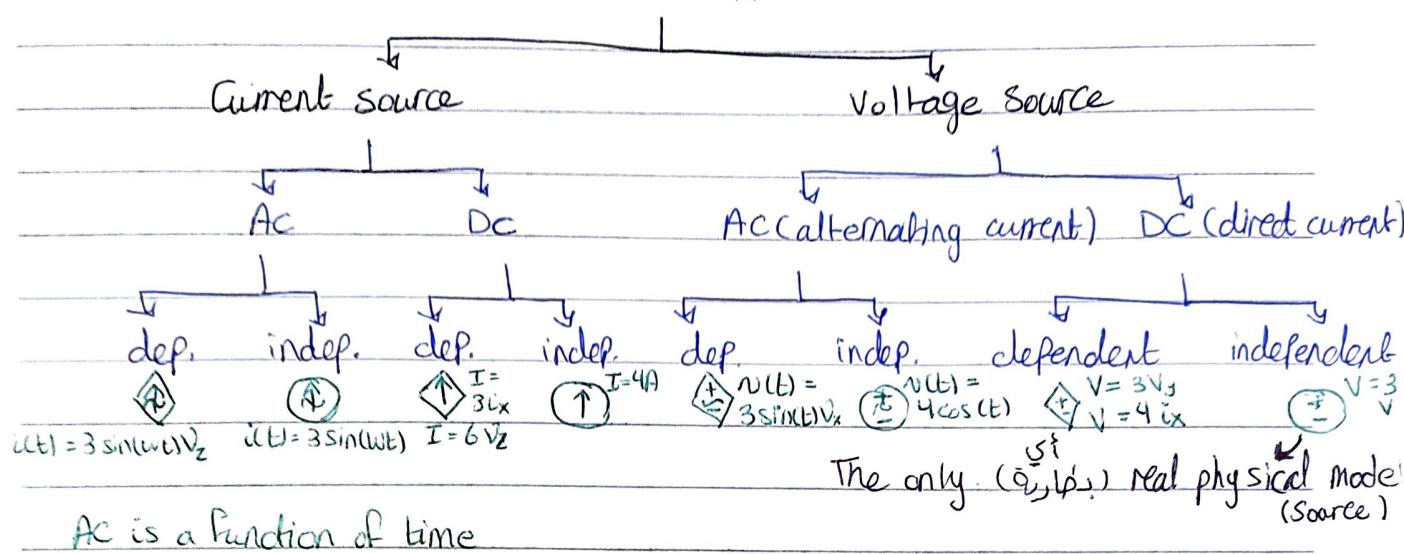

AC is a function of time

- If Power Supply \rightarrow AC \rightarrow AC circuit
DC \rightarrow DC circuit

- Electrical circuit consists of :-

1. Power supply \rightarrow Delivered Power \rightarrow net power = zero

2. Load \rightarrow consumed power \rightarrow no saving, no more power required

3. Connections (wires)

- DC :-

\rightarrow Constant magnitude and direction of time ~~at 2nd year~~

AC :-

\rightarrow Magnitude & direction change with time

26/9/2019

• Voltage definition V voltage unit = Voltage (V)

voltage at ∞ = zero

\hookrightarrow The work required to move a charge (1 coulomb) from the infinity to this point

(if +ve voltage) if -ve voltage \rightarrow from this point to ∞

$$\overset{A}{V} = 5V \quad \overset{B}{V} = -3V \quad V_{AB} = V_A - V_B = 8V$$

$$\overset{C}{V} = 9V$$

$$V_{AC} = V_A - V_C = 5 - 9 = -4V$$

• Current definition I current unit = Ampere (A)

$i = \frac{dq}{dt}$ change of charges with respect with time




IR Exam Example

- $q = 4e^{-3t}$ Find $i(t) \mid t=4 \text{ sec}$


$$i = \frac{dq}{dt} = -12e^{-3t}$$

$$i \mid_{t=4} = -12e^{-3(4)} =$$

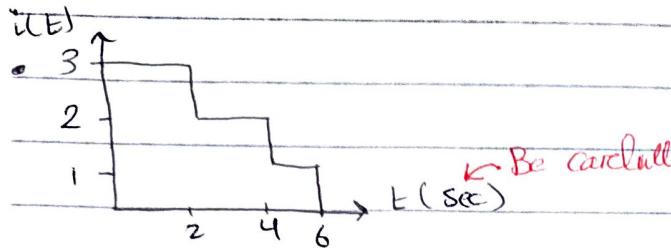Find q

$$q = \int i(t) dt$$
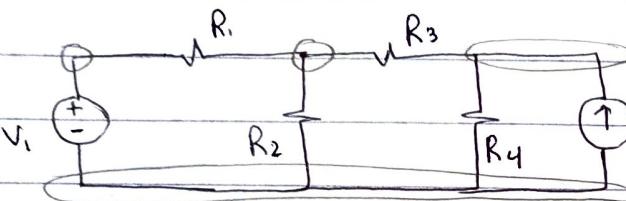
$$q = 2 \times 3 + 2 \times 2 + 2 \times 1 = 11 \text{ C}$$



6 elements

6 branches OR 5 branches

4 nodes

6 loops 3 meshes

Terminologies

mesh any closed path which doesn't have any closed path inside elements

branch any part of circuit have 1 element or more

the same current passes \rightarrow branch

node the connection point of two branches or more

loop any closed path

Power Definition P Power unit is Watt (W)


\hookrightarrow Delivered power (-ve) (produced) $\hookrightarrow \sum P = 0$

By power supplies

\hookrightarrow Absorbed power (+ve) (consumed)

By Load (resistances)

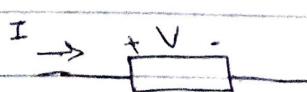* Polarity is important, You always must show the sign




$$I = 2 \text{ A}$$

$$V = 5 \text{ V}$$

$$P = IV = 2 \times 5 = +10 \text{ W} \Rightarrow \text{Absorbed}$$

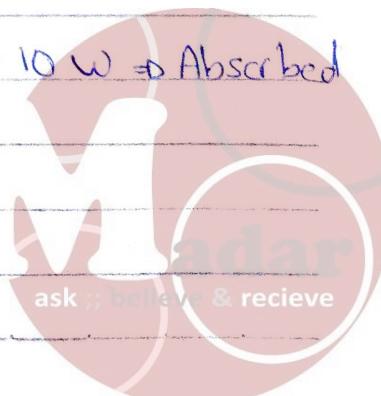
* If current passes from $+ \rightarrow +$ \rightarrow +ve Power
 $- \rightarrow -$ \rightarrow -ve Power




• every mesh loop not
every loop mesh.

No.:

Date:

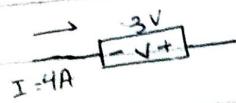

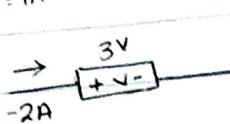
$$P = -4 \times 3 = -12 \text{ W} \rightarrow \text{Delivered power}$$



$$P = +(-2)(3) = -6 \text{ W} \rightarrow \text{Delivered}$$

Example

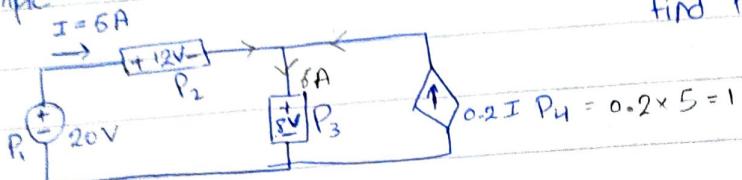

Find the Powers?

$$P_1 = -(5)(20) = -100 \text{ W}$$

$$P_2 = +(5)(12) = +60 \text{ W}$$

$$P_3 = +(6)(5) = +48 \text{ W}$$

$$P_4 = -(1)(8) = -8 \text{ W} \quad \text{OR} \quad 0 = -100 + 60 + 48 + P_4 \quad P_4 = -8$$

* Current in mesh will not be changed, voltage is opposite (In parallel series)

* Elements in parallel have the same voltage, current is opposite.


- At any node, sum of current = 0

29/9

Basic Laws

1. Ohm's Law


V : Voltage

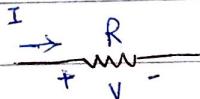

"The voltage drop across any conductor is directly proportional with current intensity passing through the conductor." $V \propto I$ $V = I \cdot R$

- Polarity & in the enter of current \rightarrow +ve polarity (In resistance)
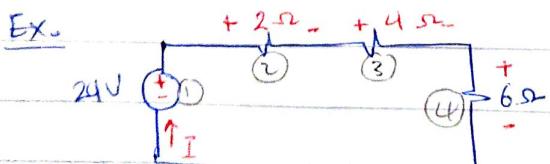
$$\text{Ex. } R = 4 \Omega \quad I = 3 \text{ A} \quad V = (3)(4) = 12 \text{ V}$$



- We can control the current direction if 1 source, current is out from the +ve polarity of the source (In source)

$$I = \frac{V}{R} = \frac{24}{2+4+6} = 2 \text{ A}$$

$$V_{6\Omega} = 12 \text{ V}$$

$$V_{4\Omega} = 8 \text{ V}$$

$$V_{2\Omega} = 4 \text{ V}$$

$$P_1 = 8 \text{ W} \quad P_3 = 16 \text{ W}$$

$$P_1 = (-24)(2) = -48 \text{ W}$$

$$P_4 = 24 \text{ W}$$




No: _____

Date: _____

$$P = V \cdot I = I^2 R = \frac{V^2}{R} \quad [P] = W$$

2* Kirchhoff's Laws

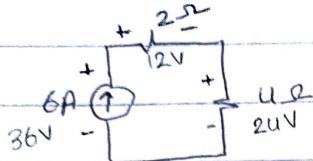


① Kirchhoff's current law (KCL)

"At any node, the algebraic sum of the currents equal zero"

$$\sum I_{in} = \sum I_{out} \text{ @ node}$$

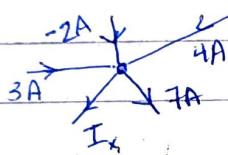
Ex. Find I_x $\sum I_{in} = \sum I_{out}$



$$\text{Find } I_x$$

$$(3) + (-2) + 4 = 7 + I_x$$

$$I_x = -2 \text{ A}$$

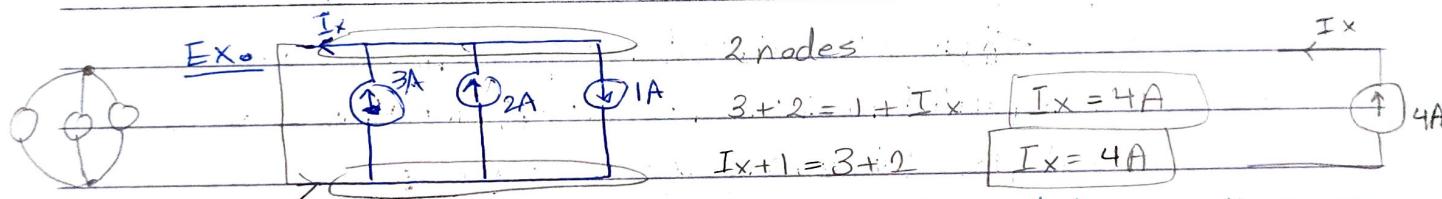

2 nodes

$$3 + 2 = 1 + I_x \quad I_x = 4 \text{ A}$$

$$I_x + 1 = 3 + 2$$

$$I_x = 4 \text{ A}$$

any element connected up in same node and down on the same node \Rightarrow connected in parallel. (only 30% of the time)


connected in the same node up & down

* Parallel current sources can be added together.

* Parallel elements have same voltages

Ex.

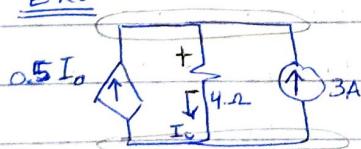Find I_o ? / By applying KCL $\sum I = 0$ @ node




$$3 + 0.5 I_o = I_o \quad 0.5 I_o = 3 \quad I_o = 6 \text{ A}$$

$$V_{4\Omega} = (6)(4) = 24 \text{ V} \quad P_{4\Omega} = (6)(24)$$

* Since the answer is +ve, the assumed direction is true.

Apply KCL $\sum I = 0$ @ node:

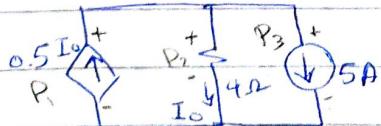

$$0.5 I_o = I_o + 5 \quad I_o = -10 \text{ A}$$

$$V_{4\Omega} = (-10)(4) = -40 \text{ V} \quad P_i = -(0.5 \times -10)(-40) = -200 \text{ W}$$


$$P_2 = P_{4\Omega} = (-10)(-40) = 400 \text{ W}$$

$$P_3 = +(5)(-40) = -200 \text{ W}$$

No: _____

Date: _____

31/10/2019

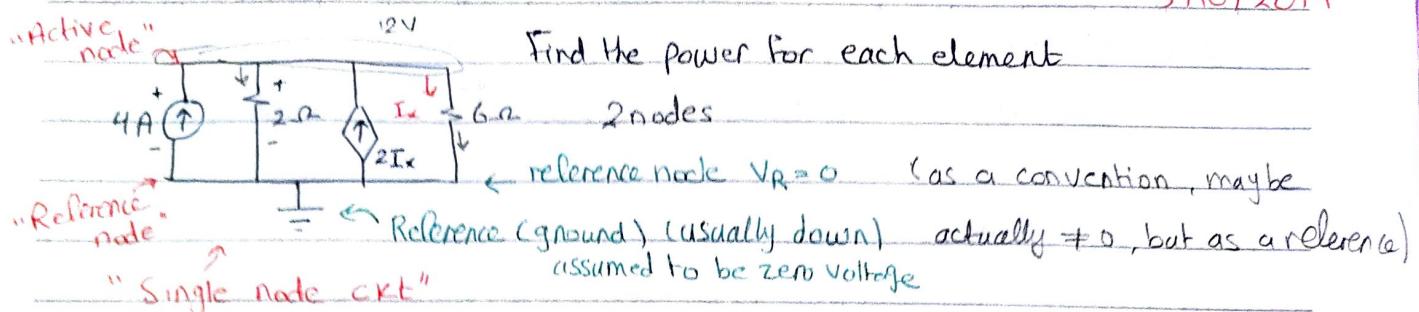

* Single node ckt Analysis

1. Assign a node (active & reference node)

2. Assign the current in each resistance (resistance between ref. & active node, the current is from active to ref. node, because I assumed $V_{\text{active}} > V_{\text{ref.}}$. so the current is from high to low voltage.)

3. Apply kirchhoff's current law for each active node. KCL

e.g.

$$\begin{array}{c} 10V \quad 4V \quad 6V \\ \text{---} \quad \text{---} \quad \text{---} \\ | \quad | \quad | \\ 2\Omega \quad 2\Omega \end{array} \quad I = V/R = 4/2 = 2A$$

Solving the above ckt

$$4 + 2I_x = \frac{V}{2} + \frac{V}{6} \quad I_x = \frac{V-0}{6} \text{ since the same direction}$$




$$4 + 2\left(\frac{V}{6}\right) = \frac{V}{2} + \frac{V}{6} \quad 4 = V + 3V - 2V \quad \frac{2V}{6} = 4 \quad V = \frac{4 \times 6}{2} = 12V$$

$$I_{2\Omega} = 6V \quad I_x = 12/6 = 2A$$

$$P_{4A} = -(4)(12) = -48W \rightarrow \text{delivered power}$$

Example

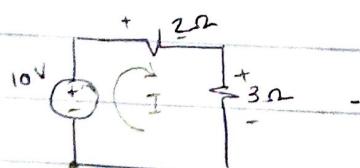

$$-10 + 2I + 3I = 0 \quad I = 2A \quad V_{2\Omega} = 4V$$

Our assumption of direction is true.

$$P_{2\Omega} = +(2)^2(2) = 8W$$

* Single mesh ckt Analysis

1. Assign current direction (current exits from +ve pole of battery). clockwise or counter clockwise

2. Assign the polarity of each resistance (+ve from enter of current)

3. Apply KVL

If more than 1 source, assume the current clockwise.


No:-----

Date:-----

② Kirchhoff's Voltage Law (KVL)

$\sum V = 0$ For any closed path , even though in loop

Example

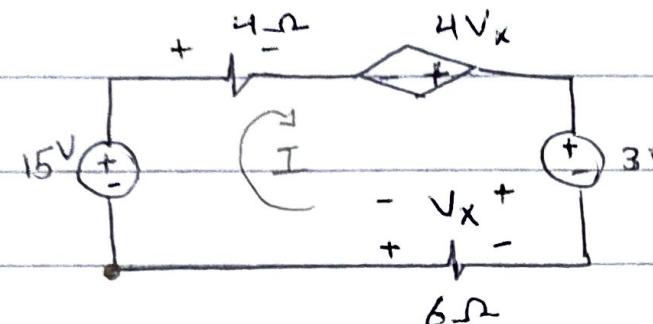

"single mesh"

$$-15 + 4I - 4V_x + 3 + 6I = 0$$

$$V_x = -6I$$

$$-15 + 4I + 24I + 3 + 6I = 0$$

$$I = 12/34 \text{ A}$$


our assumption was correct

H-W show that the total power of the cut = 0

* Resistances Connection

6/10/2019

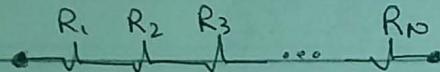(1) Series \rightarrow same current through all resistances.




$$R_T = R_1 + R_2 + \dots + R_N \quad [R] = \Omega$$

$$I_1 = I_2 = \dots = I_N$$

Conductance
conductance $\rightarrow G = \frac{1}{R}$ $[G] = \text{S}^{-1}$

(2) Parallel \rightarrow same voltages


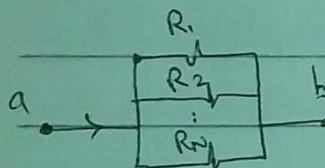


$$V_1 = V_2 = \dots = V_N$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$


$$G_T = G_1 + G_2 + \dots + G_N$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

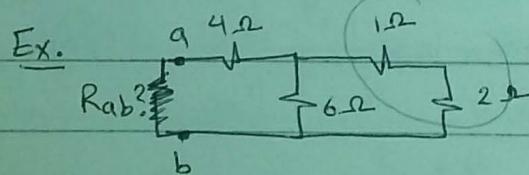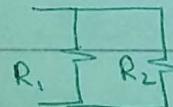


Advice

start from the end



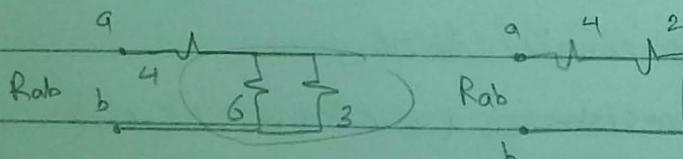


$$R_{ab} = 6 \Omega$$

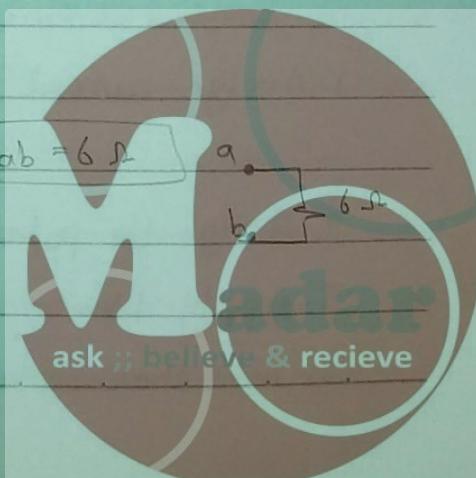


No:


Date:

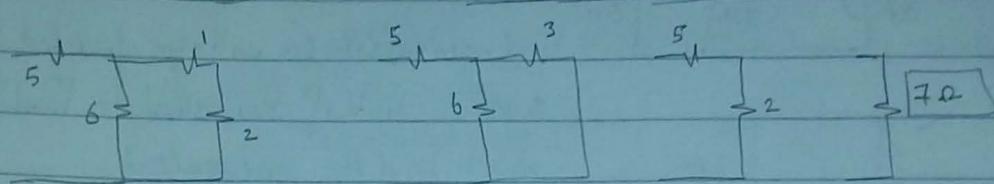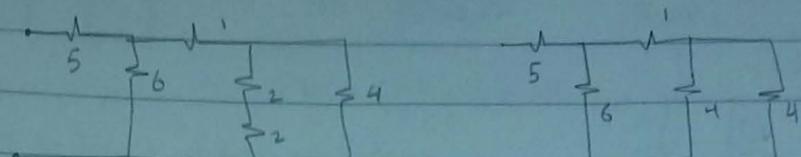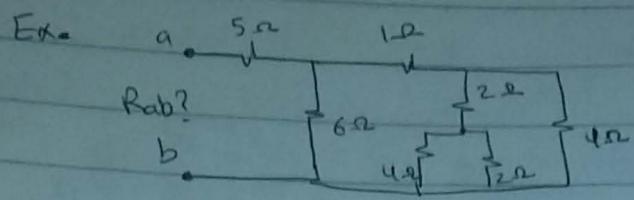

Ex.


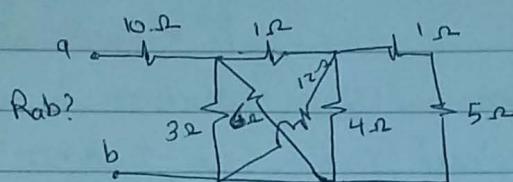


solution

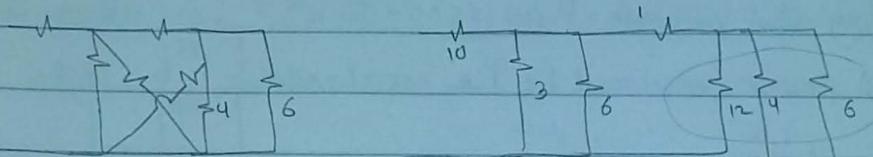


$$\frac{1}{R} = \frac{1}{12} + \frac{1}{6} + \frac{1}{4}$$

$$R = 2 \Omega$$

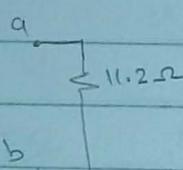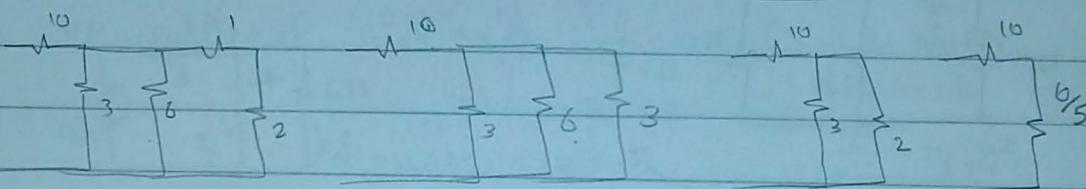

$$R_{AB} = 11.2 \Omega$$

* Voltage divider

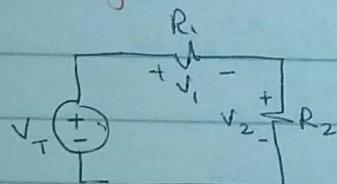


This is the standard circuit (voltage source, 2R in series)

$$V_1 = \frac{V_T R_1}{R_1 + R_2}$$

$$V_2 = \frac{V_T R_2}{R_1 + R_2} = V_T - V_1 = I R_2$$

Single mesh $I = \frac{V_T}{R_1 + R_2}$ $V_1 = I R_1 = \frac{V_T R_1}{R_1 + R_2}$

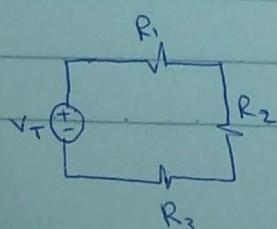
$$-V_T + I R_1 + I R_2 = 0 \quad I = \frac{V_T}{R_1 + R_2}$$



$$V_2 = \frac{V_T R_2}{R_1 + R_2 + R_3}$$


No: -----

Date: -----

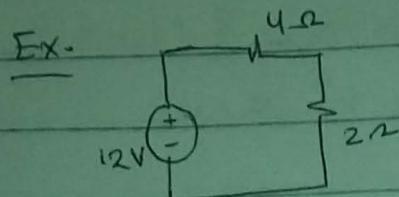


$$V_2 = \frac{12 \times 2}{4+2} = 4$$

$$V_1 = \frac{(12)(4)}{4+2} = 8$$

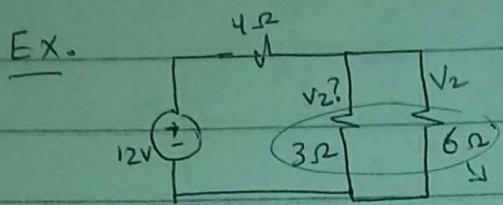

$$V_2 = \frac{(12)(2)}{2+4} = 4V$$

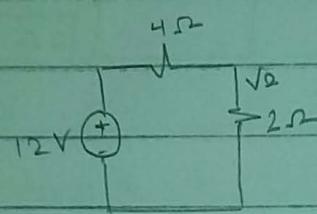

Find equivalent in voltage divider (parallel series), but if you asked to find the current don't find the equivalent.

$$I_{6\Omega} = \frac{4}{6} A \quad \text{question will ask for } I_{6\Omega}$$


simplify the circuit, then

$$I_{3\Omega} = \frac{4}{3} A$$


$$\text{go back to the complexed } I_{4\Omega} = I_{6\Omega} + I_{3\Omega} = 2$$

$$\text{after finding what you want } P_{12V} = -(12)(I_{4\Omega}) = -(12)(2) = -24W$$

Ex. Find power consumed by 1Ω resistance

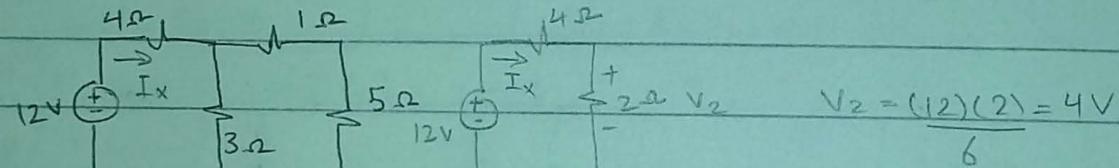

$$V_2 = \frac{(12)(2)}{6} = 4V$$

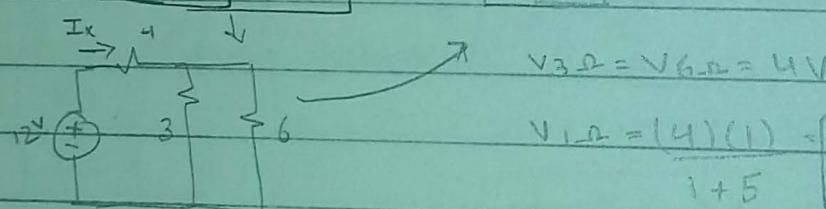

$$V_{3\Omega} = V_{6\Omega} = 4V$$


$$V_{1\Omega} = \frac{(4)(1)}{1+5} = \frac{4}{6} V$$

$$V_{5\Omega} = \frac{(4)(5)}{1+5} = \frac{20}{6} V$$

$$I_{1\Omega} = I_{5\Omega} = \frac{4}{6} A$$

$$P_{1\Omega} = + \frac{\left(\frac{4}{6}\right)^2}{1} = \frac{16}{36} W \quad \text{absorbed}$$


$$P_{5\Omega} = \frac{(2)^2}{5} = 1W$$

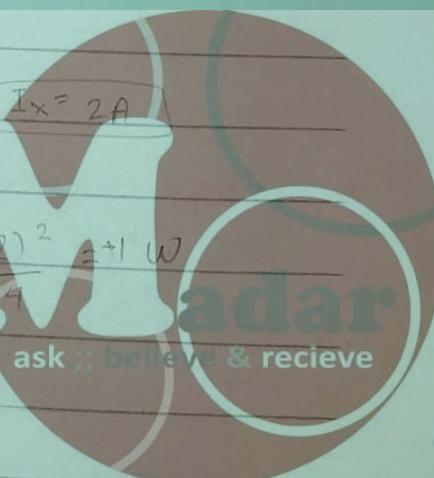

*** Current divider rule**

Standard

Form

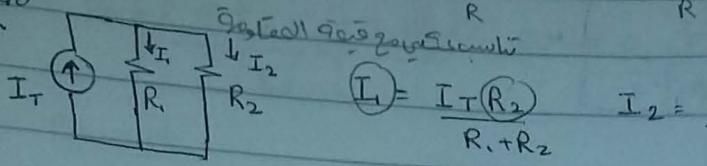

$$I = \frac{V}{R}$$


$$I \propto \frac{1}{R}$$

$$I_1 = \frac{I_T R_2}{R + R_2}$$

$$I_2 = \frac{I_T R_1}{R_1 + R_2} = I_T - I_1$$

التيار المعاكس للجهة

- Short circuit occurs as follows

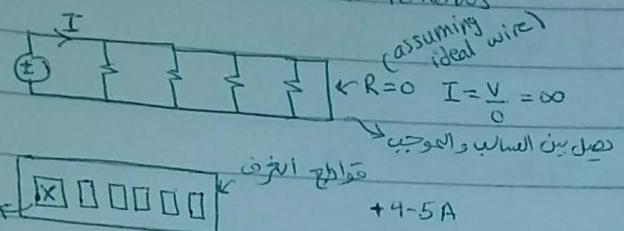


cut breakers must exist in each branch

- Difference of resistances produces because of its capacity of power

$$P = I^2 R$$


Ex:-

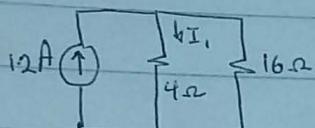

$$I_1 = \frac{(12)(16)}{20} = 9.6 \text{ A}$$


$$I_2 = \frac{(12)(4)}{20} = 2.4 \text{ A} = I_T - I_1$$

Ex:-

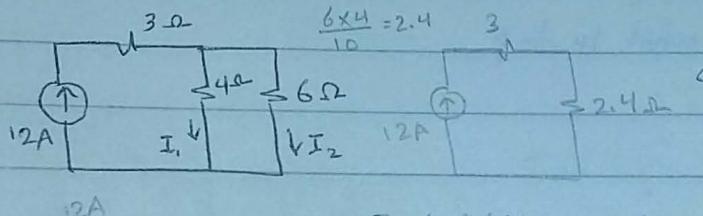

\leftarrow Don't do that
it is current division.

Ex:-

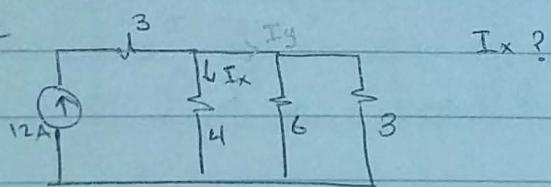

Ix ?


12A

$$I_x = \frac{(12)(2)}{4+2} = \frac{24}{6} = 4 \text{ A}$$


$$I_y = 12 - 4 = 8 \text{ A}$$

$$I_{6\Omega} = \frac{(8)(3)}{3+6} = \frac{24}{9} \text{ A}$$

$$I_{3\Omega} = \frac{(8)(6)}{3+6} = \frac{48}{6} \text{ A}$$

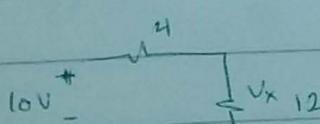you can find V_x

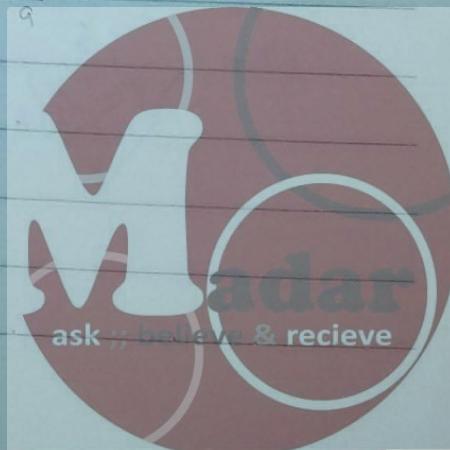
$$V_x = \frac{10 \times 12}{4 + 12} = \frac{120}{16} \text{ V}$$



No: -----

Date: -----

Ex.

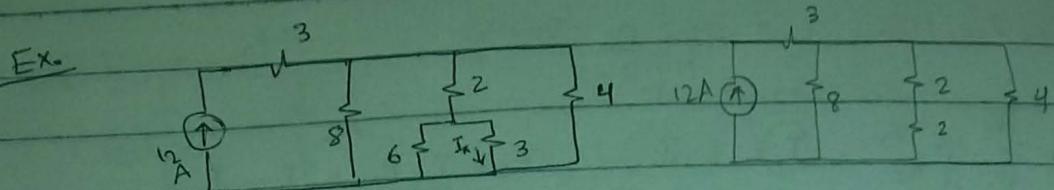


$$I_2 = \frac{(12)(\frac{32}{12})}{4 + \frac{32}{12}} = 4.8 \text{ A}$$



$$I_x = \frac{I_2(6)}{6 + 3} = 3.2 \text{ A}$$

$$I_{6\Omega} = I_2 - I_x$$

In Exam

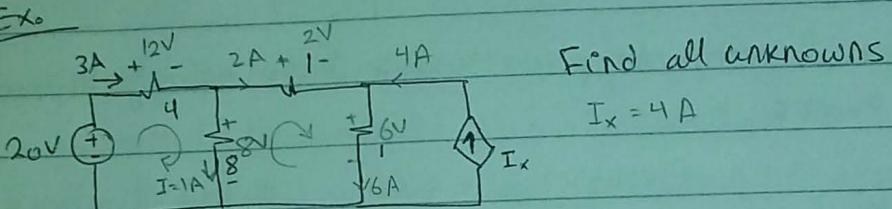

10/10/2019

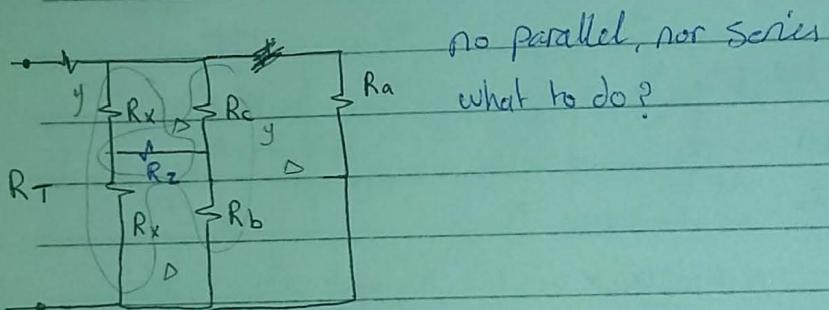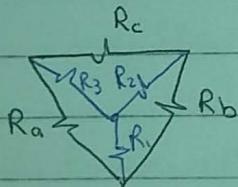
* $\Delta \leftrightarrow Y$ TransformationKeep one of them, Δ or γ $\Delta \leftrightarrow Y$ Transformation

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$

Ex.

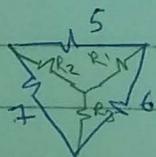

$$R_1 = \frac{5 \times 6}{5+6+7} = \frac{30}{18}$$

$$R_2 = \frac{5 \times 7}{18} = \frac{35}{18}$$

$$R_3 = \frac{6 \times 7}{18} = \frac{42}{18}$$

No:

Date:

Y to Delta Transformation

$$R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$


$$R_b = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

$$R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$


In Example

exam
Here will be better to solve in Y to Delta than in loops.

Y-D

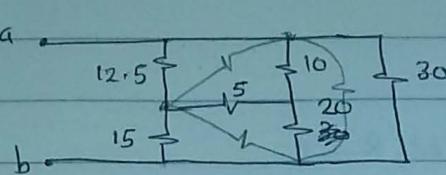Find R_{ab} ?

Y to Delta

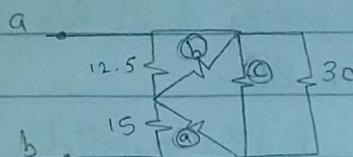


$$5 \times 10 + 20 \times 5 + 5 \times 20 = 50 + 100 + 100 = 250$$

$$(a) = 250 / 10 = 35 \Omega$$


$$(b) = 250 / 20 = 17.5 \Omega$$

$$(c) = 250 / 5 = 50 \Omega$$

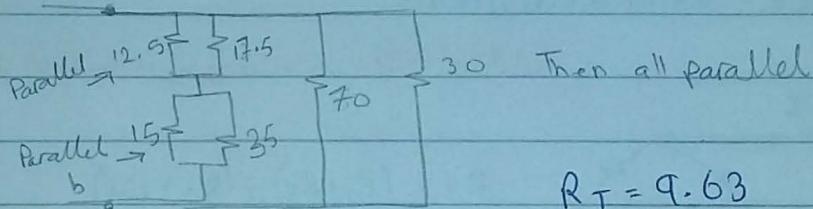

$$R_T = 9.63$$

Example

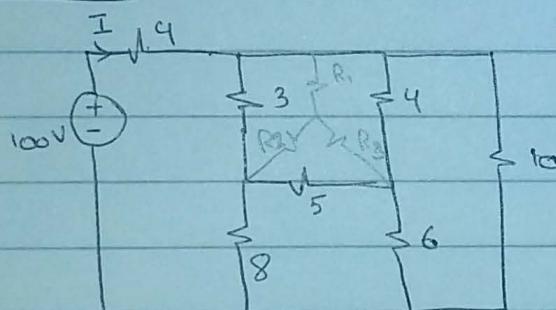Find I ? $\Delta \rightarrow Y$


Circuit plan

$$3+4+5=12$$

$$R_1 = \frac{4 \times 3}{12} = 1 \Omega$$

$$R_2 = \frac{15}{12} = 1.25 \Omega$$
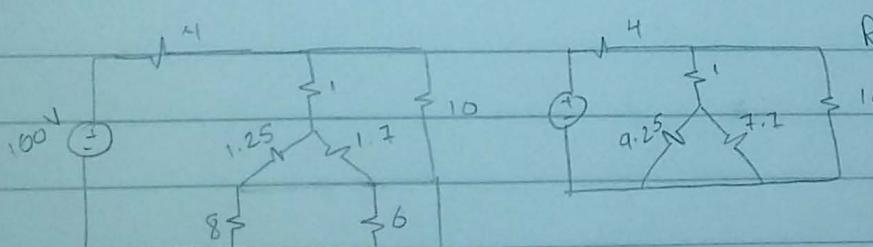
$$R_3 = \frac{20}{12} = \frac{5}{3} = 1.7 \Omega$$





$$I = \frac{V}{R_T} = \frac{100}{R_T}$$

$$R_T = 7.42 \Omega$$




No:

Date:

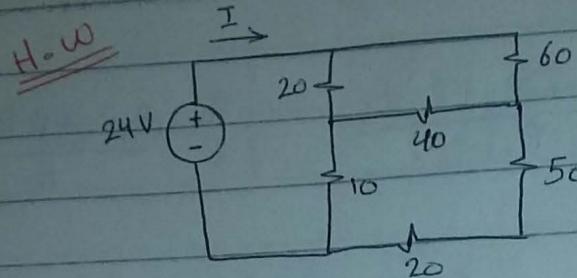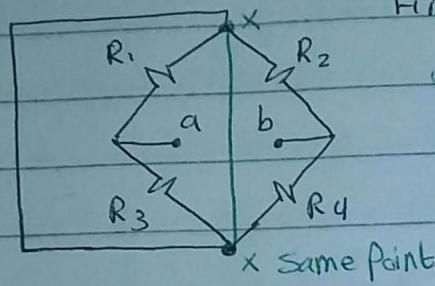
Find I & Power of the source?ExampleFind R_{ab} ?

when asking about R_{ab} , it is like you put
source there


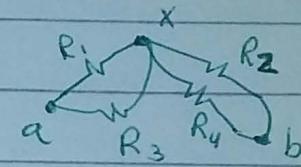
 $R_1 \& R_3$ parallel $R_2 \& R_4$ parallel

$$R_T = ((R_1 // R_3) + (R_2 // R_4))$$

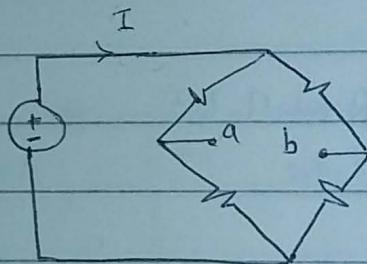جوج ٨ فیصلہ مکالمات دریافتیں اور مکالماتیں دے جائیں




$$R_T = (R_1 + R_3) // (R_2 + R_4)$$

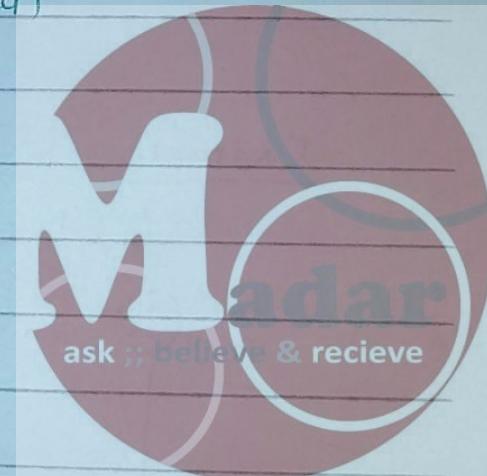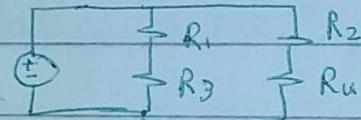


Homework Solution

13/10/2019

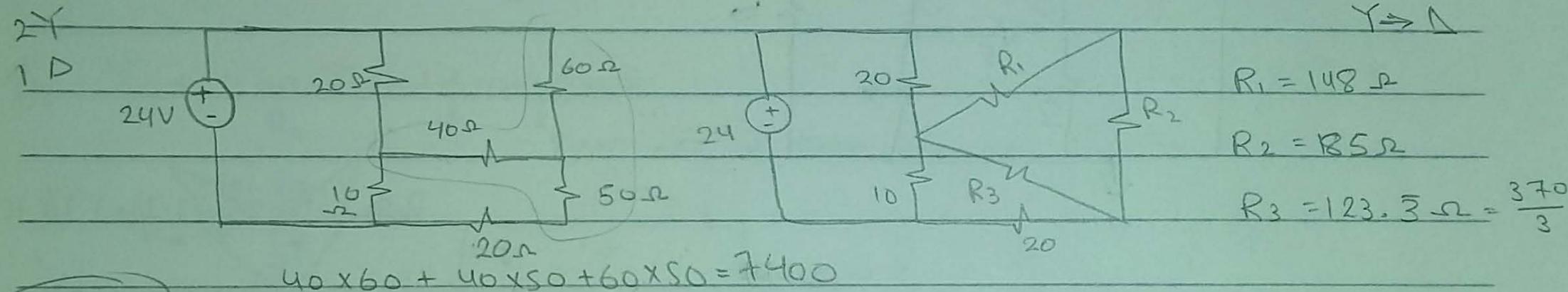

OR

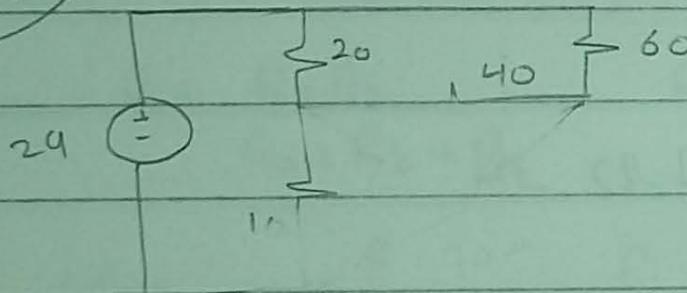


$$R_1 = 134\ \Omega \quad R_2 = 235\ \Omega \quad R_3 = 156.7\ \Omega$$

No: -----

Date: -----

* Mesh analysis for more than 1 mesh

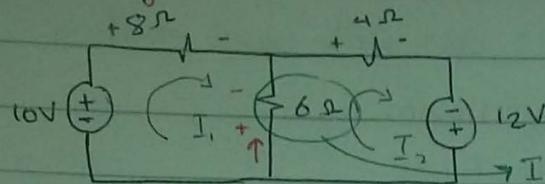

$\therefore \rightarrow$ after solving

1. Assign # mesh

2. Assign a current for each mesh (If \nexists 1 source, it is specified)

Default: clockwise

3. Assign polarity for each resistance

4. Apply KVL for each mesh

KVL Equ.

For mesh #1 :

$$-10 + 8I_1 + 6(I_1 - I_2) = 0 \quad \text{since we are in mesh 1}$$

$$4I_1 - 6I_2 = 10 \rightarrow ①$$

For mesh #2 :

$$4I_2 + 12 - 6(I_2 - I_1) = 0 \quad -6I_1 + 12I_2 = 12 \rightarrow ②$$

* Solving by Cramer's rule :-

$$\Delta = \begin{bmatrix} 14 & -6 \\ -6 & 10 \end{bmatrix}$$

$$\Delta_1 = \begin{bmatrix} 10 & -6 \\ 12 & 10 \end{bmatrix}$$

$$\Delta_2 = \begin{bmatrix} 14 & 10 \\ -6 & 12 \end{bmatrix}$$

Find the determinate

$$|\Delta| = 104$$

$$|\Delta_1| = 172$$

$$|\Delta_2| = 108$$


$$I_1 = \frac{\Delta_1}{\Delta} = 1.65$$

$$I_2 = 2.2 A$$

$$P_{10V} = -(10)(I_1)$$

$$P_{6\Omega} = +(I_2 - I_1)^2 6$$

Example

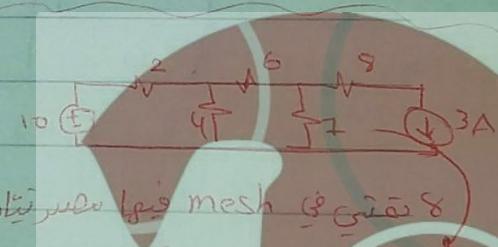

Since we are in mesh 3 \rightarrow $I_3 = 3A$

I can't write a mesh equation, I don't know

the voltage of source
ask; believe & receive

$$-10 + 2I_1 + 4(I_1 - I_2) = 0 \quad ①$$

$$6I_2 + 7(I_2 - I_3) + 4(I_2 - I_1) = 0 \quad ②$$

$$I_3 = 3$$

③




No: -----

Date: -----

15/10/2019

Special case * Super mesh

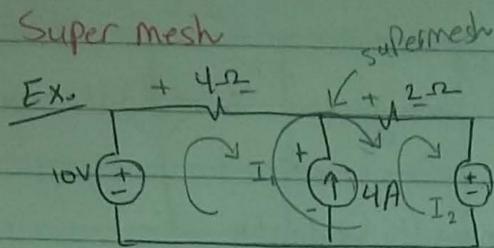

But I can't write mesh equation.

2 unknowns

2 equations

write
① Supermesh

② From current source

$$-10 + 4I_1 + 2I_2 + 6 = 0$$

$$I_2 - I_1 = 4 \rightarrow 2 \text{ like node analysis}$$

$$4I_1 + 2I_2 = 4 \rightarrow 1$$

solve equations simultaneously

$$I_1 = -\frac{2}{3} \text{ A}$$

$$I_2 = 3.3 \text{ A}$$

$$V_{U2} = (4)(-2/3) = -8/3 \text{ V}$$

$$V_{2-U} = (2)(I_2) = 6.67 \text{ A}$$

$$P_{10V} = -(10)(-2/3) = +20/3 \text{ W absorbed} \quad (\text{jigjui uzu dis})$$


I can do it here because I know $\rightarrow V_{4A} \& -10 + -8/3 + V_{4A} = 0 \quad V_{4A} = 38/3 \text{ V} = 12.6 \text{ V}$
the current and voltage in the direction

Be careful! in the loop: $P_{4A} = -(4)(12.6) = -50.6 \text{ W}$ according to our assumption

$$P_{6V} = +(6)(3.3) = +20 \text{ W absorbed}$$

Example

$$I_2 = I_3 + 5$$

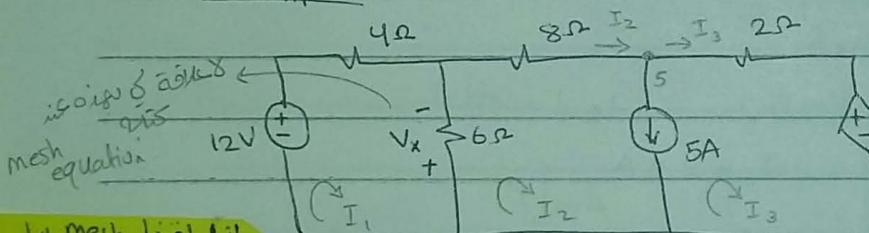

3 unknowns → 3 equations

2 supermesh 3 meshes
not necessary to go to the big mesh

② Mesh 1

$$-12 + 4I_1 + 6(I_1 - I_2) = 0$$

$$10I_1 - 6I_2 = 12 \rightarrow 2$$


③ Supermesh

$$-12 + 4I_1 + 8I_2 + 2I_3 + 3V_x = 0 \rightarrow 3 \quad V_x = 6(I_2 - I_1) \rightarrow 4$$

KVL around mesh #1
ask, believe & review

$$-12 + 4I_1 - V_x = 0 \quad V_x = 4I_1 - 12$$

Solve these 4 equations.

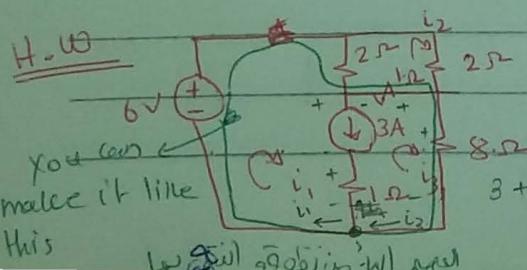

Find i1, i2, i3?

Put point from where you start

$$3 + i_3 = i_1$$


$$I_1 + I_2 = I_2 + I_3 + 1$$

$$I_1 - I_3 = 3$$

No: _____

Date: _____

20/10/2019

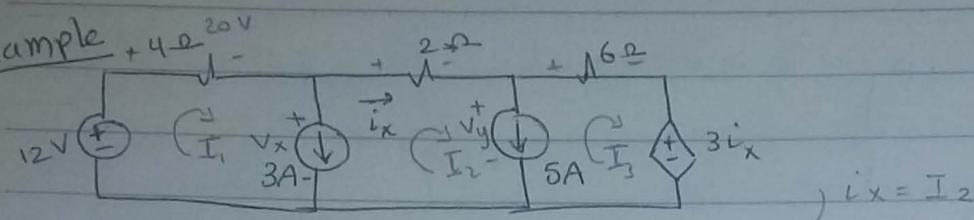Example

$$\textcircled{1} \quad -12 + 4I_1 + 2I_2 + 6I_3 + 3i_x = 0$$

$$\textcircled{2} \quad I_1 - I_2 = 3$$

$$\textcircled{3} \quad I_2 - I_3 = 5$$

$$I_1 = 5 \text{ A}$$

$$I_2 = 2 \text{ A}$$

$$I_3 = -3 \text{ A}$$

$$-12 + 20 + V_x = 0 \quad V_x = -8 \text{ V}$$

$$-V_x + 2 \times 2 + V_y = 0 \quad V_y = -12 \text{ V}$$

$$P_{3A} = + (3)(-8) = -24 \text{ W} \quad (\text{Delivered})$$

$$P_{5A} = + (5)(-12) = -60 \text{ W} \quad (\text{Del.})$$





$$P_{3i_x} = + (-3)(3 \times 2) = -18 \text{ W} \quad (\text{Delivered})$$

$$P_{12V} = - (5)(12) = -60 \text{ W} \quad (\text{Delivered})$$

$$P_{4\Omega} = + (5)^2 4 = 100 \text{ W} \quad (\text{Abs.}) \quad P_{2\Omega} = + (2)^2 (2) = 8 \text{ W} \quad (\text{abs.})$$

$$P_{6\Omega} = + (-3)^2 (6) = 54 \text{ W} \quad (\text{Abs.})$$

$$\Sigma P = 0 \quad \text{check} \quad -24 - 18 - 60 - 60 + 100 + 54 + 8 = 0 \quad \#$$

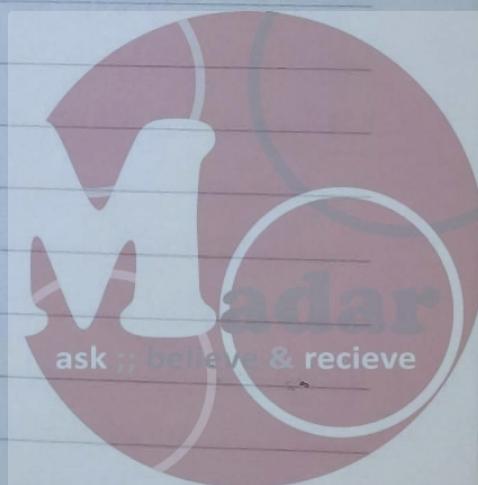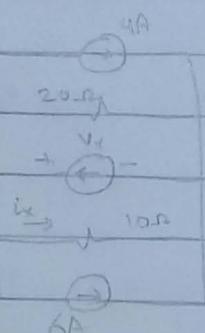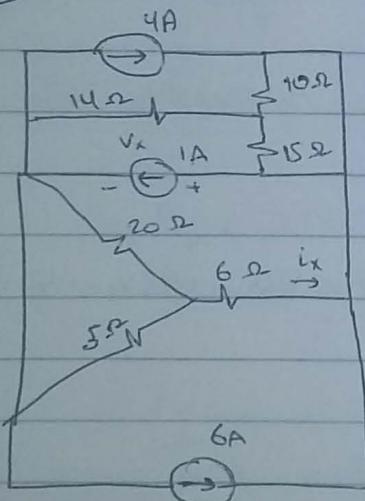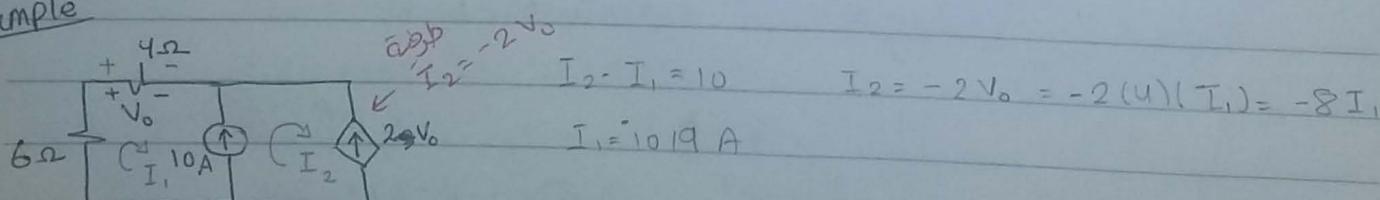ExampleExample

$$I_2 - I_1 = 10$$

$$I_1 = 10 \text{ A}$$



$$I_2 = -2V_0 = -2(4)(I_1) = -8I_1$$



giz. short cut zo sijzillie gau si *

No: -----


Date: -----

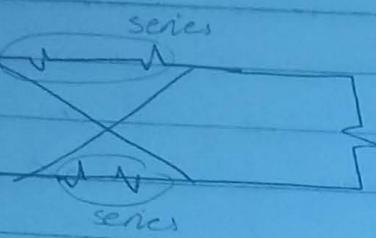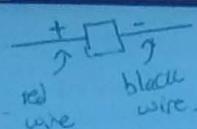

Then in parallel

22/10/2018

* Nodal Analysis

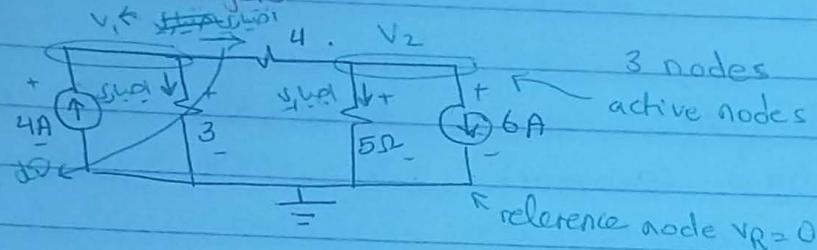

* we assume active
node voltages > 0

① Define the nodes

② Assign a voltage for each node

③ Assign a current for each resistor (current from active to reference)
resistance between two active nodes is up to you

④ Apply KCL for each ACTIVE node.

node ①

$$4 = \frac{V_1 - 0}{3} + \frac{V_1 - V_2}{4} \quad 48 = 4V_1 + 3V_1 - 3V_2 \quad 7V_1 - 3V_2 = 48 \rightarrow ①$$

node ②

$$\frac{V_1 - V_2}{4} = \frac{V_2}{5} + 6 \quad 5V_1 - 5V_2 = 4V_2 + 120 \quad 5V_1 - 9V_2 = 120 \rightarrow ②$$


$$V_1 = 1.5V \quad V_2 = -12.5V$$

$$V_{3-nr} = V_1 = V_{4A}$$

$$P_{4A} = -(4)(1.5) = -6W$$

$$I_{4-nr} = \frac{V_1 - V_2}{4} = \frac{14}{4} A$$

$$P_{6A} = +(6)(-12.5)$$

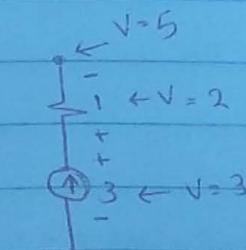


$$V_{12} = 3 \times 1 = 3$$

V



No: _____ Date: _____

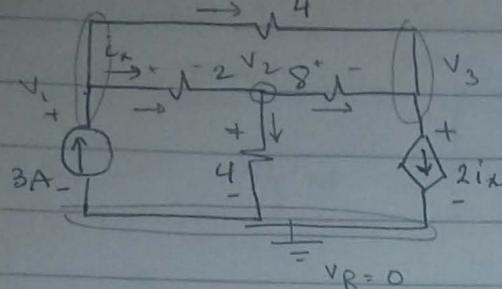

Power in each element?

4 nodes, 3 active nodes \Rightarrow 3 equations
 # branches = # terms in equation

$$\text{Node } ① \quad 3 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} / \times 4 \quad 12 = 2V_1 - 2V_2 + V_1 - V_3$$

$$12 = 3V_1 - 2V_2 - V_3 \rightarrow ①$$

$$\text{Node } ② \quad \frac{V_1 - V_2}{2} = \frac{V_2}{4} + \frac{V_2 - V_3}{8} / \times 8 \quad 4V_1 - 4V_2 = 2V_2 + V_2 - V_3$$

$$4V_1 - 7V_2 + V_3 = 0 \rightarrow ②$$

Node ③

$$\frac{V_2 - V_3}{8} + \frac{V_1 - V_3}{4} = 2ix \quad \text{But } ix = \frac{V_1 - V_2}{2}$$

$$\frac{V_2 - V_3}{8} + \frac{V_1 - V_3}{4} = V_1 - V_2 / \times 8 \quad V_2 - V_3 + 2V_1 - 2V_3 = 8V_1 - 8V_2$$

$$6V_1 - 9V_2 + 3V_3 = 0 \rightarrow ③$$

$$V_1 = 4.8V \quad V_2 = 2.4V \quad V_3 = -2.4V$$

$$P_{3A} = -3(4.8) = -14.4W$$

$$P_{\text{dep}} = +(-2.4)(4.8 - 2.4) \times 2 = -5.76W$$

$$P_{4\Omega \text{ down}} = V_2^2 / 4 = 2.4^2 / 4 = 1.44W$$

$$P_{2\Omega} = (V_1 - V_2)^2 / 2 = 2.88W$$


$$P_{8\Omega} = -(V_2 - V_3)^2 / 8 = 2.88W$$

$$P_{4\Omega \text{ up}} = +(V_1 - V_3)^2 / 4 = 12.96W$$

Check $\sum P = 0 \Rightarrow \cancel{\cancel{\cancel{X}}}$



* Supernode analysis

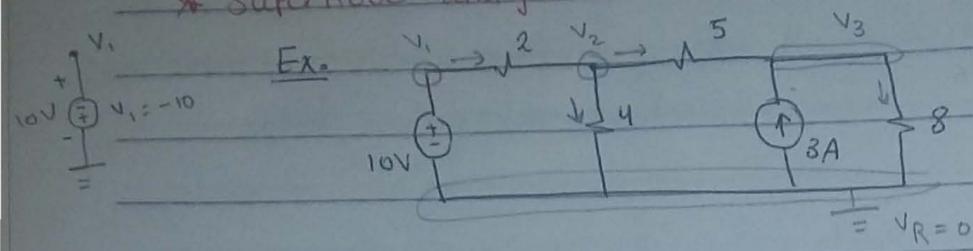

@ node ① $V_1 = 10V \rightarrow \text{Node 1}$

@ node ② $\frac{V_1 - V_2}{2} = \frac{V_2}{4} + \frac{V_2 - V_3}{5} \rightarrow \frac{V_1}{2} - \frac{1}{2}V_2 = \frac{V_2}{4} + \frac{V_2}{5} - \frac{V_3}{5} \times 20$

$$-19V_2 + 4V_3 = -100 \rightarrow \text{Eq. 2}$$


@ node ③ $\frac{V_2 - V_3}{5} + 3 = \frac{V_3}{8} \rightarrow 8V_2 - 8V_3 + 120 = V_3 \rightarrow 8V_2 - 9V_3 = -120 \rightarrow \text{Eq. 3}$

Write solution in matrix form

$$\begin{bmatrix} -19 & 4 \\ 8 & -9 \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -100 \\ -120 \end{bmatrix}$$

$$a_1x + b_1y + c_1z = D_1$$
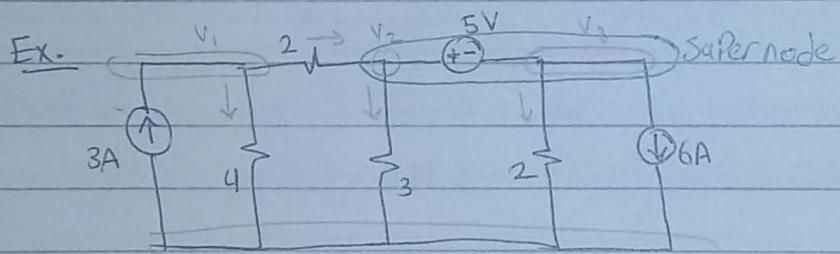
$$\begin{bmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{bmatrix} \begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} D_1 \\ D_2 \\ D_3 \end{bmatrix}$$



write available nodes

Supernode \rightarrow 1 equation

@ node ① $3 = \frac{V_1}{4} + \frac{V_1 - V_2}{2} \rightarrow 12 = 3V_1 + 2V_1 - 2V_2$

$$5V_1 - 2V_2 = 12 \rightarrow \text{Eq. 1}$$

Super node



$$\frac{V_1 - V_2}{2} = \frac{V_2 + V_3 + 6}{3} \rightarrow -3V_2 + 3V_1 = 2V_2 + 3V_3 + 36$$

$$-3V_1 + 5V_2 + 3V_3 = +36 \rightarrow \text{Eq. 2}$$

@ voltage source $V_2 - V_3 = 5$

matrix
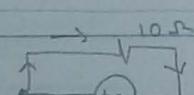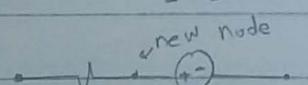
$$\begin{bmatrix} 3 & -2 & 0 \\ 3 & -5 & -3 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 36 \\ 5 \end{bmatrix}$$




Given equation $I = \frac{V_2 - V_3}{10}$

* But at end you can find current in voltage source, by applying KCL around the node.

No: -----

Date: -----

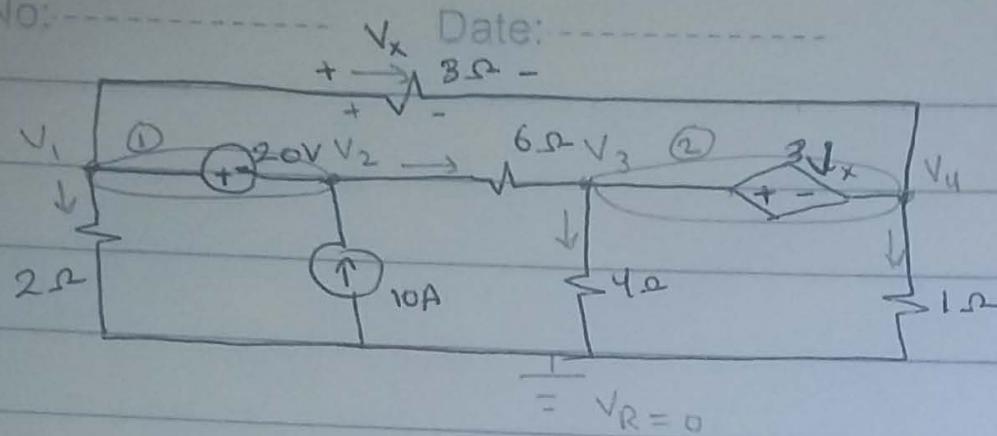

① Supernode ①

$$\frac{V_1}{2} + \frac{V_1 - V_4}{3} + \frac{V_2 - V_3}{6} = 10 \times 6$$

$$3V_1 + 2V_1 - 2V_4 + V_2 - V_3 = 60$$

$$5V_1 + V_2 - V_3 + 2V_4 = 60 \rightarrow ①$$

② Supernode ②

$$\frac{V_2 - V_3}{6} + \frac{V_1 - V_4}{3} = \frac{V_4}{1} + \frac{V_3}{4} \times 12$$

$$2V_2 - 2V_3 + 4V_1 - 4V_4 = 12V_4 + 3V_3$$

$$4V_1 + 2V_3 - 5V_2 - 16V_4 = 0 \rightarrow ②$$

③ $V_1 - V_2 = 20 \rightarrow ③$


④ $V_3 - V_4 = 3V_x$ But $V_x = V_1 - V_4$ $V_3 - V_4 = 3V_1 - 3V_4$

$$3V_1 - V_3 - 2V_4 = 0 \rightarrow ④$$

* Superposition Technique جستجوی مکانیزم

Pipe

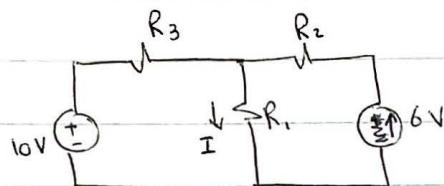effect of each one equal when added together is
the same for all of them together



I is summation of the two sources
every time one ~~depes~~ independent source

"kill all the INDEPENDENT sources except one"


kill Voltage independent source \rightarrow short cut $\textcircled{1} \oplus \textcircled{1}$

Current independent source \rightarrow open cut $\textcircled{2} \rightarrow \textcircled{2}$

NOT POWER - To calculate voltage & currents, it consists of many components

Advice: Each time you solve draw, number the sources, you have to control
the direction (polarity)


Example :-

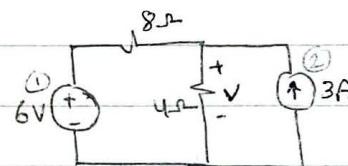

Find V using superposition (S.P)


Find the current coming from source #1
 Requires superposition.

Source 1

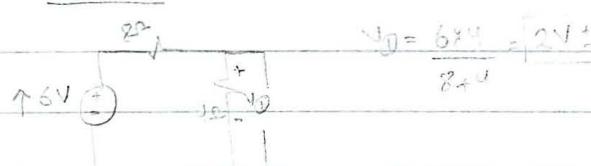

$$V_1 = \frac{6 \times 4}{8+4} = 2V$$


Source 2

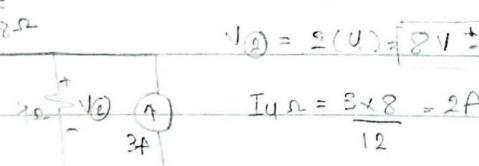

$$V_2 = 2(U) = 2 \times 8 = 16V$$

$$I_{\text{curr}} = \frac{3 \times 8}{12} = 2A$$

$$\rightarrow V = V_1 + V_2 = 2 + 8 = 10V$$

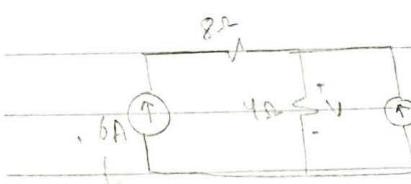


Source 1

$$V = 24V$$



No: _____


Date: _____

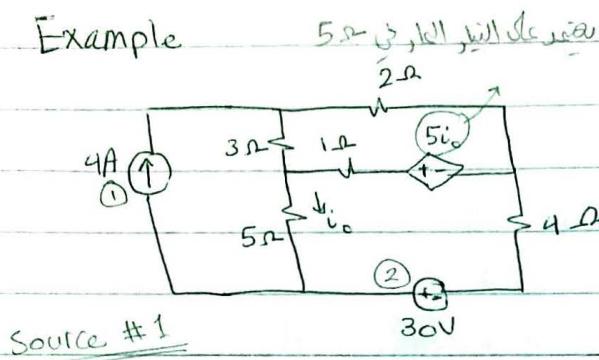ExampleFind i_o by S.P.

3 sources

2 ind. sources

twice SP.

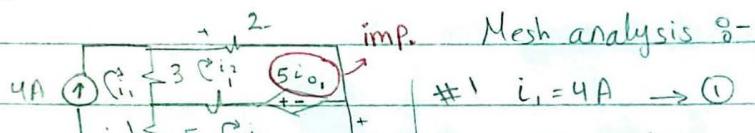
Source #1#1 $i_1 = 4A \rightarrow ①$ #2 $2i_2 - 5i_{o1} + (i_2 - i_3) + 3(i_2 - i_1) = 0$

$$i_{o1} = 4 - 0.94 = 3.05A \downarrow$$

$$i_{o1} = i_1 - i_3$$

$$2i_2 - 5i_1 + 5i_3 + i_2 - i_3 + 3i_2 - 3i_1 = 0$$

$$6i_2 + 4i_3 = 32 \rightarrow ②$$

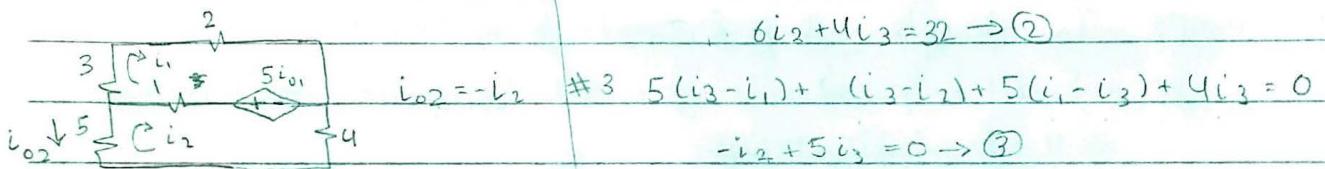

$$-i_2 + 5i_3 = 0 \rightarrow ③$$



Source #2

$$\#1 \quad 6i_1 - i_2 - 5(-i_2) = 0 \quad 6i_1 + 4i_2 = 0 \rightarrow ①$$


$$\#2 \quad 5i_2 + i_2 - i_1 + -5(-i_2) + 4i_2 = 30 \quad -i_1 + 5i_2 = 30 \rightarrow ②$$

Example

$$i_1 = -3.5 \quad i_2 = 5.3A \quad | \quad i_{o2} = -5.3A \downarrow \quad (i_o = i_{o1} + i_{o2} = -2.25A)$$

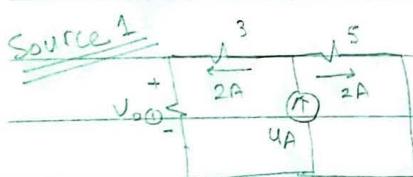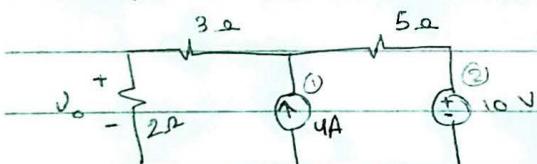


$$V_{o1} = 2 \times 2 = 4V \uparrow$$

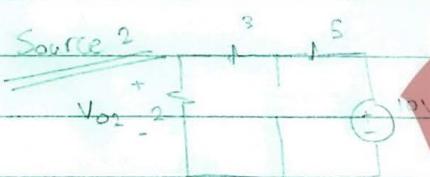

$$V_{o2} = \frac{10 \times 2}{7} = 2V \uparrow$$

$$\Rightarrow V_o = V_{o1} + V_{o2} = 4 + 2 = 6V$$

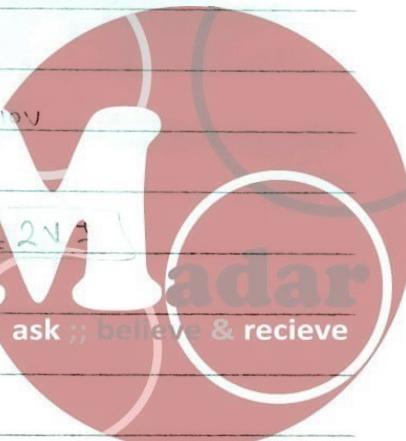**Imp** * why I can't apply Power?

- If opposite polarities, power will be added not subtracted ($\frac{V^2}{R}$ / I^2R is +ve)
- we calculate it after finding the overall current/voltage


Solve H.W. on Facebook

H.W Answer


The second source, current division rule is easier than mesh analysis

In exam The contribution of current source is _____ (Apply superposition)





→ Sources Transformation

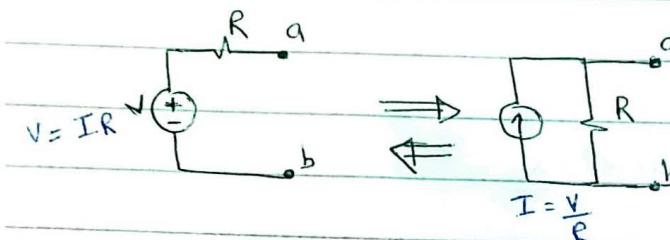

R the same value but not the same R
(not the same characteristic, like
current and voltage)

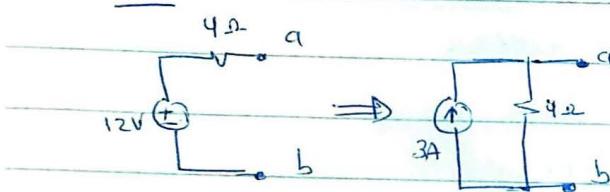Ex.

You transfer because of a reason

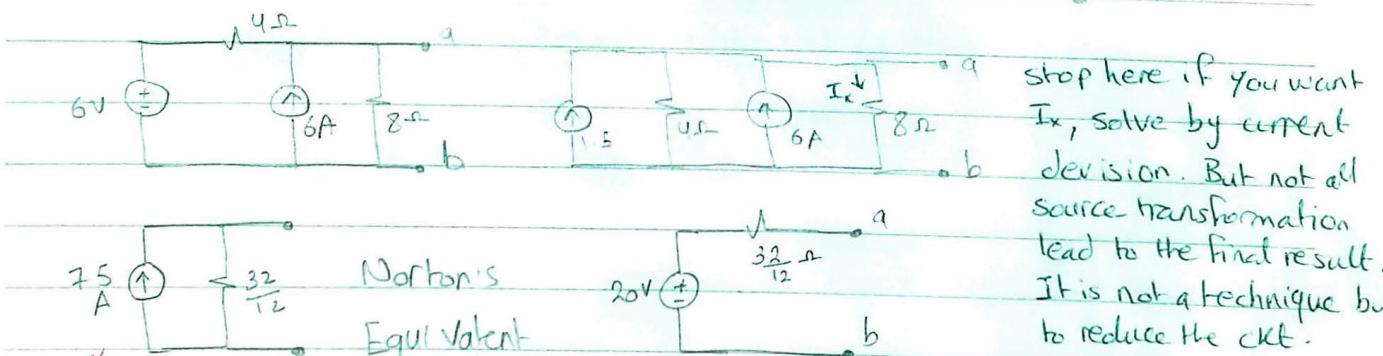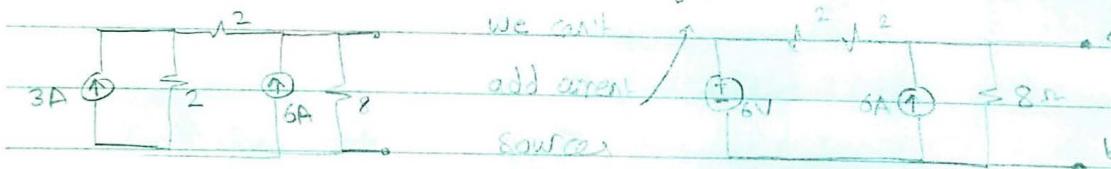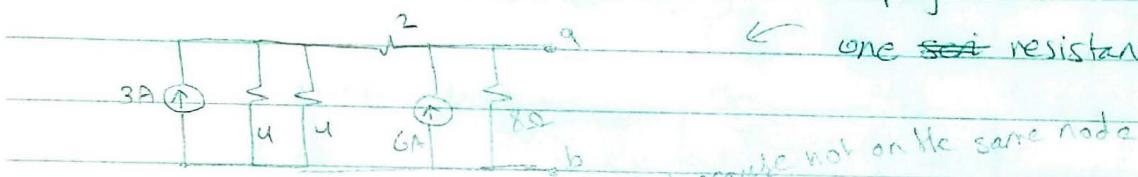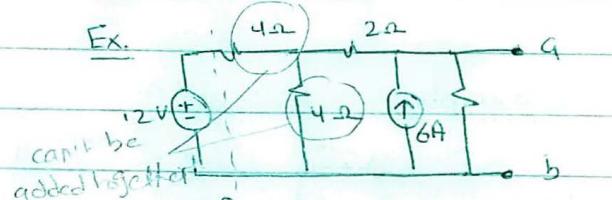

Norton's
Equivalent



any ckt can be converted to 1 current source and resistance in parallel" Norton's Equivalent

Relation
between
source
transformation

any ckt can be reduced to 1 voltage source and resistance in series "Thevenin's Equivalent"

we can apply source transformation to dependent sources

Jiggy
size
Jiggy

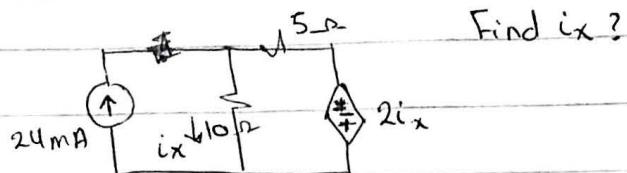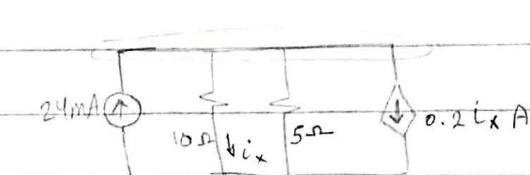ExampleFind i_x ?


Single node

$$10 \times 24 = \frac{V}{10} + \frac{V}{5} + 0.2 i_x \quad i_x = \frac{V}{10}$$


$$24 \times 10^{-3} = \frac{V}{10} + \frac{V}{5} + \frac{2}{50} V \quad \frac{24 \times 10^{-3} \times 50}{17} = V$$

$$V = 70.6 \text{ mV}$$

$$i_x = 7.06 \text{ mA}$$

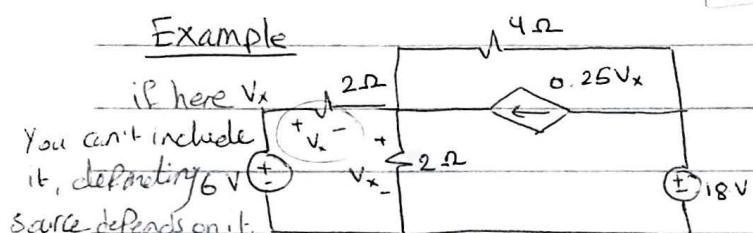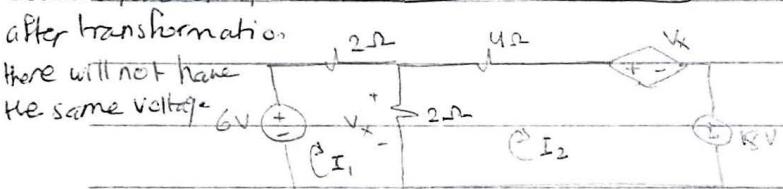ExampleFind V_x ?

By superposition, if not you can make it by nodal analysis



By mesh analysis

$$\#1 \quad -6 + 2I_1 + 2(I_{12} - I_2) = 0$$

$$\#2 \quad 2(I_2 - I_1) + 4I_2 + V_x + 18 = 0 \quad V_x = 2(I_1 - I_2)$$

$$(I_1 = -0.75 \text{ A}) \quad I_2 = -4.5 \text{ A} \quad V_x = 2(-0.75 + 4.5) = 7.5 \text{ V}$$




No: _____


Date: _____

Tuesday 12/11/2019

J5 J2 CKLS * Thevenin's Theorem


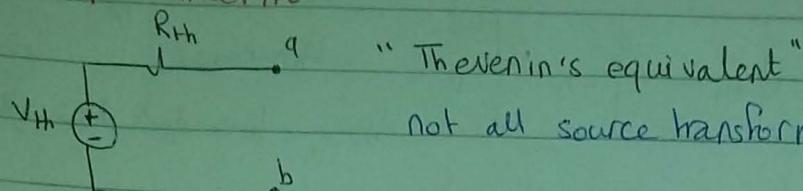


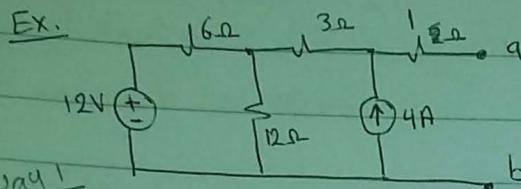not all source transformation can be solved



Find Thevenin's equivalent

way 1
Source Transformation

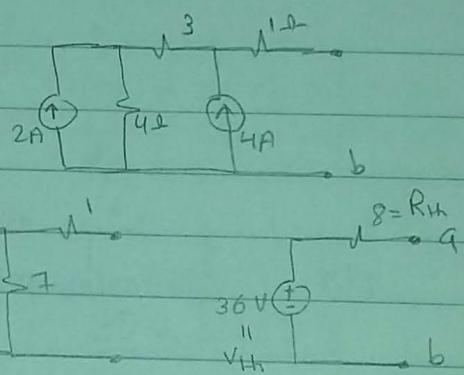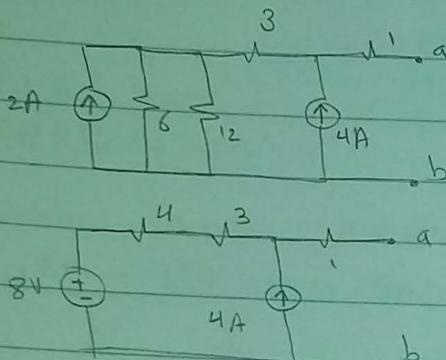


way 2

Thevenin's equivalent


• STEPS :

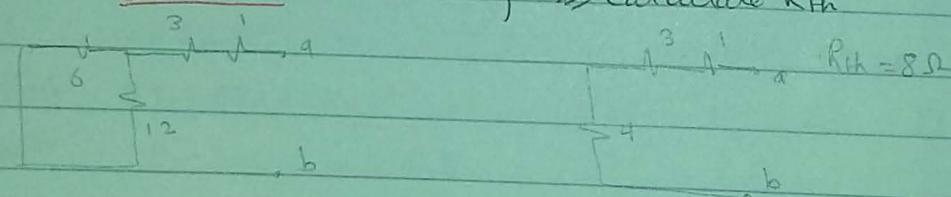1. Kill all the independent sources & Calculate R_{Th}



between a & b
open circ

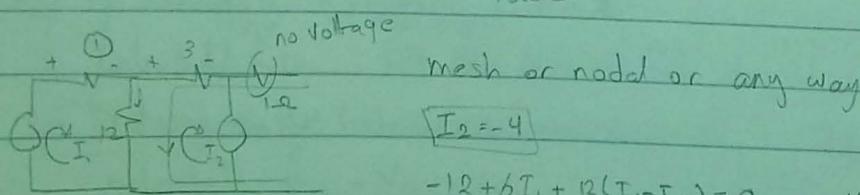2. Reconnect all the independent sources and calculate (V_{Th} , V_{OC} , V_{AB})
3 choices we have through current source → we can't
 $V_{Th} = 12V$
 $V_{AB} = 12V$



$$I_2 = -4$$

$$-12 + 6I_1 + 12(I_1 - I_2) = 0$$


$$-12 + 12 \times 4 = 18I_1 \quad I_1 = -2A$$

$V_{AB} = 1.5V$ \rightarrow 1.5V across


$$V_{AB} = V_{Th} = V_{OC} = V_{12\Omega} + V_{3\Omega} + V_{1.5\Omega}$$

$$= 0 + 12 + 1.2(I_1 - I_2)$$

$$= 0 + 12 + 1.2(-2 + 4) = 18V$$

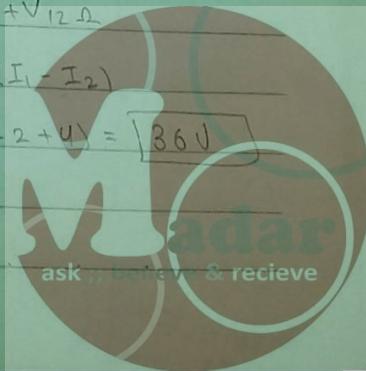


3. Draw Thevenin's equivalent

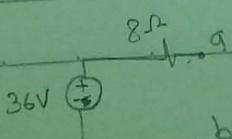

No: _____ Date: _____

Ex.

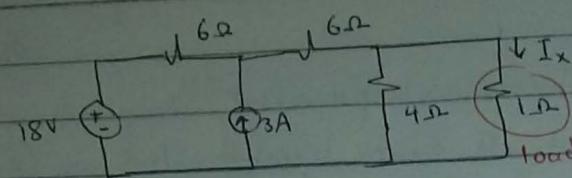


Find I_x using Thevenin's theorem

↳ $V_{oc} = 12V$, $I_{sc} = 6A$ (by direct calculation)


1. cut the load and put a, b

2. Find Thevenin's equivalent


Source transformation

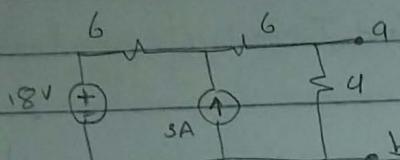

①

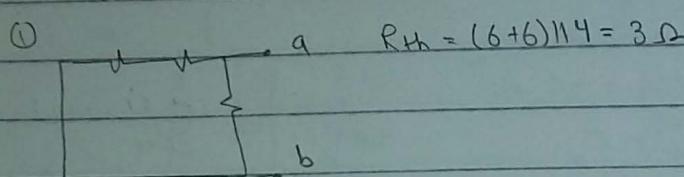

②

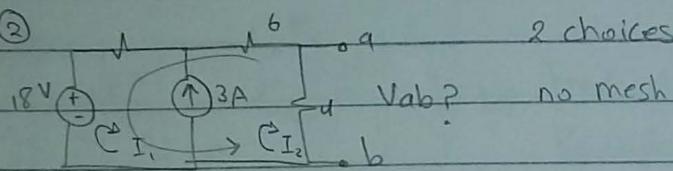

$$V_{Th} = V_{oc} = V_{ab} = V_{4\Omega} = 4I_2 = 9V$$


$$-18 + 6I_1 + 6I_2 + 4I_2 = 0 \quad 6I_1 + 10I_2 = 18 \rightarrow (1)$$

$$I_2 - I_1 = 3 \rightarrow (2)$$

$$I_1 =$$


$$I_2 = \frac{9}{4} A$$

③

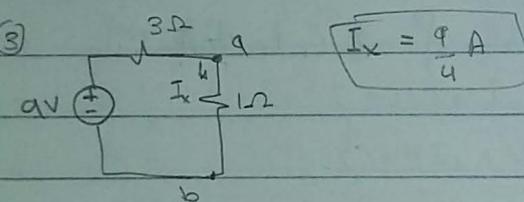


$$I_x = \frac{9}{4} A$$

Find I_x on 6Ω (the first one)

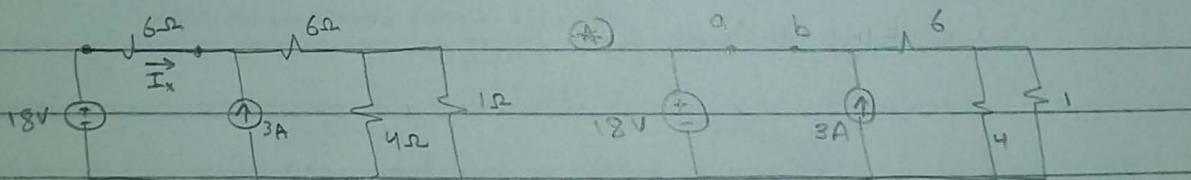


①

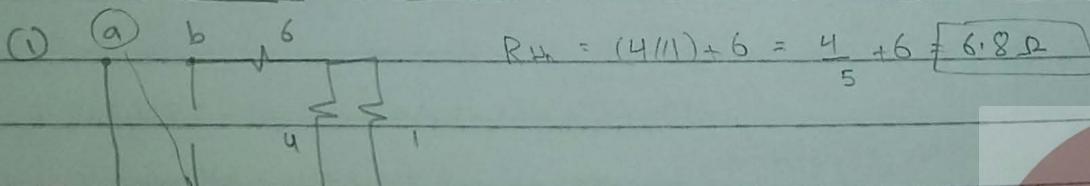

$$R_{Th} = (4//1) + 6 = \frac{4}{5} + 6 = 6.8\Omega$$

②

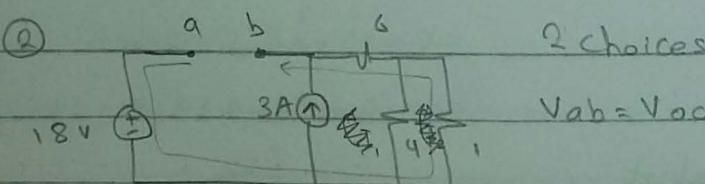


$$V_{ab} = V_{oc} = V_{th} = 18 - 24 - 18 = -2.4V$$

no current 18V

18V 6Ω 3A 4Ω 1Ω

YASSIN

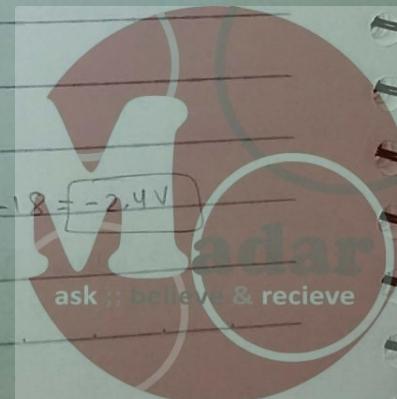


dependent source is zero

No: _____

Date: _____

Ex.

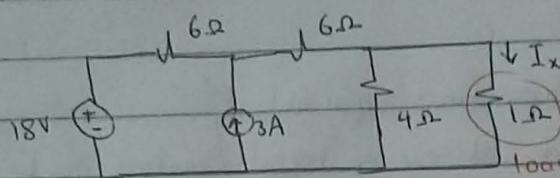


Find I_x using Thevenin's theorem

by \rightarrow loop rule draw all angles


1. cut the load and put a, b

2. Find Thevenin's equivalent

source transformation

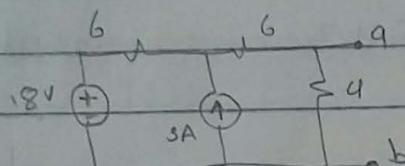


①

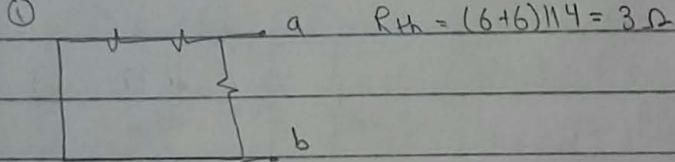

$$R_{Th} = (6+4)/4 = 3\Omega$$

②

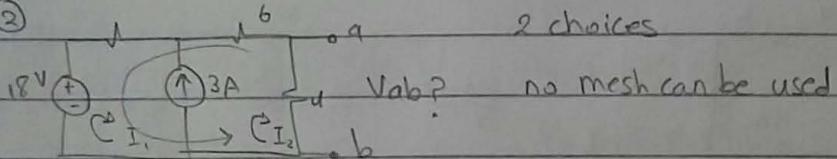

2 choices

V_{ab} ? no mesh can be used

$$V_{Th} = V_{oc} = V_{ab} = V_{4\Omega} = 4I_2 = 9V$$


$$-18 + 6I_1 + 6I_2 + 4I_2 = 0 \quad 6I_1 + 10I_2 = 18 \rightarrow ①$$

$$I_1 =$$

$$I_2 - I_1 = 3 \rightarrow ②$$


$$I_2 = \frac{9}{4}A$$

③

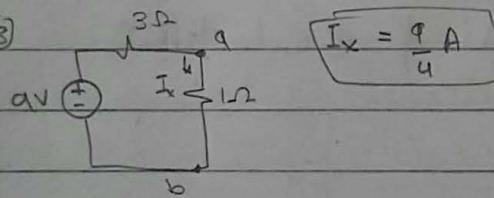


$$I_x = \frac{9}{4}A$$

Find I_x on 6Ω (the first one)

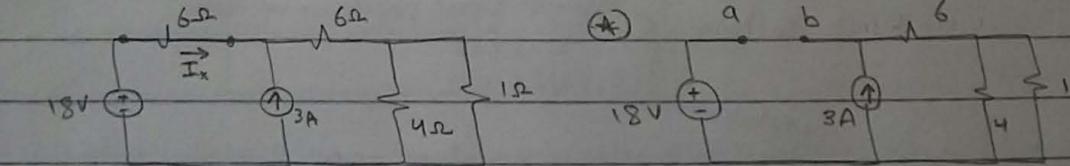


①

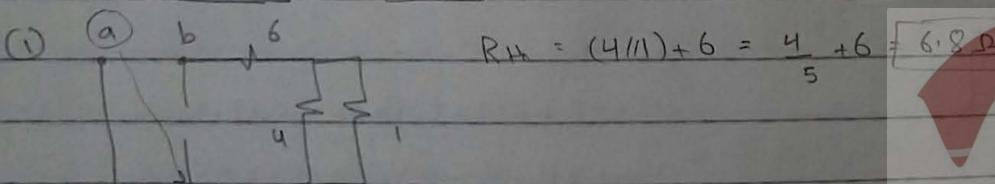



$$R_{Th} = (4/1) + 6 = 4 + 6 = 10\Omega$$

②

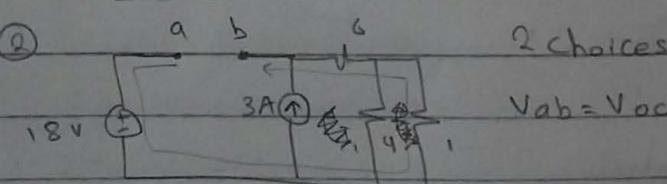

2 choices
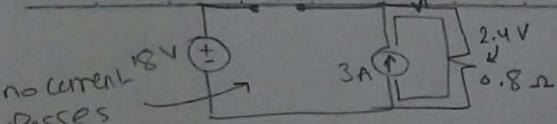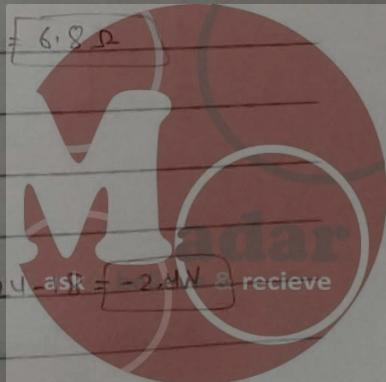
$$V_{ab} = V_{oc} = V_{Th} = 18 - 24 = -6V$$




YASSIM

dependent ~~bias~~ bias dependent

No: _____

Date: _____

Ex.

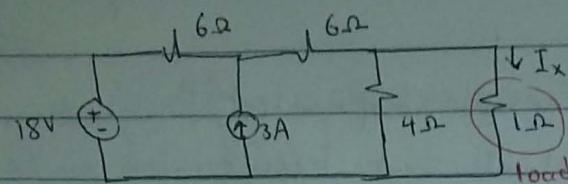


Find I_x using Thevenin's theorem

↳ $V_{oc} = 18 - 3 \times 6 = 0$ V

1. cut the load and put a, b

2. Find Thevenin's equivalent

source transformation

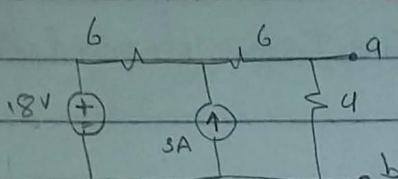


①

$$R_{Th} = (6+6) \parallel 4 = 3 \Omega$$

b

②

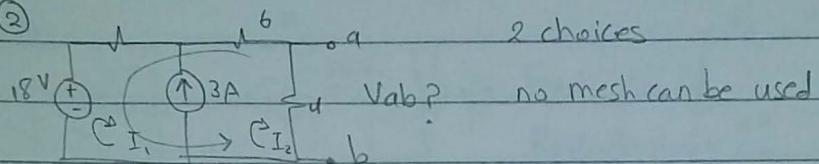

2 choices

Vab? no mesh can be used

$$V_{Th} = V_{oc} = V_{ab} = V_{4\Omega} = 4I_2 = 9V$$


$$-18 + 6I_1 + 6I_2 + 4I_2 = 0 \quad 6I_1 + 10I_2 = 18 \rightarrow (1)$$

$$I_1 =$$

$$I_2 - I_1 = 3 \rightarrow (2)$$


$$I_2 = \frac{9}{4} A$$

③

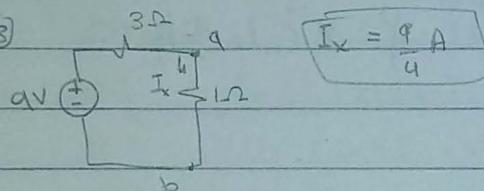

$$I_x = \frac{9}{4} A$$

Find I_x on 6Ω (the first one)

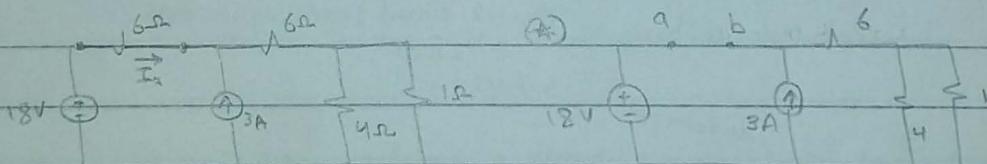


(1)

$$R_{Th} = (4 \parallel 1) + 6 = \frac{4}{5} + 6 = 6.8 \Omega$$

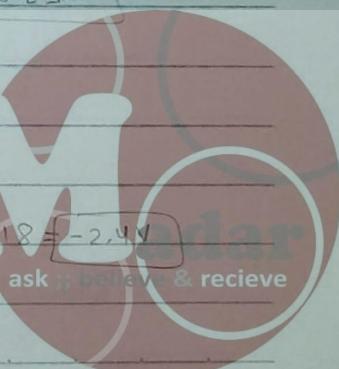(2)

2 choices

$$V_{ab} = V_{oc} = V_{Th} = 18 - 12 = 6V$$




no current passes

YASSIM®

No: _____

Date: _____


$$V = IR$$

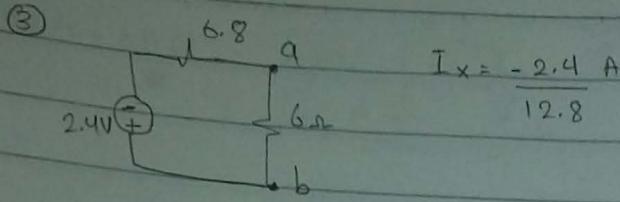


$$I_x = \frac{-2.4}{12.8} A$$

14/11/2019

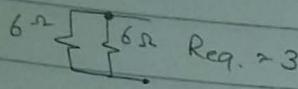- Only Physical source is the independent voltage source
- Dependent source is a resistance



$$\text{Req.} = \frac{V}{I}$$

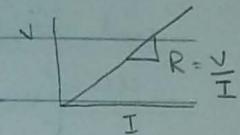


Put test source \rightarrow Find current (1A)
Find R for the black box


\rightarrow current \rightarrow find voltage (1V)

optimize your choice / amount is not
a must | linear relation between
 I & $V \rightarrow$ same req. results

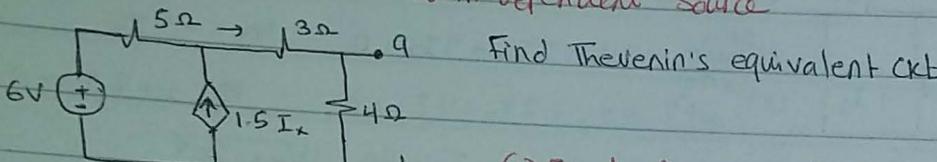* Thevenin's Theorem with dependent source



(1) Find Req. \rightarrow By test source

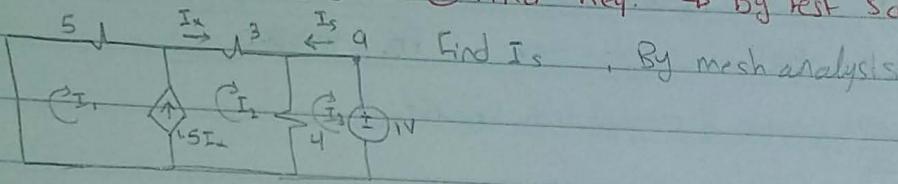

* You can
use it
also if
there is
no dependent
source.

#3

$$1 + 4I_3 - 4I_2 = 0 \quad -4I_2 + 4I_3 = -1 \rightarrow ①$$

Supermesh

$$5I_1 + 3I_2 + 4I_2 - 4I_3 = 0$$

$$5I_1 + 7I_2 - 4I_3 = 0 \rightarrow ②$$

$$I_2 - I_1 = 1.5I_x = 1.5I_2$$

$$-I_1 - 0.5I_2 = 0 \rightarrow ③$$


$$I_1 = 1A \quad I_2 = -2A \quad I_3 = -2.25A$$

$$I_S = -I_3 = 2.25A$$

$$R_T = R_{Th} = 1/2.25 = [0.4\Omega] = V_S / I_S$$

- To calculate R_{Th} , add a test source (voltage or current) then calculate R_{Th} kill the independent sources and
- Disconnect the test source and reconnect the independent source and calculate $V_{Th} = V_{oc} = V_{ab}$

② Find V_{Th}

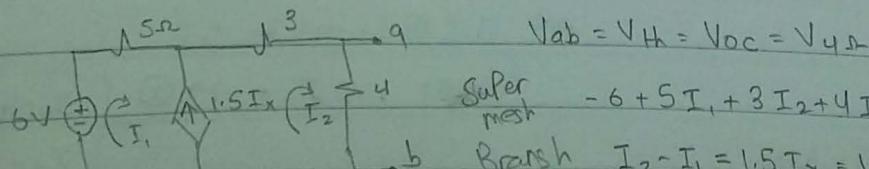

$$V_{ab} = V_{Th} = V_{oc} = V_{4\Omega}$$

By mesh analysis


$$-6 + 5I_1 + 3I_2 + 4I_2 = 0 \quad 5I_1 + 7I_2 = 6 \rightarrow ④$$

Branch



$$I_2 - I_1 = 1.5I_x = 1.5I_2$$

$$-I_1 - 0.5I_2 = 0 \rightarrow ⑤$$
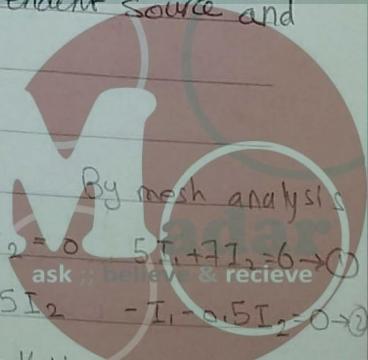
$$I_1 = -\frac{2}{3}A \quad I_2 = \frac{4}{3}A \quad V_{ab} = V_{Th} = V_{oc} = \frac{4 \times 4}{3} = \frac{16}{3}V$$




(3) Draw cut

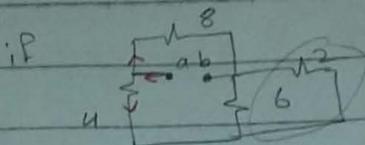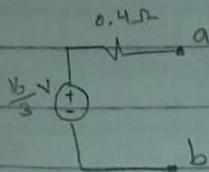

$$(2/16 + 4)/12$$

Example

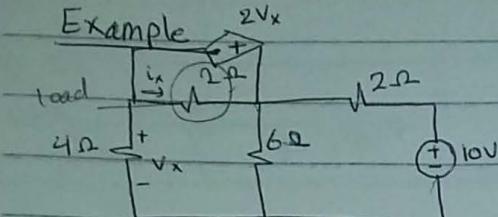Find I_x using Thevenin's theorem

(1) Take off the load


(2) Find Req.

$$\begin{aligned} \text{Nodal analysis: } & 2I_3 + 6I_2 - 6I_1 = 0 \quad -6I_1 + 8I_3 = 0 \rightarrow (1) \\ \text{Branch currents: } & I_1 - I_2 = 1 \rightarrow (2) \\ \text{Super mesh (external loop): } & -2V_x + 2I_3 + 4I_2 = 0 \quad V_x = -4I_2 \\ & 8I_2 + 2I_3 + 4I_1 = 0 \quad 12I_1 + 2I_3 = 0 \rightarrow (3) \end{aligned}$$

$$\text{Solve: } \rightarrow I_1 = 1A \quad I_2 = 0A \quad I_3 = 0A \quad \text{Assume } I_2 = 5A \quad V_x = -20V$$


$$V_{\text{dependent}} = -40V \quad V_s = 40V \quad R_{\text{th}} = 40/1 = 40\Omega$$

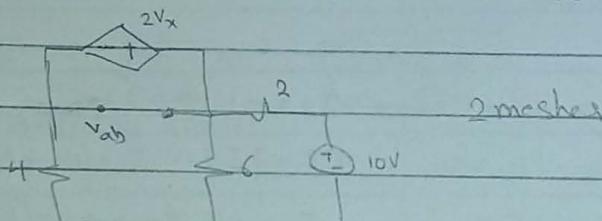(3) Disconnect test source & connect ind. source



Imp.

In exam

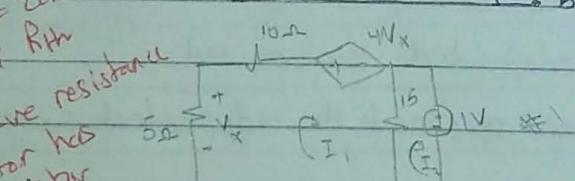Here Thevenin's
Equivalent consider
only R_{th} V_{th} comes from independent source,if no independent source $V_{\text{th}} = 0$ R_{th} comes from resistances and dependent
sources


$$5I_1 + 10I_2 + 4V_x + 15I_1 - 15I_2 = 0$$

$$V_x = -5I_1$$

$$10I_1 - 15I_2 = 0 \rightarrow (1)$$

$$1 + 15I_2 - 15I_1 = 0 \rightarrow (2)$$

$$-15I_1 + 15I_2 = -1 \rightarrow (2)$$

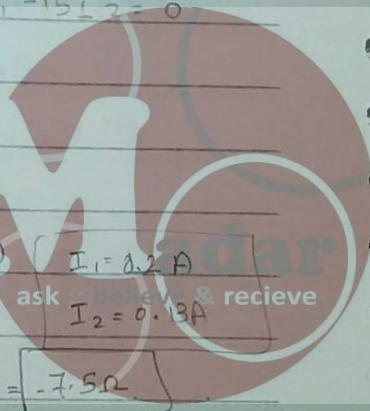

$$I_1 = 0.2A$$

$$I_2 = 0.13A$$

Because we don't have


any independent source.

$$I_s = -0.13 \quad R_{\text{th}} = \frac{1}{-0.13} = 7.69 \Omega$$

No: -----

Date: -----

→ Norton Theorem

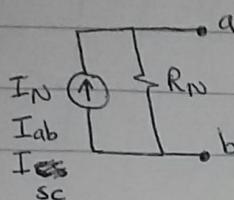


① R_N by the same way of Thevenin
cut the load

② kill the independent sources & Find R_N as seen between
a & b

③ Reconnect all the independent sources & Find $I_N \rightarrow$ making sc
between a & b

④ Draw Norton equivalent

Ex.

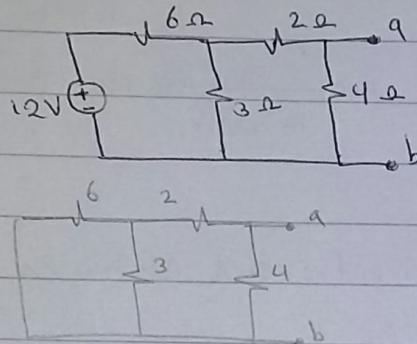


Find Norton equivalent

$$R_N = ((6/3) + 2)/4 = 2\Omega$$

In
Ex- I_N %

Short cut between
a & b

(2). ~~now calculate I_N~~

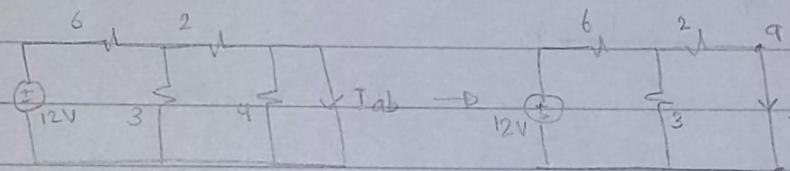


voltage division

then current division


$$2/3 = \frac{6}{5}$$

$$\sqrt{\frac{6}{3}} = \sqrt{\frac{12}{6}} = 2V$$
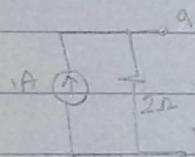
$$I_N = I_{ab} = I_{sc} = I_{2\Omega} = 2/2 = 1A$$




Example %

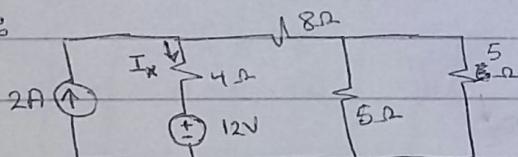Find I_x using Norton theorem.

You can
convert
Thevenin
to Norton

By source
transformation


(1) Kill load and ind. source

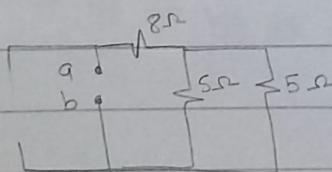

$$R_N = (5/5) + 8 = 10.5\Omega$$

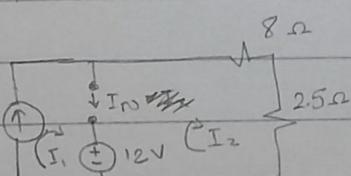(2) Reconnect


Given I_N pass
through where I_x
is NOT pass, I_x is
the same to
calculate it. (3)
Draw
Norton
equivalent



$$I_x = -12 + 10.5 I_2 = 0 \quad I_2 = 1.14 A$$


$$I_{ab} = I_N = I_{sc} = 2 - 1.14 = 0.86 A$$

$$I_x = 0.86 \times 10.5 = 14.5$$

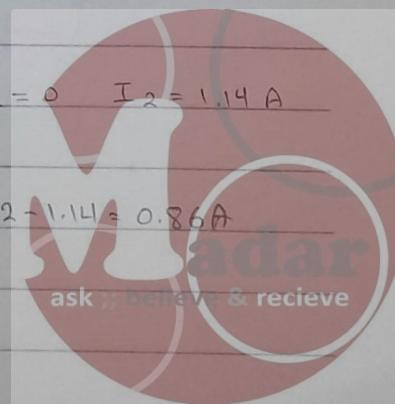


No: -----


Date: -----

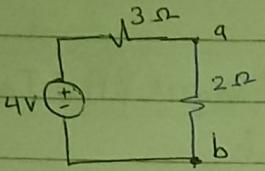Norton's
short cktif load is 8Ω , $R_N = 6.5\Omega$ Imp Max. Power \rightarrow when $R_L = R_{Th}$ 

$$P_1 = 1.28 \text{ W}$$

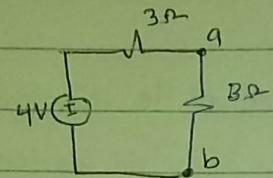


$$P_2 = 1.33 \text{ W}$$

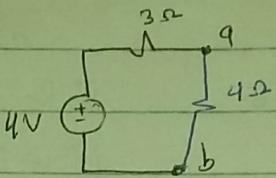


$$P_3 = 1.31 \text{ W}$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

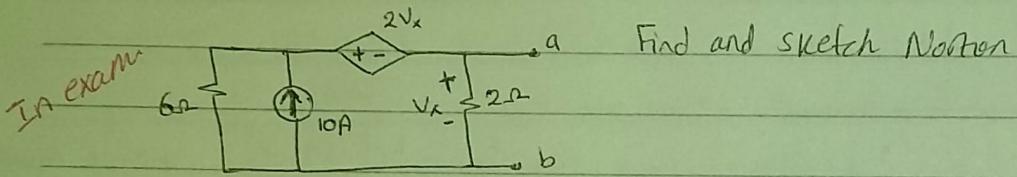Find R which will have max. power.
to transferExample

Find and sketch Norton equivalent

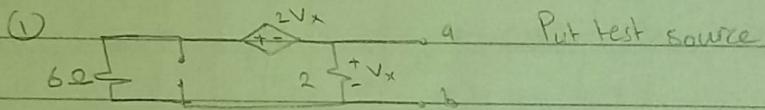


Put test source

$$\begin{aligned} V_x &= 3 \\ \frac{V_x}{3} &= \frac{1}{6} \\ &= Y_{2A} \end{aligned}$$

$$I_{Sp} = 3/6 = 0.5 \text{ A}$$


$$I_x = 0.5 \text{ A} \quad I_s = 0.5 + 0.5 = 1 \text{ A}$$

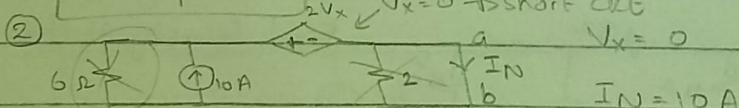Imp.

short ckt


$$V_x = 0$$


$$I_N = 10 \text{ A}$$

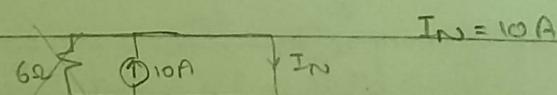no current
passes here

$$I_N = 10 \text{ A}$$

(3)

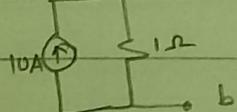

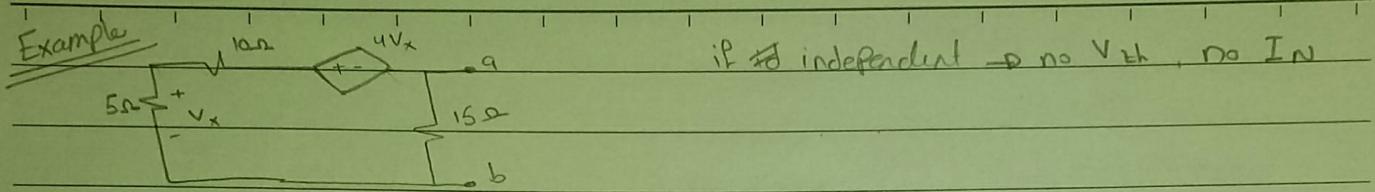

If uV_x independent \rightarrow no V_{th} , no I_N

CHAPTER #6 % Energy storage elements

* Energy storage elements \rightarrow capacitor $\frac{C}{F}$ $[C] = F$ (Faraday)

↓ inductor $\frac{L}{H}$ $[L] = H$ (Henry)

① Capacitor \rightarrow used to store charge $q = C \cdot V$


A: Area of plate

d: distance between two plates


ϵ_0 : permittivity 8.8

ϵ_R : relative permittivity

C: capacitance

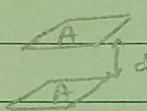

$$C = \frac{\epsilon_0 A}{d}$$

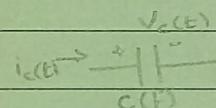

$$i_c(t) = C \frac{dV_c(t)}{dt}$$

$$V_c(t) = 4 \cos(10t)$$

$$C = \frac{3}{\pi} F$$

$$i_c(t) = 3\pi - 4 \times 10 \sin(10t) = -120 \sin(10t)$$

Calculator in rad.

$$\omega \frac{\pi \text{ rad}}{s} \times s = \text{rad}$$


$$i_c(3) = -120 \sin(30\pi)$$

Imp: if voltage dmp DC Not AC

Voltage DC \rightarrow constant \rightarrow derivative of constant = 0


$i = 0 \rightarrow$ open cut

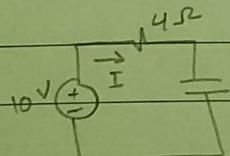In DC cut the capacitor is open cut BECAUSE $i = 0$
CAPACITOR works as OC in cut.




$$I_C = 0$$


$$V_C = 10$$

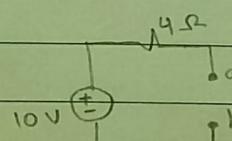

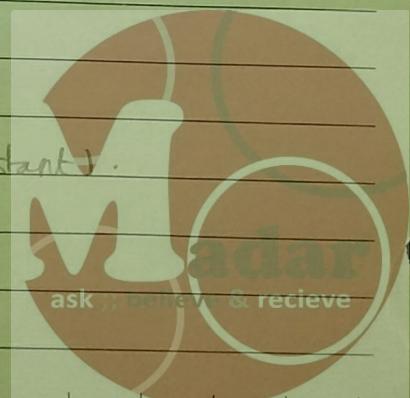* AC is a function of time, while DC NOT (it is constant).



Series

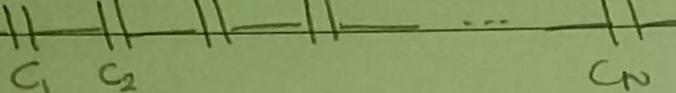


$$q_T = q_1 = q_2 = q_3 = \dots = q_N \quad \text{with same}$$

$$\frac{1}{C_{eq.}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

$$q_T = q_1 + q_2 + \dots + q_N$$


Parallel

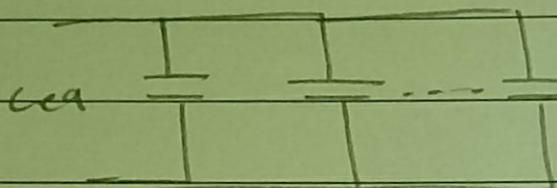

$$C_{eq.} = C_1 + C_2 + \dots + C_N$$

Example

Find $C_{eq.}$

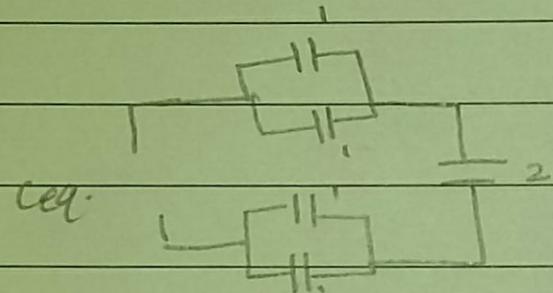

$$\frac{1}{C_{eq.}} = \frac{1}{C_2} + \frac{1}{C_4} + \frac{1}{C_6} = \frac{3}{2}$$

$$C_{eq.} = \frac{2}{3} F$$



No: _____

Date: _____

open circuit $I=0$ $V \neq 0$
 short circuit $V=0$ $I \neq 0$

21/11/2019

Big question
in exam:
what about q ?

The inductor

$$\text{Diagram: } \begin{array}{c} + \\ \text{---} \\ | \\ \text{---} \\ - \end{array} \quad [L] = H \text{ (Henry)} \quad V_L = L \frac{di}{dt} \quad I_L = \frac{1}{L} \int_0^t [V_L(t)] dt + I_0$$

If energy stored initially = 0 $\rightarrow I_0 = 0$ initial current

$$E = W = \frac{1}{2} L I^2$$

inductors acts as

IF DC power supply \rightarrow Short circuit

Existence of 1 DC in huge # of AC \rightarrow acts like this (sc)

Example

$$\textcircled{1} \quad I_L = 3 \text{ A} \quad L = 4 \text{ mH}$$



$$E = W = \frac{1}{2} \times 4 \times 3^2 \times 10^{-3} \text{ J}$$

$$V_L = 0$$

$$\textcircled{2} \quad i_L(t) = 4e^{-6t} \quad L = 3 \text{ H}$$

$$V_L(t) = L \frac{di}{dt} = 3(4)(-6)e^{-6t} = -72e^{-6t}$$
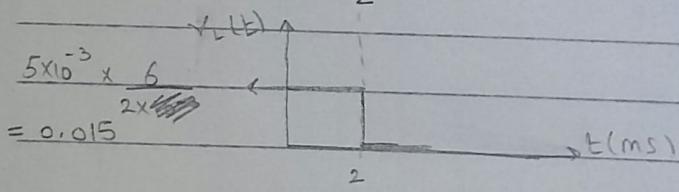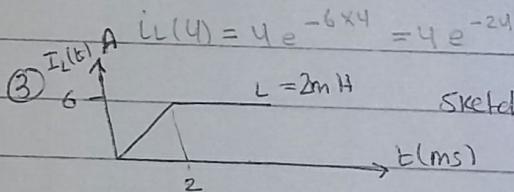
$$\textcircled{3} \quad E_1 = \frac{1}{2} \times 3 \times (i_L(4))^2 = \frac{1}{2} \times 3 \times (4e^{-24})^2 \text{ J}$$




Series

$$\text{Series: } L_1 \text{ --- } L_2 \text{ --- } L_N \quad L_{\text{eq.}} = L_1 + L_2 + \dots + L_N$$

Parallel

$$\text{Parallel: } \frac{1}{L_{\text{eq.}}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

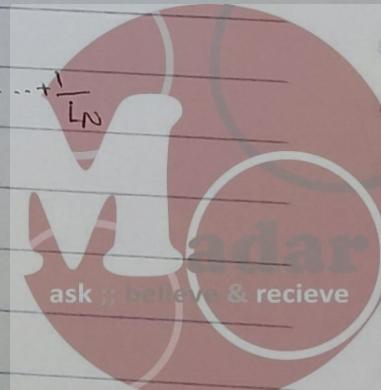
calculator has
in reactant
for sin and
cos





$$L = N \frac{d\Phi}{dt}$$

No: _____ Date: _____

Ex.

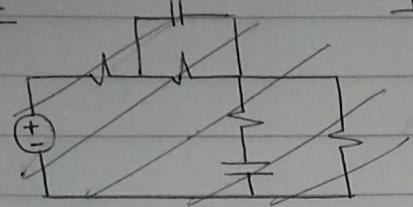

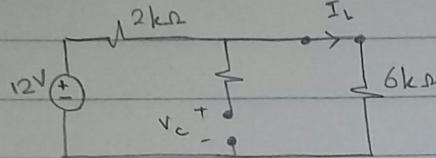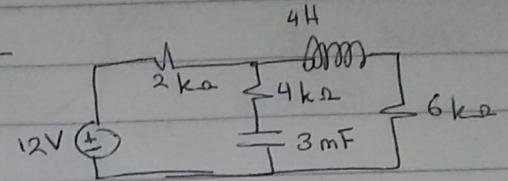Find energy stored
Find I_L , V_C ,
 E_L , E_C



$$I_L = \frac{12}{8 \times 10^3} = 1.5 \text{ mA}$$


$$V_C = V_{6k\Omega} = 1.5 \times 6 = 9 \text{ V} \quad \text{or voltage division}$$

$$E_L = \frac{1}{2} \times 4 \times 1.5 \times 10^{-3} =$$

$$E_C = \frac{1}{2} \times 3 \times 10^{-3} \times 9^2 =$$

Imp. Ex. ***

Repeat

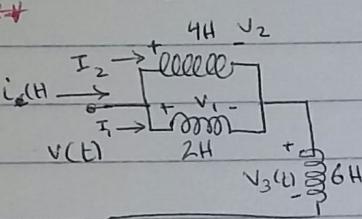

$$\text{let } i_1(t) = 0.6 e^{-4t}$$

$$i_1(0) = 1.4 \text{ A}$$

Find $i_2(0)$, $v_1(t)$, $v_2(t)$, $v_3(t)$, $i_2(t)$, $i_3(t)$,
energy stored in 4H inductor at $t=3.5$,
total $v(t)$

$$\rightarrow i(t) = i_1(t) + i_2(t) \quad i(0) = 1.4 \quad i_1(0) = 0.6$$

$$i_2(0) = 1.4 - 0.6 = 0.8 \text{ A}$$

$$\rightarrow i_2(t)$$

Because $v_1(t) = v_2(t) = \frac{di}{dt} = 2 \times -4 \times 0.6 e^{-4t} = -4.8 e^{-4t} \text{ V}$

$$i_2(t) = C_2 \frac{dv_2(t)}{dt} + i_2(0) = -4.8 e^{-4t} + 0.8$$

$$i_2(t) = \frac{1}{4} \times \int_0^t -4.8 e^{-4t} dt + 0.8 = \frac{-4.8 e^{-4t}}{16} \Big|_0^t = 0.3 e^{-4t} - 0.3 + 0.8$$

$$i_2(t) = 0.3 e^{-4t} + 0.5 \text{ A}$$

$$\rightarrow v_3(t)$$

$$i(t) = i_1(t) + i_2(t) = 0.6 e^{-4t} + 0.3 e^{-4t} + 0.5 = 0.9 e^{-4t} + 0.5$$

$$v_3(t) = L_3 \frac{di}{dt} = 6 \times 0.9 \times -4 e^{-4t} = -21.6 e^{-4t} \text{ V}$$


$$\rightarrow v(t) = v_1(t) + v_3(t) \quad \text{OR} \quad v_2(t) + v_3(t) \quad \text{OR equivalent L}$$

$$L_{\text{equ.}} = (4 \parallel 2) + 6 = 7.33 \text{ H}$$

$$V = L_{\text{equ.}} \frac{i(t)}{dt}$$

$$V(t) = 7.33 \times \frac{di(t)}{dt} = 7.33 \times 0.9 \times -4 e^{-4t} = -26.28 e^{-4t} \text{ V}$$

$$\rightarrow E_{4H} \Big|_{t=3.5} = \frac{1}{2} \times 4 \times (i_2(3.5))^2 = \frac{1}{2} \times 4 \times (0.3 \times e^{-4 \times 3} + 0.5)^2 = 0.5 \text{ J}$$

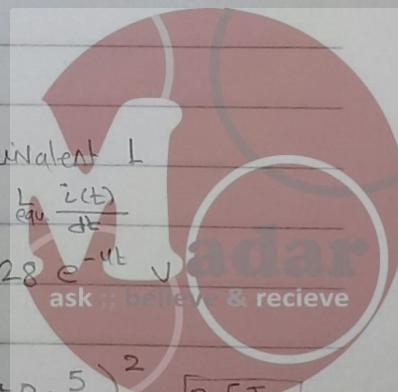


No: -----

Date: -----

sketch $i_2(t)$

$$i_2(0) = 0.8$$

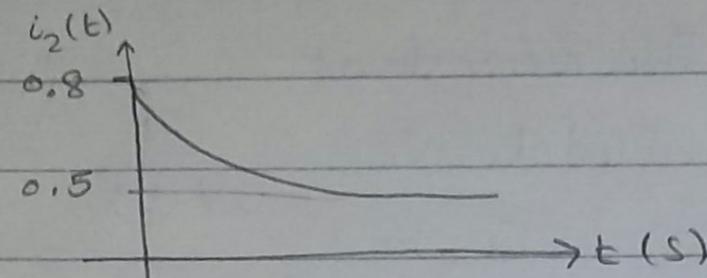


No: _____


Date: _____

Revision Formid


24/11/2019

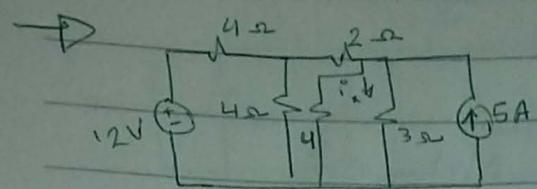i_x with Norton

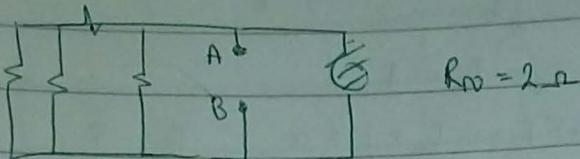resistance → cancel
Parallel current
Voltage




$$R_{\text{eq}} = 2 \Omega$$

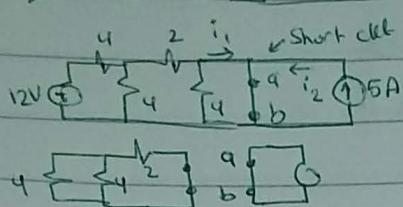

$$\rightarrow \text{like sum of two circuits } I_N = i_1 + i_2 \\ = 5 + \frac{3}{2} = 6.5$$

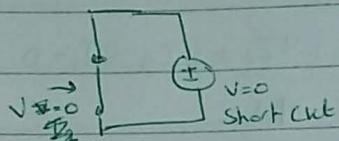
if voltage source it will be voltage source \rightarrow only i_1



$V=0$ Short cut

→ Capacitors \rightarrow Parallel \rightarrow same voltage
Series \rightarrow same current

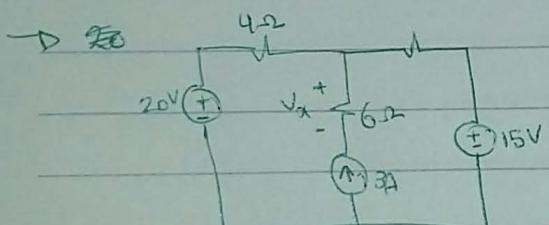→ If no independent source \rightarrow max. power = 0 / Power = 0




contribution of 20V source on V_N is equal to?

Trevorin

$$I = \frac{V}{2R_{\text{th}}}$$


$$P = I^2 \cdot R_{\text{th}} = \frac{V^2}{4R_{\text{th}}} \cdot R_{\text{th}} = \frac{V^2}{4R_{\text{th}}}$$

Norton

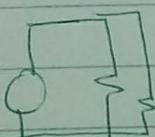

$$I_L = \frac{I_N R_N}{2R_N}$$


$$V_{\text{th}} = I_N R_N$$

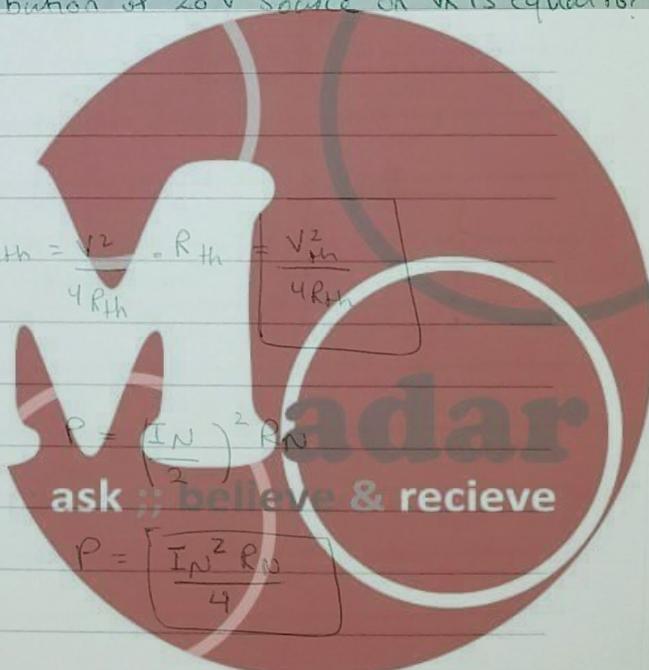


No:-----

Date:-----

Capacitor

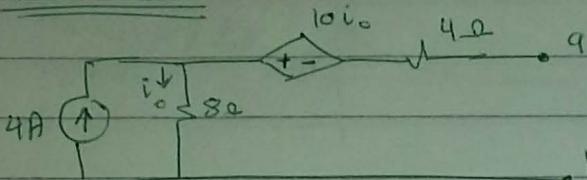Series \rightarrow same I
Parallel \rightarrow summation.Test Source

Norton's circuit

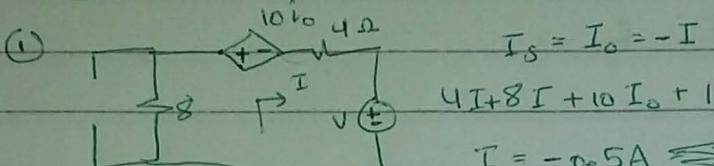single
method
voltage


$$I_S = I_o = -I$$

$$4I + 8I + 10I_o + 1 = 0$$

$$I_o = -1$$

$$I = -0.5A$$

$$R_N = \frac{1}{0.5} = 2\Omega$$

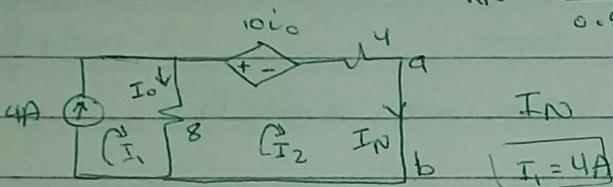



$$10I_o + 4I_2 + 8I_2 - 8I_1 = 0$$

$$I_1 = 4A$$


$$I_o = I_1 - I_2$$

$$I_2 = -4A$$


$$I_o = 4 - I_2$$

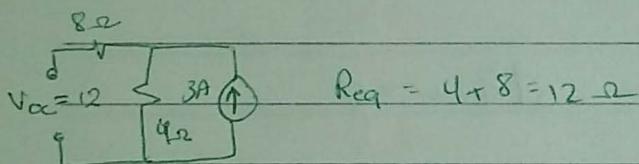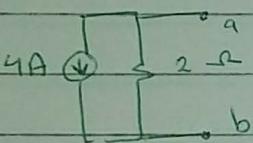

$$Req = 4 + 8 = 12 \Omega$$

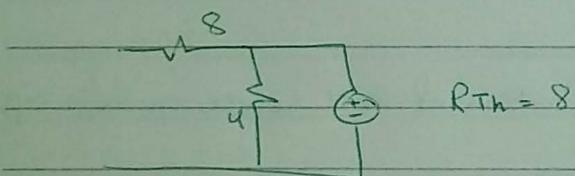

$$R_{Th} = 8$$

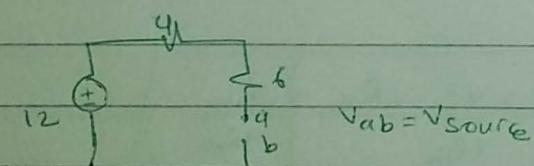

$$V_{ab} = V_{source}$$

Rth = series



adar
ask ; believe & receive

No:-----

Date:-----

Revision

26/11/2019

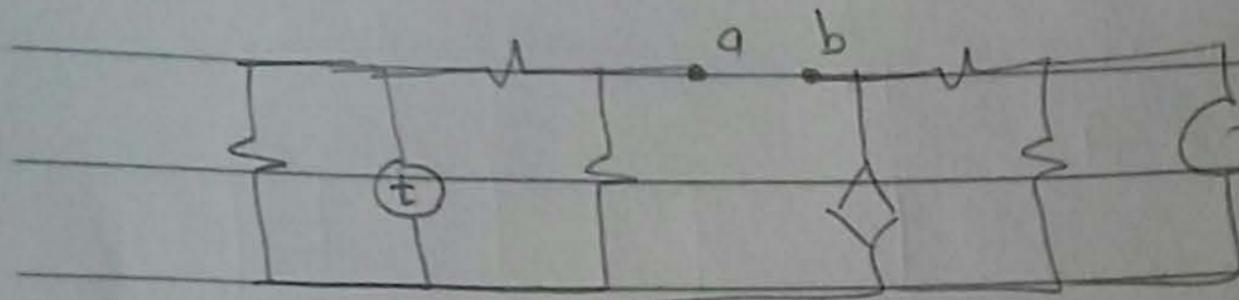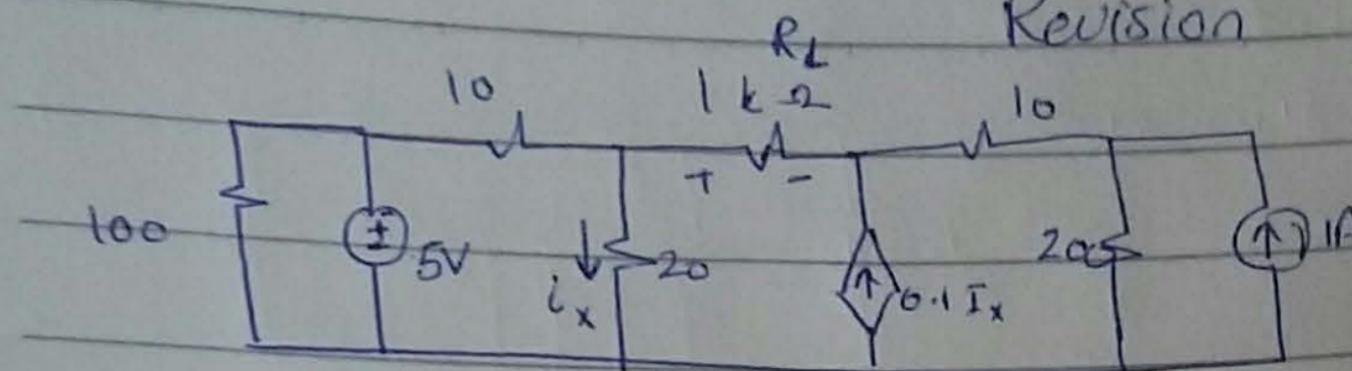

No: _____


Date: _____

$$\text{Euler Identity} \quad r \angle \theta = r \cos \theta + j r \sin \theta$$

11/12/2019

i(t) or v(t)

AC - ANALYSIS (complex, polar, work)

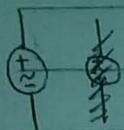

\rightarrow changing value & direction

Phasor

Sources OR

$$i(t) = I_m \cos(\omega t + \theta)$$

$$v(t) = V_m \cos(\omega t + \theta)$$

V_m % amplitude (max. value)

$$f = \frac{\omega}{2\pi} \quad \omega = 2\pi f$$

$$T = \frac{1}{f}$$

ω % angular frequency (rad/s)

θ % phase shift.

Time domain signal

We will use it as a vector

$$V = V_m \angle \theta$$

$$I = I_m \angle \theta$$

even in sin. Find parameters according to sin, don't convert to cos.

Loads

① R

② L

③ C

OR combination of them

Identity

$$\cos(x) = \frac{e^{jx} + e^{-jx}}{2}$$

$$\sin(x) = \frac{e^{jx} - e^{-jx}}{2j}$$

$$\text{Euler identity } \Rightarrow e^{\pm jx} = \cos x \pm j \sin x$$

$$\text{e.g. } i(t) = 4 \cos(2\pi t + 30^\circ) \quad (\text{Time domain})$$

$$\text{if you want to find } i(t), \text{ convert all to radian degree} \quad I_{\text{max}} = 4A \quad \omega = 2\pi \quad f = 1 \text{ Hz} \quad T = \frac{1}{f} = 1 \text{ s} \quad \theta = 30^\circ$$

$$\text{in polar coordinates } I = 4 \angle 30^\circ$$


- T % Periodic time \rightarrow time needs the signal to repeat itself

- ~~ONLY~~ polar if ~~cos~~ Time domain, if sin, convert if cos


$$\sin x = \cos(x - 90^\circ)$$

$$-\sin x = \cos(x + 90^\circ)$$

$$-\cos(x) = \cos(x \pm 180^\circ) \quad \text{up to you + or -}$$

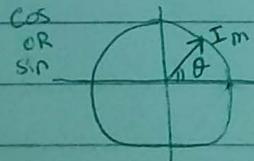vertical $I_m \sin \theta$ horizontal $I_m \cos \theta$

$$3+4j$$

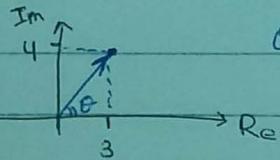

$$\theta = \tan^{-1}(4/3)$$

$$3+4j = 5 \angle 53^\circ$$


Cartesian complex

YASSIN ®

Polar phasor

$$r = \sqrt{a^2 + b^2} \quad a = r \cos \theta$$
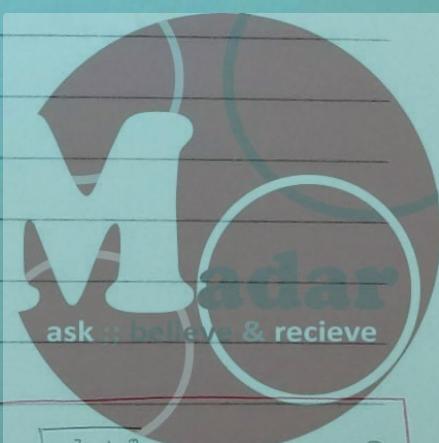
$$\theta = \tan^{-1} \frac{b}{a} \quad b = r \sin \theta$$



No:-----

Date:-----

No signals adding
in time domain

⇒ Adding & Subtracting & multiplication & Dividing

$$(3 \angle 60^\circ) \cdot (5 \angle 70^\circ) = 15 \angle 130^\circ$$

$$\frac{(3 \angle 60^\circ)}{(5 \angle 70^\circ)} = \frac{3}{5} \angle -10^\circ$$

- multiplication $r_1 \angle \theta_1 \cdot r_2 \angle \theta_2 = r_1 r_2 \angle \theta_1 + \theta_2$

- Division $\frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \frac{r_1}{r_2} \angle \theta_1 - \theta_2$

- adding & subtracting only in cartesian form

Example

$$i(t) = 6 \sin(100t - 30^\circ)$$

$$i(t) = 6 \cos(100t - 120^\circ) = 6 \angle -120^\circ A$$

Imp.
In ExamExample

$$v_1(t) = 4 \cos 10t \rightarrow 4 \angle 0^\circ$$

$$v_2(t) = 3 \sin 10t \rightarrow 3 \cos(10t - 90^\circ) \rightarrow 3 \angle -90^\circ$$

فراء الراوی، احمد

$$v_3(t) = -\cos(10t + 30^\circ) \rightarrow \cos(10t - 150^\circ) \rightarrow 1 \angle -150^\circ$$

$$\text{let } v(t) = v_1 + v_2 + v_3$$

Find $v(t)$



You can't add Time domain \rightarrow Frequency domain $\xrightarrow{\text{convert to}}$ return in time domain

$$V = 4 \angle 0^\circ + 3 \angle -90^\circ + 1 \angle -150^\circ = 4.7 \angle -48^\circ = 4.7 \cos(10t - 48^\circ) V$$

~~All Formulas~~ $\xrightarrow{\text{complex}}$ complex $\xrightarrow{\text{polar}}$ polar $\xrightarrow{\text{time domain}}$ time domain

~~Area~~
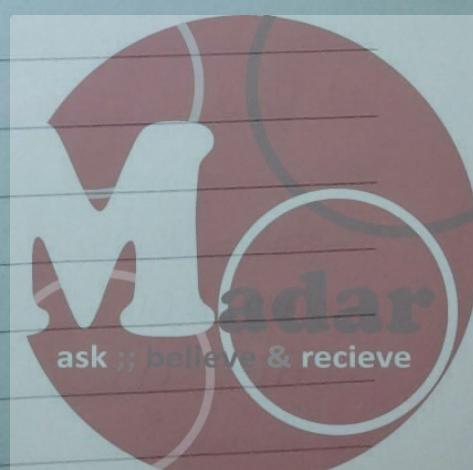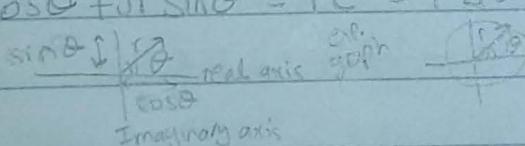
$$r \cos \theta + j r \sin \theta = r e^{j\theta} = r \angle \theta = r \cos(\omega t + \theta)$$



No: _____


Date: _____

Frequency \equiv Polar \equiv phasorTuesday
3/12/2019 \Rightarrow Lead & Lag

$$V_1(t) = 4 \cos(10t - 30^\circ)$$

$$V_2(t) = 3 \cos(10t + 60^\circ)$$

phasor

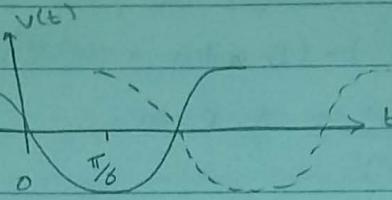
 V_2 leads V_1 by 90° ($60^\circ - (-30^\circ) = 90^\circ$)

 V_1 lags V_2 by 90°

$$V_1(t) = 4 \sin(10t + 30^\circ)$$

$$V_2(t) = 2 \sin(10t + 50^\circ)$$

 V_2 leads V_1 by 20°

Circumstances to compare the signals

 * They should have the same ω and form

f.g. T both sin or cos

You can compare current and voltage together.

$$i(t) = 4 \sin(10t - 30^\circ) \rightarrow \text{You can't compare}$$

$$v(t) = 5 \sin(100t + 60^\circ)$$

$$v = 4 \sin(10t) \rightarrow 4 \cos(10t - 90^\circ)$$

$$i = 5 \cos(10t - 100^\circ)$$

 v leads i by 10°
A-WO 9.9

Exercises on calculator

$$4 \angle 30^\circ + 6 \angle -50^\circ F 2 \angle 30^\circ = 9.19 \angle -10^\circ$$

$$\frac{(3+j4)(2-j2)}{6+j5} = 1.81 \angle -31^\circ$$

$$5 \angle 30^\circ \rightarrow 5 \cos(\omega t + 30^\circ)$$

 \Rightarrow Loads (converting to frequency domain)

Time

Freq. / Polar. / phasor

 $\rightarrow R(\omega)$ $R(\omega)$

Impedance

resistive

 $\rightarrow L(H)$ $Z_L = j\omega L(\omega)$

inductive

 $\rightarrow C(F)$ $Z_L = \frac{1}{j\omega C} (\omega)$


capacitive

capacitive


capacitive

in series

parallel

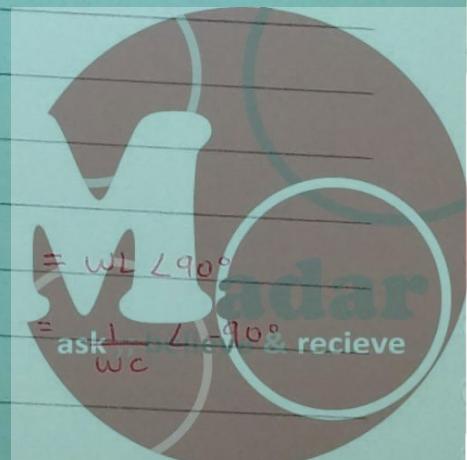
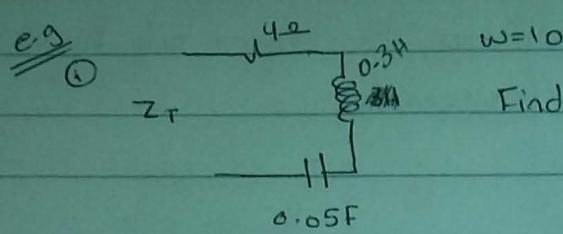
$$j^2 = 1 \quad j = \sqrt{-1} \quad \frac{1}{j} = -j$$




$4\angle 0^\circ$

$3\angle 0^\circ \Omega$

$\frac{1}{j(40)(0.05)} = -j2\angle 90^\circ$
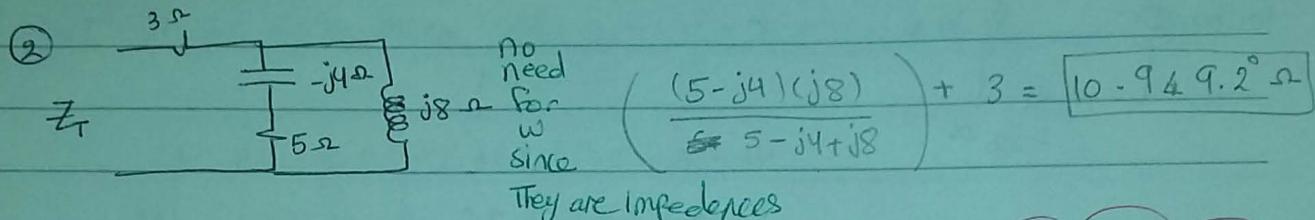
$$Z_T = 4 + j3 + -j2 = [4 + j\angle 0] = 4.12 \angle 14^\circ \Omega$$




⇒ Admittance

Y : admittance $\sim V$


$$Y = \frac{1}{Z} \sim V \text{ (Siemen's, } \Omega \text{ mho)}$$

$V = IZ$ in AC
not IR

Example

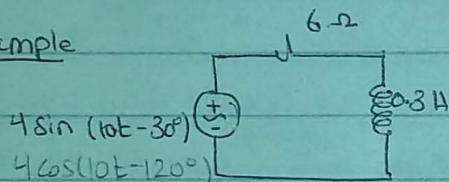

Find I, V_L ?

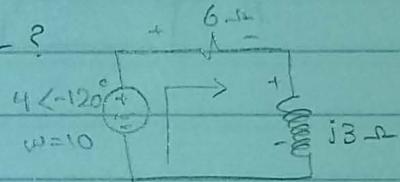

$$Z_L = j\omega L = j(10)(0.3) = 3j\angle 90^\circ$$

$$-4L-120^\circ + 6I + 3jI = 0$$

$$I = \frac{4\angle -120^\circ}{6 + j3} = [0.6 \angle -146.5^\circ 5A] = I_L$$


$$V_L = 0.6 \angle -146.5^\circ \times 3j = -1.8 \angle -56^\circ V$$

$$V_R = 6 \times 0.6 \angle -146.5^\circ = 3.6 \angle -146.5^\circ V$$


I_L angle $\angle -146.5^\circ \Rightarrow V$ lead by 90°
 $\angle -856.5^\circ$

Jeff
Imp

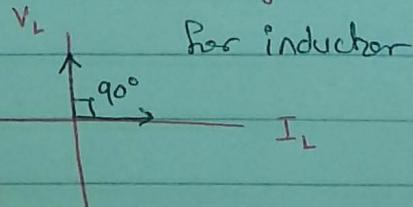- In the inductor, the voltage leads the current by 90° .
- In the resistor, the voltage and current are in-phase.



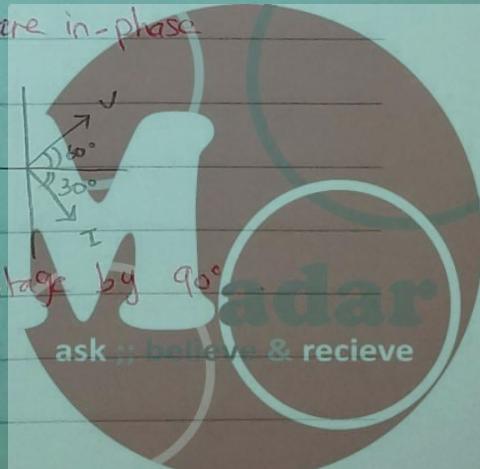- In the capacitor, the current leads the voltage by 90° .



105 = -225

$P = -4 \text{ W}$

or

$P = 4 \text{ W delivered}$

No: _____

Date: _____

$$(3 \angle -180)^\circ =$$

\downarrow
 3°

\downarrow
 180°

$\frac{180}{2}$

lead or lag
the same difference


5/12/2019

$-3 \rightarrow 3 \angle +180^\circ$

$3j \rightarrow 3 \angle 90^\circ$

$-3j \rightarrow 3 \angle -90^\circ$

we must use Cramer's rule to find
the unknowns.

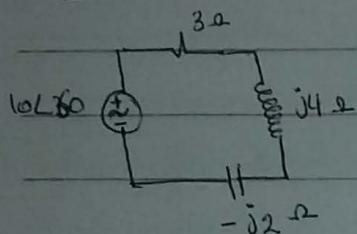
Ex.Find i , V_L , V_R , V_C

$I = V = \frac{10 \angle 60}{\Sigma Z} = \frac{10 \angle 60}{3.6 \angle 33.7} = I_R = I_L = I_C$

$V_R = 3 \times 2.77 \angle 26.3^\circ = 8.3 \angle 26^\circ \checkmark$

 $V_L = 11.08 \angle 116.3^\circ \checkmark$ is leading by 90°

$V_C = 5.54 \angle -68.7^\circ \checkmark$ is lagging by 90° in phase shift

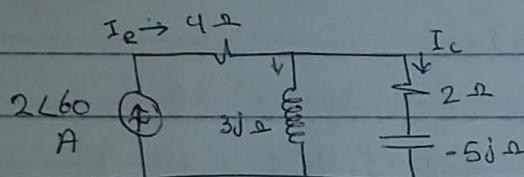Ex.Find I_C ?

$I_C = \frac{2 \angle 60 \times 3j}{2 - 5j + 3j} = 2.12 \angle -165^\circ \checkmark$



$V_C = I_C \times -5j = 10.61 \angle -255^\circ \checkmark$

~~voltage leading current by 90°~~ lead and lag.

$V_L = 3j I_L = 11.4 \angle 126^\circ \checkmark$

~~voltage lead current by 90° .~~


$I_L = I_T - I_C = 3.8 \angle 36.8^\circ \text{ A}$

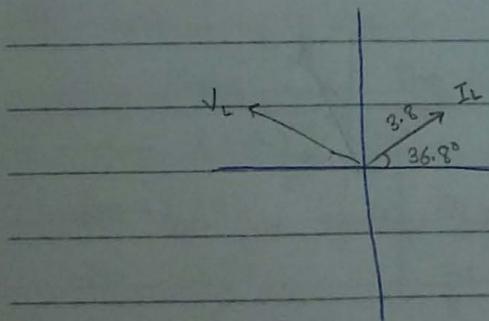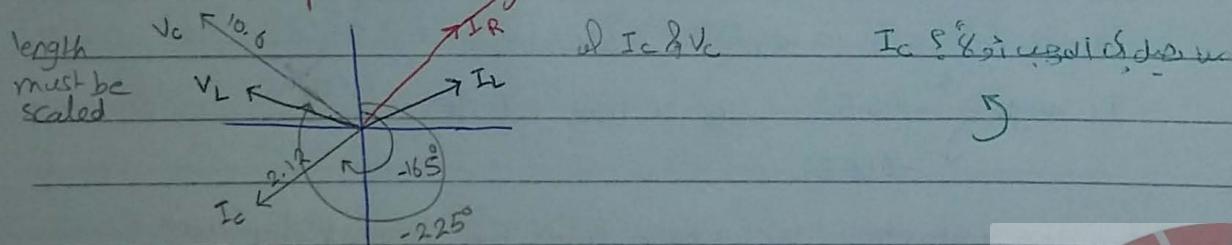 \Rightarrow Draw the phasor diagram

no conformating between I_L and I_C

No: _____ Date: _____

In exam

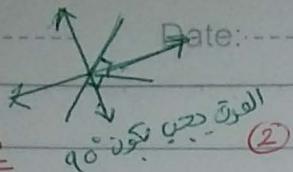

$$I_y = 3 \angle 90^\circ \quad \textcircled{1} \text{ quarter}$$

I_R (since in phase)

$$I_R = 1.5 \angle 0^\circ \quad V_R, V_L, V_C = V_s$$

$$V = 4V \angle 0^\circ$$


Draw ckt

Find value of

\textcircled{3}

each component

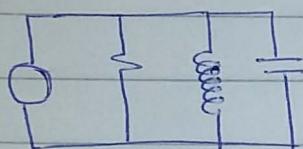Since 3 components, R, L, C are in parallel (since same Voltage)




$$I_y = I_C$$



$$I_x = I_L$$

$$R = V_R / I_R$$

$$Z_C = V_C / I_C$$

$$Z_L = V_L / I_L$$

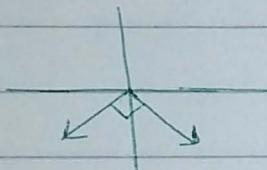

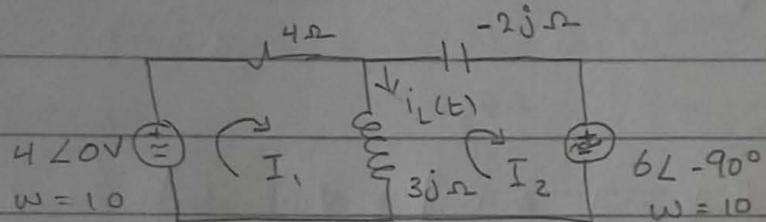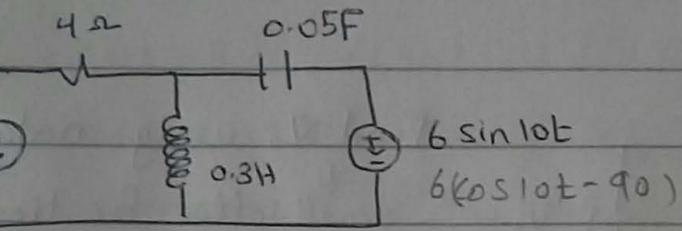Examplemesh #1

$$-4L_0 + 4I_1 + 3jI_1 - 3jI_2 = 0 \quad (4+3j)I_1 - 3jI_2 = 4L_0 \rightarrow ①$$

mesh #2

$$-2jI_2 + 6L - 90^\circ + 3jI_2 - 3jI_1 = 0 \quad -3jI_1 + jI_2 = -6L - 90^\circ \rightarrow ②$$

Using Cramer's Rule


$$\Delta = \begin{bmatrix} 4+3j & -3j \\ -3j & j \end{bmatrix} = 6j \quad \Delta_1 = \begin{bmatrix} 4\angle 0^\circ & -3j \\ 6\angle 90^\circ & j \end{bmatrix} = -18 + 4j$$

$$\Delta_2 = \begin{bmatrix} 4+3j & 4\angle 0^\circ \\ -3j & 6\angle 90^\circ \end{bmatrix} = -18 + 36j$$

$$I_1 = \frac{\Delta_1}{\Delta} = 2.5 L - 21^\circ A \quad I_2 = 5.5 L 82^\circ A$$


$$I_L = I_1 - I_2 = 6 L - 90^\circ$$

$\therefore i_L(t) = 6.5 \cos(10t - 76)$

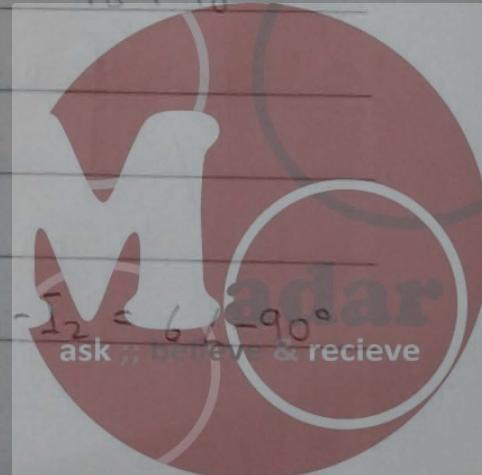

No: -----

Date: -----

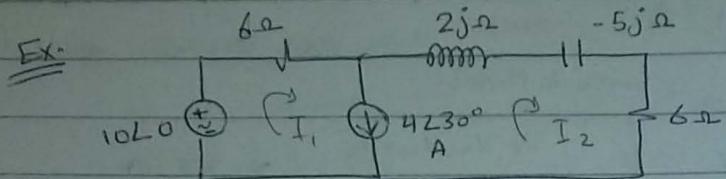

Find V_L By mesh analysis

Big loop

$$-10\angle 0^\circ + 6I_2 + 2jI_2 - 5jI_2 + 6I_2 = 0$$

$$6I_1 + (6 - 3j)I_2 = 10\angle 0^\circ \rightarrow ①$$

Branch

$$I_1 - I_2 = 4\angle 30^\circ \rightarrow ②$$

$$\Delta = \begin{bmatrix} 6 & 6-3j \\ 1 & -1 \end{bmatrix} = 2.37 - j84.4 \quad \Delta_2 = \begin{bmatrix} 6 & 10\angle 0^\circ \\ 1 & 4\angle 30^\circ \end{bmatrix} = 16.7 + j12j$$


$$\Delta_{12} = \begin{bmatrix} 10\angle 0^\circ & 6-3j \\ 4\angle 30^\circ & -1 \end{bmatrix} = 32.36L - j84 - 368 - j6j$$

$$I_1 = \Delta_1 / \Delta =$$

$$V_L = 2.6L - 27.7^\circ$$

$$V_L(t) = 2.6 \cos(\omega t - 27.7^\circ)$$

Ex:

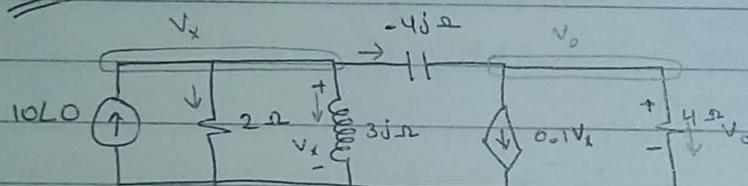

Find V_o using nodal analysis
small letter for time domain

Node V_x

$$10\angle 0^\circ = \frac{V_x}{2} + \frac{V_x - V_o}{3j} + \frac{V_x - V_o}{-j4} = V_x \left[\frac{1}{2} + \frac{1}{3j} + \frac{1}{-j4} \right] + V_o \left[\frac{1}{j4} \right] = 10\angle 0^\circ$$

$$V_x (0.51L - 9.46) + V_o (-0.25j) = 10\angle 0^\circ \rightarrow ①$$


Node V_o

$$\frac{V_x - V_o}{-4j} = 0.1V_x + \frac{V_o}{4} \quad V_x \left[\frac{1}{4j} + \frac{1}{10} \right] + V_o \left[\frac{1}{4} - \frac{1}{j4} \right] = 0$$

$$V_x (0.27L - 68.2^\circ) + (0.35 \angle 45^\circ) V_o = 0 \rightarrow ②$$



$$\Delta = \begin{bmatrix} 0.51L - 9.46 & -0.25j \\ 0.27L - 68 & 0.34 \angle 45^\circ \end{bmatrix}$$
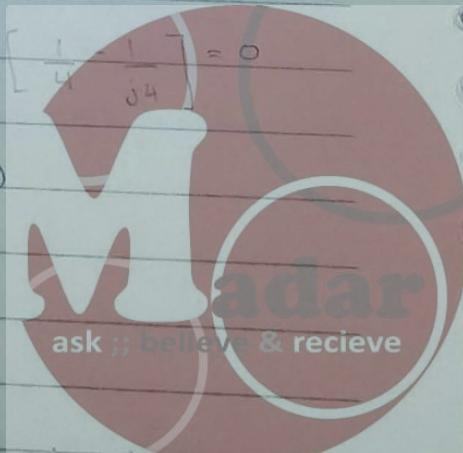
$$V_x = \frac{\Delta_1}{\Delta} \quad V_o = \frac{\Delta_2}{\Delta}$$



No:-----

Date:-----

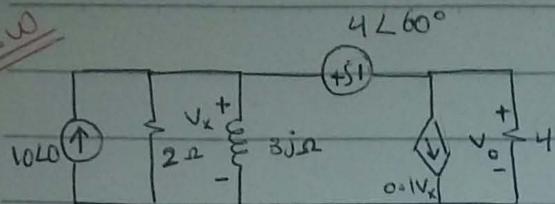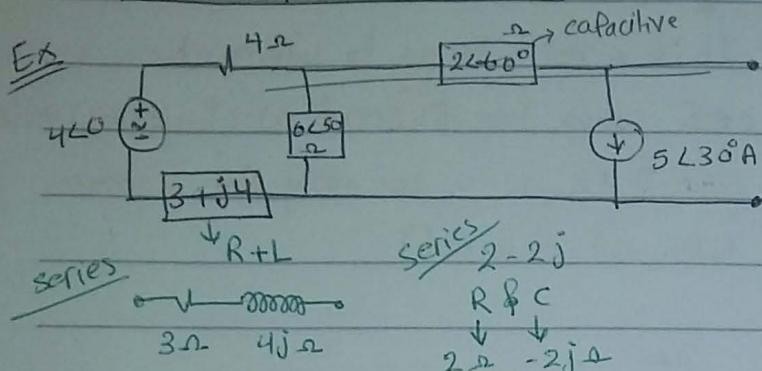
Source transformation
is the same principle in ACH.W.By supernode, find V_x & V_o .

Polar Form :-

+ve angle $\rightarrow R \& L$ inductive load-ve angle $\rightarrow R \& C$ capacitive load

19/12/2019

Find Norton equivalent

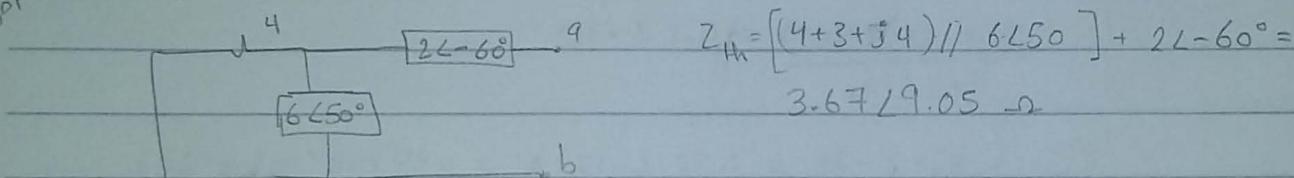(1) killing \rightarrow impedance Z_{th} 

$$Z_{th} = [(4 + 3 + j4) // 6L50] + 2L - 60^\circ =$$

$$3.67 / 9.05 \Omega$$

(2) $V_{ab} = V_{th}$

$$I_2 = 5L30^\circ$$




$$-4L0 + 4I_1 + 6L50I_1 - 6L50 \times 5L30^\circ + 3+j4I_1 = 0 \quad I_1 = 0.447L - 34.3^\circ$$

$$V_{ab} = (-2L - 60)I_2 + 6L50(I_1 - I_2) = V_{th}$$

(3)

You can convert it
by source transformation.


Example

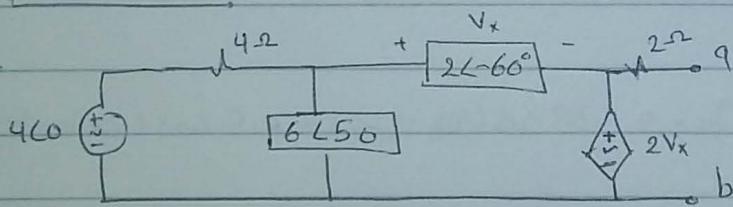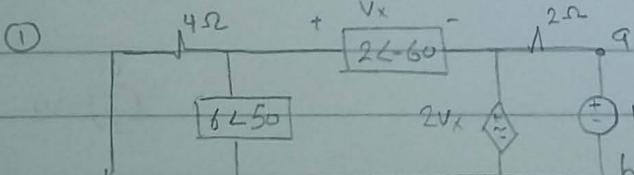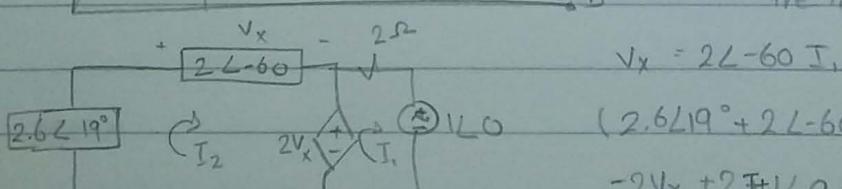Find Thevenin's
equivalentTo avoid 3 meshes, add
the impedances

$$V_x = 2L - 60 I_1$$

$$(2.6L19^\circ + 2L - 60) I_2 = -2V_x$$

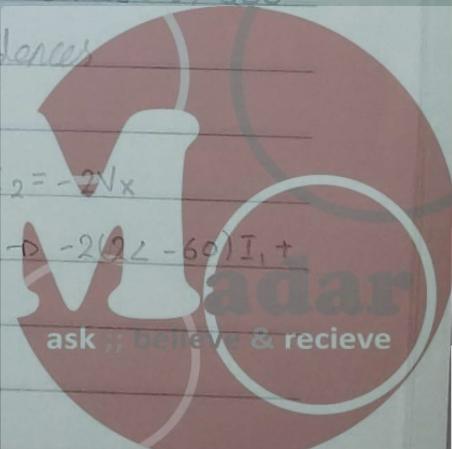
$$-2V_x + 2I_1 L_0 = 0 \rightarrow -2(2L - 60) I_1 +$$



No:-----

Date:-----


when one source, mesh is long

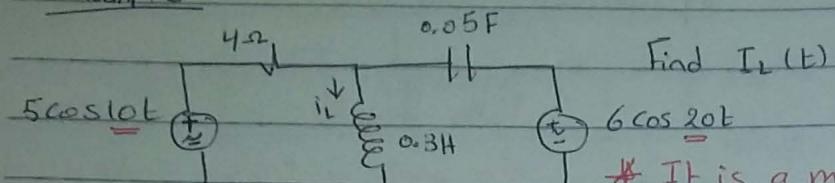ImpExample

* It is a must to go to superposition, since each source has different ω (frequency) value even if DC, $\omega=0$, but apply the constraints (open and close cut)

Apply superposition


① Source 1

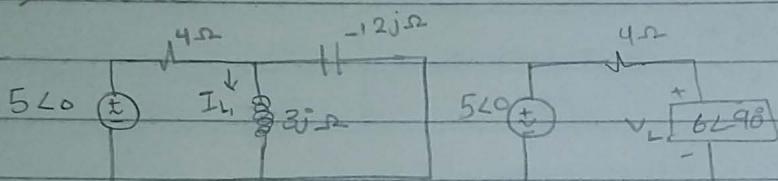

$$V_L = \frac{5L_0 (6L - 90^\circ)}{4 + 6L - 90^\circ} = 4.1 \angle -33^\circ$$

$$I_{L1} = \frac{4.1 \angle -33^\circ}{3j} = 1.38 \angle -123^\circ A = 1.38 \cos(10t - 123)$$


②

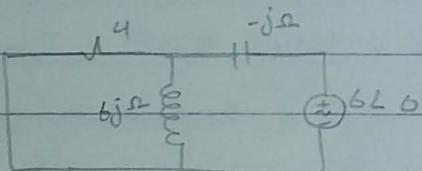

$$\frac{V_L}{2} = 3.3 \angle 33.7^\circ \quad I_{L2} = 0.5 \angle -56^\circ A = 0.5 \cos(20t - 56)$$

Superposition
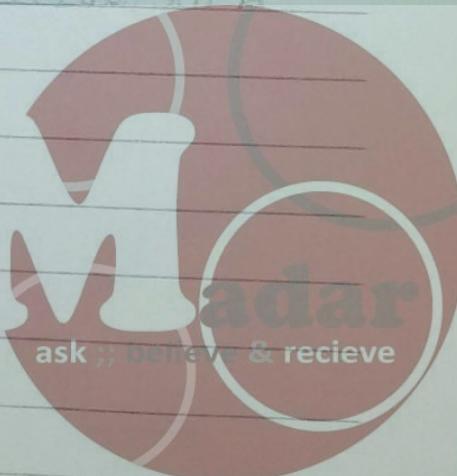
$$I_L = I_{L1} + I_{L2} = 1.38 \cos(10t - 123) + 0.5 \cos(20t - 56) A$$



No: _____

Date: _____

AC - Power

22/12/2019

$$\text{In DC} \quad P = IV = I^2R = V^2/R \quad [P] = W$$

$$\text{In AC} \rightarrow \text{Instantaneous power} \quad P(t) = i(t) \cdot v(t) \quad [P(t)] = W$$

$$\xrightarrow{\text{Average}} \text{Average power (Real / mean / Active power)} \quad P = \frac{1}{2} |I| |V| \cos(\theta_v - \theta_i) \quad [P] = W$$

can't be negative because $\cos(\theta) = \cos(-\theta)$

$$\text{Example} \quad I = 4 \angle 30^\circ$$

$$V = 6 \angle -15^\circ$$

$$P = \frac{1}{2} \times 4 \times 6 \times \cos(-15 - 30) = 12 \cos(-45) = [12\sqrt{2}] W = 8.4 W$$

*(i) Current
(ii) Voltage
(iii) Power)*

$$\text{Reactive power} \quad Q = \frac{1}{2} |I| |V| \sin(\theta_v - \theta_i) \quad [Q] = \text{VAR} \quad \text{Volt Ampere Reactive}$$

$$\text{e.g. } Q = \frac{1}{2} \times 4 \times 6 \times \sin(-45) = \frac{-12}{\sqrt{2}} \text{ VAR} \rightarrow \text{capacitive load} = -8.4 \text{ VAR}$$

Q in resistance, the phase shift = 0 ($\theta_v = \theta_i$)

	P	Q	
R	$\frac{1}{2} IV$	0	$\theta_v - \theta_i = 0 \quad \cos(0) = 1$
L	0	+ve	$\theta_v - \theta_i = 0 \quad \sin(0) = 0$
C	0	-ve	$\theta_v - \theta_i = 90^\circ \quad \cos(90) = 0$ $\theta_v - \theta_i = +90^\circ \quad \sin(\theta_v - \theta_i) \text{ +ve}$

impedance & phase shift

$\cos(-90) = 0$
 $\sin(-90) = -ve$


$$\text{Complex Power} \quad S = P + jQ \quad [S] = \text{VA} \quad \text{Volt Ampere}$$

$$\text{in the previous example} \quad S = 8.4 - j8.4 \quad \text{VA} = 11.87 \angle -45^\circ \text{ VA}$$

$$|S| : \text{Apparent Power} \quad |S| = 11.87 \text{ VA}$$

Power Triangle

$$3 + j4$$

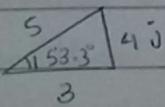

change the sign of angle θ_i

~~Also, $S = \frac{1}{2} V I^*$~~

$$\text{As values} \quad S = \frac{1}{2} \times 6 \angle -15^\circ \times 4 \angle 30^\circ = 12 \angle -45^\circ \text{ VA}$$


$$\text{So } S = \frac{1}{2} \times V \times \frac{V}{Z} = \frac{1}{2} V \times V^*/Z$$

$$I = 4 \angle 30^\circ$$

$$V = 6 \angle -15^\circ$$

$$Z = 2 \angle 30^\circ$$

$$Z = 1.5 \angle 45^\circ$$

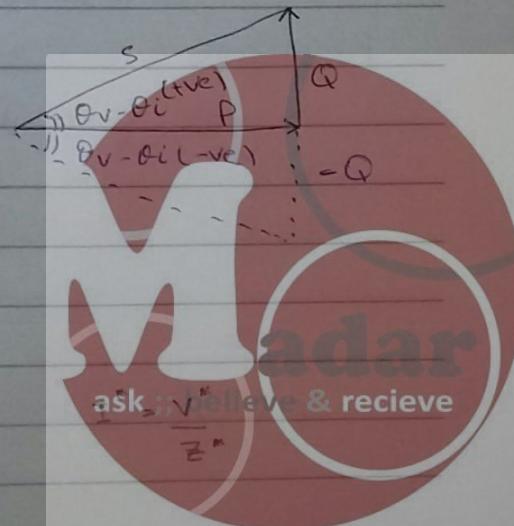


No: _____

Date: _____

$$\begin{aligned} & \frac{1}{2} |I| |V| \\ & = \frac{1}{2} \times |I| |I| |Z| \end{aligned}$$

Example

Find P, Q, S for each element

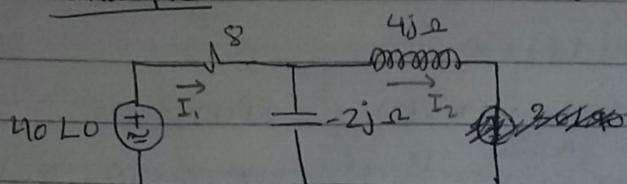

$$\frac{(j4)(-j2)}{2j} = 4 L - 90^\circ \quad Z_T = 8 - j4$$

$$I_1 = \frac{40L0}{8-4j} = 4.47 L 26.5^\circ \quad I_2 = \frac{40L0}{4j-2j} = 4.47 L -153.4^\circ A$$

$$P_{j4\Omega} = 0 \quad P_{-2j\Omega} = 0 \quad Q_R = 0$$

$$V_2 = 17.88 L - 63.4^\circ$$

$$Q_L = \frac{1}{2} \times 4.47 |17.88| \sin(-63.4 - 153.4) + 90^\circ = 39.97 \text{ VAR}$$

$$S_L = 0 + 39.9 j \text{ VA} \quad S_L = \frac{1}{2} \times 17.88 L - 63.4 \times 4.47 L + 153.4 = 39.9 L 90^\circ$$

$$S_R = P_R = \frac{1}{2} \times |V_R| \times |I_R|$$


→ S in the source, two ways

$$\textcircled{1} \quad P_{\text{source}} = S_{\text{loads}} \quad Q_{\text{source}} = S_Q$$

$$\textcircled{2} \quad S = \frac{1}{2} \sqrt{I^*} = \frac{1}{2} \times 40L0 \times 4.47 L - 26.5 = 89.4 L - 26.5 = 80 + -39.9 j \text{ VA}$$

$$P_R = \overline{Q_R} = \overline{Q_S} - \overline{Q_L}$$

Source Power Triangle

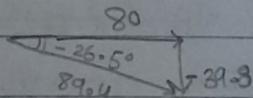

$$\rightarrow \cos(\theta_V - \theta_I) \Rightarrow \text{Power Factor (PF)} \quad 0 < \text{PF} < 1$$

cos is an even function.


$$P.F = \cos(-26.5) = 0.89 \text{ leads}$$

Generally, the dominant in the circuit is the

S angle → +ve P.F leads

capacitive load (because -ve angle sign)

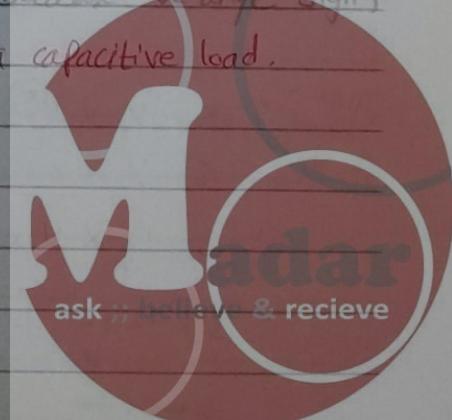w.r.t -ve P.F leads → circuit behaves like a capacitive load.



$P_{\text{source}} = P_{\text{load}}$
 $Q_{\text{source}} = Q_{\text{load}}$
 $S_{\text{source}} = S_{\text{load}}$

use $S_{\text{source}} \rightarrow P$

24/11/21


$$S^* = P + jQ$$

ذريعة كل loads ينبع من X, S فهو دلالة على او اذريعة كل

$$S^* = \frac{1}{2} V I^*$$

$$S_{\text{Total}} = \sum S_i$$

Imp. Example

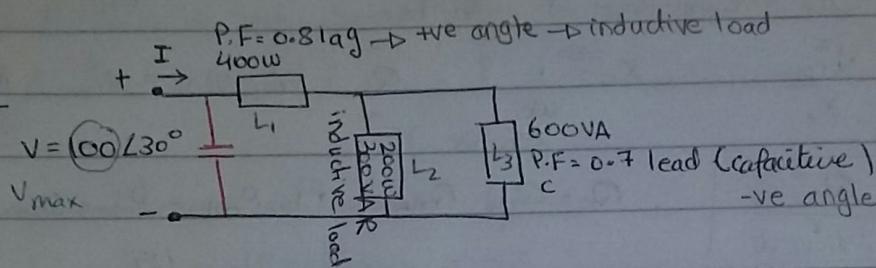

Every load, given

2 informations

Find P, Q, S, θ


from P.F

$$P = S \cos \theta$$

Find the total S ($S_{\text{source}}, \text{P.F}_{\text{source}}, I$)

$$S^* = \frac{P+Q}{\sin \theta}$$

$$S = \frac{P}{\text{P.F}}$$

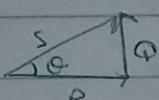

$$P = S \cos \theta = S \times \text{P.F} \quad S = P / \text{P.F}$$

~~Load #1~~

$$S_1 = \frac{400}{0.8} = 500$$

$$S_1 = 500 \angle 36.86^\circ \text{ VA}$$

$$\cos^{-1}(0.8) = 36.86^\circ$$

~~Load #2~~

$$P = 200 \text{ W}$$

$$S_2 = P + jQ$$

$$Q = 300 \text{ VAR}$$

$$= 200 + 300j = 360.5 \angle 56.3^\circ \text{ VA}$$

~~Load #3~~

$$S = 600 \text{ VA}$$

$$S = 600 \angle -45.6^\circ \text{ VA}$$

$\Rightarrow S_{\text{Total}} = S_1 + S_2 + S_3$ regardless of type of connection.

$$\Rightarrow S_{\text{source}} = S_{\text{Total}} = [850 \angle 40.9^\circ \text{ VA}] = 642.5 + 556.5j \text{ VA}$$

$$\Rightarrow \text{P.F}_{\text{source}} = \cos(40.9) = 0.76 \text{ lags}$$

$$\Rightarrow P_{\text{Total}} = 642.5 \text{ W}$$

$$S = \frac{1}{2} V I^*$$

$$850 \angle 40.9^\circ = \frac{1}{2} \times 100 \angle 30^\circ I^*$$

$$Q_{\text{Total}} = 556.5 \text{ VAR}$$

$$I^* = 17 \angle 10.9^\circ$$

$$I = 17 \angle -10.9^\circ \text{ A}$$


Imp.

\downarrow Pay $\downarrow S$ by $\downarrow Q$ & keep P value

$\downarrow \theta \uparrow \text{P.F} (\uparrow \cos \theta)$

In exam

How to correct the P.F?

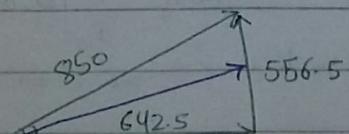


* To improve the P.F, we have to add a capacitor in PARALLEL with the POWER SUPPLY. (in order to know its voltage)

Imp.

Ideal case $\rightarrow \text{P.F} = 1 \quad \theta = 0$

In exam
decided
voltage

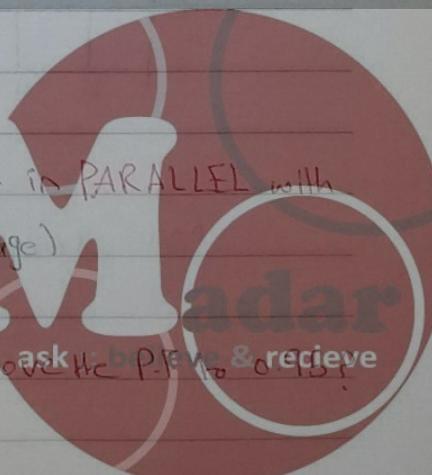What is the value of the capacitor to be added to improve the P.F. assuming $f = 60 \text{ Hz}$.




No: ----- Date: -----

1. Find $\theta_{\text{new}} = \cos^{-1}(P/F_{\text{new}}) = 18.2^\circ$

2. $Q_{\text{new}} = P \times \tan \theta = 211.2 \text{ VAR}$

3. $Q_{\text{capacitor}} = Q_{\text{old}} - Q_{\text{new}} = 345.3 \text{ VAR}$

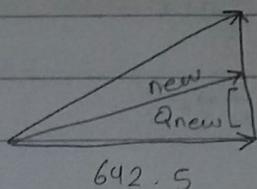~~it is the voltage drop of capacitor~~

4. $Q_C = \frac{V_{\text{rms}}^2}{X_C} \quad X_C = \frac{1}{\omega C} \quad Q_C = V_{\text{rms}}^2 \omega C = V_{\text{rms}}^2 \cdot 2\pi f C$

$$C = \frac{Q_C}{V_{\text{rms}}^2 \omega} \quad Q_C = Q_{\text{old}} - Q_{\text{new}} = P \tan \theta_{\text{old}} - P \tan \theta_{\text{new}}$$

$$C = \frac{P(\tan \theta_{\text{old}} - \tan \theta_{\text{new}})}{V_{\text{rms}}^2 \cdot 2\pi f} \quad \text{Find } C \text{ to make the P.F unity} \rightarrow Q_C = Q_{\text{old}}$$

$$C = 1.8 \times 10^{-4} \text{ F} = 180 \mu\text{F}$$

$\rightarrow V_{\text{rms}}$ root mean squared value - rms - effective

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

- physically, it means if replaced with DC device, it gives the same power that was putted for the same AC device.


$$\text{For sinusoidal sign } \begin{cases} \sin \\ \cos \end{cases}, V_{\text{rms}} = \frac{V_{\text{max}}}{\sqrt{2}}$$

$$\text{e.g. } I(t) = 6 \sin(10t)$$

$$I_{\text{rms}} = 6/\sqrt{2}$$

$$v(t) = 10 \cos(\omega t)$$

$$V_{\text{rms}} = 10/\sqrt{2}$$

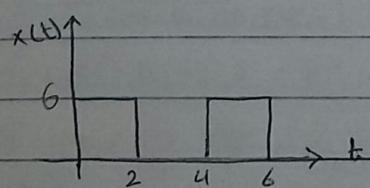


$$T = 4$$

$$x_{\text{avg}} = \frac{1}{4} \int_0^2 6 \cdot dt$$

$$\Leftrightarrow 2 \rightarrow 4 = 0$$

$$X_{\text{rms}} = \sqrt{\frac{1}{4} \int_0^2 6^2 \cdot dt} = \sqrt{\frac{1}{4} \cdot 36 \cdot 1} = \sqrt{18}$$

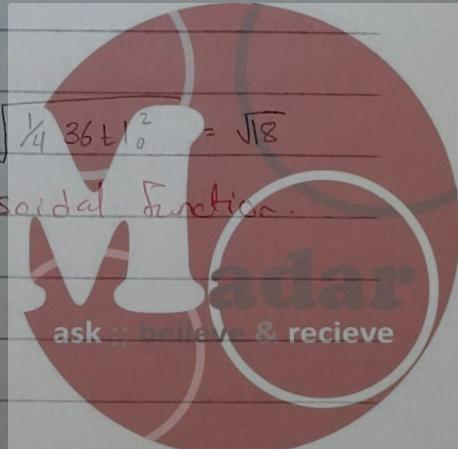Not $X_{\text{rms}} = X_{\text{max}}/\sqrt{2}$ BECAUSE Not sinusoidal function.



No:-

Date:-

26/12/2019

Source

Y



Y

Load


Y

Δ

3-phase system

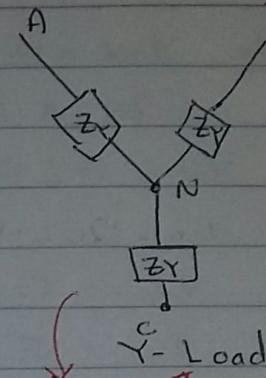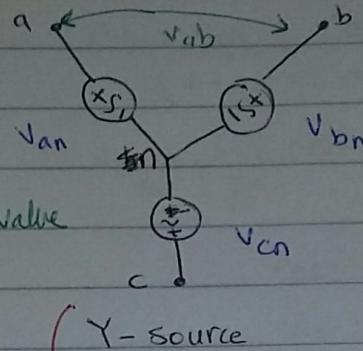

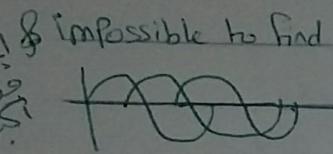~~it's hard to find a point at zero value~~
Y.



-120° with clockwise → +ve sequence

$$\theta \text{ difference} = 120^\circ$$

$$V_{an} = 10 L 0^\circ$$

$$V_{bn} = 10 L -120^\circ$$

$$V_{cn} = 10 L -240^\circ$$

$$V_{ab} = 10 \sqrt{3} L 30^\circ$$

$$V_{bc} = \sqrt{3} \times 10 L -90^\circ$$

$$V_{ca} = \sqrt{3} \times 10 L -210^\circ$$

"Phase Voltage"

"line voltage" $\rightarrow V_{ab} = \sqrt{3} V_{an} L 30^\circ$

Ex.

$$V_{an} = 100 L 60^\circ$$

$$V_{ab} = 100 \sqrt{3} L 90^\circ$$

if V_{ba} (- vector)

$$V_{bn} = 100 L -60^\circ$$


$$V_{bc} = 100 \sqrt{3} L -30^\circ$$

$$V_{cn} = 100 L -180^\circ$$

$$V_{ca} = 100 \sqrt{3} L -150^\circ$$

V_p "Phase voltage"

"Line voltage" V_L

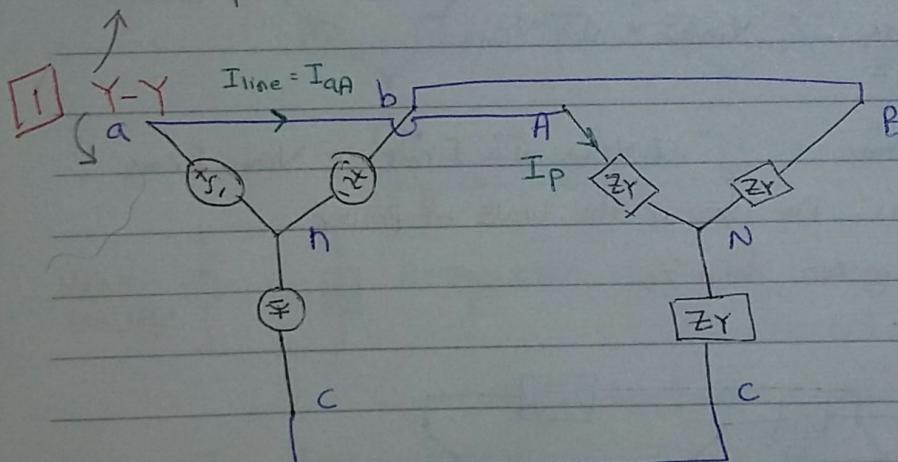


in Y-Y

$$I_{\text{line}} = I_{\text{phase}}$$

$$V_{\text{line}} = \sqrt{3} V_{\text{phase}} = \frac{V_{an}}{\sqrt{3} ZY}$$


since balanced load

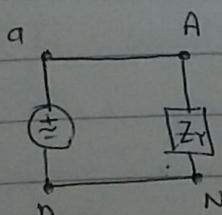

$$I_{aa} = \frac{V_{an}}{ZY}$$

$$I_{bb} \text{ Just } -120^\circ$$

$$I_{cc} \text{ Just } -240^\circ$$

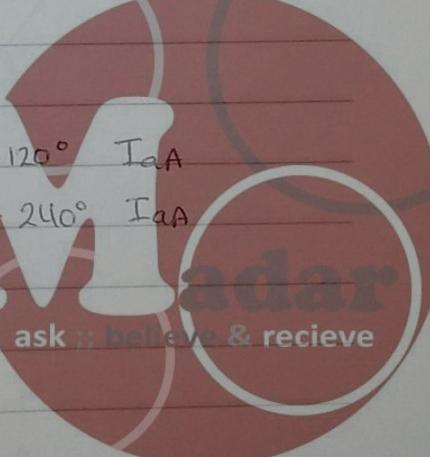

Example $V_{bn} = 120 \angle 70^\circ$

$$Z_Y = 4 \angle 10^\circ$$

$$V_{an} = 120 \angle 190^\circ = V_{AN}$$

$$V_{cn} = 120 \angle -60^\circ$$

$$V_{ab} = \sqrt{3} 120 \angle 220^\circ$$

$$V_{bc} = \sqrt{3} 120 \angle 100^\circ$$

$$V_{ca} = \sqrt{3} 120 \angle -20^\circ$$

$$I_{aA} = \frac{V_{an}}{Z_Y} = \frac{120 \angle 70^\circ}{4 \angle 10^\circ} = 30 \angle 180^\circ$$

$$I_{bB} = 30 \angle 60^\circ$$

$$I_{cC} = 30 \angle -60^\circ$$

$\rightarrow I_{aA} + I_{bB} + I_{cC} = 0 = I_{NN}$ ONLY in balanced load

Find the complex power in load

$$S = \frac{1}{2} V I^* \leftarrow \text{For 1 phase} \quad \text{max}$$

$$\text{For 3 phase} \rightarrow S = 3 \times \frac{1}{2} \times [V_{an}] I_{aA}^*$$

$$S = 1.5 \times (120 \angle 190^\circ) (30 \angle -180^\circ) = 5400 \angle 10^\circ \text{ VA}$$

\rightarrow With rms

$$V_{rms} = \frac{V_{max}}{\sqrt{2}} \quad V_{max} = \sqrt{2} V_{rms}$$


$$\frac{1}{2} V_{max} I_{max}^* = \frac{1}{2} \sqrt{2} V_{rms} \sqrt{2} I_{rms}^* = V_{rms} I_{rms}$$

If with rms, no $\frac{1}{2}$ in the laws of power

\rightarrow If complex power given, find Z_L


Example

impedance on line

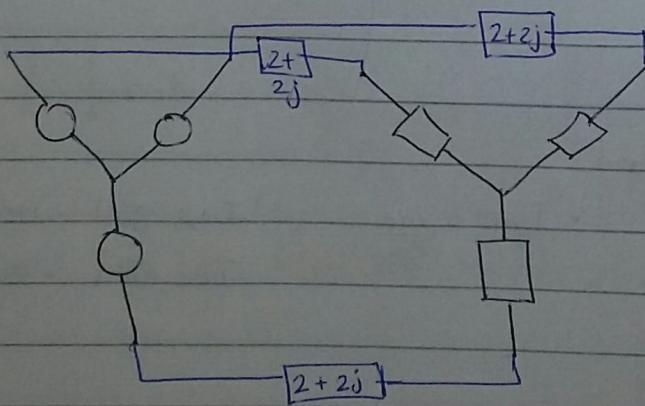

$$V_{ab_{rms}} = 173 \angle 30^\circ \text{ V} \quad Z_Y = 4 \angle 10^\circ$$

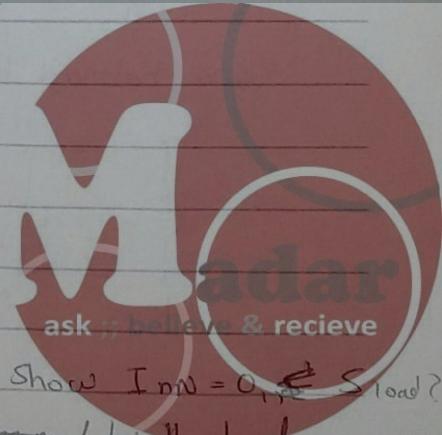
$$S = 210 \angle 76^\circ \text{ VA} \quad \leftarrow \text{Complex Power consumed by the load.}$$



Show $I_{NN} = 0, \therefore S_{load}?$

No: _____

Date: _____

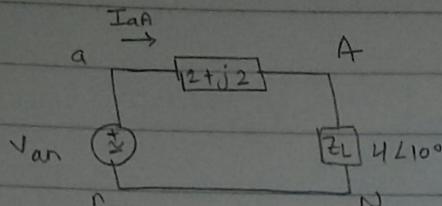(Collective) $r_{\text{rms}} = 0.01 \Omega$
 $\max \theta = 5^\circ$ 

$$I_{aA} = \frac{V_{an}}{(2+j2) + 4L10^\circ} = 15 L - 24 A$$

$$V_{an} = \frac{173 L 0}{\sqrt{3}} = 100 L 0$$

$$I_{bB} = 15 L - 144$$

$$I_{cc} = 15 L - 264$$

Complex Power consumed by load $\theta_S = \theta_Z$

$$S = 3 \times \sqrt{V_{AN}^2} I_{aA}^*$$

NOT V_{an} , There is voltage consuming

$$V_{AN} = I_{aA} Z_Y = 15L - 24 \cdot 4L10^\circ = 60L - 14 V$$

$$S = 3 \times 60 L - 14 \times 15 L 24 = 2700 L 10 VA$$

$$\text{P.F. load} = \cos(10) \log$$


→ Complex Power delivered by the source

$$S_{\text{source}} = 3 V_{an} I_{aA}^* = 3 \times (100 L 0) \times (15 L 24) = 4500 L 24$$

$$\text{P.F. source} = \cos(24) \log$$

→ Complex power consumed by line $S_{\text{line}}^{\text{Transmission}} = S_{\text{source}} - S_{\text{load}}$

Example

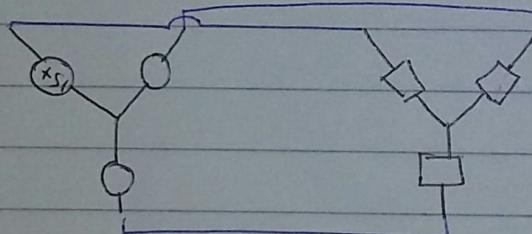

$$V_{an} = 100 L 45^\circ V$$

$$S_{\text{load}} = 200 L 60^\circ VA$$

Find Z , I_{aA} , P.F. source

$$V_{an} = \frac{100 L 45^\circ}{Z_Y} \quad S = \frac{200 L 60^\circ}{3}$$

$$S = 3 V_{an} I_{aA}^*$$

$$200 L 60^\circ = 3 (100 L 45^\circ) I_{aA}^*$$

$$I_{aA} = 0.67 L - 15^\circ A$$

$$Z_Y = \frac{V_{AN}}{I_{aA}} = \frac{100 L 45}{0.67 L - 15} = 150 L 60 - \Omega$$


$$\text{P.F.}_L = \cos(60) \log$$

$S_{\text{load}} = S_{\text{source}}$ ONLY for ideal transmission



No: _____

Date: _____

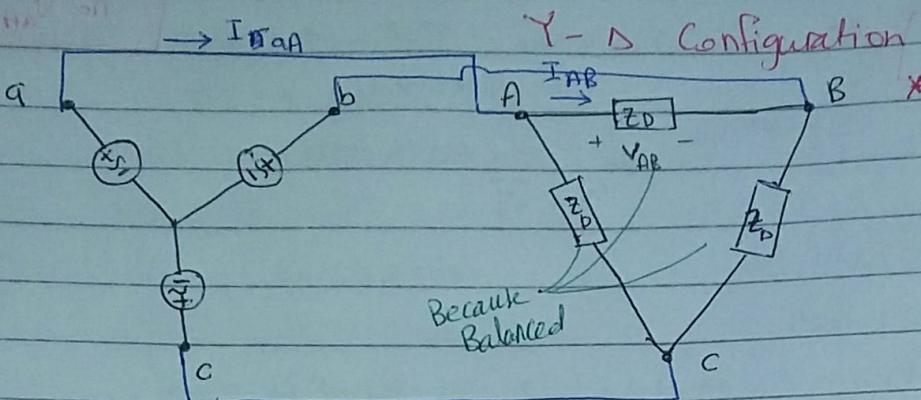You can convert Δ to Y

$$Z_Y = Z_\Delta / 3$$

$$I_{AA} = \sqrt{3} I_{AB} L + 30^\circ$$

$$V_{an} \rightarrow V_{ab} \rightarrow V_{AB} \rightarrow I_{AB} = \frac{V_{AB}}{Z_\Delta} \rightarrow I_{AA}$$

$$V_{ab} = V_{AB}$$

 Z_Δ given \rightarrow Find I_{AA} Example

$$Z_\Delta = 4 L 15^\circ$$

$$V_{an} = 100 L 60^\circ$$

Complex power consumed by load? delivered by source?

$$V_{an} \rightarrow V_{AB}$$

$$V_{ab} = \sqrt{3} V_{an} L + 30^\circ \rightarrow V_{ab} = 173 L 90^\circ V$$

$$(\sqrt{3} (100) L 90)$$

$$V_{ab} = V_{AB}$$

$$I_{AB} = \frac{V_{AB}}{Z_\Delta} = \frac{173 L 90}{4 L 15} = 43.25 L 75 A$$

$$S_{load} = \frac{1}{2} \times 3 \times V_{AB} \times I_{AB}^* = 11223.4 L 15 VA$$

$$\overline{\theta}_{load} = \overline{\theta}_{Zload}$$

Consumed by phasor AB, for 1 load, without 3

$$S_{source} = \frac{1}{2} \times 3 \times V_{an} \times I_{AA}^* = S_{load} = S_{delivered} = 11223.4 L 15 VA$$

$$I_{AA} = \sqrt{3} \times 43.25 L 45^\circ = 74.9 L 45^\circ A$$

$$I_{CC} = 74.9 L 45 - 240$$

$$V_{BC} = V_{AB} L - 120 + \theta$$



No:.....

Date:.....

Y-Y

$$I_L = I_P \quad I_{aA} = I_{AN}$$

$$V_L = \sqrt{3} V_P \quad V_{ab} = \sqrt{3} V_{an}$$

Y-Δ

$$I_L = \sqrt{3} I_P \quad I_{aA} = \sqrt{3} I_{AB}$$

$$V_L = V_P \quad V_{ab} = V_{AB}$$

Imp. Example

Find line current $\rightarrow I_{aA}, I_{bb}, I_{cc}$, same source phase current

load \rightarrow Phase current $\rightarrow I_{AB}, I_{BC}, I_{CA}$

Phase voltage $\rightarrow V_{AB}$

line voltage $\rightarrow V_{ab}$

Avg. Power $\rightarrow P$

Given

$$V_{an\text{ rms}} = 220 L 0$$

$$\tilde{V}_{bn} = 220 L -120$$

$$\tilde{V}_{cn} = 220 L 120 \text{ (or } -240)$$

$$Z_D = 9 - j6$$

$$\tilde{V}_{ab} = 381 L 30 = \tilde{V}_{AB} \quad \tilde{V}_{bc} = 381 L -90 = \tilde{V}_{BC} \quad \tilde{V}_{ca} = 381 L -210 = \tilde{V}_{CA}$$

$$I_{AB} = \frac{V_{AB}}{Z_A} = \frac{35.2 L 63.7}{Z_A} \quad I_{BC} = 35.2 L -56.4 \quad I_{CA} = 35.2 L -176.4 A$$

$$I_{aA} = \sqrt{3} I_{AB} L^{30} + 0$$

$$I_{aA} = 60.9 L 33.6 \quad I_{bb} = 60.9 L -86.4 \quad I_{cc} = 60.9 L -206.4 A$$

$$\leftarrow S_{\text{source}} = 3 \tilde{V} \tilde{I}^* = 3 \tilde{V}_{an} I_{aA}^* = 3(220 L 0)(60.9 L -33.6) = 4094 L -33.6 \text{ VA}$$

$$P.F_{\text{source}} = \cos(-33.6) = 0.83 \text{ leading}$$

$$S_{\text{load}} = S_{\text{source}}$$

$$S_{\text{1phase}} = S_{\text{source}} / 3$$

\rightarrow If the power delivered by load = $4094 L -33.6$, given V_{an} , find Z_D ?

$$S_{\text{1phase}} = S / 3 \rightarrow S = \tilde{V} \tilde{I}^*$$

$$\checkmark \quad \checkmark \downarrow \quad \text{from } I \rightarrow \frac{V}{I} = Z_D$$

