

# Electrical



**Summer  
2025/2026**



Perpared By:

Dr:

**hedaya Abu Alhamed**

**Yazid khattabi**

# *Chapter 1*

## Chapter (1)

### [1] Units :

Time  $\rightarrow$  sec.

Electrical current  $\rightarrow$  Ampere  $\rightarrow$  A

voltage  $\rightarrow$  volt

mass  $\rightarrow$  Kg

length  $\rightarrow$  m

power  $\rightarrow$  watt

charge  $\rightarrow$  coulomb

### [2] Prefixes :

Pico  $\rightarrow 10^{-12}$

nano  $\rightarrow 10^{-9}$

micro  $\rightarrow 10^{-6}$

milli  $\rightarrow 10^{-3}$

Kilo  $\rightarrow 10^3$

Mega  $\rightarrow 10^6$

Giga  $\rightarrow 10^9$

### [3] Power supply :


a) types :

- 1) voltage source

- 2) current source.

b) output signal :

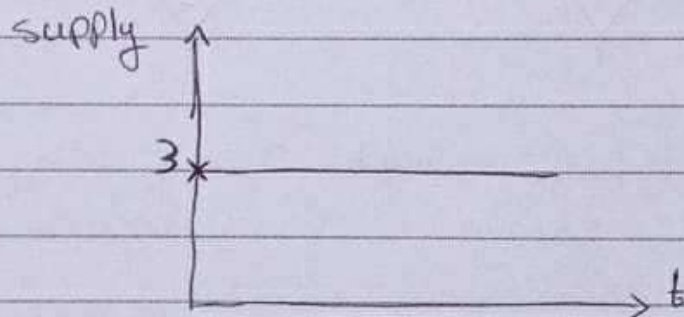- 1) DC output signal & value of the supply is fixed with time.




Ex : supply  $V = 3$  volt

$I = 2$  A = constant

DC - supply

Ex :  $V(t) = 3 \sin(4t)$  2) AC output signal & its value vary with time.

$$I(t) = 2 e^{-t}$$

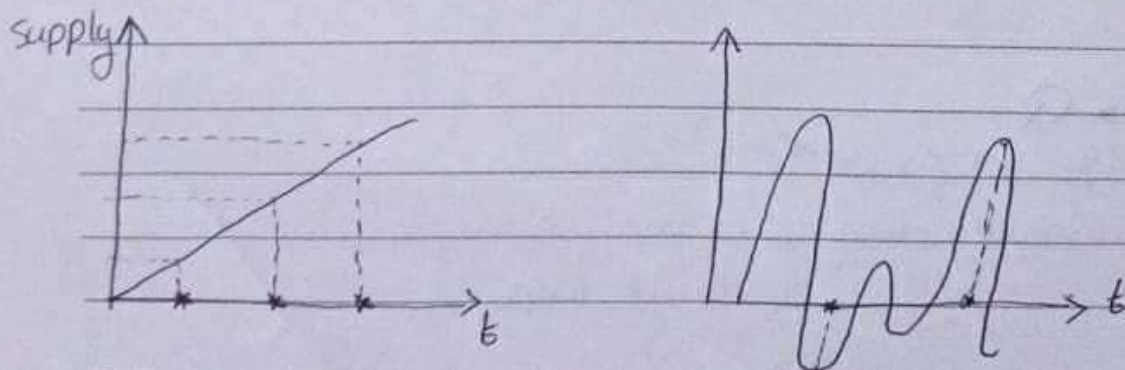



## \* charge , current. → 1.3


\*  $I \rightarrow$  التيار هو سيل من الإلكترونات

$$e = 1.6 \times 10^{-19} \text{ C. } \text{ و } Q = ne$$

$$i = \frac{dq}{dt}$$

مقدار الشحنة (e) الإلكترونات

$$Q = \int_{t_2}^{t_1} i \, dt$$

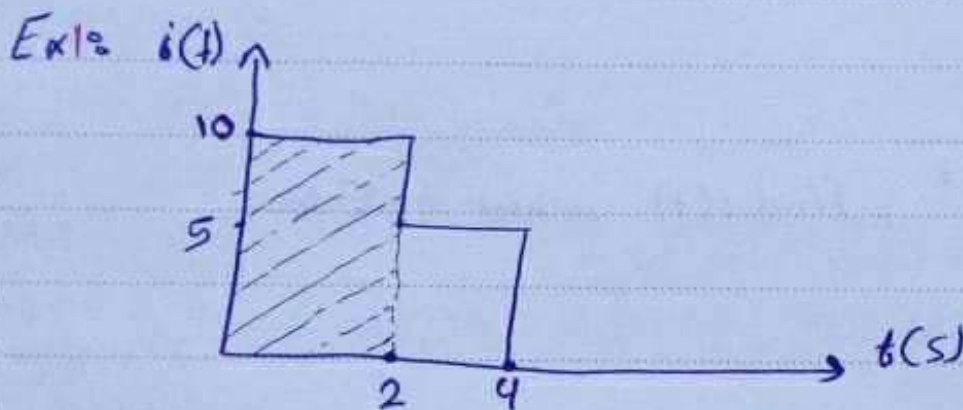


\* Find  $Q$ .  $t \ 0 \rightarrow 2$


$$Q = \int_0^2 i(t) \, dt \Rightarrow \text{Area}$$

$$Q = 2 \times 10 = 20 \text{ Coulomb.}$$

Ex 2: Find  $i(t)$

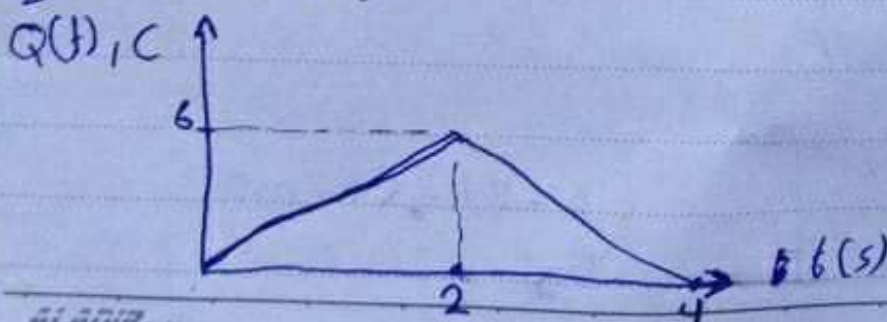



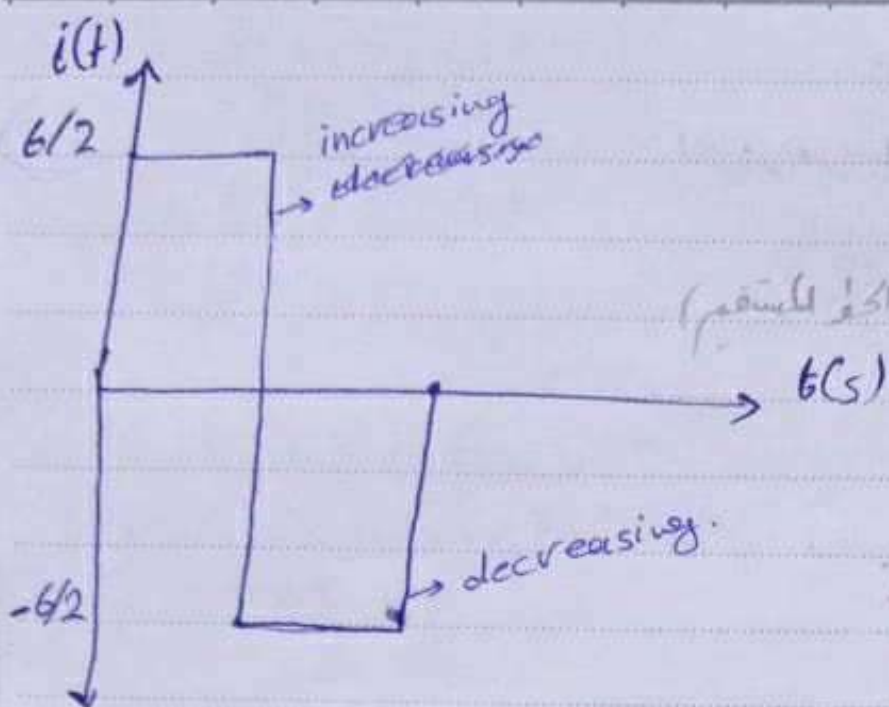

\* current wave form

والتي، بدأ من العزم ثم ازداد

ووصل قيمة معينة ثم بقيت (عبارة عن اكو المستقيم)

وبعد هذا بدأ بالانخفاض ليصل

إلى قيمة معينة ثم بقيت (عبارة عن)

خط مستقيم) ويعود إلى العزم

Ex:3  $Q(t) = 10 - 10e^{-2t}$ , Find  $i(t)$  when  $t = 5$  sec.

$$i = \frac{dq}{dt} = 0 + 20e^{-2t}$$

$$i(t) = 20e^{-2t}$$

$$i(5) = 20e^{-2 \times 5} = 9.1 \times 10^{-4} \text{ A.}$$

Ex(4) :

$i(t) = (3t^2 - t) \text{ A}$ , Find  $Q$  when  $t=1$ ,  $t=2$

$$Q = \int i(t) dt$$

$$= \int_1^2 (3t^2 - t) dt$$

$$= \left[ \frac{3t^3}{3} - \frac{t^2}{2} \right]_1^2 = (8 - 2) - (1 - 0.5) = 5.5 \text{ C}$$

\* voltage :- work

\*  $V_a \rightarrow$  voltage of point @

\*  $V_b \rightarrow$  voltage of point @

\* توضيح ال voltage

If I have in  $(\infty)$  charge equal 1 coulomb.

\* the work need to bring a charge of 1C to point @

from  $\infty$  إذا بقي أحيث شحنة مقدارها 1 كولوم وجوبه بال  $(\infty)$  في أي نقطة من  
في حركة الشحنة (a)

$$* V = \frac{dw}{dq}, \quad w: \text{work} \\ q: \text{charge.}$$

$$V_a = 5V$$

$$V_c = -4V$$

$$V_b = 3V$$

$$V_{ab} = V_a - V_b = 5 - 3 = 2V$$

$$V_{ac} = V_a - V_c = 5 - (-4) = 9V$$

\* Power and Energy:

$$P(w)$$

$$E(J)$$

$$P = \frac{dw}{dt}$$

$$W = \int P \cdot dt$$

Ex: (5) a.

b. Find  $V$  if  $q = 2C$ .

$$-30J$$

$$V = \frac{W}{q} = \frac{-30}{2} = -15V$$



Ex(6): find the power if  $t = 3\text{ms}$ ,

$$i = 5 \cos(60\pi t)$$


$$v = 3i$$

$$P = I \cdot V$$

$$P = i \cdot v = 5 \cos(60\pi t) (3)(5 \cos 60\pi t)$$
$$= 75 \cos^2(60\pi t)$$

at  $3\text{ms}$

$$P = 75 \cos^2(60\pi (3 \times 10^{-3})) \rightarrow \text{Radiation, لا أساس له}$$
$$= 53.5 \text{ w}$$

Ex(7): we have lamp  has  $P = 100\text{w}$ , work in 2 hours  
How much energy?

$$W = Pt$$

$$= 100 \times 2 \times 3600$$

$$= 72 \times 10^4 \text{ J}$$

\* Circuit Elements:

→ Power source (Produce Power)


→ load (consums Power)

→ concentration



## \* Power source
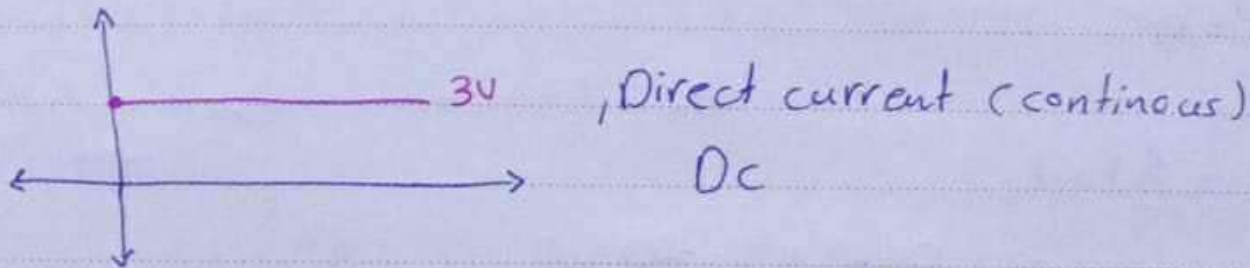
### ① Independent voltage source. $\oplus$



### Independent current source. $\uparrow$

### ② Dependent power source.




dep.  $\Rightarrow$  voltage source. (يعتمد على قيمة تيار مرجعية  $I_x$ )



dep.  $\Rightarrow$  current source. (يعتمد على قيمة جهد مرجعي  $V_x$  أو فرق الجهد)

## Power supply.

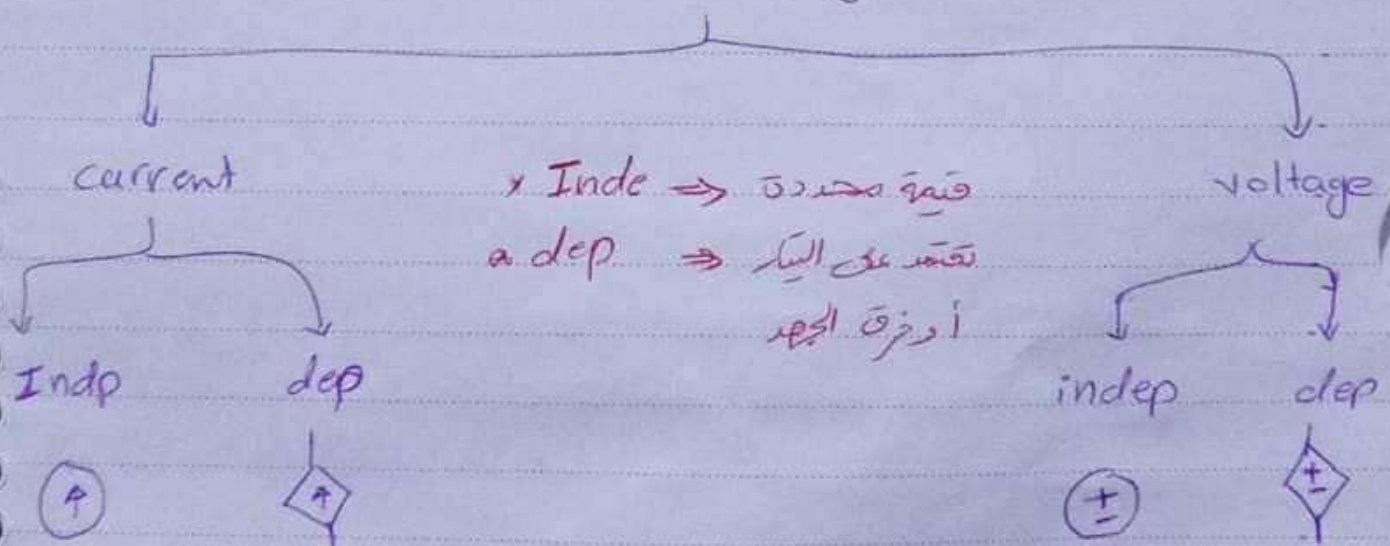


\* For any electrical circuit

$$\sum P = 0$$

$$\sum P_{in} = \sum P_{out}$$

$$P = -5 \times 4 = -20 \text{ W}$$

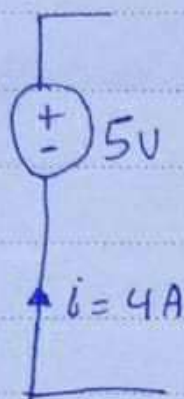


→ إذا دخل التيار في القطب السالب لمصدر فرق الجهد  
تكون ال Power سالبة، وتسمى  
produce, generate, deliver power.

→ إذا دخل في القطب الموجب لمصدر فرق الجهد  
تكون ال Power موجبة، وتسمى  
consumed power.

$$P = -(5)(-3) = 15 \text{ W}$$

يخرج التيار  
في اتجاه المعرف

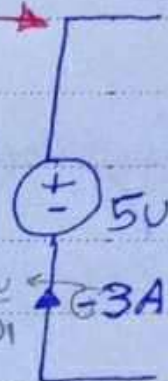



particle problem.

1.1  $\Rightarrow Q = ?$  ,  $n = +6 \times 10^6$  proton

$$Q = n[e] \rightarrow \text{نعوض القيمة دون إشارة}$$
$$= 6 \times 10^6 \times 1.6 \times 10^{-19}$$
$$= +9.6 \times 10^{-13} \text{ C}$$

1.3  $\Rightarrow$

$$i = \begin{cases} 4 \text{ A}, & 0 < t < 1 \\ 4t^2 \text{ A}, & t > 1 \end{cases} \quad Q, t=0 \rightarrow t=2$$

$$Q = \int_{t_1}^{t_2} i \, dt$$

$$= \int_0^1 4 \, dt + \int_1^2 4t^2 \, dt$$

$$= 4t \Big|_0^1 + \frac{4t^3}{3} \Big|_1^2$$

$$= 4 + \frac{4}{3}(8-1)$$

$$= 13.33 \text{ C}$$


1.5  $\Rightarrow P = ?$  ,  $i = 5 \cos 60\pi t$  ,  $t = 5 \text{ ms}$  ,  $v = 10 + 5Q$

$$P = IV = 5 \cos(60\pi t) \times \left( 10 + 5 \int_0^5 5 \cos 60\pi t \, dt \right) = 29.7 \text{ W}$$

$\frac{25 \sin(60 \times \pi \times 5)}{60 \times \pi}$  ←



Ex 8

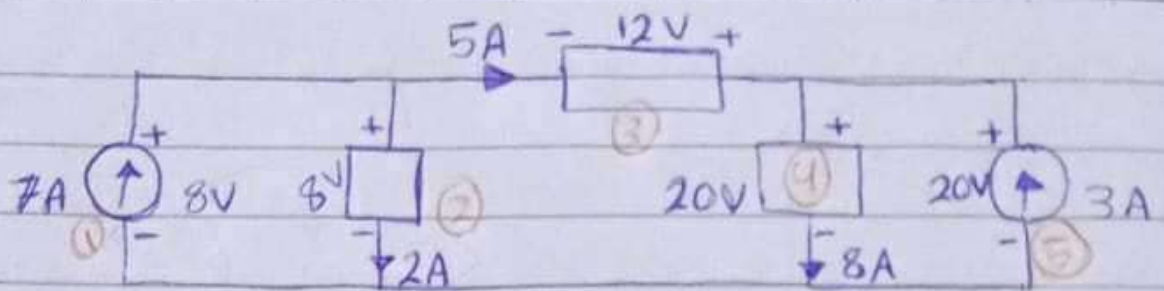

\* Find power for each element

$$P_1 = (-)(7)(8) = -56 \text{ W} \rightarrow \text{generated}$$

$$P_2 = (+)(2)(8) = 16 \text{ W} \rightarrow \text{consumed}$$

التيار في الجهد

التيار في الجهد

$$P_3 = (-)(5)(12) = -60 \text{ W} \rightarrow \text{generated}$$

$$P_4 = (+)(8)(20) = +160 \rightarrow \text{consumed}$$


$$P_5 = (-)(3)(20) = -60 \rightarrow \text{generated}$$

Law of conservation energy  $\Rightarrow \sum P_{\text{consumed}} = \sum P_{\text{generated}}$

$$16 + 160 \stackrel{?}{=} +56 + 160 + 60$$

$$176 \stackrel{?}{=} 176 \checkmark$$

$$\sum P = 0$$

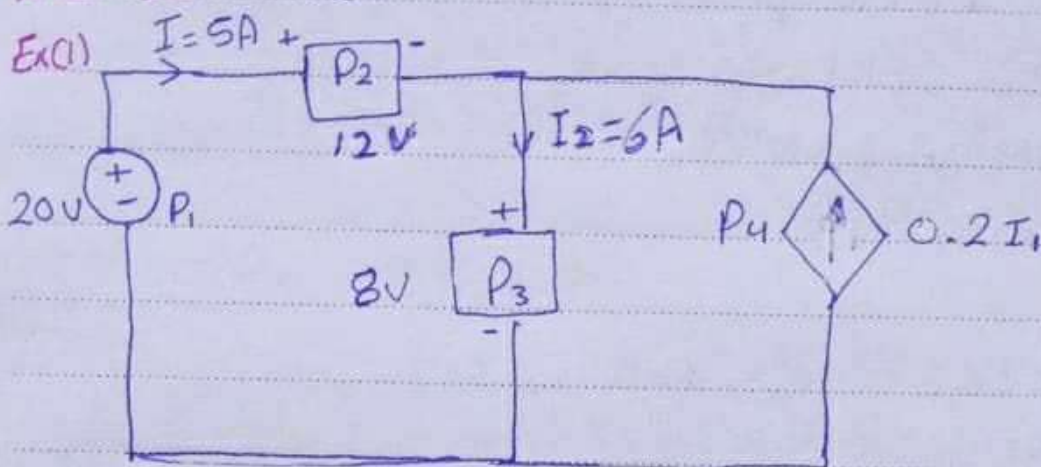

$$P_1 = (20)(5) = -100 \text{ W (produces, deliver)}$$

إذا دخل التيار القطب

$$P_2 = +(5)(12) = +60 \text{ W (cons.)}$$


السالب إذا (-) P3

إذا دخل التيار القطب

$$P_3 = +(6)(8) = +48 \text{ (cons.)}$$

الموجب إذا (+) P4
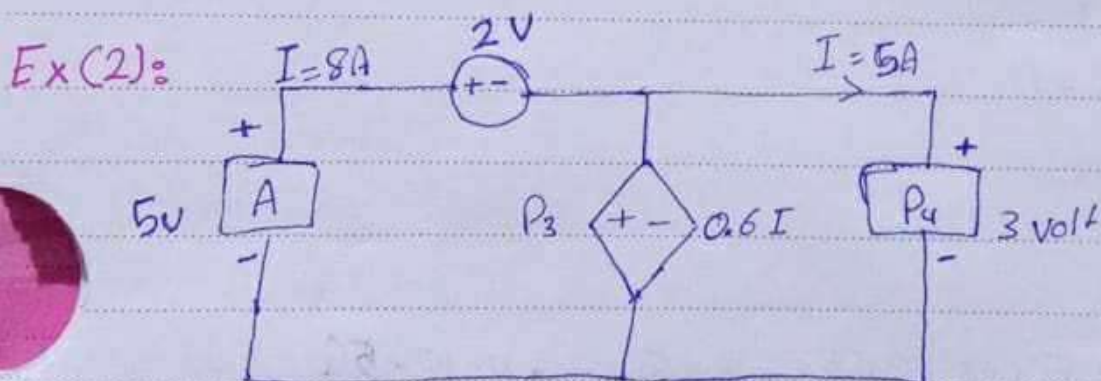
$$\sum P = 0, \text{ so } P_4 = -8 \text{ W}$$



$$P_1 = (-5)(8) = -40 \text{ W}$$

$$P_2 = (+2)(8) = +16 \text{ W} \Rightarrow -40 + 16 + P_3 + 15 = 0$$

$$P_3 = ?$$



$$P_3 = +9 \text{ W}$$

$$P_4 = +(5)(3) = +15$$

End of chapter one

# *Chapter 2*



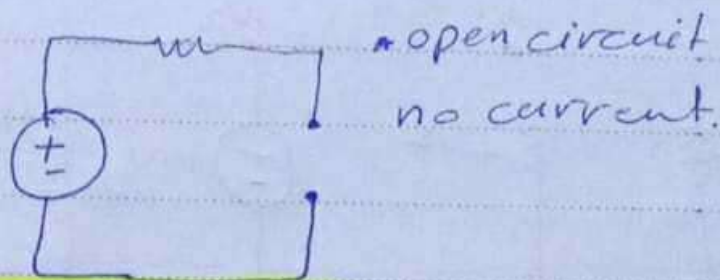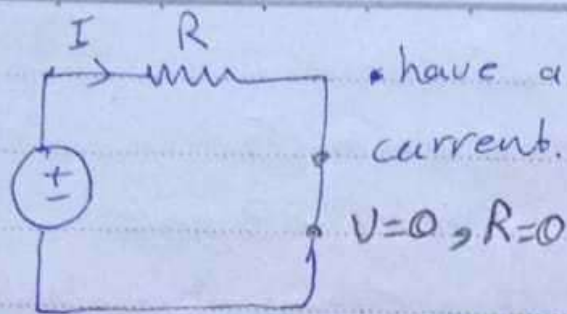


## Ohm's law (2.2)

poli anty (التيار) ←  $I$   $\xrightarrow{+V+}$   
للمقاومة  $R$

حيث مكان خروج التيار  $V = IR$

هو القطب الموجب  $P = IV = I^2 R = V^2 / R$

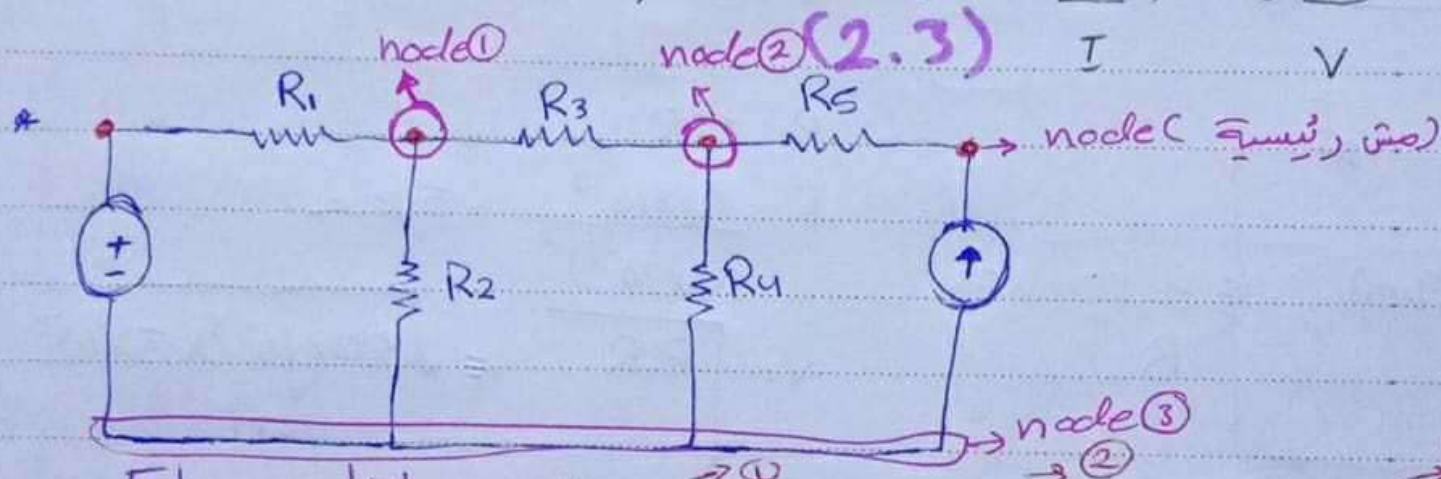\* Conductance:  $G = 1/R$ ,  $V = IR \Rightarrow R = \frac{V}{I}$ ,  $G = \frac{I}{V}$



→ Element (7) → voltage source, current source, Resistor

→ Branch (7/5) → any part has an element.

→ Node → connection point of two branches or more.


→ loop (6) → any closed path. (علم نقطة وأرجع إليها)

→ mesh → any closed that doesn't have another path put ← closed loop or path.

كل mesh هو loop

كل loop هو mesh

Ex:

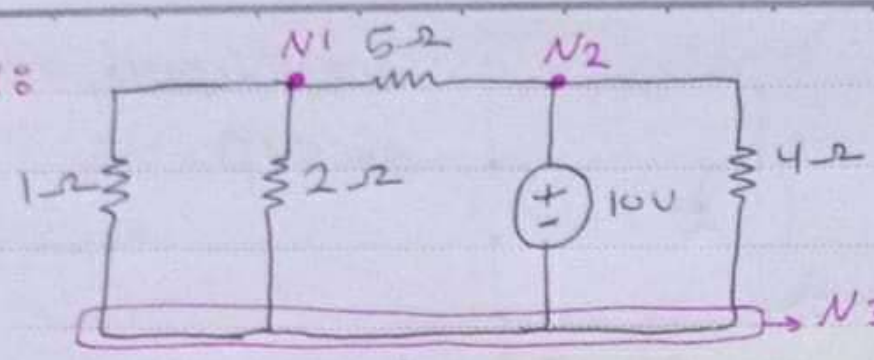


- \* Element = 5
- \* branch = 5
- \* Node = 3 node.

\* loop  $\rightarrow 6$  \* mesh  $\rightarrow 3$

نقطة واحدة.   
 \* يمكن معرفة أي element بقدر الكو N3

Ex:

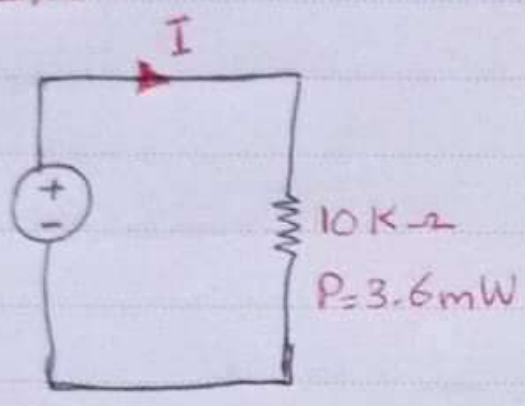


$$P = IV = \frac{V^2}{R} = I^2 R$$

$$V = \sqrt{3.6 \times 10^{-3} \times 10 \times 10^3} = 6 \text{ Volt}$$

$$I = \sqrt{\frac{3.6 \times 10^{-3}}{10 \times 10^3}} = 6 \times 10^{-4} \text{ A}$$

Ex:

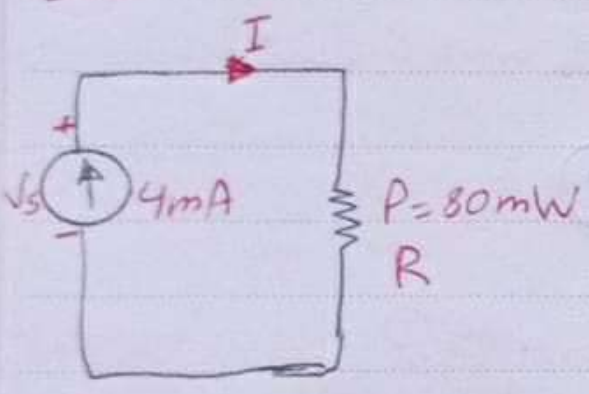

$$P = I^2 R =$$

$$R = \frac{80 \times 10^{-3}}{(4 \times 10^{-3})^2} = 5 \text{ k}\Omega$$

$$V = \sqrt{P R} = \sqrt{80 \times 10^{-3} \times 5 \times 10^3} = 20 \text{ Volt}$$

Ex:

A 100 Watt high bulb is illuminated on for one hour only. How many joules of electrical energy have been used by the lamp.

$$\begin{aligned} \text{Energy} &= \text{Power} \times \text{time} \\ &= 100 \times 60 \times 60 \\ &= 360 \text{ KJ} \end{aligned}$$




Ex: How much energy does a 1200W dishwasher use when it runs for 30 minutes (1800s)?

$$\text{Energy} = \text{Power} \times \text{Time}$$

$$= 1200 \times 1800$$

$$= 2160 \text{ KJ}, 2.16 \text{ MJ}$$

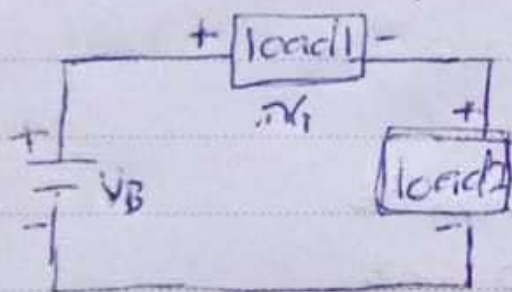Ex: Power dissipated or generated by each element.




$$V_1 = 8V \quad P_B = -V_B \times i = -12 \times 0.1 = -1.2 \text{ W}$$

$$V_2 = 4V \quad P_1 = V_1 \times i = 8 \times 0.1 = 0.8 \text{ W}$$

$$V_2 = 4V \quad P_2 = V_2 \times i = 4 \times 0.1 = 0.4 \text{ W}$$

$$i = 0.1 \text{ A}$$

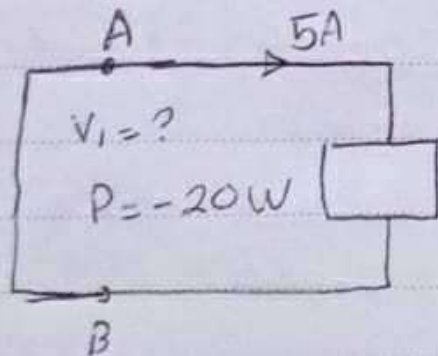
Ex: Determine the unknown voltage or unknown current.



$$P = IV$$

$$V = \frac{P}{I} = \frac{-20}{5} = -4 \text{ volt}$$

$$I = 5$$

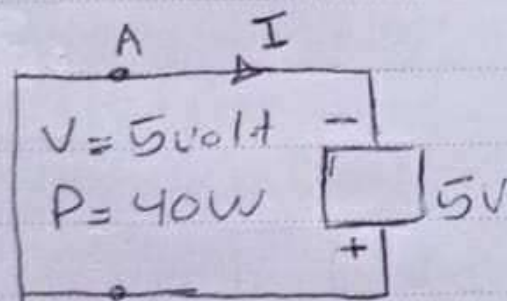

$$P = IV$$

$$I = \frac{P}{V} = \frac{40}{5} = 8 \text{ A}$$


$$V = 5$$

Ex: Calculate the current (i), the conductance (G)

$$V = IR \Rightarrow I = V/R = 30 / 5 \times 10^3 = 6 \times 10^{-3} \text{ Volt}$$


$$G = 1/R \Rightarrow 1 / 5 \times 10^3 = 2 \times 10^{-4} \text{ S}$$
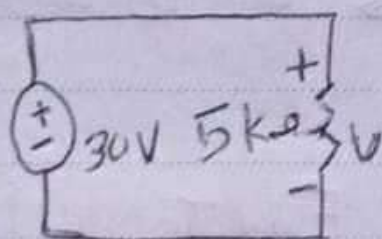
$$P = IV = 30 \times 6 \times 10^{-3} = 0.18 \text{ W}$$





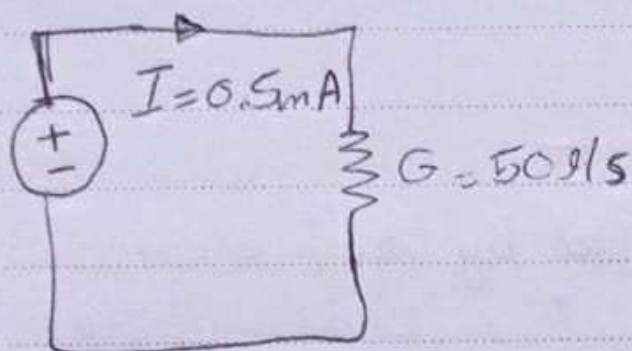Ex: Given the following circuit find, the value of the voltage source and the power absorbed by the R.




$$V = \frac{I}{G} = \frac{0.5 \times 10^{-3}}{50 \times 10^{-6}}$$

$$= 10 \text{ volt}$$

$$P = IV = 10 \times 0.5 \times 10^{-3} = 5 \times 10^{-3} \text{ W}$$

Ex:

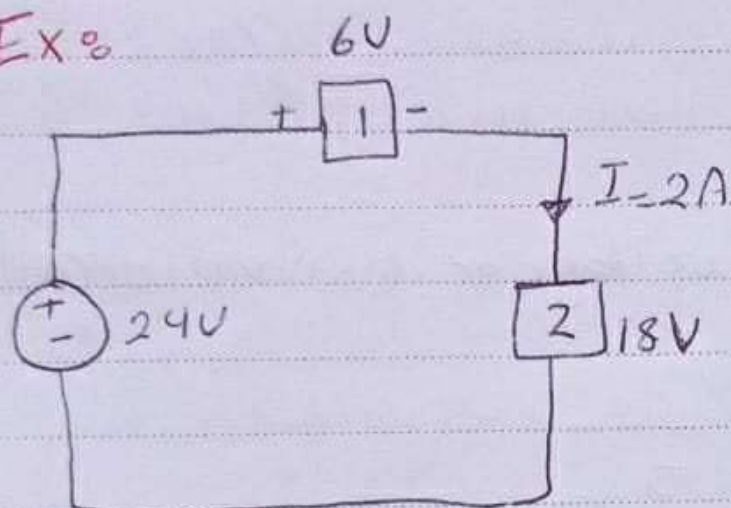

Ex:

$$P = 20 \cos^2 t$$

$$v = 10 \cos t$$

$$P = IV$$

$$I = \frac{P}{V} = \frac{20 \cos^2 t}{10 \cos t} = 2 \cos t$$


$$R = \frac{V}{I} = \frac{10 \cos t}{2 \cos t} = 5 \Omega$$

$$P_a = IV = 2 \times 24 = 48 \text{ W}$$

$$P_1 = IV = 2 \times 6 = 12 \text{ W}$$

$$P_2 = IV = 18 \times 2 = 36 \text{ W}$$

Ex:

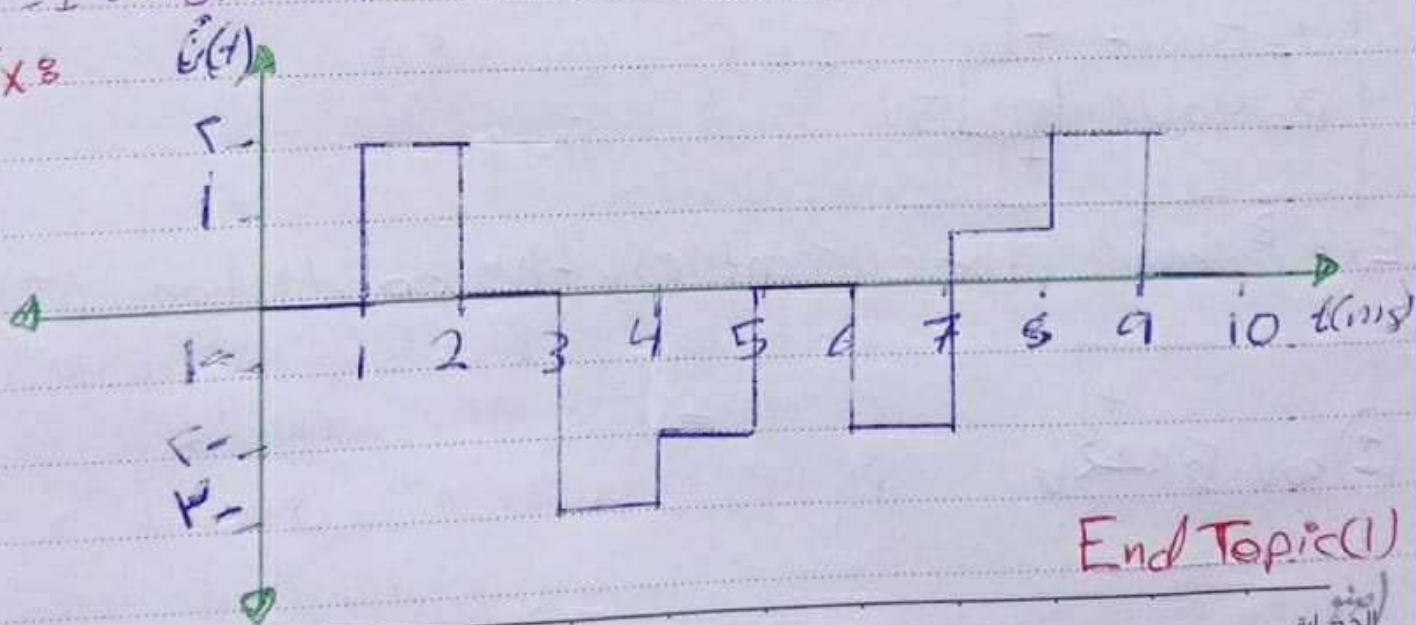

End Topic (1)

## Topic(2)

### 2.4: Kirchof law.


① Kirchof current law (KCL)

② Kirchof voltage law (KVL)

→ KCL is for any node  $\sum I = 0$

$$\sum I_{in} = \sum I_{out}$$

Ex 8 Find  $I_x$ .


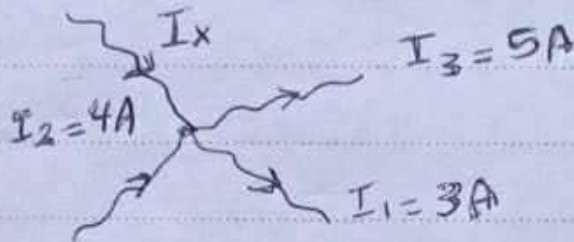


$$I_x + I_2 = I_1 + I_3$$

$$I_x + 4 = 3 + 5$$

$$I_x = 4A$$


Ex 8

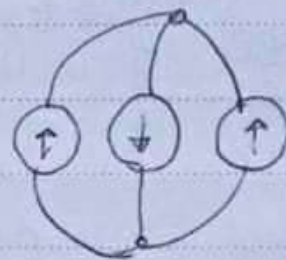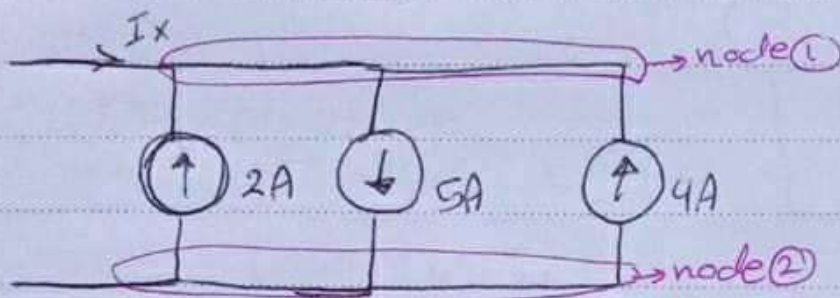

$$I_x + 2 + 4 = 5 \Rightarrow I_x = -1A$$

→ KVL is for any loop (Any closed loop)  $\sum V = 0$

Ex 8

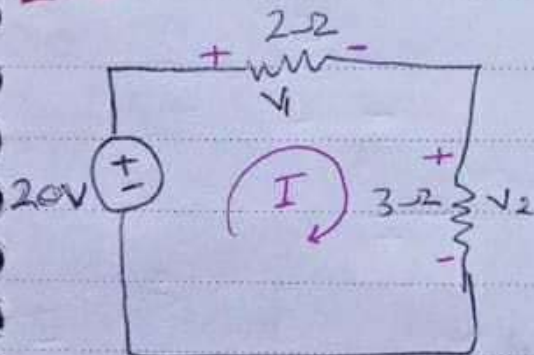

في البطارية، ويخرج من القطب السالب في المقاومة.

① Assigning the current (التيار يخرج من القطب الموجب)

② Assigning the polarity of each voltage

③ Apply KVL.

$$-20 + V_1 + V_2 = 0 \quad V_1 = I \times 2$$

$$-20 + 2I + 3I = 0 \quad V_2 = I \times 3$$

$$I = 4A$$

$$V_1 = 2 \times 4 = 8 \text{ volt}$$


$$V_2 = 3 \times 4 = 12 \text{ volt}$$



2.4


/ /

\* Particle problem (2.5)

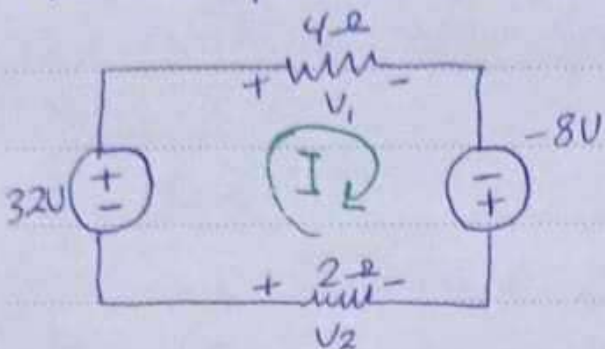

$$\begin{aligned} -32 + V_1 - 8 - V_2 &= 0 & V_1 &= 4 \times 4 \\ V_1 - V_2 &= 24 \text{ volt} & &= 16 \text{ volt} \\ 2 + 4 &= 6 \Omega & V_2 &= 4 \times -2 \\ 24 &= I \times 6 & &= -8 \text{ volt} \\ I &= 4 \text{ A} \end{aligned}$$

particle problem (2.8)

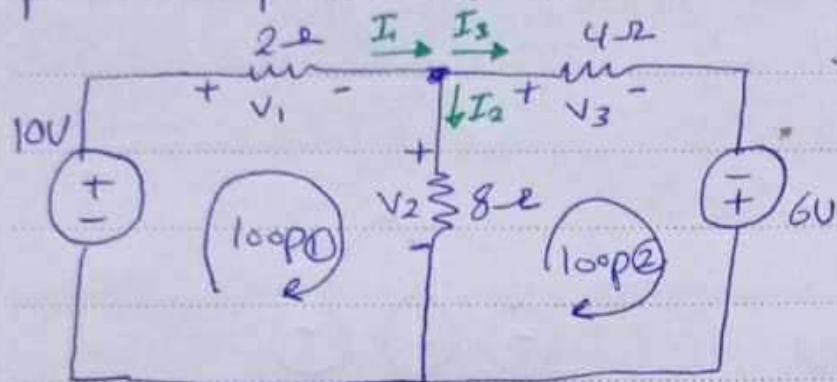

$$I_1 = ? , I_2 = ? , I_3 = ?$$

\* apply KVL at loop ①:

$$-10 + 2I_1 + 8I_2 = 0$$

$$2I_1 + 8I_2 = 10 \quad \text{--- ①}$$

\* apply KVL at loop ②:

$$-8I_2 + 4I_3 - 6 = 0$$

$$-8I_2 + 4I_3 = 6 \quad \text{--- ②}$$

$$I_1 = I_2 + I_3 \quad \text{--- ③}$$

$$I_1 - I_2 - I_3 = 0$$

$$I_1 = 3 \text{ A}$$

$$2(I_2 + I_3) + 8I_2 = 0$$

$$I_2 = 0.5 \text{ A}$$

$$10I_2 + 2I_3 = 0 \quad \text{--- ④}$$

$$I_3 = 2.5 \text{ A}$$

solving equ. ② & ④:



16 / 7 / 2025

\* Series elements have same current. يمر فيها نفس التيار. • التوالي

①  $R_{eq} = R_1 + R_2 + R_3 \dots$

② voltage division  $\Rightarrow V_1 = \frac{R_1}{R_{eq}} \times V$  و  $V_2 = \frac{R_2}{R_{eq}} \times V$   
 لم يطبق فقط على التوالي


\* parallel elements have same voltage. • التوازي يمر فيها نفس الجهد

①  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$  و  $R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2} \Rightarrow$  two resistance

$G_{eq} = G_1 + G_2 + \dots + G_N$

② current division  $\Rightarrow I_1 = \frac{R_2}{R_1 + R_2} I$  و  $I_2 = \frac{R_1}{R_1 + R_2} I$


Particle problem (2.9)

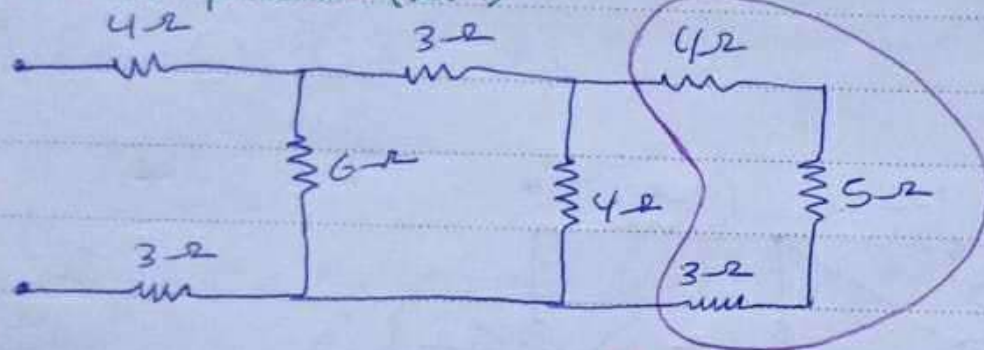


Device 3

① بدأ من اليمين  
 ② الرسم أول بأول


$R_{eq.①} = 4 + 5 + 3 = 12 \Omega$

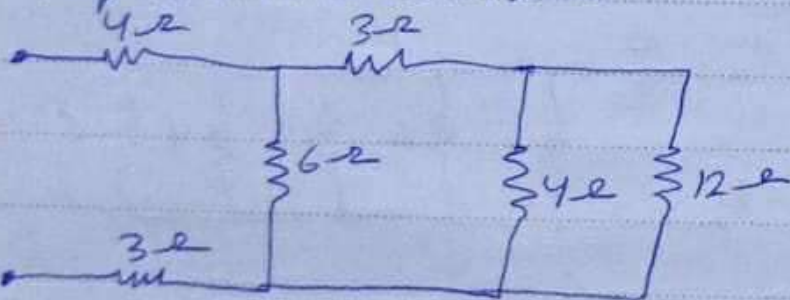

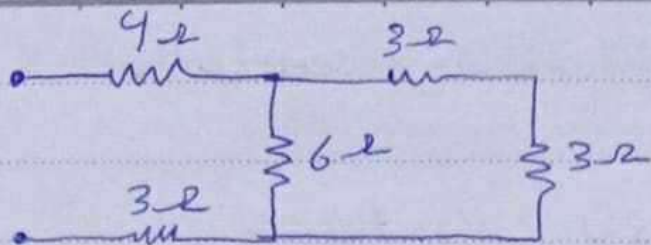
$R_{eq.②} = 12 // 4 = \frac{12 \times 4}{12 + 4} = 3 \Omega$



$$\text{Req. ③} = 3 + 3 = 6 \Omega$$

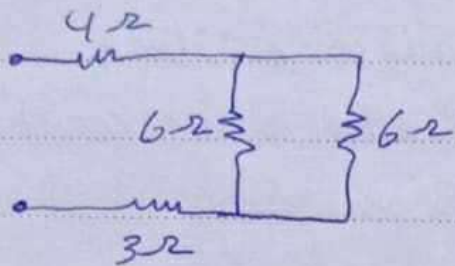

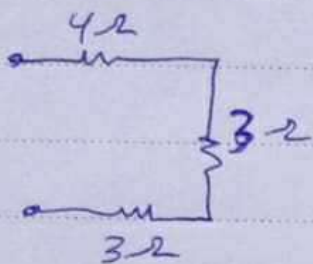
$$\text{Req. ④} = \frac{6 \times 6}{6 + 6} = 3 \Omega$$




$$\text{Req. ⑤} = 4 + 3 + 3 = 10 \Omega$$

Example (2.10)

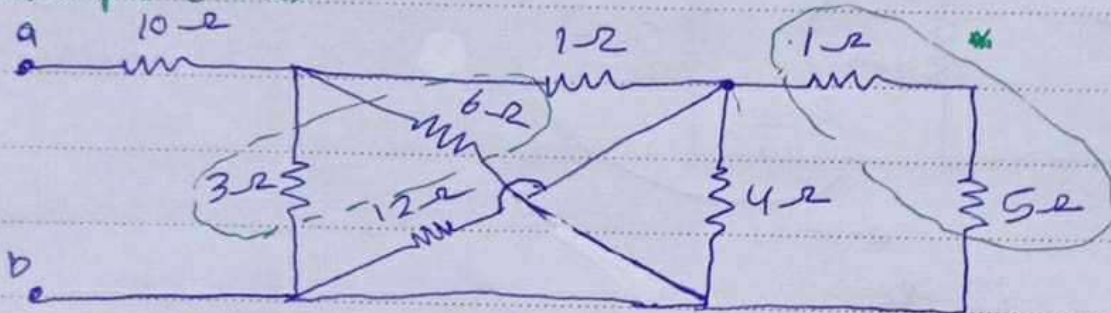


$$\text{Req. ①} = 5 + 1 = 6 \Omega$$

10  $\Omega$

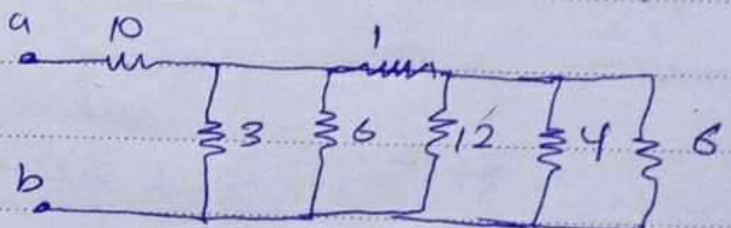




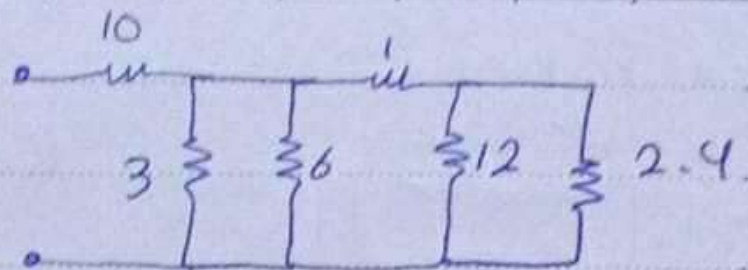
$$\text{Req. (2)} = \frac{6 \times 4}{6 + 4} = 2.4 \Omega$$



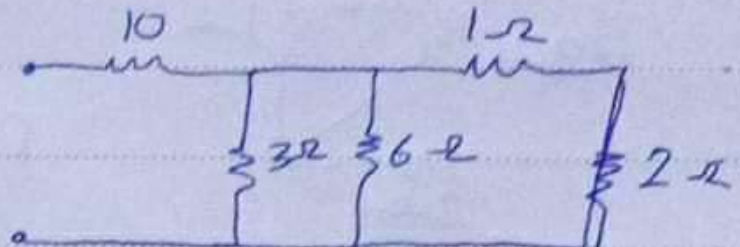
$$\text{Req. (3)} = \frac{2.4 \times 12}{12 + 2.4} = 2 \Omega$$




$$\text{Req. (4)} = 2 + 1 = 3 \Omega$$

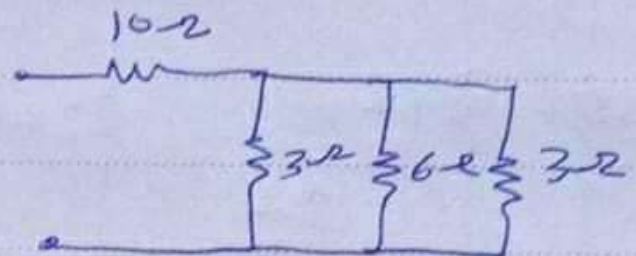
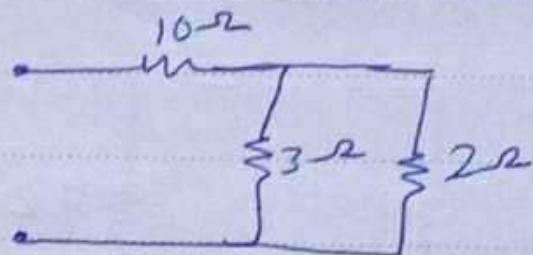
$$\text{Req. (5)} = \frac{3 \times 6}{3 + 6} = 2 \Omega$$



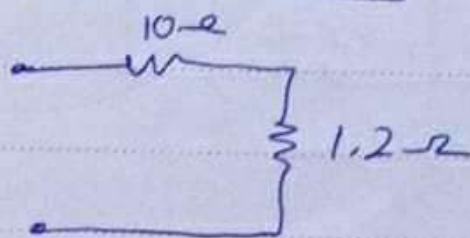
$$\text{Req. (6)} = \frac{2 \times 3}{2 + 3} = 1.2 \Omega$$



$$\text{Req. (7)} = 10 + 1.2 = 11.2 \Omega$$





## Practice Problem (2.10)

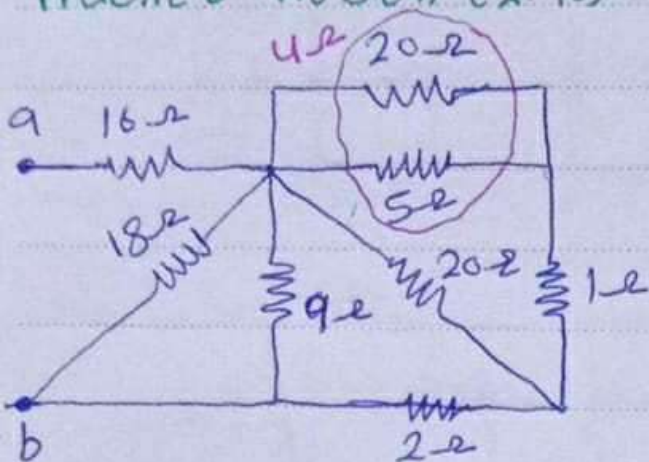

$$\text{Req. ①} = \frac{20 \times 5}{20 + 5} = 4 \Omega$$

$$\text{Req. ②} = 4 + 1 = 5 \Omega$$
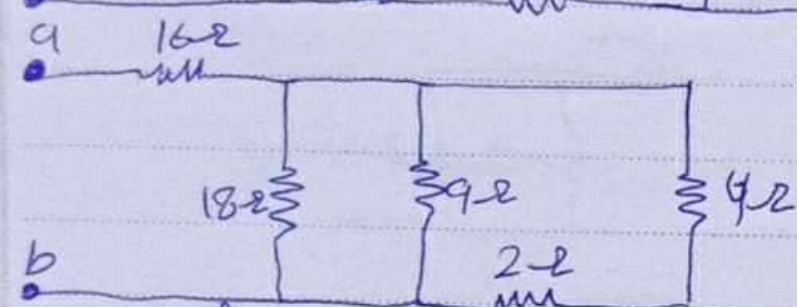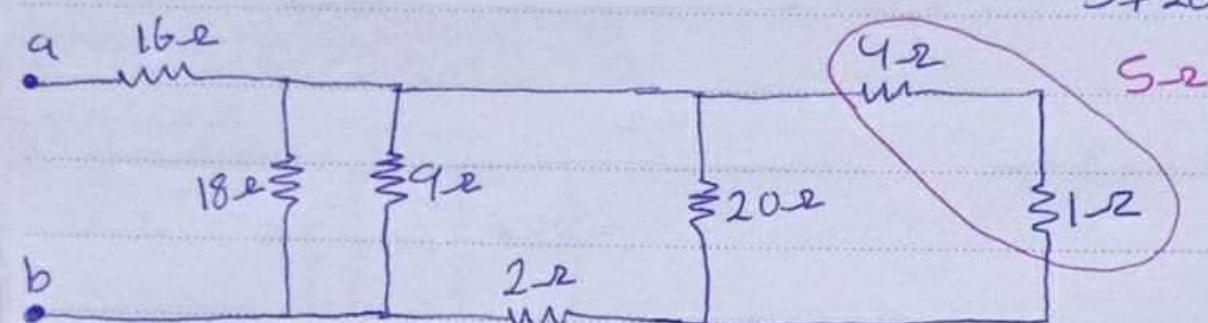
$$\text{Req. ③} = \frac{5 \times 20}{5 + 20} = 4 \Omega$$




$$\text{Req. ④} = 4 + 2 = 6 \Omega$$



$$\text{Req. ⑤} = \frac{6 \times 9}{6 + 9} = 3.6 \Omega$$

$$\text{Req. ⑥} = \frac{3.6 \times 18}{3.6 + 18} = 3 \Omega$$

$$\text{Req. ⑦} = 3 + 16 = 19 \Omega$$

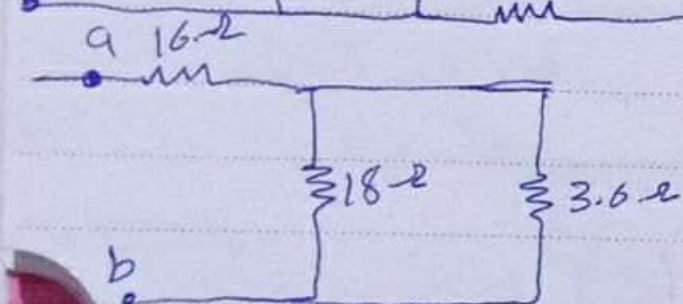

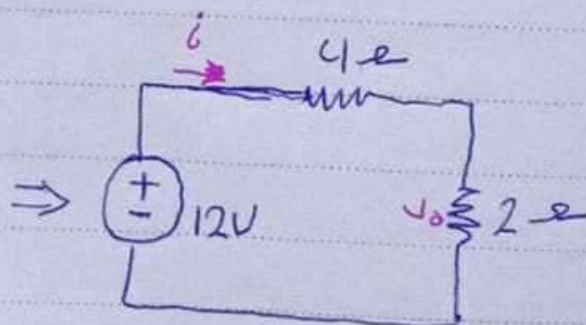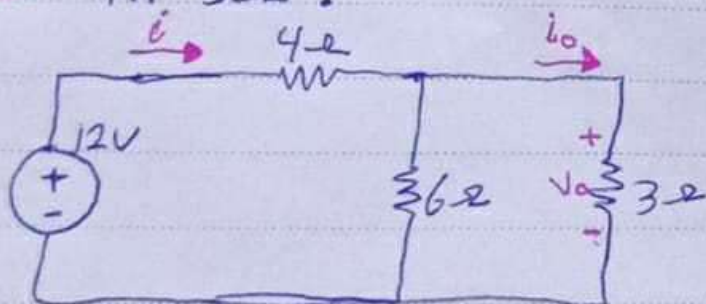Example (2.12): Find  $i_o$  and  $V_o$ . Calculate the power in  $3 \Omega$ .




voltage division  $\Rightarrow V_o = \frac{2 \times 12}{2+4} = 4 \text{ volt.}$

$i = \frac{V}{R_{eq}} = \frac{12}{6} = 2 \text{ A}$

$V_o = I_o R \Rightarrow i_o = \frac{V_o}{R} = \frac{4}{3} \text{ A}$


$P_o = V_o i_o = 4 \times \frac{4}{3} = 5.333 \text{ W}$

Particulate ~~part~~ problem (2.12):

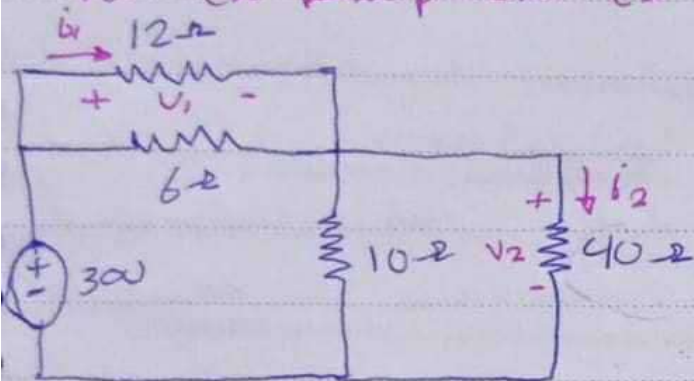

Req. ① =  $\frac{40 \times 10}{40+10} = 8 \Omega$

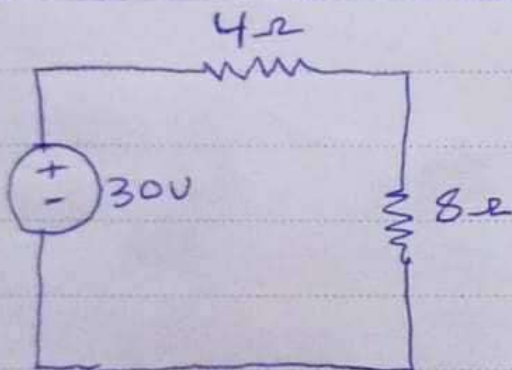Req. ② =  $\frac{12 \times 6}{12+6} = 4 \Omega$



voltage division on series

$V_1 = \frac{30 \times 4}{12} = 10 \text{ volt} \rightarrow \text{same in } 12 \Omega$

$V_2 = \frac{30 \times 8}{12} = 20 \text{ volt} \rightarrow \text{same in } 40 \Omega$

$V = IR \Rightarrow I = V/R$

$i_1 = 10/12 = 0.833 \text{ A}$


$\rightarrow P_1 = i_1 V_1 = 10 \times 0.833 = 8.3 \text{ W}$

$i_2 = 20/40 = 0.5 \text{ A}$

$\rightarrow P_2 = i_2 V_2 = 0.5 \times 20 = 10 \text{ W}$



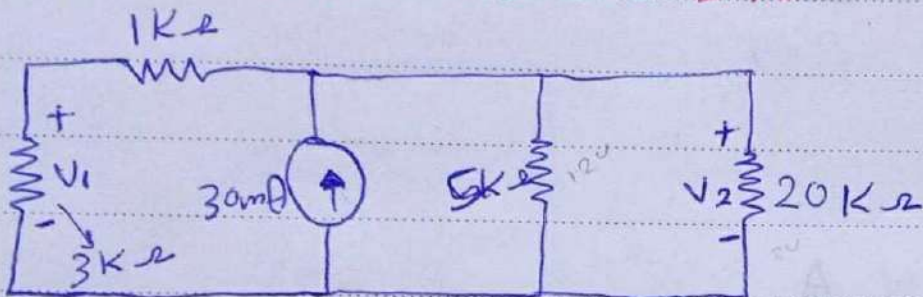
# Practice Problem (2.13) : $\rightarrow 76$



$$\text{Reqd. ①} = \frac{20 \times 5}{20 + 5} = 4k\Omega$$

$$\text{Reqd. ②} = 3 + 1 = 4k\Omega$$

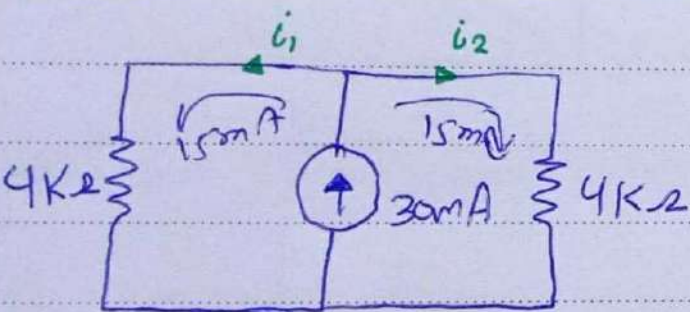

$$i_1 = \frac{30 \times 4}{8} = 15A$$

$$i_2 = \frac{30 \times 4}{8} = 15A$$


$$V_1 = i_1 R = 15 \times 3 = 45V$$

$$V_2 = i_2 R = 15 \times 4 = 60V$$



## Topic (2), Example.

### Example:

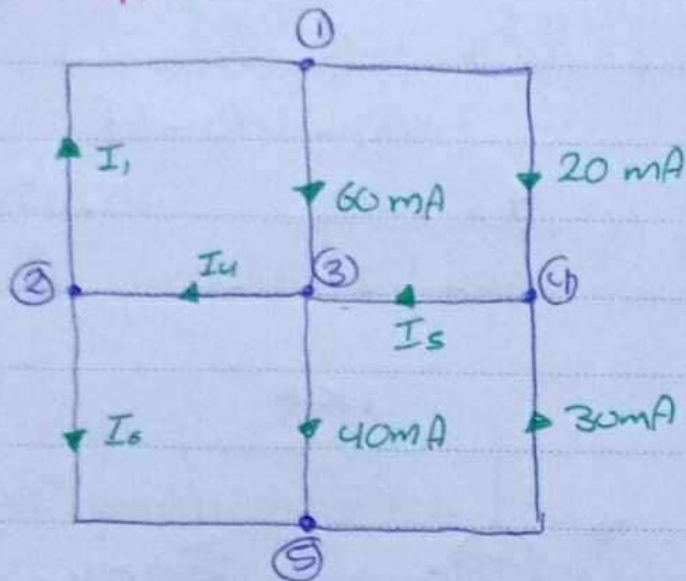


$$I_3 = 50 \text{ mA} = 20 + 30$$

$$I_4 = 60 + 50 - 40 = 70 \text{ mA}$$

$$I_1 = 20 + 60 = 80 \text{ mA}$$

$$I_6 = 70 - 80 = -10 \text{ mA}$$


### Example 8

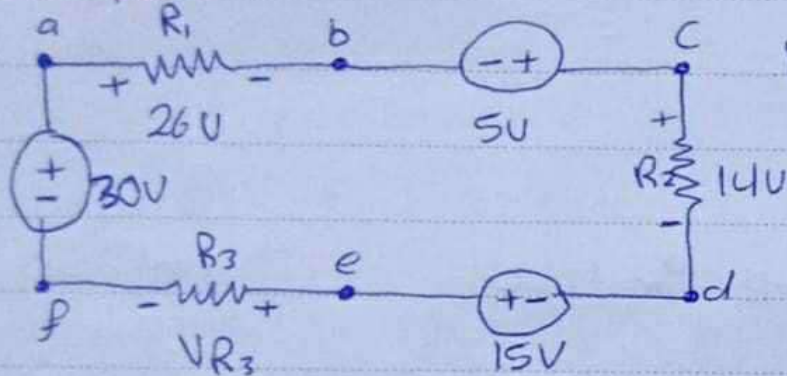

$$\text{KVL} \Rightarrow 26 + 5 + 14 - 15 + VR_3 - 30 = 0$$

$$VR_3 = 10 \text{ volt.}$$

### Example:

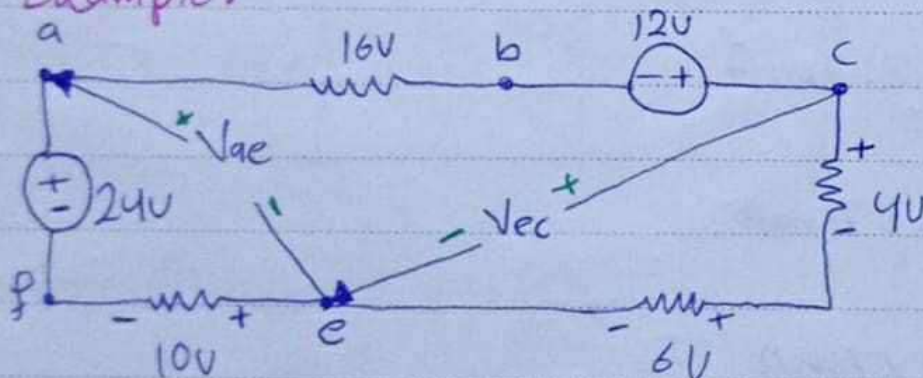


$$\text{KVL} \Rightarrow -24 + V_{ae} + 10 = 0$$

$$V_{ae} = 14 \text{ volt}$$

$$\text{KVL} \Rightarrow 4 + 6 - V_{ec} = 0$$

$$V_{ec} = 10 \text{ volt}$$



Example 2

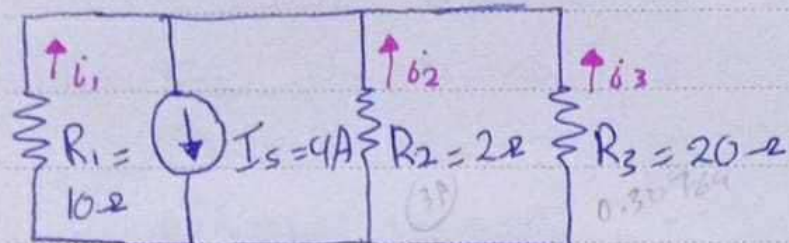

$$i = I_s \times \frac{1/R_1}{1/R_1 + 1/R_2 + 1/R_3}$$

$$i_1 = \frac{4 \times 1/10}{1/10 + 1/2 + 1/20} = 0.6154 \text{ A}$$

Example 3

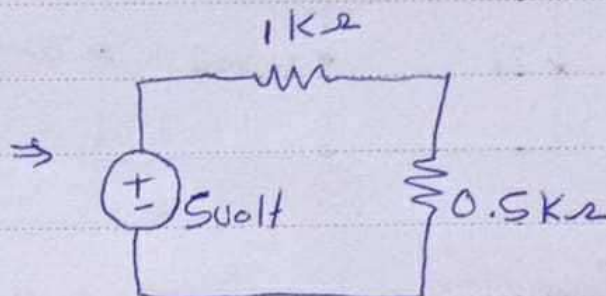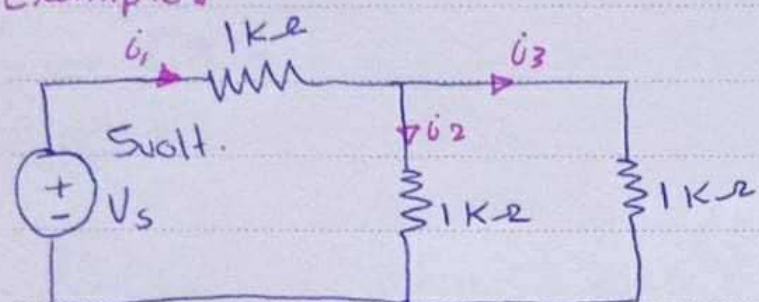

$$V_1 = \frac{5 \times 1}{1.5} = 3.3 \text{ volt}$$

$$V_2 = \frac{5 \times 0.5}{1.5} = 1.67 \text{ volt} \Rightarrow \text{voltage for } 1\text{K}\Omega$$


$$i_1 = \frac{V_1}{R_1} = \frac{3.3}{1 \times 10^3} = 3.3 \text{ mA}$$

$$i_2 = \frac{V_2}{R_2} = \frac{1.67}{1 \times 10^3} = 1.67 \text{ mA}$$

$$i_3 = \frac{V_3}{R_3} = \frac{1.67}{1 \times 10^3} = 1.67 \text{ mA}$$



Example:

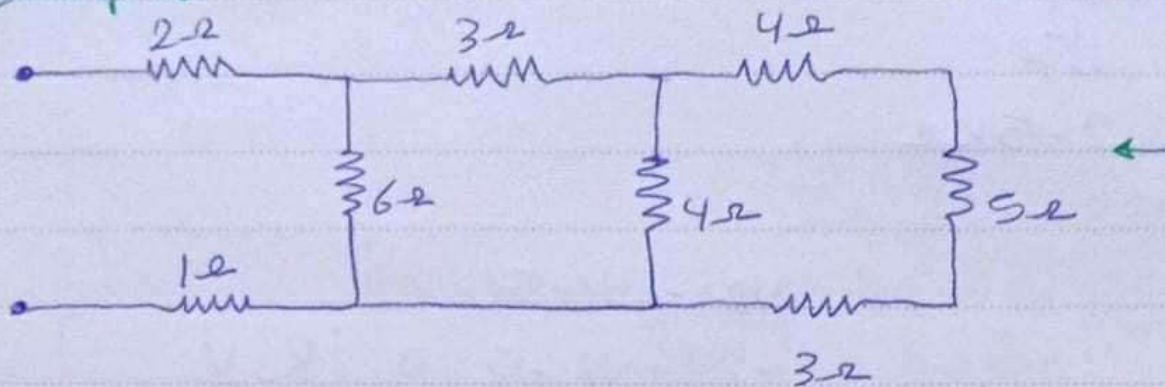

$$\text{Requ. ①} = 4 + 5 + 3 = 12\Omega$$



$$\text{Requ. ②} = \frac{12 \times 4}{12 + 4} = 3\Omega$$

$$\text{Requ. ③} = 3 + 3 = 6\Omega$$


$$\text{Requ. ④} = \frac{6 \times 6}{6 + 6} = 3\Omega$$

$$\text{Requ. ⑤} = 3 + 1 + 2 = 6\Omega$$

3Ω  
Trunk  
⇒

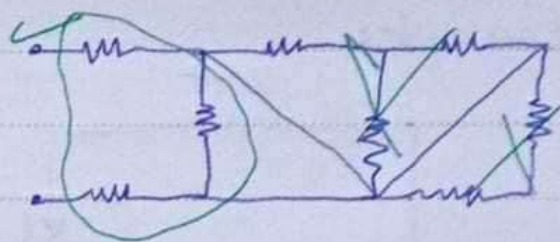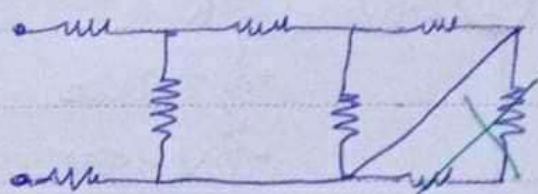

Example 8

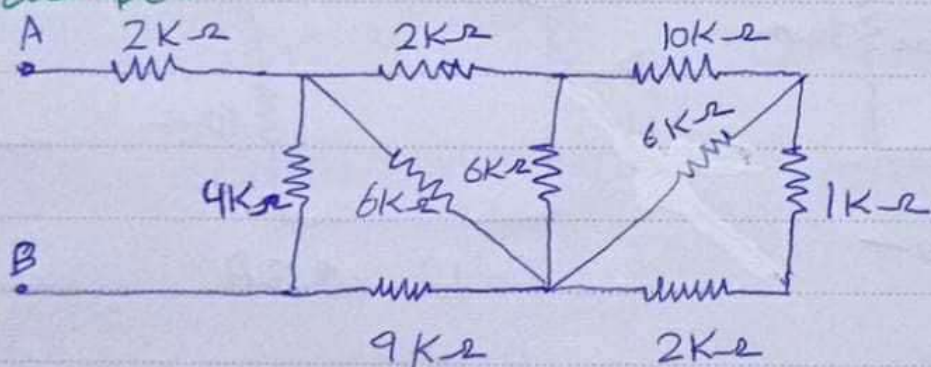

$$\text{Requ. ①} = 2 + 1 = 3K\Omega$$

$$\text{Requ. ②} = \frac{3 \times 6}{6 + 3} = 2K\Omega$$

$$\text{Requ. ③} = 10 + 2 = 12K\Omega$$


$$\text{Requ. ④} = \frac{12 \times 6}{6 + 12} = 4K\Omega$$

$$\text{Requ. ⑤} = 12 + 2 = 14K\Omega$$

$$\text{Requ. ⑥} = \frac{14 \times 6}{6 + 14} = 4.2K\Omega$$

$$\text{Requ. ⑦} = 4.2 + 9 = 13.2K\Omega$$

Requ. ⑧

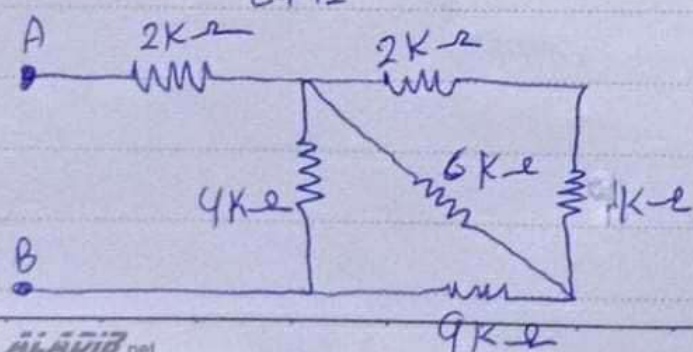




$$R_{\text{equ. 8}} = \frac{12}{\frac{12}{2} \times 4} = 3 \text{ K}\Omega$$

$$R_{\text{equ. 9}} = 3 + 2 = 5 \text{ K}\Omega$$

Examples

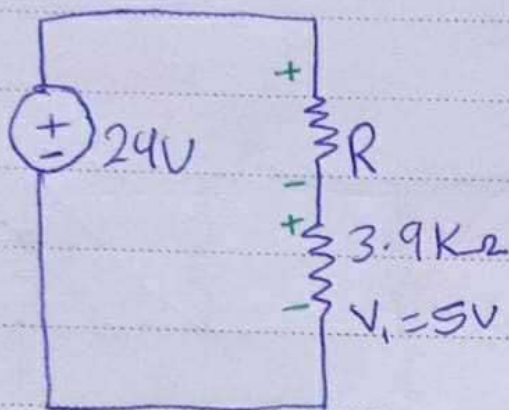

$$V_R = 24 + 5$$

$$-24 + V_R + 5 = 0$$

$$V_R = 19 \text{ V}$$



$$I = \frac{5}{3.9} = 1.3 \text{ A}$$

$$R = \frac{V}{I}$$

$$= \frac{19}{1.3}$$

$$= 14.6 \text{ K}\Omega$$

Example:

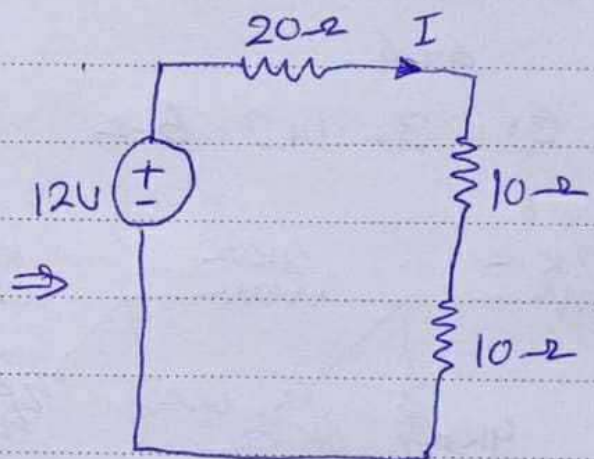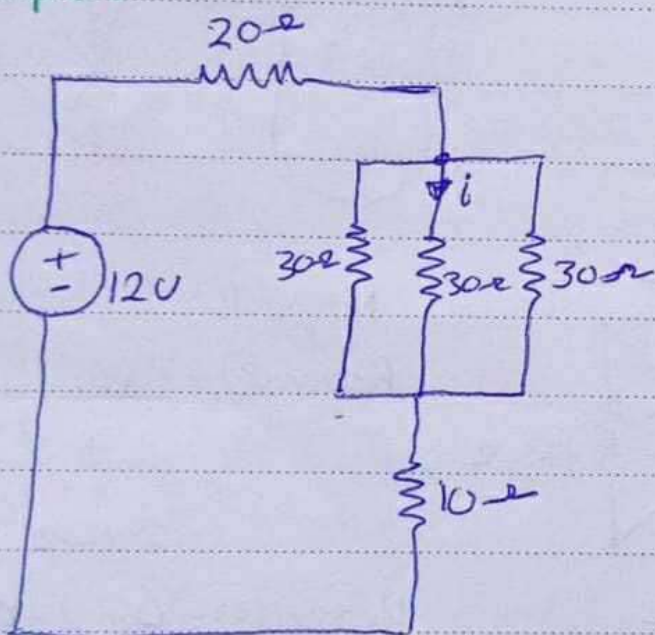


$$I = \frac{12}{10 + 10 + 20} = 0.3 \text{ A}$$

$$i = \frac{0.3}{3} = 0.1 \text{ A}$$



Example:

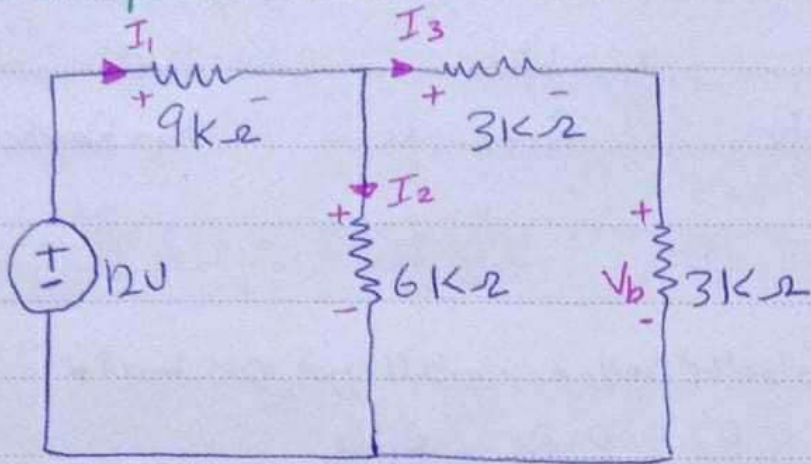

KVL loop ①:

$$-12 + 9I_1 + 6I_2 = 0 \rightarrow \textcircled{1}$$

KVL loop ②:

$$3I_3 + 3I_3 - 6I_2 = 0$$

$$-6I_2 + 6I_3 = 0 \rightarrow \textcircled{2}$$

nodes

$$I_1 = I_2 + I_3$$

$$I_1 - I_2 + I_3 = 0 \rightarrow \textcircled{3}$$

$$I_1 = 1A \quad I_2 = 0.5A \quad I_3 = 0.5A$$


$$V_b = IR = 0.5 \times 3 = 1.5 \text{ volt.}$$



## Topic (2) $\Delta$ to Y connection

17/Jul/2025


\* From  $\Delta$  to Y  $\Rightarrow$

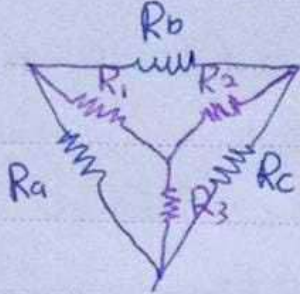

المسطح ناتج ضرب المقاومتين المتجاورتين مقادير  $Y$  والمقام مجموع المقاومات

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}, \quad R_2 = \frac{R_b R_c}{R_a + R_b + R_c}, \quad R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$

\* From Y to  $\Delta \Rightarrow$

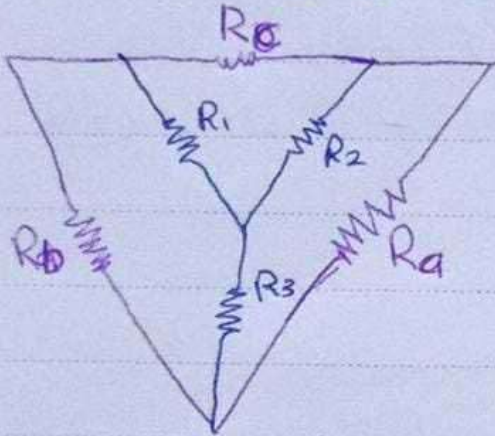

المسطح ناتج ضرب المقاومات  $\Delta$  والمقام مجموع المقاومات البعيدة


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

\* In case  $R_1 = R_2 = R_3 \rightarrow R_Y = \frac{R_\Delta}{3}, R_\Delta = 3 R_Y$

Example :

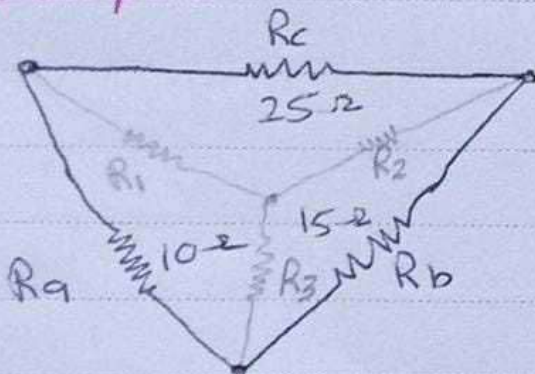


$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{25 \times 10}{25 + 10 + 15} = 5 \Omega$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{15 \times 25}{25 + 10 + 15} = 7.5 \Omega$$

$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c} = \frac{15 \times 10}{25 + 10 + 15} = 3 \Omega$$



### Particle Problem (2.14):

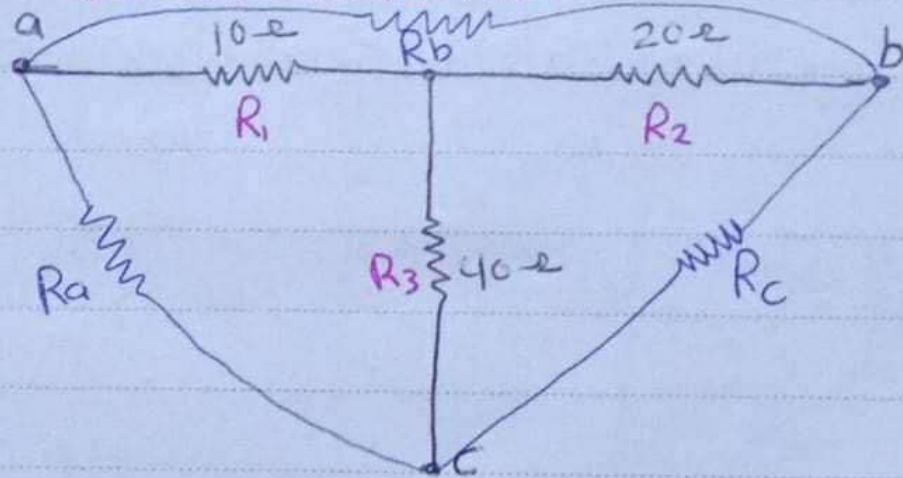


$$R_a = \frac{(10 \times 40) + (10 \times 20) + (20 \times 40)}{20}$$

$$= 70 \Omega$$

$$R_b = \frac{1400}{40} = 35 \Omega$$

$$R_c = \frac{1400}{10} = 140 \Omega$$

### Example (12.15):

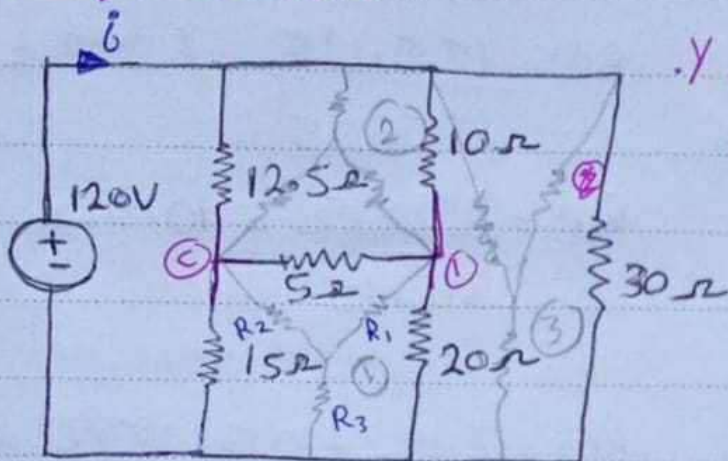


طرق الحل  
طريقة تحويل من  $\Delta$  إلى  $Y$   
طريقة تحويل من  $Y$  إلى  $\Delta$

$$R_1 = \frac{20 \times 5}{20 + 15 + 5} = 2.5 \Omega$$

$$R_2 = \frac{5 \times 15}{20 + 15 + 5} = 1.875 \Omega$$
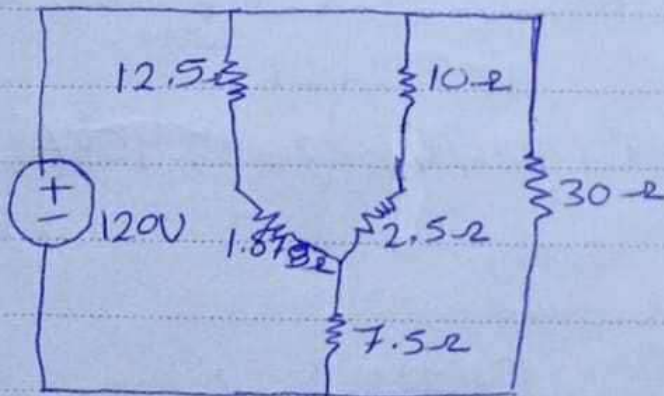
$$R_3 = \frac{20 \times 15}{20 + 15 + 5} = 7.5 \Omega$$



$$R_{eq(1)} = 2.5 + 10 = 12.5 \Omega$$

$$R_{eq(2)} = 12.5 + 1.875 = 14.375 \Omega$$

$$R_{eq(3)} = \frac{12.5 \times 14.375}{12.5 + 14.375} = 6.686 \Omega$$

$$R_{eq(4)} = 6.686 + 7.5 = 14.186 \Omega$$

$$R_{eq(5)} = \frac{14.186 \times 30}{14.186 + 30} = 9.63 \Omega$$

$$I = \frac{V}{R} = \frac{120}{9.63} = 12.46 A$$




Convert Y to Δ

$$R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1} = \frac{(10 \times 20) + (20 \times 5) + (5 \times 10)}{10} = \frac{350}{10} = 35 \Omega$$

$$R_b = \frac{350}{20} = 17.5 \Omega$$

$$R_c = \frac{350}{5} = 70 \Omega$$

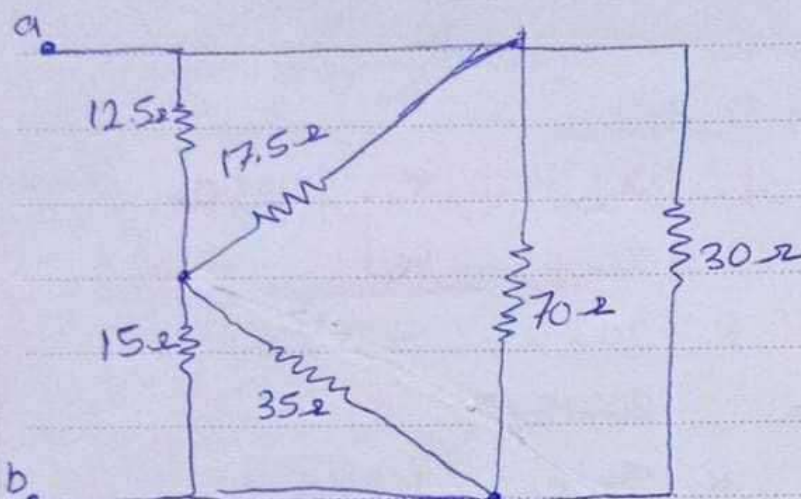

$$R_{(1)} = \frac{30 \times 70}{30 + 70} = 21 \Omega$$


$$R_{(2)} = \frac{17.5 \times 12.5}{17.5 + 12.5} = 7.292 \Omega$$

$$R_{(3)} = \frac{35 \times 15}{35 + 15} = 10.5 \Omega$$

$$R_{(4)} = 7.292 + 10.5 = 17.792 \Omega$$


$$R_{(5)} = \frac{17.792 \times 21}{17.792 + 21} = 9.632 \Omega$$

$$I = 120 / 9.632 = 12.458 \text{ A}$$

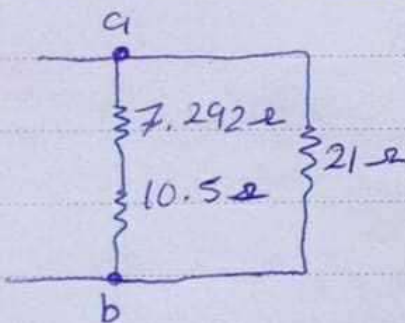

مثالين السيرات

Ex(1) :

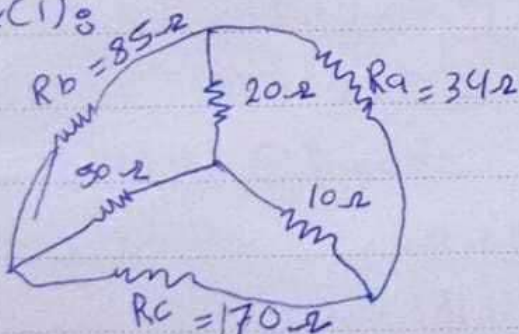

$$R_3 = \frac{144}{6}$$

$$= 24 \text{ K}\Omega$$

Ex(2) : Y → Δ


$$R_1 = \frac{(6 \times 1) + (4 \times 12) + (12 \times 7)}{4}$$

$$= 36 \text{ K}\Omega$$

$$R_2 = \frac{144}{12} = 12 \text{ K}\Omega$$



# Practice Problem (2.15)

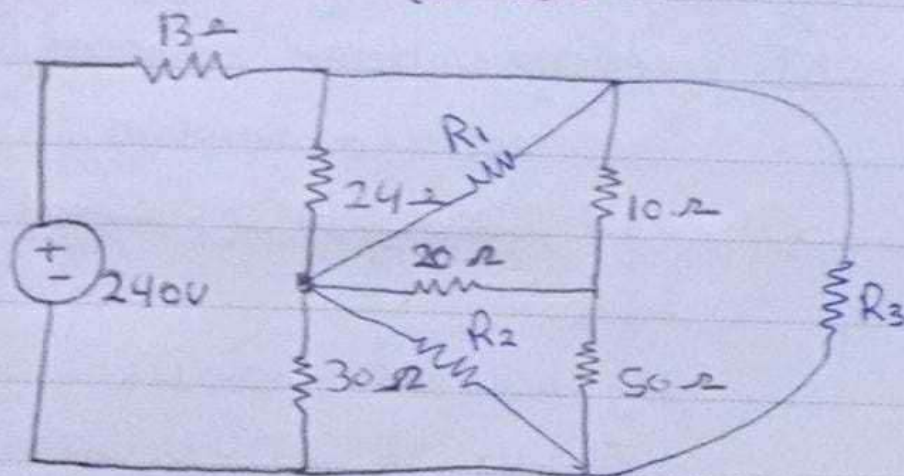


$$R_1 = (10 \times 50) + (50 \times 20) + (10 \times 20) / 50 =$$

$$= 1700 / 50 = 34 \Omega$$

$$R_2 = 1700 / 10 = 170 \Omega$$

$$R_3 = 1700 / 85 = 19.9 \Omega$$

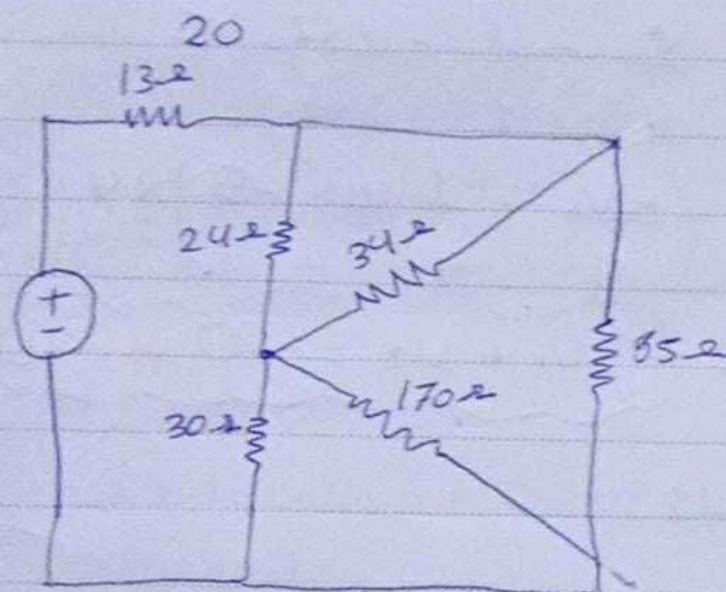


$$R_{(1)} = \frac{34 \times 24}{34 + 24} = 14 \Omega$$

$$R_{(2)} = \frac{30 \times 170}{30 + 170} = 25.5 \Omega$$


$$R_{(3)} = 25.5 + 14 = 39.5 \Omega$$

$$R_{(4)} = \frac{85 \times 39.5}{85 + 39.5} = 27 \Omega$$

$$R_{(5)} = 27 + 13 = 40 \Omega$$

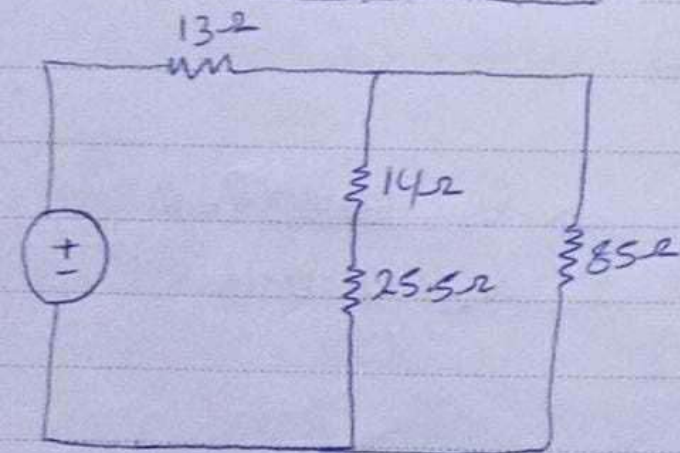

$$I = \frac{240}{40} = 6 \text{ A}$$

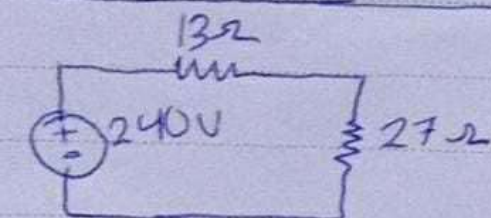

# *Chapter 3*



CH3

## Nodal analysis


\* we are interested in finding the node voltage.

→ Nodal analysis for CKTs with no voltage sources.

→ " " " " " voltage sources.

\* عند فرض الاتجاه للتيار القطب الموجب عنده جهة أكبر من القطب السالب

Example (3.1) :

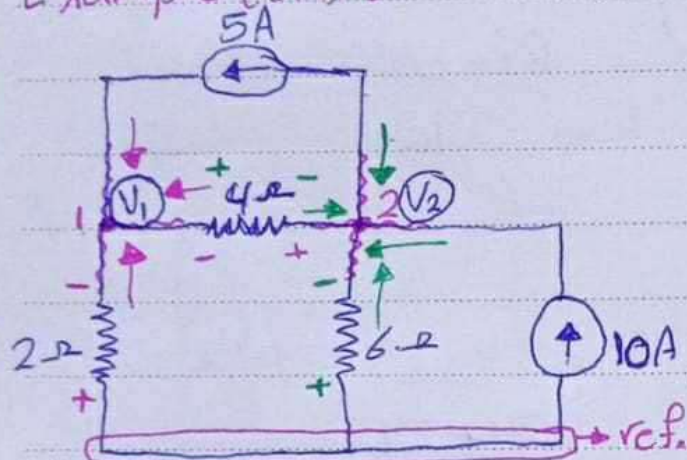

apply KCL at node ① :

$$5 + \frac{V_2 - V_1}{4} + 0 - \frac{V_1}{2} = 0$$

$$\frac{V_2}{4} - \frac{V_1}{4} - \frac{V_1 \times 2}{2 \times 2} = -5$$

$$\left( \frac{-3V_1}{4} + \frac{1}{4} V_2 = -5 \right) \times 4$$

\* KCL at node ② :

$$-5 + 10 + \frac{V_1 - V_2}{4} + 0 - \frac{V_2}{6} = 0$$

$$-3V_1 + V_2 = -20 \quad \text{--- (1)}$$

$$\left( \frac{1}{4} V_1 - \frac{10}{24} V_2 = -5 \right) \times 12$$

$$-3V_1 + 5V_2 = 60 \quad \text{--- (2)}$$


$$\begin{bmatrix} -3 & 1 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -20 \\ 60 \end{bmatrix}$$

$$\Rightarrow V_1 = 13.33 \text{ volt}$$

$$V_2 = 20 \text{ volt.}$$



Example (3.2):

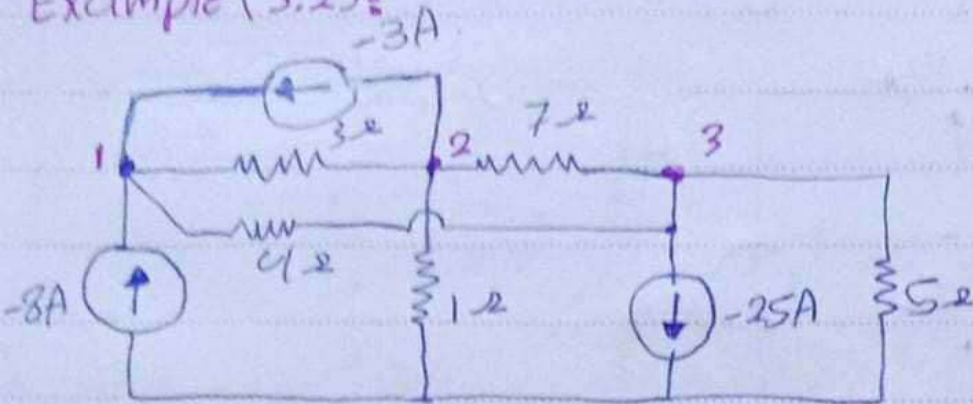

at node ①:

$$\left( -3 + -8 + \frac{V_2 - V_1}{3} + \frac{V_3 - V_1}{4} = 0 \right) \times 12$$

$$-\frac{V_1}{3} - \frac{V_1}{4} + \frac{V_2}{3} + \frac{V_3}{4} = 11 \Rightarrow -0.583V_1 - 0.333V_2 + 0.25V_3 = 11 \quad \text{--- (1)}$$

$$-7V_1 + 4V_2 + 3V_3 = 132 \quad \text{--- (1)}$$

at node ②:

$$3 + \frac{V_1 - V_2}{3} + 0 - \frac{V_2}{1} + \frac{V_3 - V_2}{7} = 0$$


$$0.333V_1 + 1.476V_2 + 0.1429V_3 = 3 \quad \text{--- (2)}$$

at node ③:

$$25 + 0 - \frac{V_3}{5} + \frac{V_2 - V_3}{7} + \frac{V_1 - V_3}{4} = 0$$

$$0.25V_1 + 0.1429V_2 + 0.5929V_3 = -25 \quad \text{--- (3)}$$

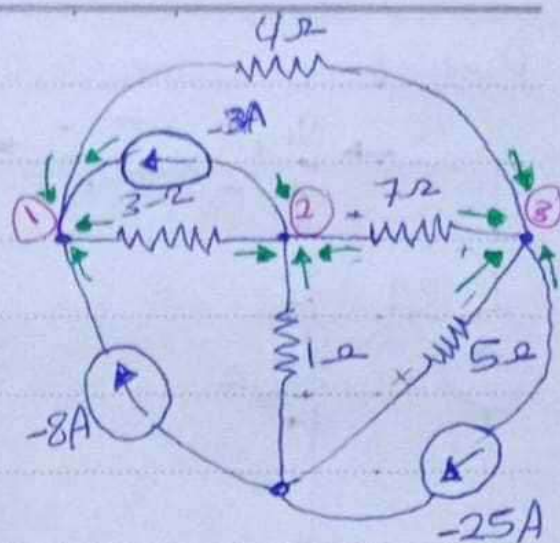
$$V_1 = 5.4 \text{ volt} \quad V_2 = 7.7 \text{ volt} \quad V_3 = 46.3 \text{ volt.}$$





Particle problem (3.1)s
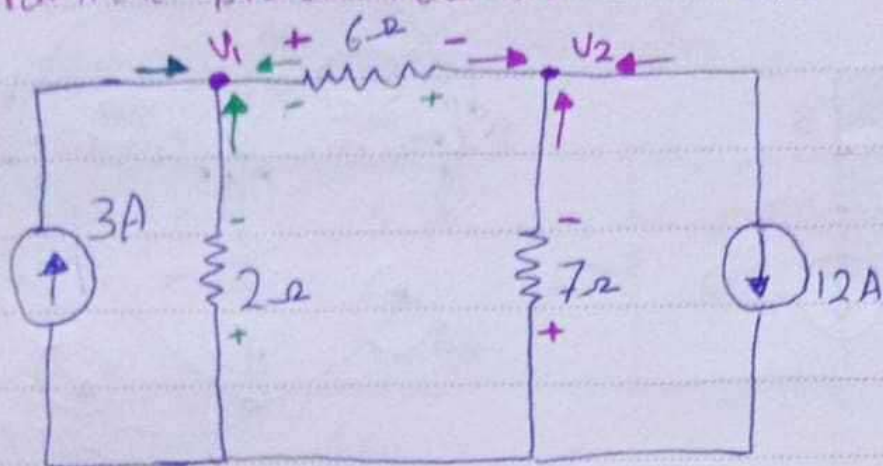
$$V_1 = -6 \text{ volt}, V_2 = -42 \text{ volt}$$



\* at node ① KCL:

$$3 + \frac{0 - V_1}{2} + \frac{V_2 - V_1}{6} = 0$$

$$\left( -\frac{V_1}{2} - \frac{V_1}{6} + \frac{V_2}{6} = -3 \right) \times 6$$

$$3V_1 + V_1 - V_2 = 18 \quad \text{--- (1)}$$

$$4V_1 - V_2 = 18 \quad \text{--- (1)}$$

at node ② KCL:

$$-12 + \frac{0 - V_2}{7} + \frac{V_1 - V_2}{6} = 0$$

$$\left( \frac{V_1}{6} - \frac{V_2}{6} - \frac{V_2}{7} = 12 \right) \times 42$$

$$7V_1 - 7V_2 - 6V_2 = 288 \text{ } 504$$


$$7V_1 - 13V_2 = 288 \text{ } 504 \quad \text{--- (2)}$$

$$V_1 = -6 \text{ volt}$$

$$V_2 = -42 \text{ volt}$$

# Supernode

Ex:

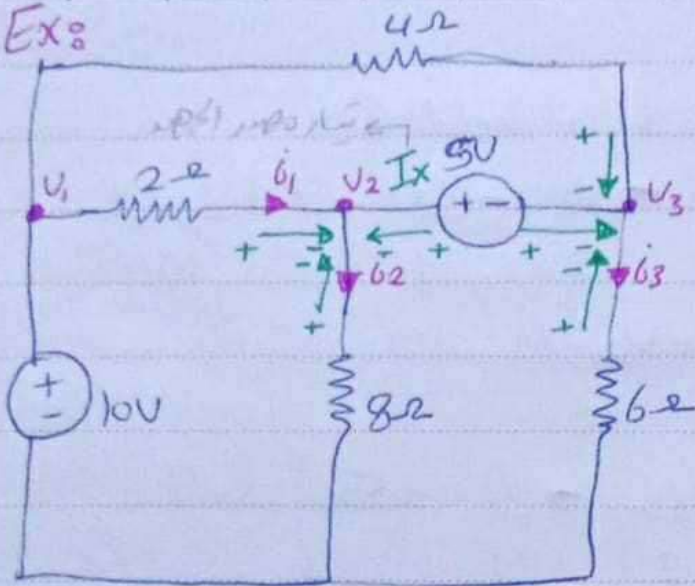

Case 1: If a voltage source is connected between the reference node and a nonreference node, voltage equal the voltage source

Case 2: If the voltage source (dependent or independent) is connected between two nonreference nodes, called **supernode**

case(1)  $\Rightarrow V_1 = 10 \text{ volt}$

case(2)  $\Rightarrow V_2 - V_3 = 5 \text{ volt} \Rightarrow V_2 = 5 + V_3 \Rightarrow V_2 = 5 - 5.84 = -0.84$

apply KCL node ①:

$$\frac{10 - V_2}{2} + \frac{0 - V_2}{8} + I_x = 0$$

apply KCL node ②:

$$\frac{10 - V_3}{4} + \frac{-V_3}{6} - I_x = 0$$

و شانه آن را خلاص من (I<sub>x</sub>) جمع المعادلتين

$$\frac{10 - V_2}{2} - \frac{V_2}{8} + \frac{10 - V_3}{4} - \frac{V_3}{6} = 0$$


$$\frac{10 - 5 - V_3}{2} - \frac{5 + V_3}{8} + \frac{10 - V_3}{4} - \frac{V_3}{6} = 0$$

$$\frac{5}{2} - \frac{V_3}{2} - \frac{5}{8} + \frac{V_3}{8} + \frac{10}{4} - \frac{V_3}{4} - \frac{V_3}{6} = 0$$

$$\frac{-19}{24} V_3 = \frac{37}{8} \Rightarrow V_3 = -5.84 \text{ volt}$$



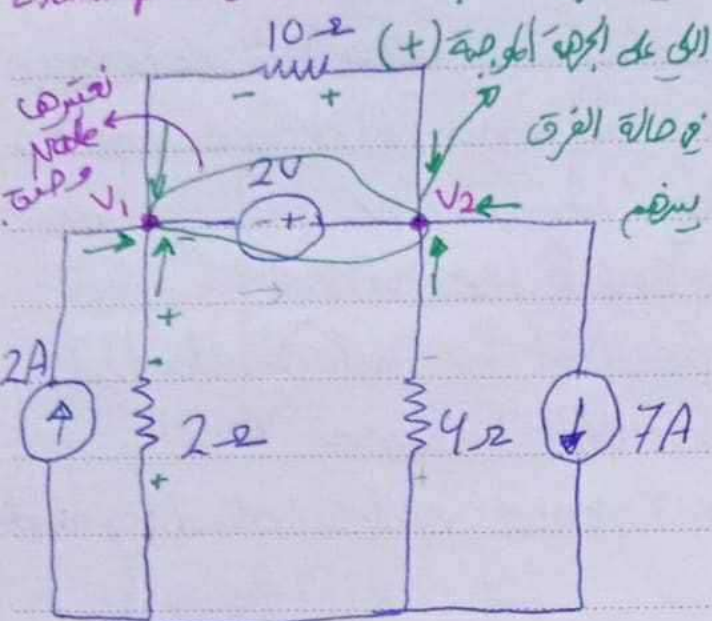Example 3.3: النقطة على المحاور السالبة (-)



super nodes

$$V_2 - V_1 = 2 \rightarrow V_2 = V_1 + 2 \quad \text{--- ②}$$

KCl at node ①:

$$\frac{2 + V_1}{2} - \frac{V_2}{4} = -7 + \frac{V_1 - V_3}{10}$$

$$\frac{+V_2 - V_1}{10} = 0$$

$$\left( \frac{V_1}{2} + \frac{V_2}{4} = 5 \right) \quad x-4$$

$$2V_1 + V_2 = -20 \quad \text{--- (1)}$$

$$\rightarrow V_1 = -7.333 \text{ volt}$$

$$\hookrightarrow V_2 = -5.333 \text{ volt}$$



## / /

- ② " " " " " " "


$$I_3 = I_1 - I_2 = 1 - 1 = 0 \text{ A}$$

⑤ تحديد *plenty* على المقامات.

الحضارة



P.P(3.5)

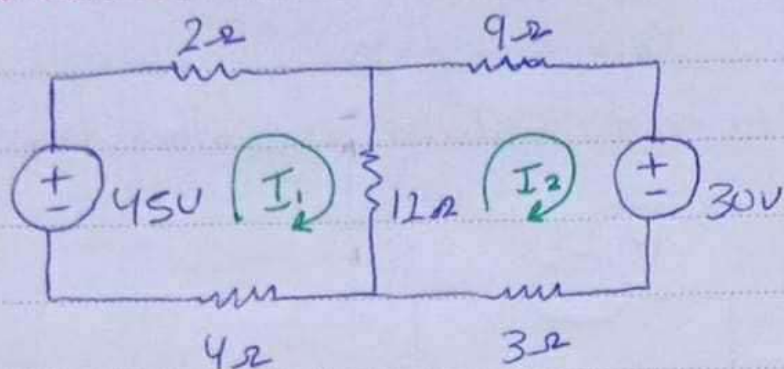

KVL at mesh ①:

$$-45 + 2I_1 + 12(I_1 - I_2) + 4I_1 = 0$$

$$2I_1 + 12I_1 - 12I_2 + 4I_1 = 45$$

$$18I_1 - 12I_2 = 45 \quad \text{--- (1)}$$

KVL at mesh ②:

$$12(I_2 - I_1) + 9I_2 + 30 + 3I_2 = 0$$


$$12I_2 - 12I_1 + 9I_2 + 3I_2 = -30$$

$$-12I_1 + 24I_2 = -30 \quad \text{--- (2)}$$

$$I_1 = 2.5A$$

$$I_2 = 0$$

Ex 8

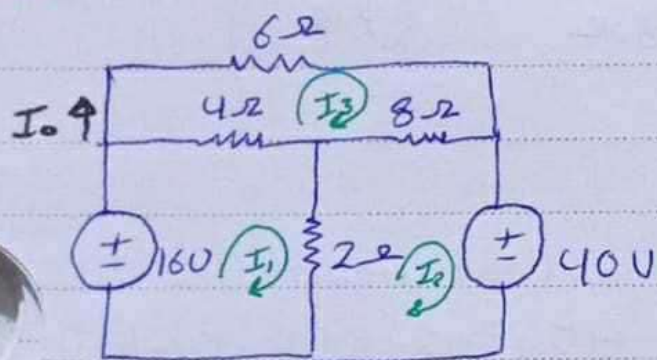

$$I_1 = 3A$$

$$I_2 = -2.1A$$

$$I_3 = 1.61A$$

$$I_0 = 3 - 1.61 = 1.39A$$

KVL at mesh ①:

$$-16 + 4(I_1 - I_3) + 2(I_1 - I_2) = 0$$

$$4I_1 + 2I_1 - 2I_2 - 4I_3 = 16$$

$$6I_1 - 2I_2 - 4I_3 = 16 \quad \text{--- (1)}$$

KVL at mesh ②:

$$2(I_2 - I_1) + 8(I_2 - I_3) + 40 = 0$$

$$2I_2 + 8I_2 - 2I_1 - 8I_3 = -40$$

$$-2I_1 + 10I_2 - 8I_3 = -40 \quad \text{--- (2)}$$

KVL at mesh ③:

$$6I_3 + 4(I_3 - I_1) + 8(I_3 - I_2) = 0$$


$$-4I_1 + 8I_2 + 6I_3 + 4I_3 + 8I_3 = 0$$

$$-4I_1 + 8I_2 + 18I_3 = 0 \quad \text{--- (3)}$$


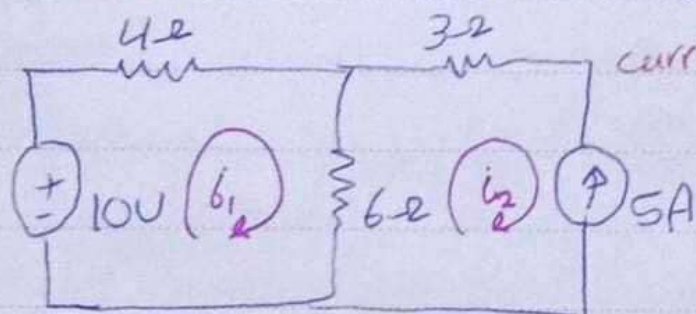
# Mesh analysis with current source.


Case 1: when a current source exists only in one mesh



current source في mesh على KVL

$$i_2 = -5A$$

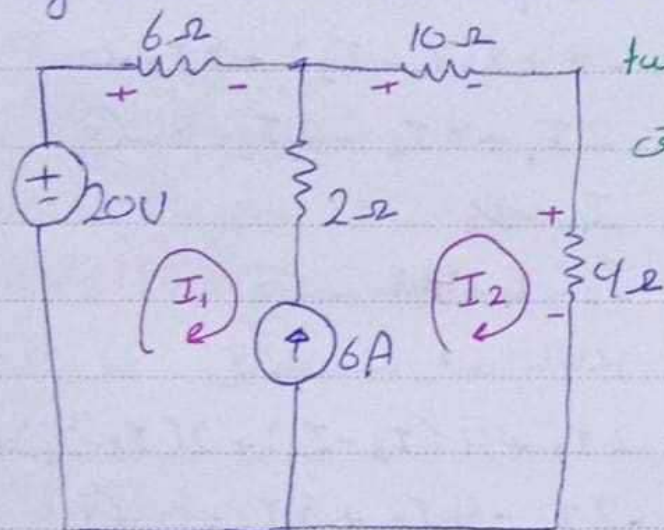Case 2: when a current source exists between two meshes:  
We create a **supermesh** by excluding the current source and any elements connected in series with it.




في حالة وجود current source بين two meshes

اعتبر الـ two meshes عبارة عن one mesh ويطبق KVL.

$$-20 + 6I_1 + 10I_2 + 4I_2 = 0$$

$$I_1 - I_2 = 6$$

Ex:

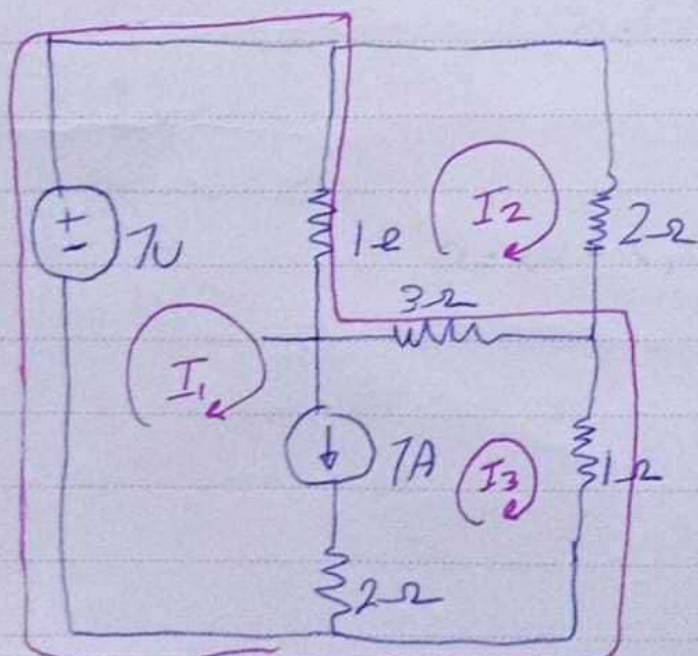

طريقتين للحل:

الطريقة الأولى: أخرجنا  $V_x$  للـ current source و  
اعل KVL للـ mesh ② و ③ وأطلع معادلتين  
وأقلع من  $V_x$ .

الطريقة الثانية: Super mesh at ① و ③:

$$-7 + 1(I_1 - I_2) + 3(I_3 - I_2) + 1I_3 = 0$$

$$I_1 - 4I_2 + 4I_3 = 7 \dots ①$$



mesh 2:

$$1(I_2 - I_1) + 2I_2 + 3(I_2 - I_3) = 0$$

$$-I_1 + 6I_2 - 3I_3 = 0 \quad \text{--- (2)}$$


Super mesh:  $I_1 - I_3 = 7 \quad \text{--- (3)}$

$$I_1 = 9A$$

$$I_2 = 2.5A$$

$$I_3 = 2A$$

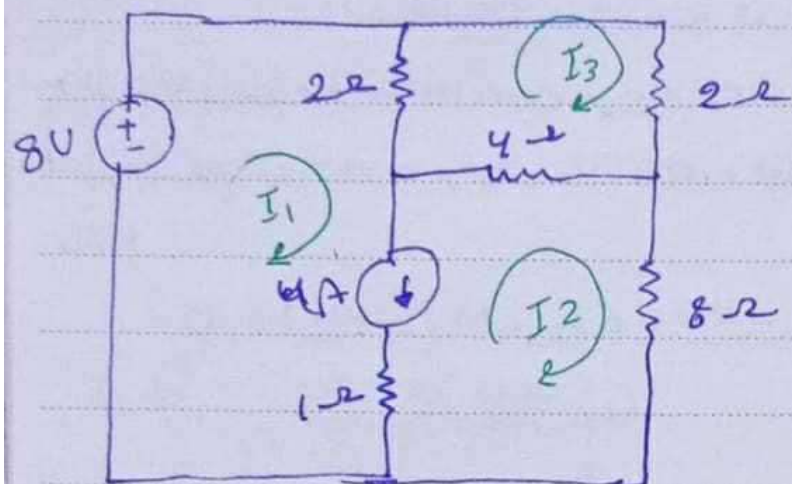P.P.C(3.7): Find  $I_1$  &  $I_2$  &  $I_3$ .



• Super mesh:

$$-8 + 2(I_1 - I_3) + 8I_2 = 0$$

$$2I_1 + 8I_2 - 2I_3 = 8 \quad \text{--- (1)}$$

$$I_1 - I_2 = 4A$$

$$I_2 - I_1 = -4A \quad \text{--- (2)}$$

KVL at mesh 3:

$$2I_3 + 4(I_3 - I_2) + 2(I_3 - I_1) = 0$$

$$-2I_1 - 4I_2 + 8I_3 = 0 \quad \text{--- (3)}$$

KVL at mesh 1:

$$-8 + 2(I_1 - I_3) + V_x + 1(I_1 - I_2) = 0$$


$$3I_1 - I_2 - 2I_3 + V_x = 8$$

KVL at mesh 2:

$$4(I_2 - I_3) + 8I_3 + 1(I_2 - I_1) - V_x = 0$$

$$-I_1 + 5I_2 + 4I_3 - V_x = 0$$

$$2I_1 + 4I_2 + 2I_3 = 0$$

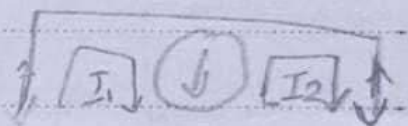


$$I_1 - I_2 = 4A$$



CH3

## Example

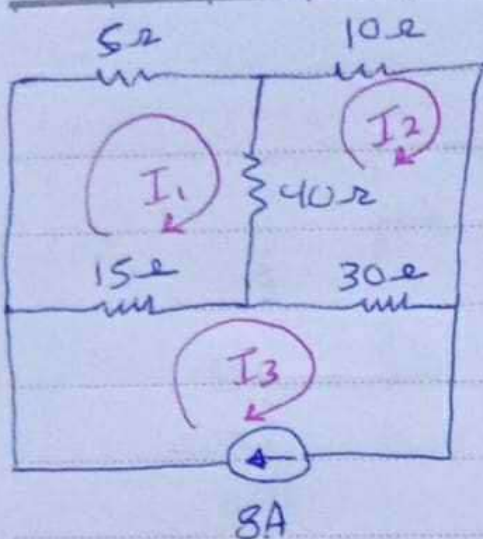

① By inspection  $\Rightarrow I_3 = 8A$

② KVL at mesh #①:

$$5I_1 + 40(I_1 - I_2) + 15(I_1 - 8) = 0$$


$$60I_1 - 40I_2 = 120 \quad \text{--- (1)}$$

③ KVL at mesh #②:

$$10I_2 + 30(I_2 - 8) + 40(I_2 - I_1) = 0$$

$$-40I_1 + 80I_2 = 240 \quad \text{--- (2)}$$

$$I_1 = 6A, I_2 = 6A$$

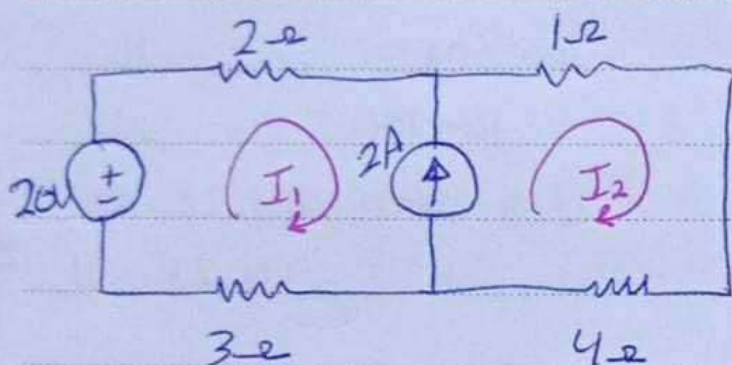

\* super mesh:

$$-I_1 + I_2 = 2A \quad \text{--- (1)}$$

KVL at super mesh:

$$-20 + 2I_1 + 1I_2 + 4I_2 + 3I_1 = 0$$


$$5I_1 + 5I_2 = 20 \quad \text{--- (2)}$$

$$I_2 = 3A$$

$$I_1 = I_2 - 2 = 3 - 2 = 1A$$

$$V = 15V \text{ volt.}$$

## Ex3

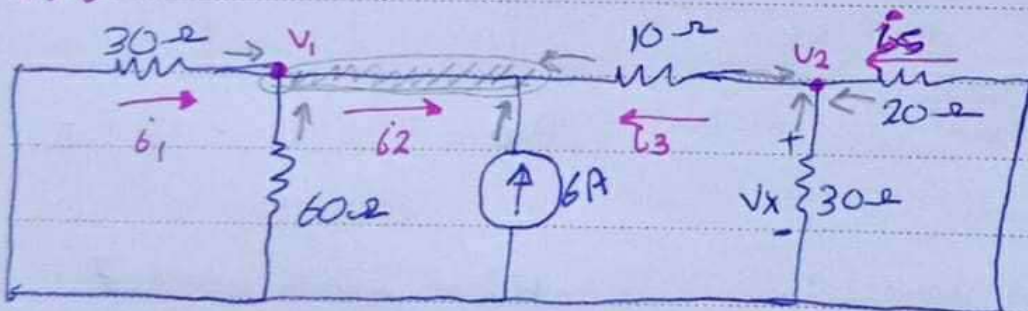

KCL at node ②:

$$\frac{V_1 - V_2}{10} + \frac{0 - V_3}{3} + \frac{0 - V_2}{20} = 0 \Rightarrow 6V_1 - 11V_2 = 0 \quad \text{--- (2)}$$



KCL at node ①:




$$\frac{-V_1}{30} + \frac{V_1}{60} + \frac{V_2 - V_1}{10} + 6 = 20 \rightarrow \left( \frac{-3}{20} V_1 + \frac{V_2}{10} = \frac{-6}{20} \right) \times 20$$

$$-3V_1 + 2V_2 = -120$$

$$V_1 = 62.9 \text{ volt}$$

$$V_2 = 39.2$$


Ex:

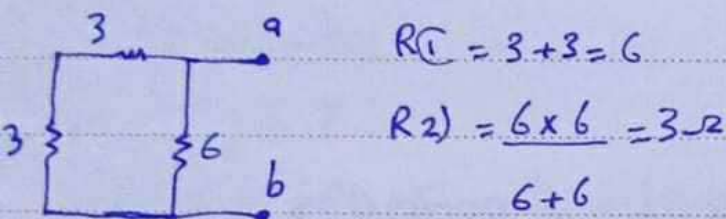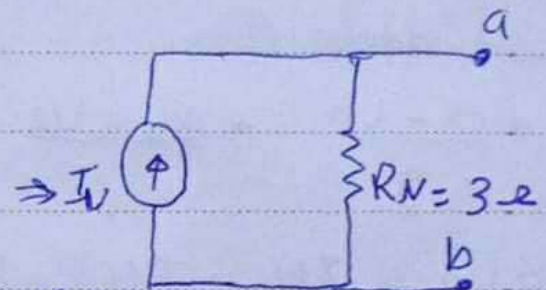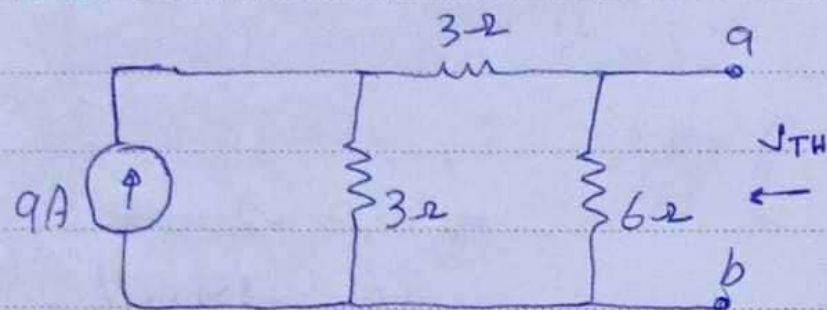

$$R_1 = 3 + 3 = 6$$

$$R_2 = \frac{6 \times 6}{6 + 6} = 3\Omega$$



$$I_N = \frac{13.5}{3} = 4.5 \text{ A}$$

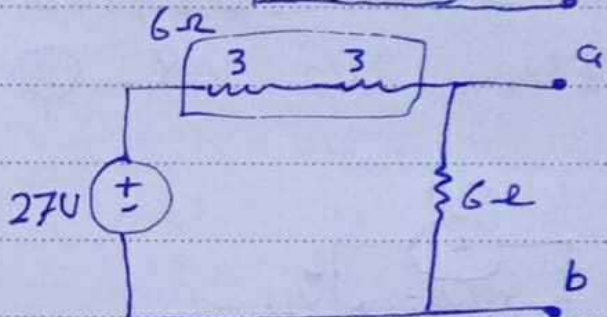

$$V_{ab} = \frac{27 \times 6}{2 + 6} = 13.5 \text{ volt}$$


Ex:

3

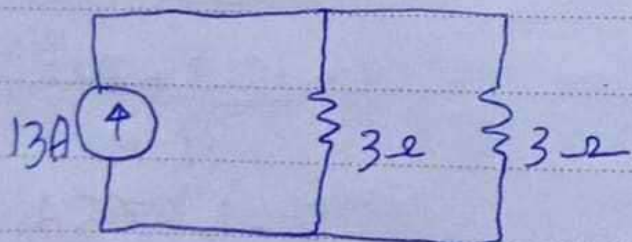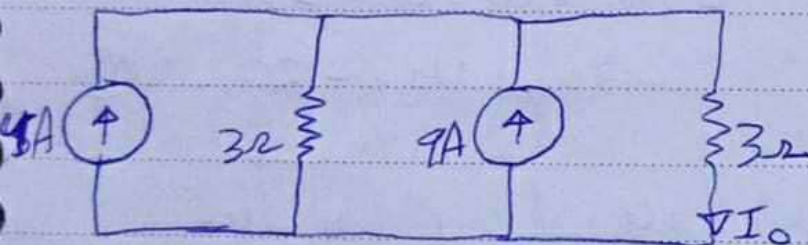

$$I_N = \frac{13.5}{1.5} = 9 \text{ A}$$

Exs

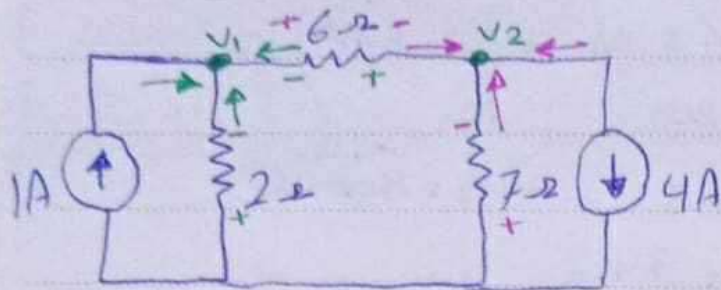

KCL at node ①:

$$\left( 1 + \frac{0 - V_1}{2} + \frac{V_2 - V_1}{6} = 0 \right) \times 6$$

$$-3V_1 + V_2 - V_1 = -6$$

$$-4V_1 + V_2 = -6 \quad \text{--- (1)}$$

KCL at node ②:

$$\left( -4 + \frac{0 - V_2}{7} + \frac{V_1 - V_2}{6} = 0 \right) \times 42$$


$$-6V_2 + 7V_1 - 7V_2 = 168$$

$$7V_1 - 13V_2 = 168 \quad \text{--- (2)}$$

$$\Rightarrow V_1 = -20 \text{ volt}$$

$$V_2 = -14 \text{ volt.}$$

Exs

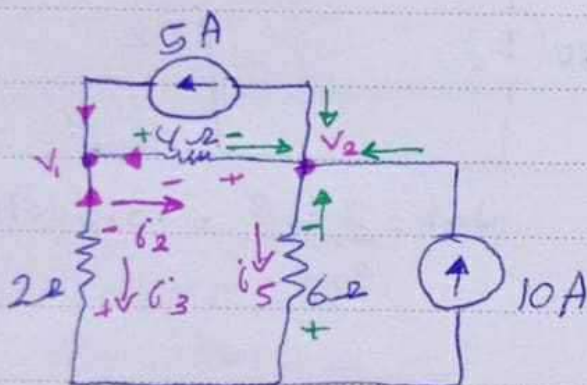

KCL at node ①:

$$\left( 5 + \frac{0 - V_1}{2} + \frac{V_2 - V_1}{4} = 0 \right) \times 4$$

$$-2V_1 + V_2 - V_1 = -20$$

$$-3V_1 + V_2 = -20 \quad \text{--- (1)}$$

KCL at node ②:

$$\left( 10 - 5 + \frac{0 - V_2}{6} + \frac{V_1 - V_2}{4} = 0 \right) \times 24$$

$$-4V_2 + 6V_1 - 6V_2 = -120$$

$$6V_1 - 10V_2 = -120 \quad \text{--- (2)}$$

$$V_1 = 13.3 \text{ volt}$$

$$V_2 = 20 \text{ volt.}$$

$$i_2 = \frac{V_1 - V_2}{4}$$

$$= \frac{13.3 - 20}{4}$$


$$= -1.675 \text{ A}$$



$$I_3 = \frac{V_1 - 0}{2} = \frac{13.3}{2} = 6.65 \text{ A}$$

$$I_5 = \frac{V_2 - 0}{6} = \frac{20 - 0}{6} = 3.33 \text{ A}$$

Ex 8

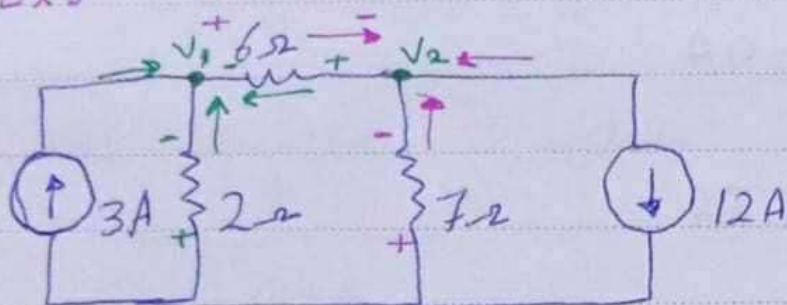

KCL at node ①:

$$6 \times \left( \frac{3 + 0 - V_1}{2} + \frac{V_2 - V_1}{6} = 0 \right)$$

$$-3V_1 + V_2 - V_1 = -18$$

$$-4V_1 + V_2 = -18 \quad \text{--- (1)}$$

$$\left( \frac{-12 + 0 - V_2}{7} + \frac{V_1 - V_2}{6} = 0 \right) \times 42$$


$$-6V_2 + 7V_1 - 7V_2 = +504$$

$$7V_1 - 13V_2 = 504 \quad \text{--- (2)}$$

$$V_1 = -6 \text{ volt}$$

$$V_2 = -42 \text{ volt}$$

Ex 8

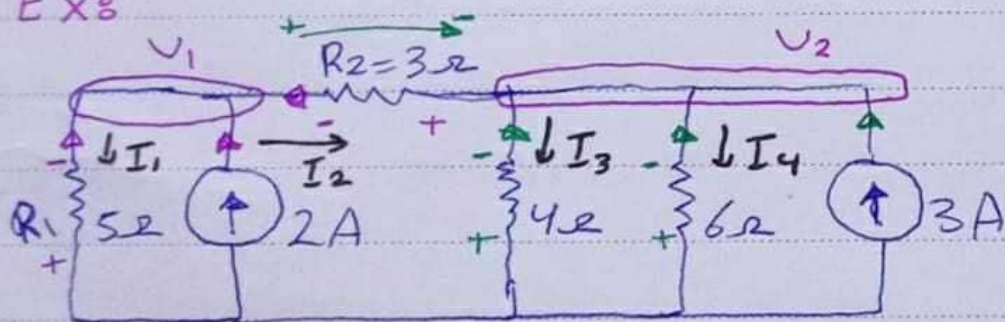

KCL at node ①:

$$\left( \frac{2 + 0 - V_1}{5} + \frac{V_2 - V_1}{3} = 0 \right) \times 15 \Rightarrow -3V_1 + 5V_2 - 5V_1 = -30$$

$$-8V_1 + 5V_2 = -30 \quad \text{--- (1)}$$

KCL at node ②:

$$\left( \frac{V_1 - V_2}{3} + \frac{0 - V_2}{4} + \frac{0 - V_2}{6} + 3 = 0 \right) \times 12 \Rightarrow 4V_1 - 4V_2 - 3V_2 - 2V_2 + 36 = 0$$

$$4V_1 + 10V_2 = -36 \text{ mV} \text{ (2)}$$

$$V_1 = 8 \text{ Volt}$$

$$V_2 = 6.8 \text{ Volt}$$

$$I_1 = \frac{V_1 - 0}{5} = \frac{8 - 0}{5} = 1.6 \text{ A}$$


$$I_2 = \frac{V_1 - V_2}{3} = \frac{8 - 6.8}{3} = 0.4 \text{ A}$$

$$I_3 = \frac{V_2 - 0}{4} = \frac{6.8 - 0}{4} = 1.7 \text{ A}$$

$$I_4 = \frac{V_2 - 0}{6} = \frac{6.8 - 0}{6} = 1.13 \text{ A}$$



Ex:

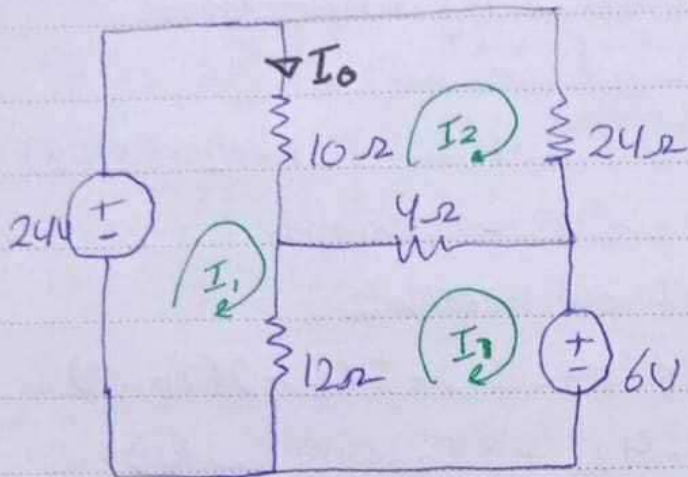

$$I_1 = 2.25 \text{ A}$$

$$I_2 = 0.75 \text{ A}$$

$$I_3 = 1.5 \text{ A}$$

$$I_0 = I_1 - I_2 = 2.25 - 0.75 = 1.5 \text{ A}$$

KVL at mesh ①:

$$-24 + 10(I_1 - I_2) + 12(I_1 - I_3) = 0$$

$$10I_1 + 12I_1 - 10I_2 - 12I_3 = 24$$

$$22I_1 - 10I_2 - 12I_3 = 24 \quad \text{--- ①}$$

KVL at mesh ②:

$$10(I_2 - I_1) + 24I_2 + 4(I_2 - I_3) = 0$$

$$-10I_1 + 10I_2 + 24I_2 + 4I_2 - 4I_3 = 0$$

$$-10I_1 + 38I_2 - 4I_3 = 0 \quad \text{--- ②}$$


KVL at mesh ③:

$$12(I_3 - I_1) + 4(I_3 - I_2) + 6 = 0$$

$$-12I_1 + 4I_2 + 12I_3 + 4I_3 = -6$$

$$-12I_1 + 4I_2 + 16I_3 = -6 \quad \text{--- ③}$$

Ex:

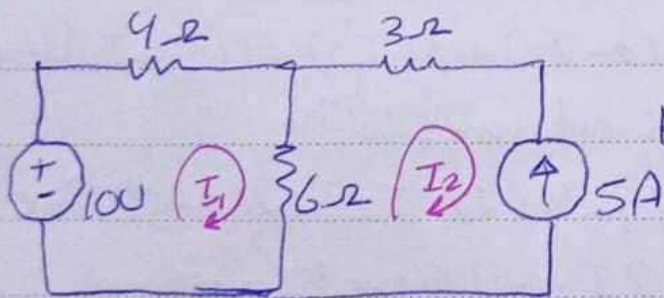


$$I_2 = -5 \text{ A}$$

$$\text{KVL} \Rightarrow 10 + 4I_1 + 6(I_1 + 5) = 0$$

$$I_1 = -2 \text{ A}$$



Ex 8

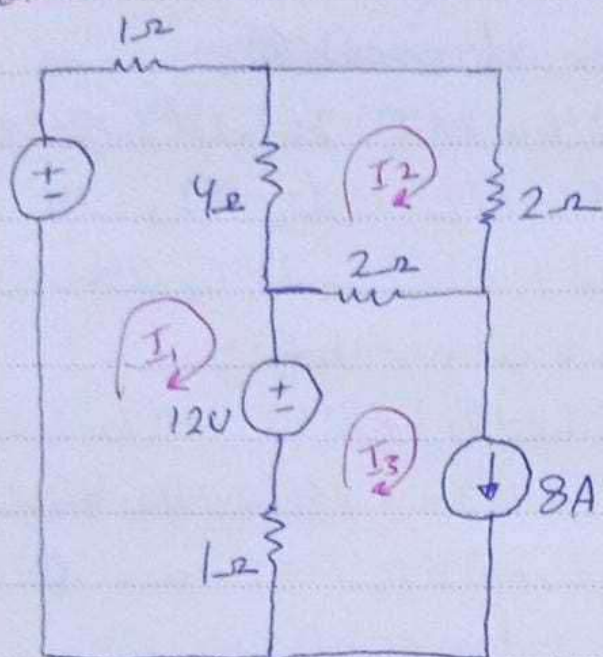

$I_3 = 8A \Rightarrow$  By Inspection

KVL at mesh ① :


$$28 = I_1 + 4(I_1 - I_2) + 12 + (I_1 - 8) \\ = 6I_1 - 4I_2 + 4 \quad \text{--- (1)}$$

KVL at mesh ② :

$$0 = 4(I_2 - I_1) + 2I_2 + 2(I_2 - 8) \\ = -4I_1 + 8I_2 - 16 \quad \text{--- (2)}$$

$$I_1 = 8A \quad I_2 = 6A$$

Ex 9

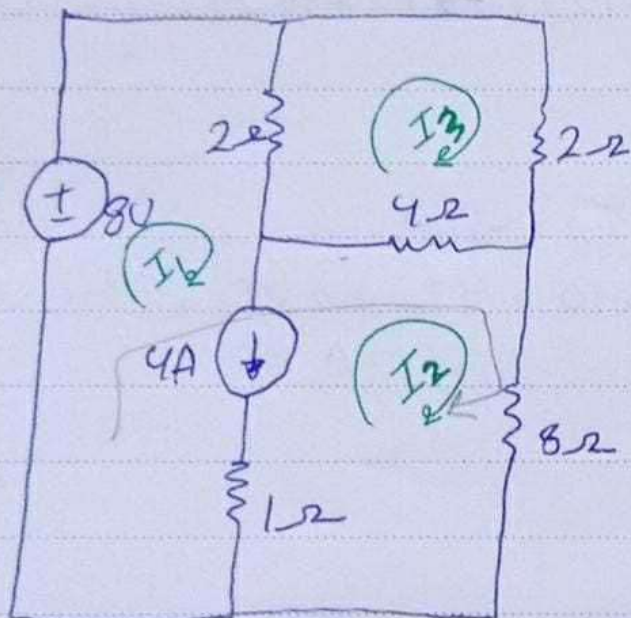

KVL at mesh ① :

$$-8 + 2(I_1 - I_3) + 4 + 1(I_1 - I_2) = 0$$

KVL at mesh ② :

$$4(I_2 - I_3) + 8(I_2) + 1(I_2 - I_1) - 4 = 0$$

KVL at mesh ③ :

$$2I_3 + 4(I_3 - I_2) + 2(I_3 - I_1) = 0$$

$$-2I_1 - 4I_2 + 8I_3 = 0$$

Supermesh :

$$I_1 - I_2 = 4, \quad -8 + 2(I_1 - I_3) +$$

$$4(I_2 - I_3) + 6I_2 = 0$$

$$\Rightarrow I_1 = 4.63A$$

$$I_2 = 0.63A$$

$$I_3 = 1.47A$$

$$\begin{bmatrix} 2 & 12 & -6 \\ 2 & -4 & 8 \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 8 \\ 0 \\ 4 \end{bmatrix}$$



# *Chapter 4*


# Linearity Property.

a linearity is the property of an element describing a linear relationship between cause (input) and effect (response or output).

\* The linearity property is a combination of both:

① the homogeneity (scaling) property  $\Rightarrow x \rightarrow \boxed{\phantom{0}} \rightarrow y \rightarrow \text{in} = \text{out}$

② the additivity property.

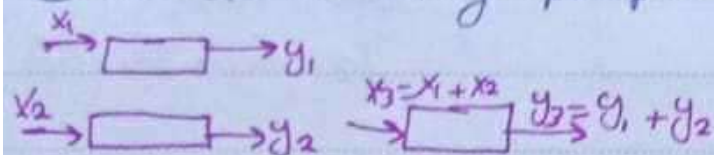


على الـ in و الـ out في الفرضيات

\* The independent source are linear elements.

\* The dependent source is linear if its output current or voltage is proportional only to first power of a specified current or voltage variable in the circuit.

Ex:  $I_s = 30A$ ,  $I_s = 45A$

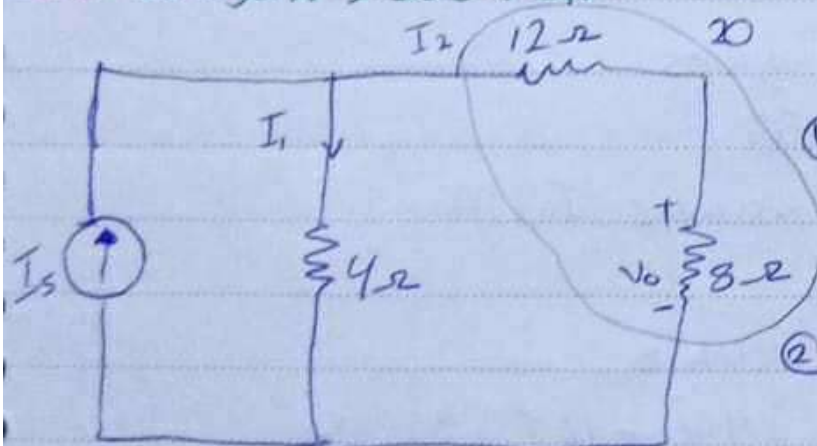

$$R_{eq} = 12 + 8 = 20 \Omega$$

$$\textcircled{1} I_2 = \frac{30 \times 4}{4 + 20} = 5A$$


$$V_s = 5 \times 8 = 40 \text{ volt}$$

$$\textcircled{2} I_2 = \frac{45 \times 4}{4 + 20} = 7.5A$$

$$V_s = 7.5 \times 8 = 60 \text{ volt}$$



Ex: assume  $I_0 = 1A$

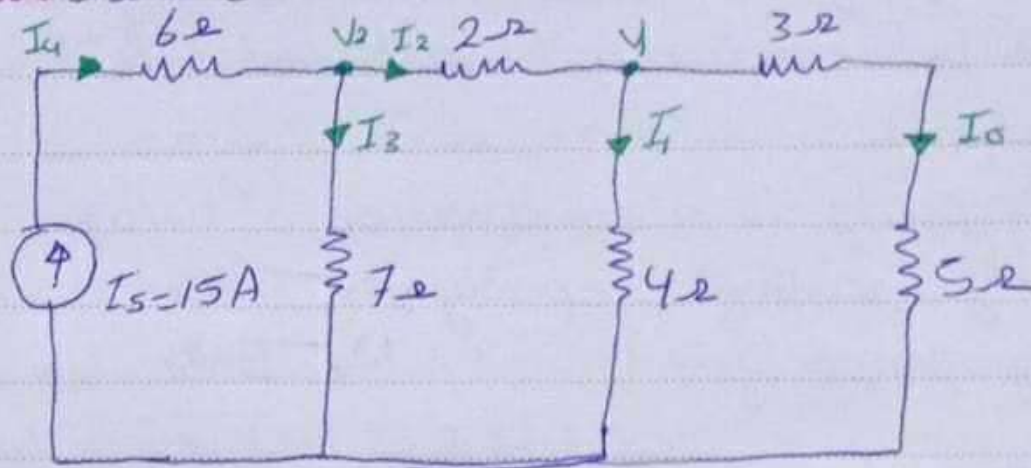

apply KCL at node ①

$$V_1 = (3+5) I_0 = 8 \text{ volt.}$$

$$I_1 = \frac{V_1}{4} = 2A.$$

$$I_2 = I_1 + I_0 = 3A$$

$$\frac{V_2 - V_1}{2} = 3$$

2

$$\frac{V_2 - 8}{2} = 3 \Rightarrow V_2 = 14 \text{ volt.}$$

2

$$I_3 = \frac{V_2}{7} = 2A.$$


7

\* apply KCL at node ② gives

$$I_4 = I_3 + I_2 = 5A$$

$$I_s = 5A \text{ when assume } I_0 = 1A.$$

Ex:

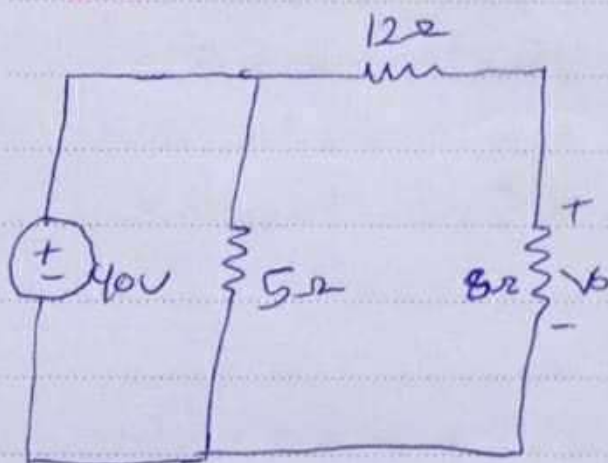

KVL :

$$-40 + 12I + 8I = 0$$

$$40 = 20I$$

$$I = 2A$$


$$V_0 = IR = 2 \times 8 = 16 \text{ volt.}$$

# Superposition


24 / 7 / 2025

\* To apply superposition must have two or more independent sources.

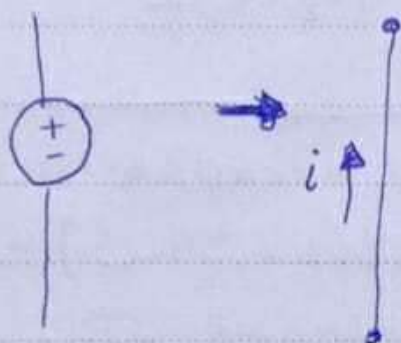
→ To Kill (Turn off) an independent voltage source, replace it by short circuit.



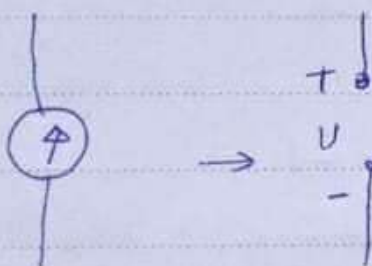→ To Kill (Turn off) current source, replace it by Open.



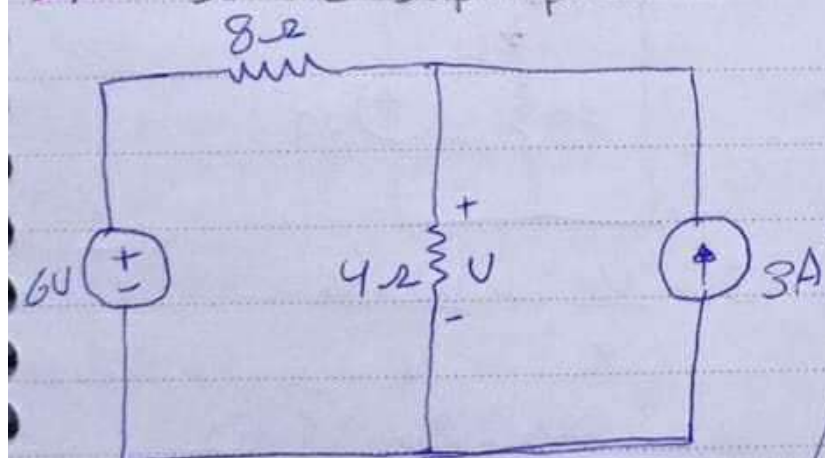
Ex: Use the superposition theorem to find  $V$  in the c.




$$I_3 = \frac{8 \times 3}{8 + 4} = 2 \text{ A}$$

$$V_2 = 4 \times 2 = 8 \text{ volt}$$
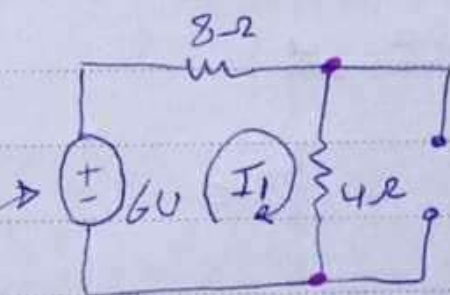
$$V_{\text{total}} = V_1 + V_2 = 8 + 2 = 10 \text{ volt}$$



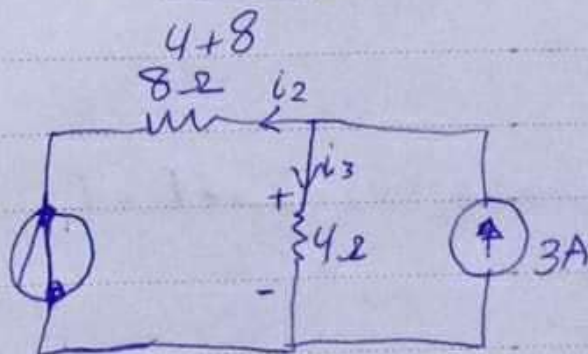
$$V_1 = \frac{4}{4 + 8} \times 6 = 2 \text{ volt}$$






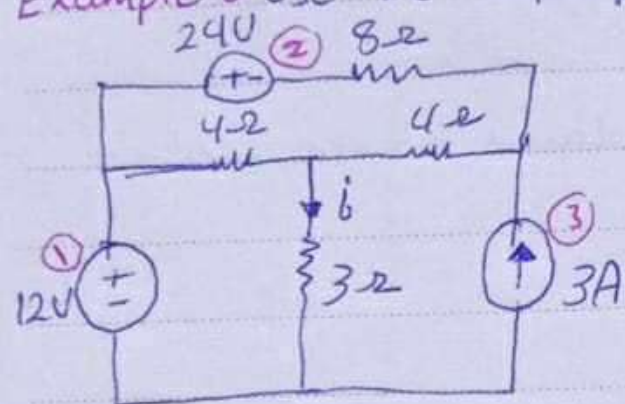Example: Use the superposition to find  $i$ .




↓

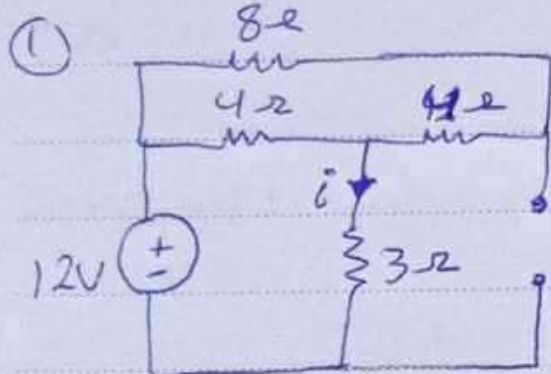


$$R_{eq. ①} = 4 + 8 = 12\Omega$$
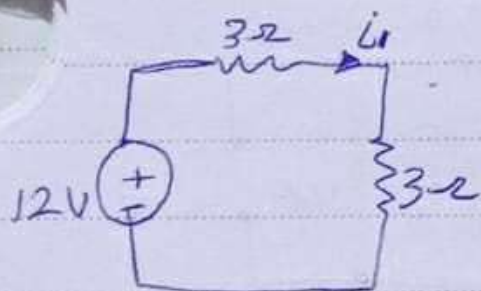
$$R_{eq. ②} = \frac{12 \times 4}{4 + 12} = 3\Omega$$



$$i_1 = \frac{12}{6} = 2A$$

$$i = i_1 + i_2 + i_3 = 2 + 6 + 1 = 9A$$

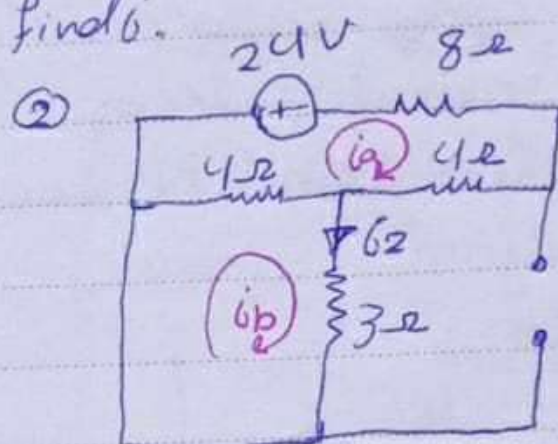

+4( $i_a - i_b$ ) KVL at mesh ① &


$$24 + 8i_a + 4i_a (6i_a - 4i_b + 24 = 0) \div 4$$

$$4i_a - i_b = -6 \quad \text{--- (1)}$$

$$7i_b - 4i_a = 0$$

$$i_a = \frac{7}{4} i_b$$

$$i_2 = i_b = -1$$

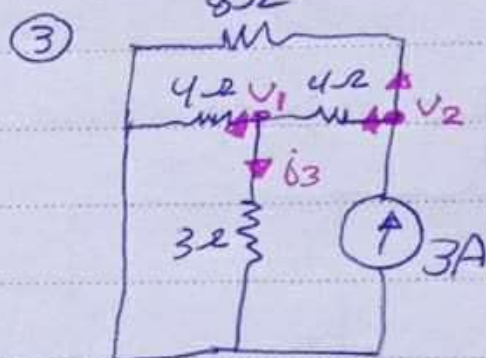

$$3 = \frac{V_2}{8} + \frac{V_2 - V_1}{4}$$

$$24 = 3V_2 - 2V_1 \quad \text{--- (1)}$$


$$\frac{V_2 - V_1}{4} = \frac{V_1}{4} + \frac{V_1}{3}$$

$$V_2 = \frac{10}{3} V_1 \quad \text{--- (2)}$$

3

1      1  
Superposition

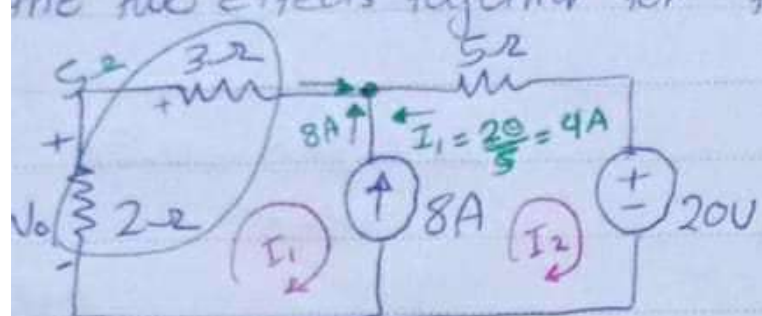**Ex:** Consider the effects of 8A and 20V one by one, then add the two effects together for final  $V_o$ .



KVL at mesh ①:


$$+2I_1 + 3I_1 + 5I_2 + 20 = 0$$

$$5I_1 + 5I_2 = -20 \quad \text{--- ①}$$

$$I_2 - I_1 = 8$$


$$I_1 = -6A \quad I_2 = 2A$$

$$V_o = 6 \times 2 = 12 \text{ volt}$$

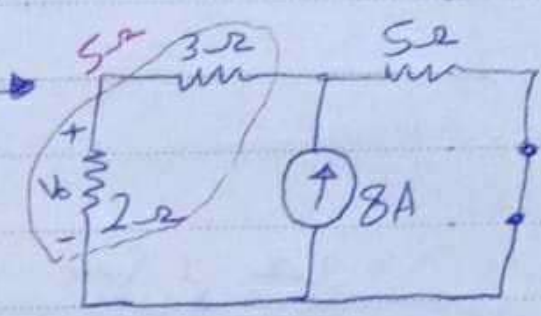

$$I = \frac{8 \times 5}{5 + 5} = 4A$$

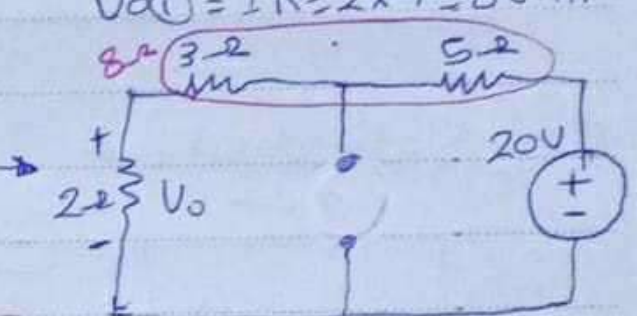
$$V_{o①} = IR = 2 \times 4 = 8 \text{ volt}$$



$$V_{o②} = \frac{2 \times 20}{2 + 8} = 4 \text{ volt}$$

$$V_o = 4 + 8 = 12 \text{ volt}$$

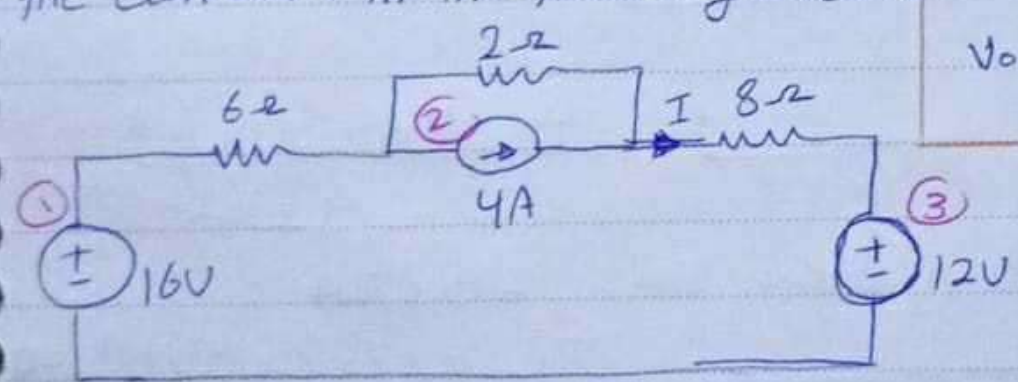
**Ex:** Using superposition principle find the current  $I$  in the following circuits



$$\rightarrow I = I_1 + I_2 + I_3$$



$$= 1 + 0.5 - 0.75$$

$$= 0.75A$$

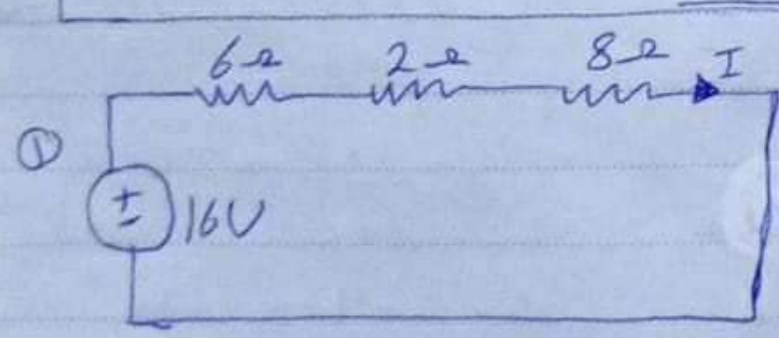


$$I = \frac{16}{16} = 1A$$



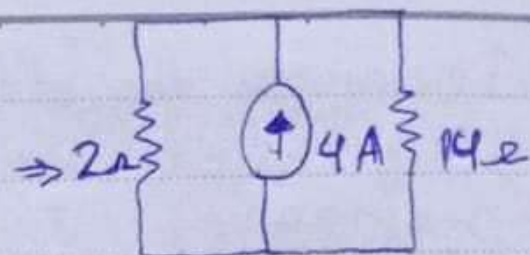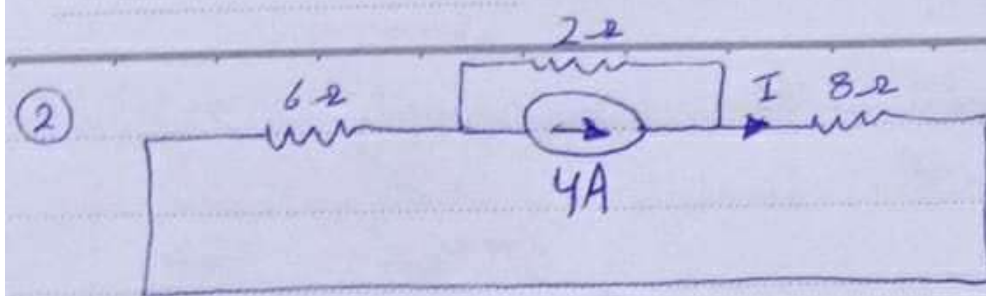


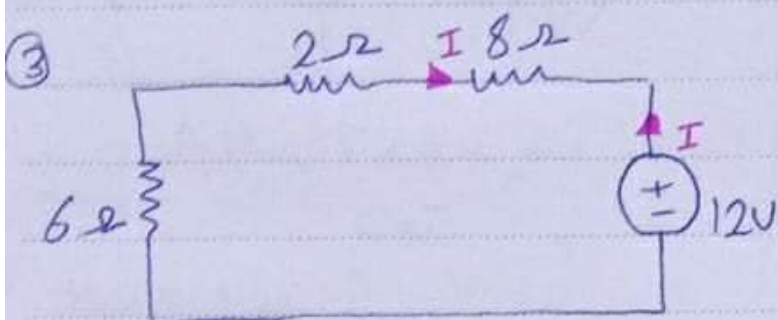
$$I_2 = \frac{4 \times 2}{14 + 2} = 0.5A$$



$$V_8 = \frac{12 \times 8}{16} = 6 \text{ volt (p; 8 walelo)}$$

$$I = -12/16 = -0.75$$


Ex: Superpositions

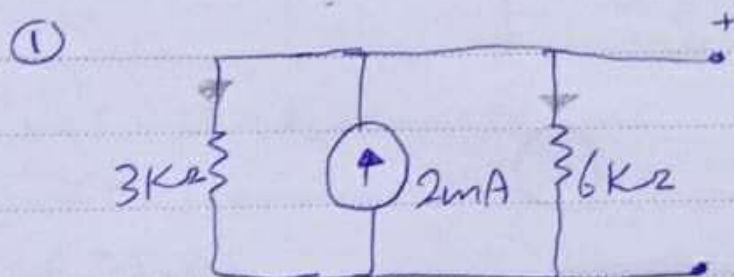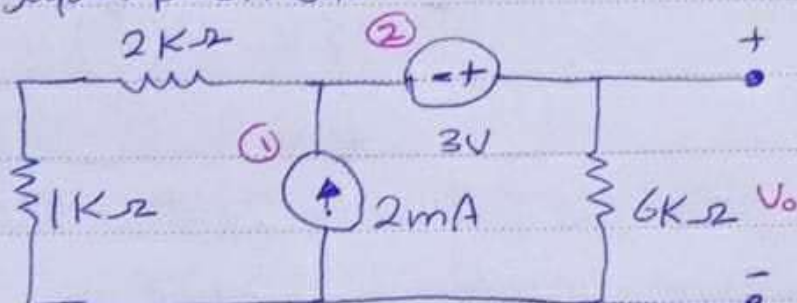

$$I_o = \frac{2 \times 10^{-3} \times 3 \times 10^3}{9 \times 10^3}$$

$$= 0.67 \text{ mA}$$
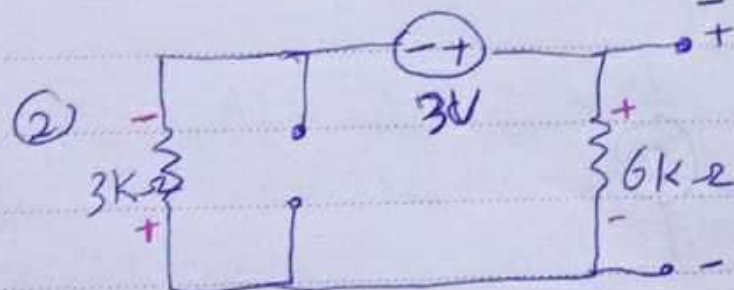
$$V_o = 0.67 \times 6 \times 10^3 \times 10^{-3} = 4V$$




$$V_o = \frac{3 \times 6}{3 + 6} = 2 \text{ volt}$$


$$V_o = 2 + 4 = 6 \text{ volt}$$
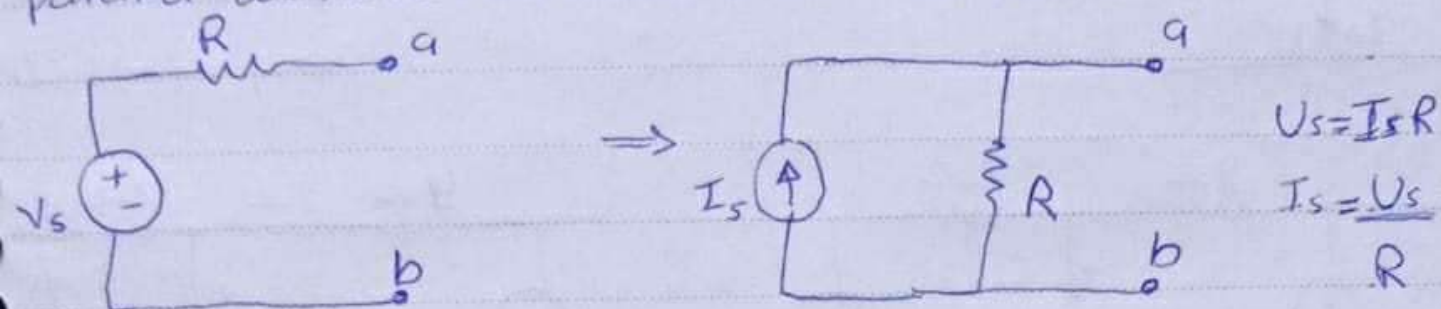
# Source Transformation.

is the process of replacing a voltage source  $V_s$  in series with a resistor  $R$  by a current source  $I_s$  in parallel with a resistor  $R$  or vice versa.




Ex:

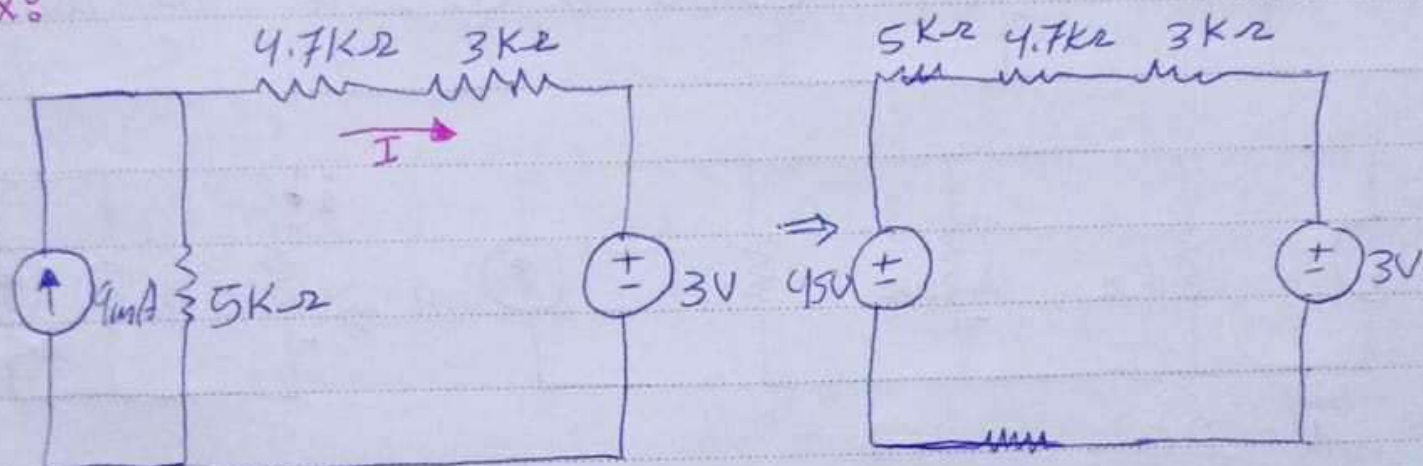


$$3 + -45 + 5000I + 4700 + 3000 = 0$$

$$I = 3.307 \text{ mA}$$

Ex:

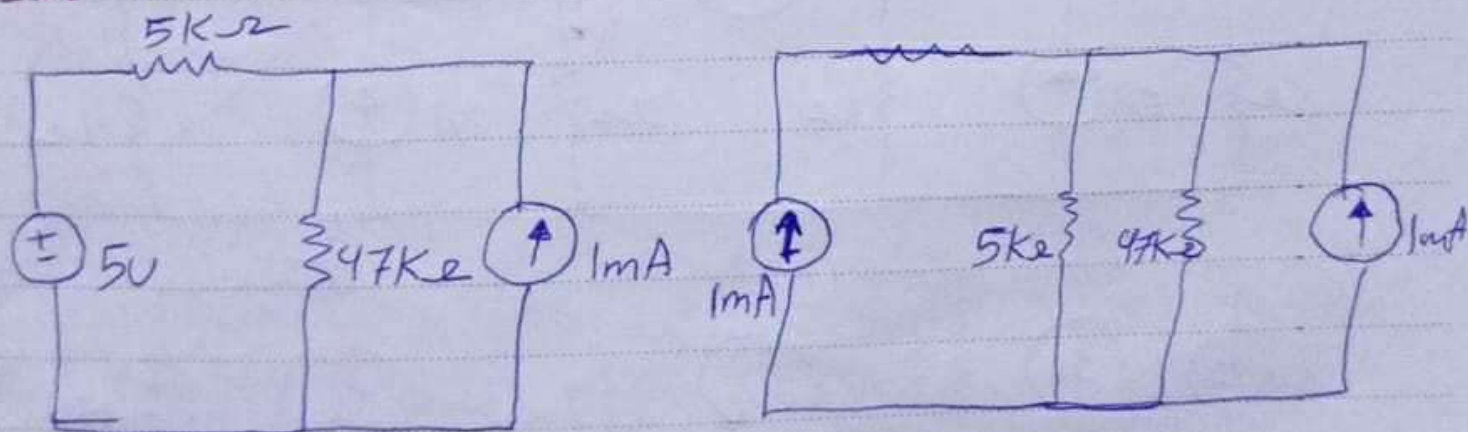






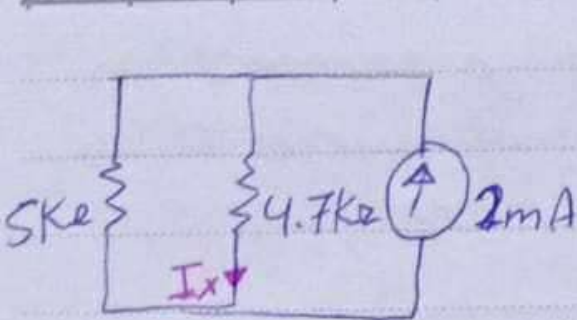

$$I_x = \frac{2 \times 5}{4.7 + 5} = 1A$$

١٦ سؤالي  
two current source  
parallel  
منه الاتجاه بسهم



Ex:

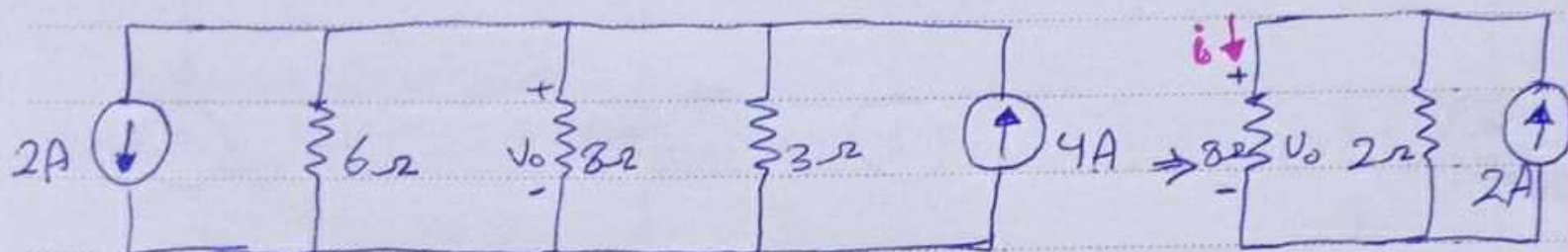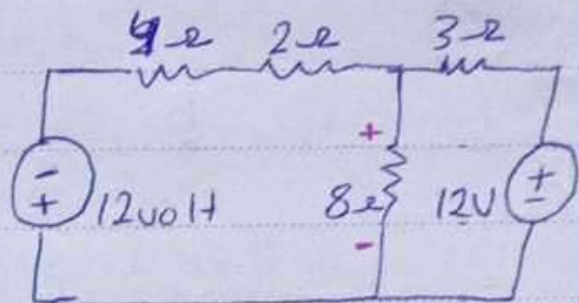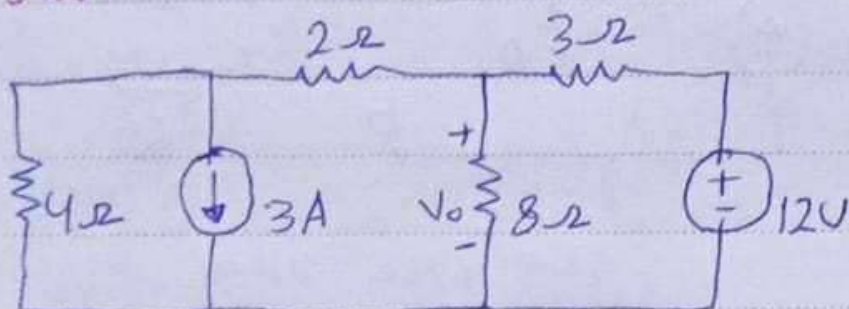

$$i = \frac{2 \times 2}{2 + 8} = 0.4A$$

$$V_0 = 8 \times 0.4 = 3.2V$$

Ex8

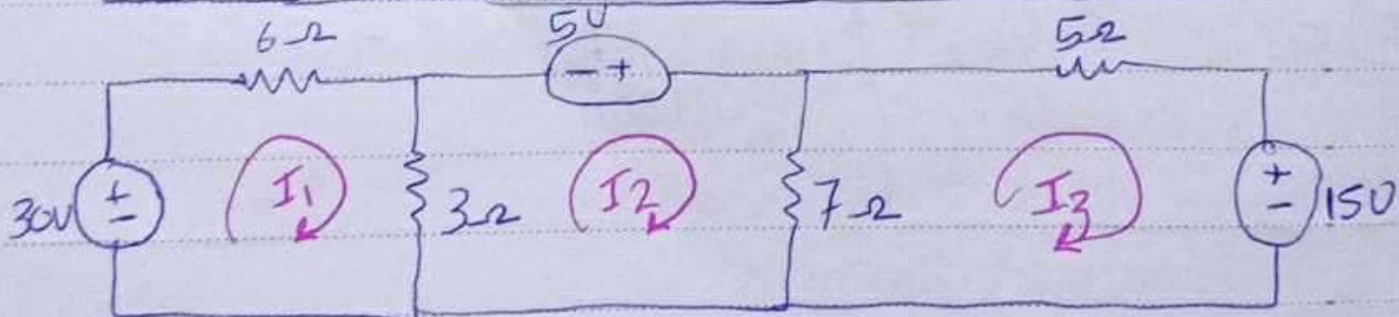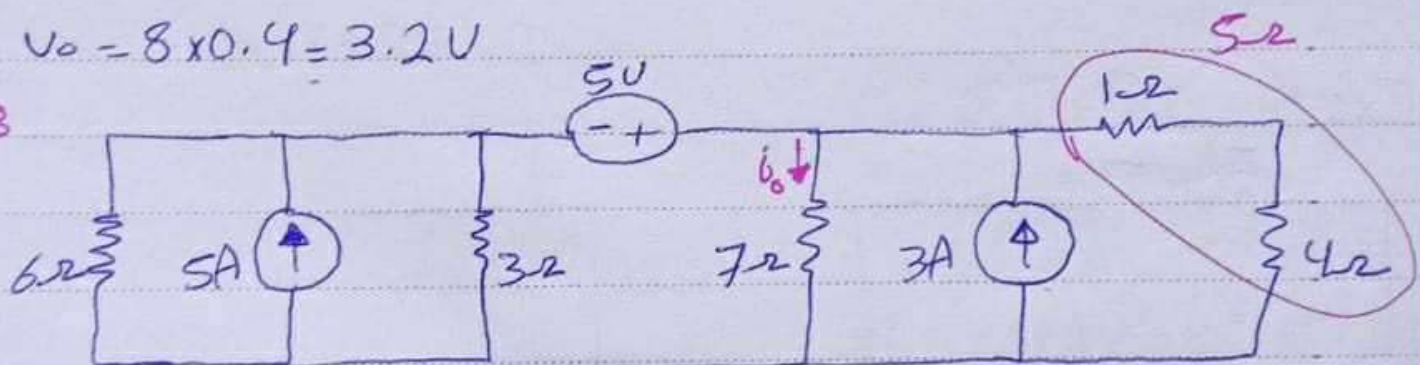

KVL at mesh ①:

$$-30 + 6I_1 + 3(I_1 - I_2) = 0$$

$$-30 + 6I_1 + 3I_1 - 3I_2 = 0$$

$$9I_1 - 3I_2 = 30 \dots (1)$$

$$I_1 = 2.76 \text{ A}$$

$$I_2 = 1.27 \text{ A}$$

$$I_3 = -0.5 \text{ A}$$

KVL at mesh ②:

$$3(I_2 - I_1) - 5 + 7(I_2 - I_3) = 0$$

$$3I_2 - 3I_1 - 5 + 7I_2 - 7I_3 = 0$$

$$-3I_1 + 10I_2 - 7I_3 = 5 \dots (2)$$

$$I_0 = I_2 - I_3$$

$$= -0.5 - 1.27$$

$$= -1.77 \text{ A}$$



KVL at mesh ③:

$$7(I_3 - I_2) + 5I_3 + 15 = 0$$

$$7I_3 - 7I_2 + 5I_3 + 15 = 0$$

$$-7I_2 + 12I_3 = -15 \dots (3)$$


Ex:

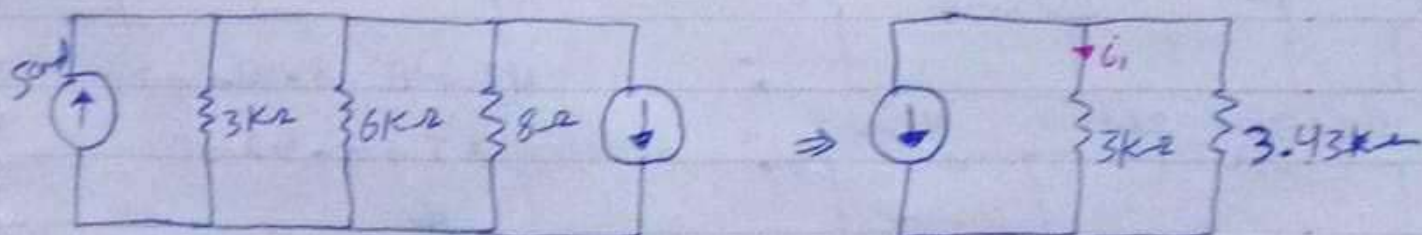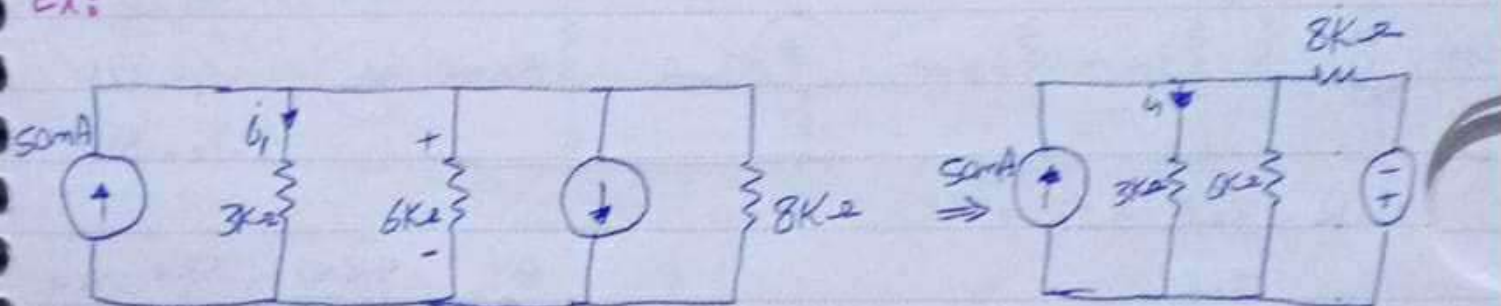





Example of slide.




Examples

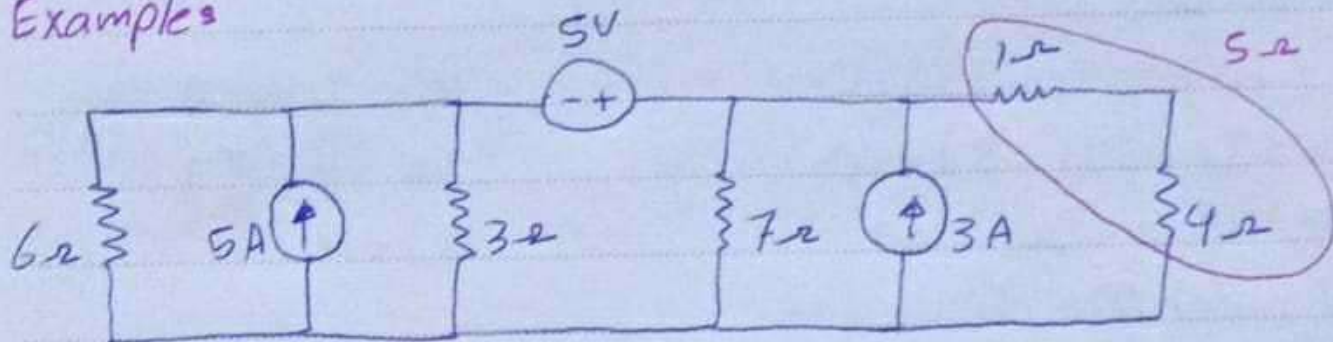

Examples

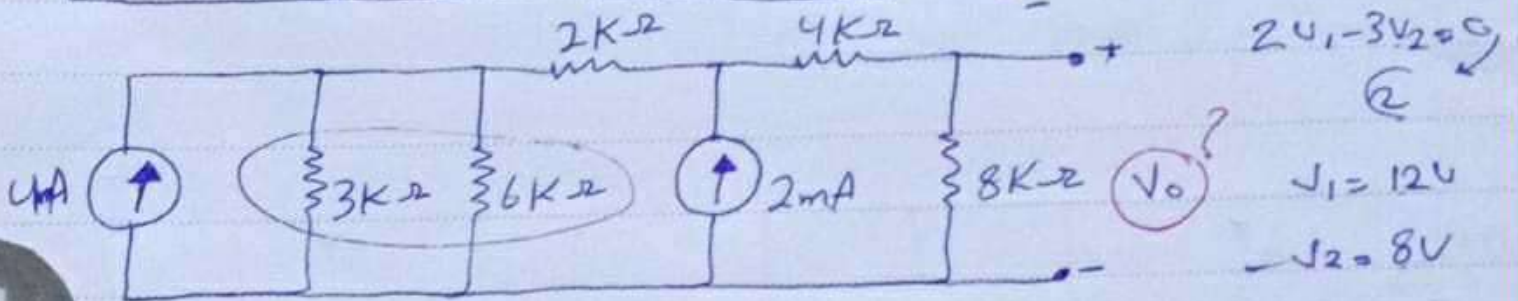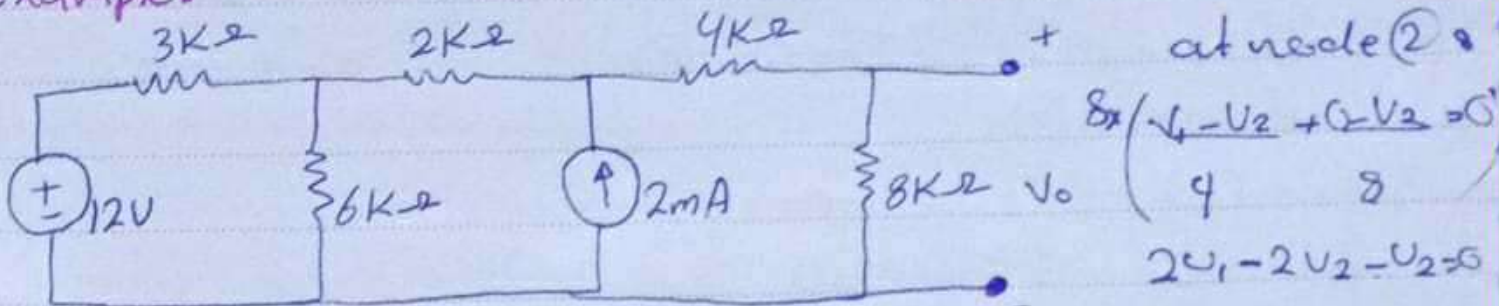
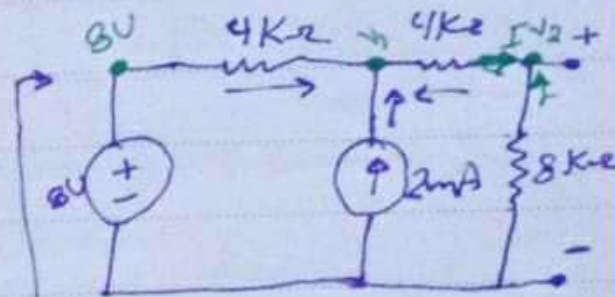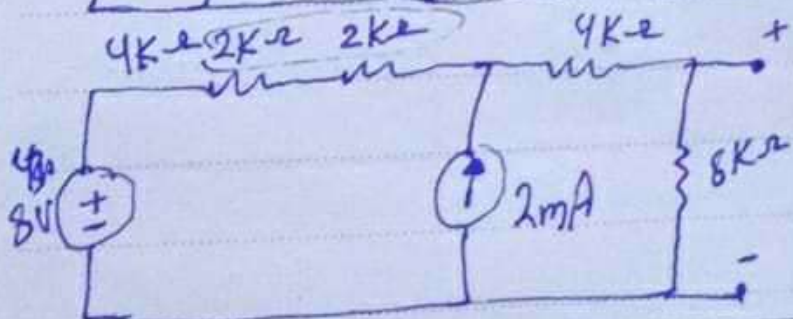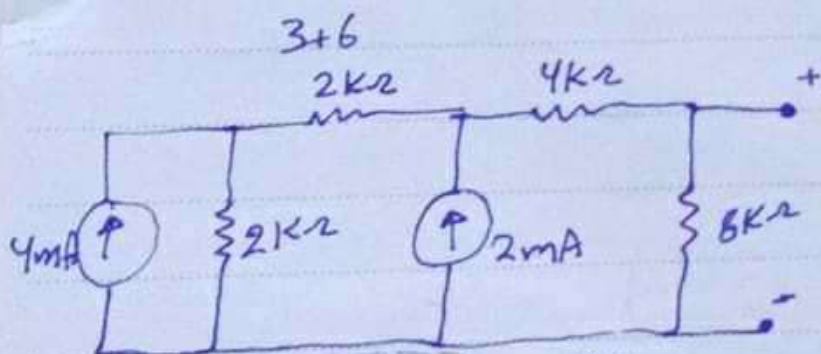
$$R = \frac{3 \times 6}{3+6} = 2K\Omega$$



$$4I + 4I + 8 - V_o = 0$$

$$8I + 8 - 8I = 0$$

$$\text{at node ①} \quad \frac{8 - V_1}{4} + 2 + \frac{V_2 - V_1}{4}$$

$$-2V_1 + V_2 = -16 \quad \text{--- (2)}$$






# Thevenin's Equivalent Theorem.

28 / 7 / 2025

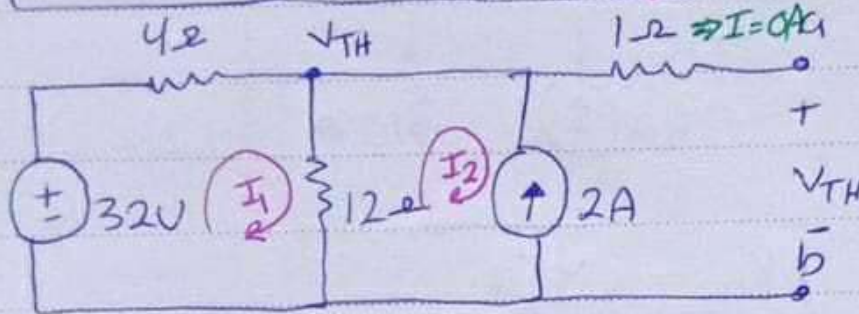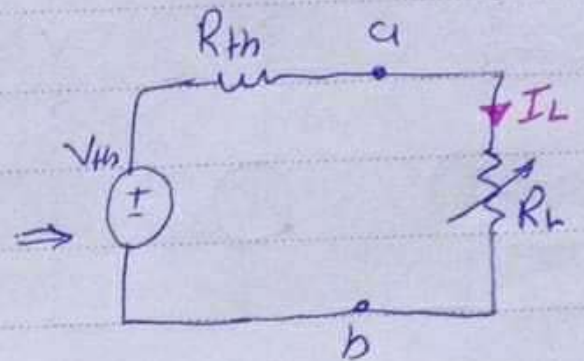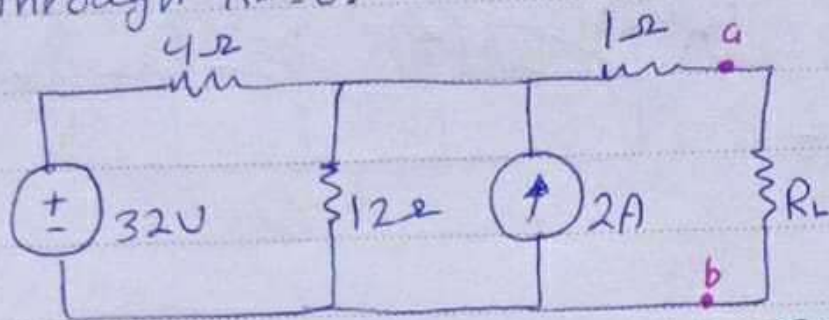**Example:**

Find the Thevenin equivalent circuit, Then find the current through  $R_L = 6$ .




$$-32 + 4I_1 + 12(I_1 - I_2) = 0$$


$$I_2 = -2A$$

$$V_{TH} = 12(I_1 - I_2) = 12(0.5 + 2) = 30V$$

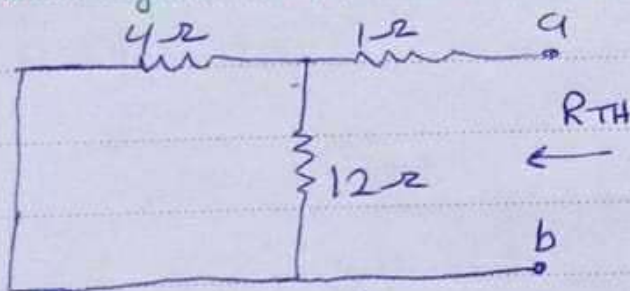\* To get  $R_{TH}$  we must Kill all sources.


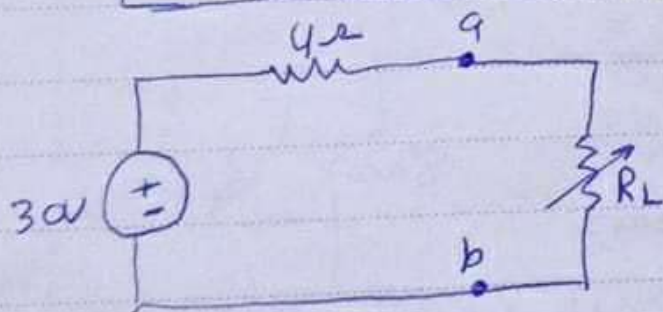
$$R_{TH} = \frac{12 \times 4}{4 + 12} + 1 = 4\Omega$$





$$I_L = \frac{V_{TH}}{R_L + R_{TH}} = \frac{30}{6 + 4} = 3A$$

~~Is = 3A~~




Ex: Find  $R_{TH}$  &  $I$ .

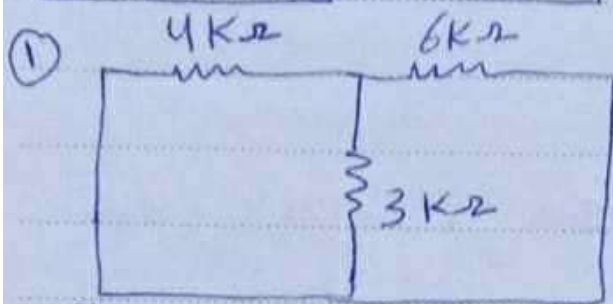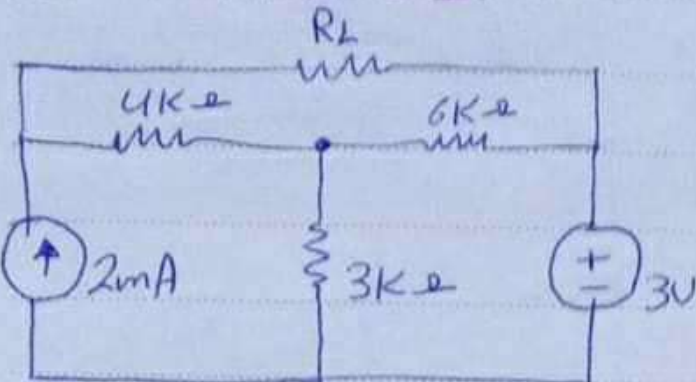

①  $R_{eq} = \frac{4 \times 3}{3+4} = 2K\Omega$

②  $R_{TH} = 2 + 4 = 6K\Omega$

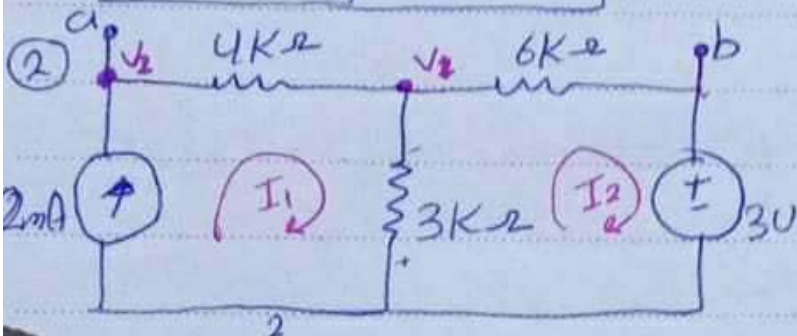

$I_1 = 2mA$

$3(I_2 - I_1) + 6I_2 + 3 = 0$

$3(I_2 - 2) + 6I_2 + 3 = 0$

$I_2 = 0.3mA$



$V_1 = 6 \times 10^3 \times 2 \times 10^{-3} = 12V$

$V_{OC} = V_1 + V_2 = 12 + 8 = 20V$

$V_2 = 4 \times 10^3 \times 0.3 \times 10^{-3} = 1.2V$

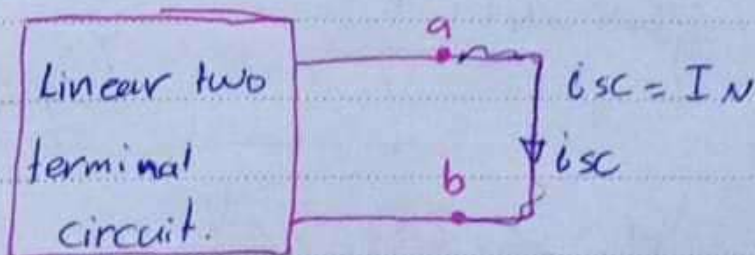
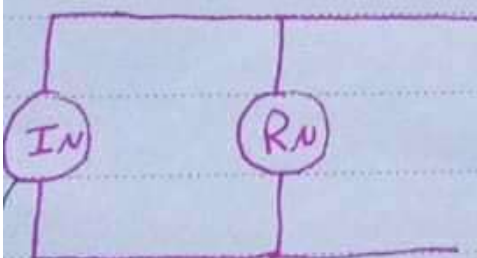
## Norton's Theorem

\*  $R_N = R_{TH} \rightarrow$  it's same.






$\frac{V_{TH}}{R_{TH}} \rightarrow$  same as  $I_N$

Ex:

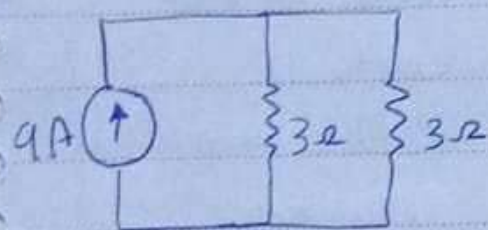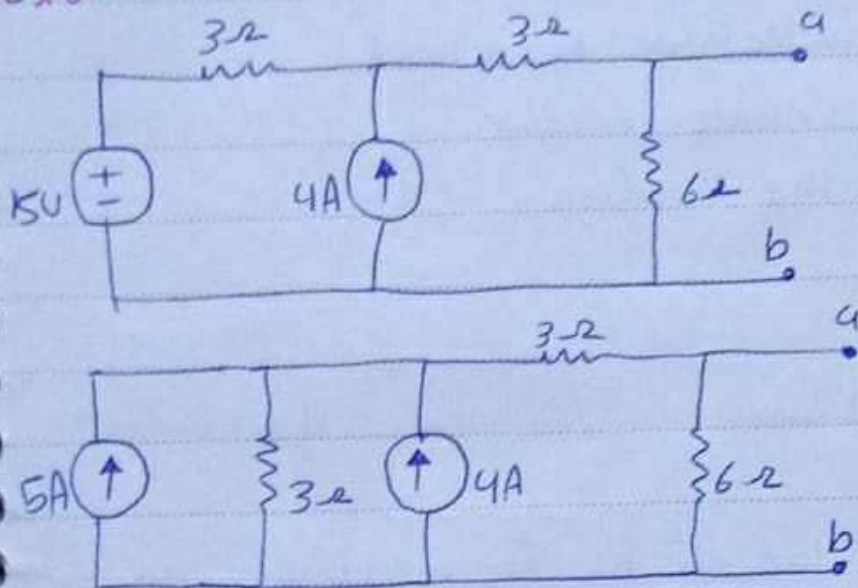


$$I = \frac{13 \times 9}{3+3} = 4.5A$$

Ex: Find the Norton equivalent circuit.

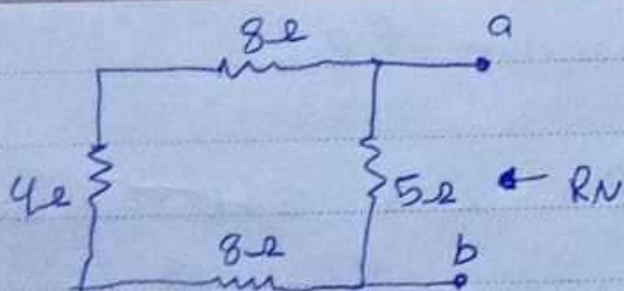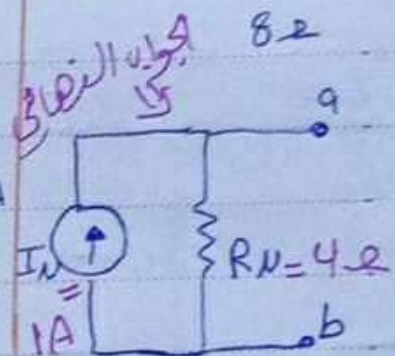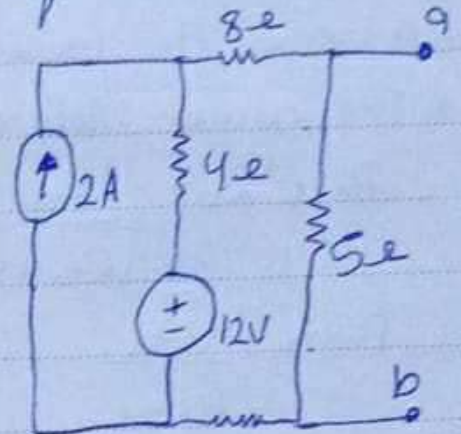

$$R_{eq.1} = 8 + 8 + 4 = 20\Omega$$

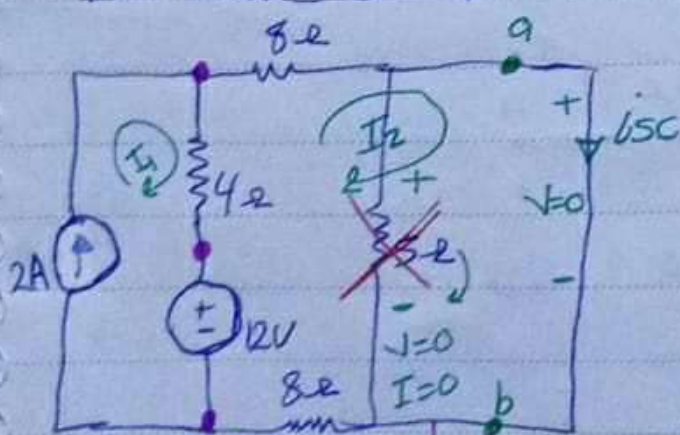
$$R_{eq.2} = \frac{20 \times 5}{20 + 5} = 4\Omega$$



$$I_1 = 2A$$

$$20I_2 - 4I_1 - 12 = 0$$

$$I_2 = 1A = I_{SC} = I_N$$

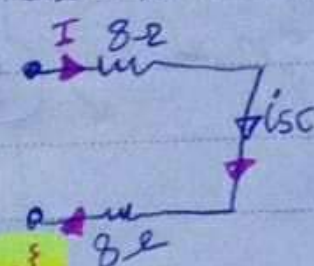

ل نفس التيار

أي مقاومة متوازية

مع س. ح. التيار فيها




# Maximum power Transfer.

- \* The Thevenin equivalent is useful in finding the maximum power a linear circuit can deliver to a load.
- \* Assume the load has variable resistor.
- \* The power delivered to the load is:


$$P = i^2 R_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} \Rightarrow R_L = R_{max}$$

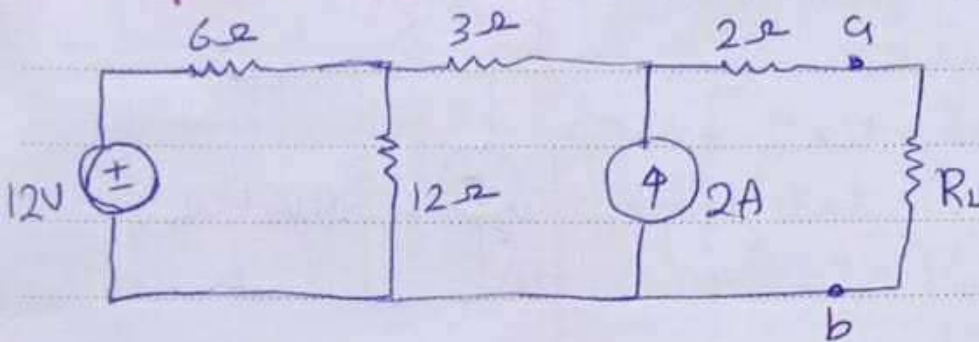
**Example (4.13):** Find the value of  $R_L$  for maximum power transfer in the circuit. Find the maximum power.



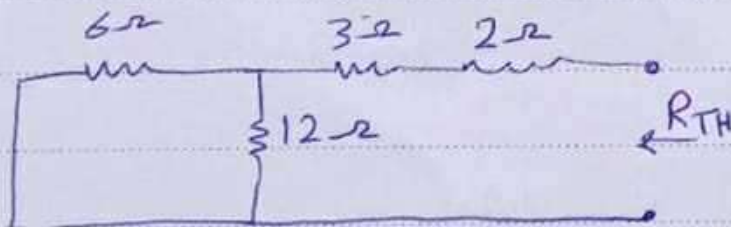$R_L = R_{TH} \rightarrow$  maximum value of  $R_L$ .


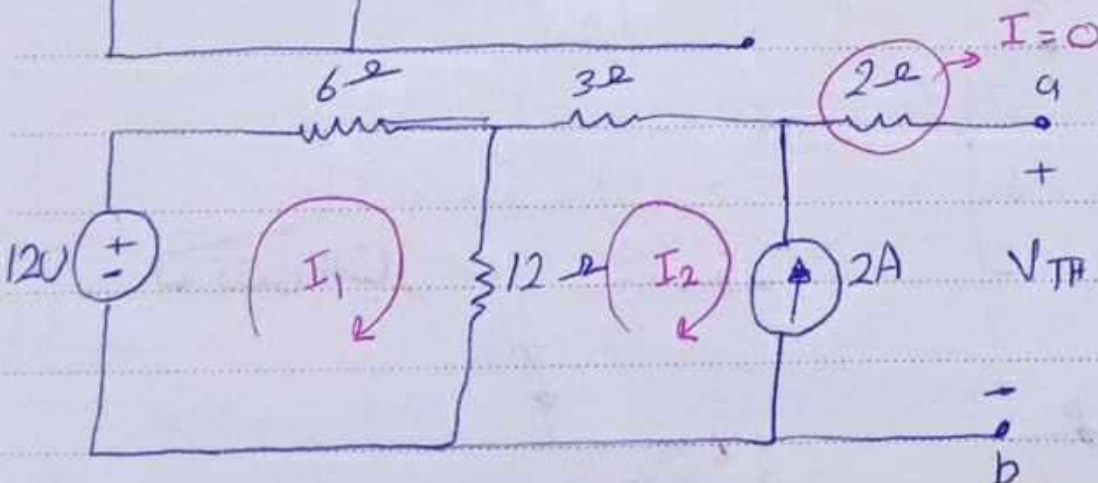
$$R_{TH} = 2 + 3 = 5 + \frac{12 \times 6}{18} = 9\Omega$$



$$-12 + 6I_1 + 12(I_1 - I_2) = 0$$

$$I_2 = -2A$$


$$18I_1 - 12I_2 = 12 \quad (*)$$

$$I_1 = -2/3A$$

$$-12 + 6I_1 + 3I_2 + 2(0) + V_{TH} = 0 \Rightarrow V_{TH} = 22V$$


$$P_{max} = \frac{V_{TH}^2}{4R_L} = \frac{(22)^2}{4 \times 9} = 13.44W$$

Ex:

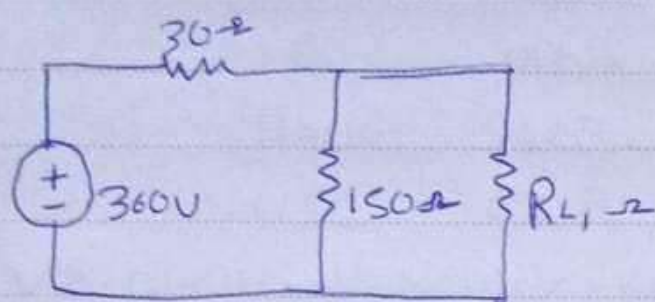


$$V_{TH} = \frac{360 \times 150}{150 + 30} = 300 \text{ Volt.}$$
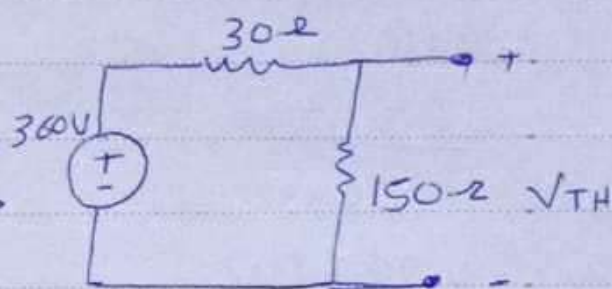
$$R_{TH} = \frac{150 \times 30}{150 + 30} = 25 \Omega$$




$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{(300)^2}{4 \times 25} = 900W$$

Ex:

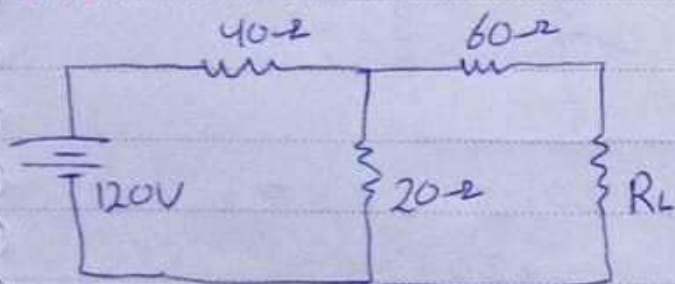

$$R_{TH} = \frac{40 \times 20}{40 + 20} + 60 = 73.3 \Omega$$

$$-120 + 40I + 20I = 0 = 40V$$

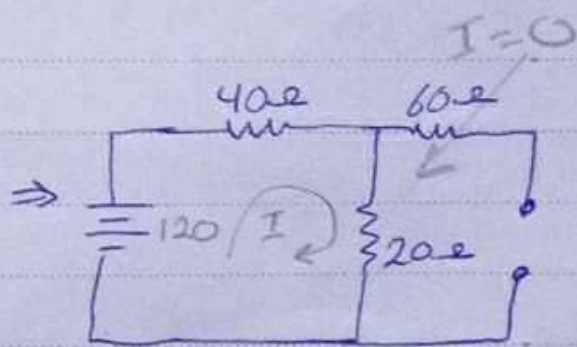


$$V_{TH} = \frac{20}{40 + 60} (120) \quad P_{max} = \frac{(40)^2}{4 \times 73.3}$$

$$= 5.46W$$


$$60I = 120 \rightarrow I = 2A \quad V = IR = 2 \times 20 = 40V$$



Ex 8

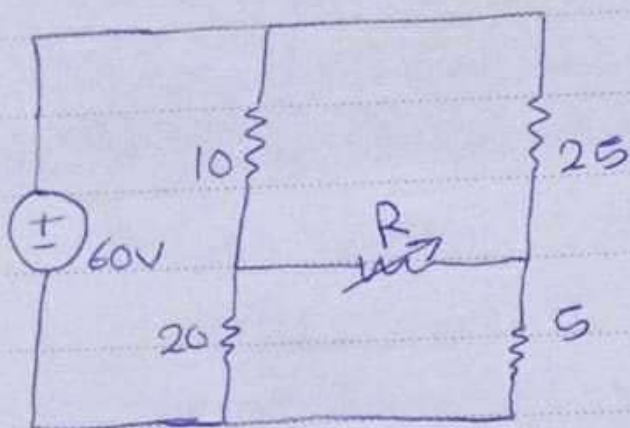

① evaluate  $V_{TH}$

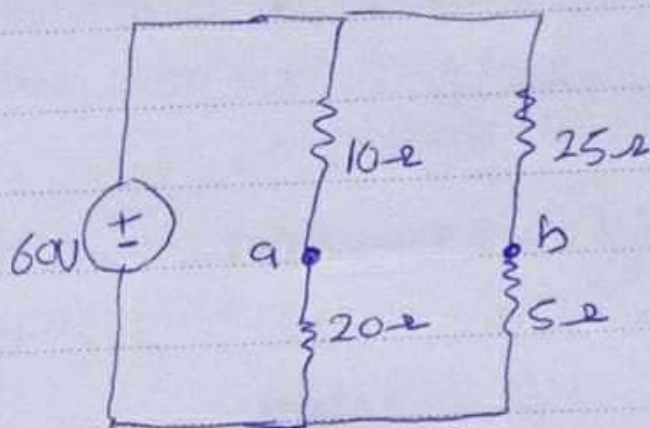

③

$$P_{max} = \frac{(V_{TH})^2}{4R_L}$$

$$= \frac{(30)^2}{4 \times 10.83}$$


$$= 20.77W$$

$$V_a = \frac{20 \times 60}{20 + 10} = 40V$$

$$V_b = \frac{5 \times 60}{5 + 25} = 10V$$

$$V_{th} = V_{ab} = V_a - V_b = 40 - 10 = 30V$$

②  $R_{TH}$


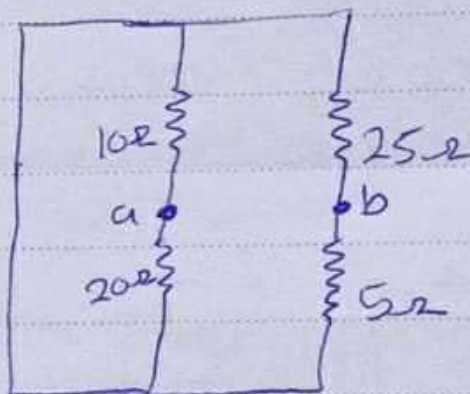


$$R_1 = \frac{20 \times 10}{10 + 20} = 6.67\Omega$$

$$R_2 = \frac{25 \times 5}{25 + 5} = 4.16\Omega$$

$$R_{TH} = 6.67 + 4.16 = 10.83\Omega$$

Ex 3

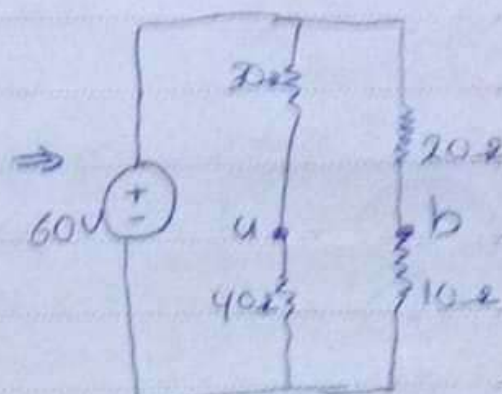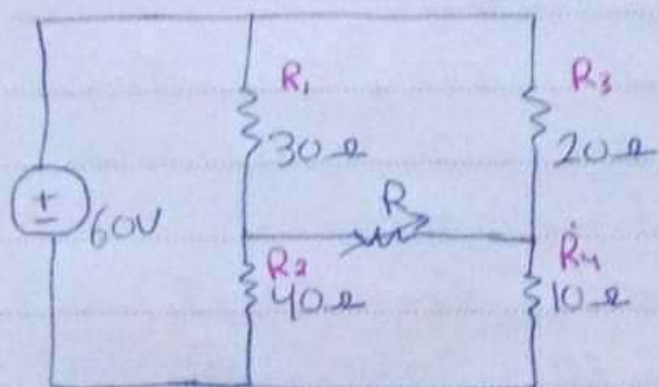

$$P_{max} = \frac{(V_{TH})^2}{4R_L}$$


$$= \frac{(14.28)^2}{4 \times 23.8}$$

$$= 2.14 \text{ W}$$

$$V_A = \frac{60 \times 40}{40 + 70} = 34.28 \text{ volt}$$

$$V_B = \frac{60 \times 10}{10 + 20} = 20 \text{ volt}$$
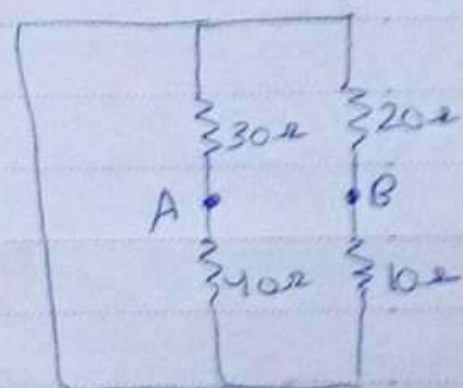
$$V_{AB} = V_{TH} = 34.28 - 20 = 14.28 \text{ volt}$$



$$R_{\text{①}} = \frac{30 \times 40}{30 + 40} = 17.1 \text{ ohms}$$

$$R_{\text{②}} = \frac{20 \times 10}{10 + 20} = 6.7 \text{ ohms}$$

$$R_{TH} = 17.1 + 6.7 = 23.8 \text{ ohms}$$



*Midterm-*  
*Exam*


Grade: 26 / 30

**ANSWER SHEET**

QUESTION #	ANSWER			
1.	a	b	c	d
2.	a	b	c	d
3.	a	b	c	d
4.	a	b	c	d
5.	a	b	c	d
6.	a	b	c	d
7.	a	b	c	d
8.	a	b	c	d
9.	a	b	c	d
10.	a	b	c	d
11.	a	b	c	d
12.	a	b	c	d
13.	a	b	c	d
14.	a	b	c	d
15.	a	b	c	d
16.	a	b	c	d

Select the correct answer for each of the following statements and fill the correct answer in the Answer Sheet provided. Show the calculations for all Questions

1.	The current $I$ in the circuit shown below is:....			
a.	$I = -0.8 \text{ A}$	b.	$I = 0.8 \text{ A}$	
c.	$I = -0.2 \text{ A}$	d.	$I = 0.2 \text{ A}$	

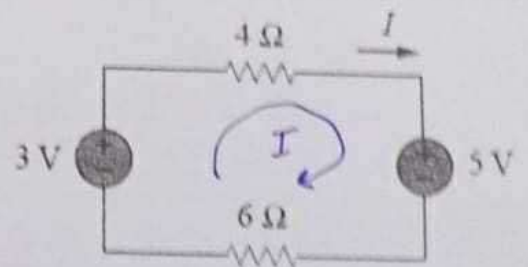


$$-3 + 4I + 5 + 6I = 0$$

$$\frac{10I}{10} = \frac{-2}{10}$$

$$I = -0.2 \text{ A}$$




2.	For the circuit shown below, assuming $i_0 = 2\text{ A}$ and $i_2 = -7\text{ A}$ , use KCL to determine the unknown currents $i_1$ and $i_3$ in the circuit shown below.		
a.	$i_1 = 9\text{ A},$ $i_3 = -7\text{ A}$	b.	$i_1 = 5\text{ A},$ $i_3 = 1\text{ A}$
c.	$i_1 = -5\text{ A},$ $i_3 = 13\text{ A}$	d.	$i_1 = -5\text{ A},$ $i_3 = -13\text{ A}$

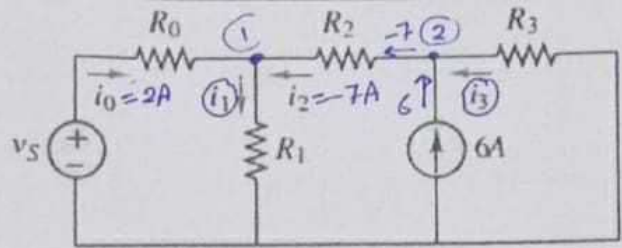

$$1) 2 - 7 = i_1 \\ i_1 = -5\text{ A}$$

$$2) i_3 + 6 = -7 \rightarrow i_3 = -13\text{ A}$$

3.	For the circuit below, the voltage $V_o$ is ....		
a.	$V_o = 15\text{ V}$	b.	$V_o = 32\text{ V}$
c.	$V_o = 2\text{ V}$	d.	$V_o = 18\text{ V}$

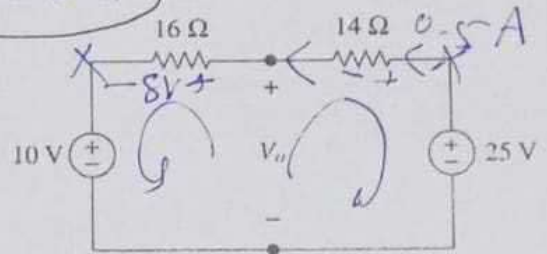

$$25 - 10 = 15$$

$$(-10 + 16I + 14I + 25 = 0$$


$$15 + 30I = 0$$

$$30I = -15 \rightarrow I = -0.5$$

التيار

4. The voltage  $V_o$  in the circuit below is:....

- |    |                    |    |                      |
|----|--------------------|----|----------------------|
| a. | $V_o = 1\text{ V}$ | b. | $V_o = 2\text{ V}$   |
| c. | $V_o = 4\text{ V}$ | d. | $V_o = 0.5\text{ V}$ |

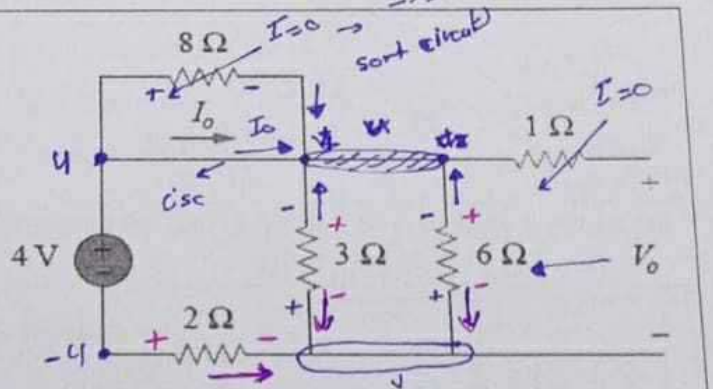

$$4 - I_o + \frac{0 - V}{3} + \frac{0 - V}{6} = 0$$

$$\left( -\frac{4 - V}{2} + \frac{0 - V}{3} + \frac{0 - V}{6} = 0 \right) \times 6$$

$$-2 - \frac{V}{2} - \frac{V}{3} - \frac{V}{6} = 0$$

$$-\frac{V}{2} - \frac{V}{3} - \frac{V}{6} = 2$$

$$-V = 2 \\ V = -2\text{ volt.}$$

①  $V_{16\Omega} = \frac{16 \times 20}{16+4} = 16V$

②  $I_{total} = I_{16\Omega} = 16/16 = 1A$

③  $1/3A \rightarrow R_0$

④  $16V$

⑤  $1/3 = 12\Omega$

⑥  $R_0 = 6\Omega$

⑦  $16V$

⑧  $16\Omega$

⑨  $16V$

⑩  $16V$

⑪  $16V$

⑫  $16V$

⑬  $16V$

⑭  $16V$

⑮  $16V$

⑯  $16V$

⑰  $16V$

⑱  $16V$

⑲  $16V$

⑳  $16V$

㉑  $16V$

㉒  $16V$

㉓  $16V$

㉔  $16V$

㉕  $16V$

㉖  $16V$

㉗  $16V$

㉘  $16V$

㉙  $16V$

㉚  $16V$

㉛  $16V$

㉜  $16V$

㉝  $16V$

㉞  $16V$

㉟  $16V$

㊱  $16V$

㊲  $16V$

㊳  $16V$

㊴  $16V$

㊵  $16V$

㊶  $16V$

㊷  $16V$

㊸  $16V$

㊹  $16V$

㊺  $16V$

㊻  $16V$


㊼  $16V$

㊽  $16V$


㊾  $16V$

㊿  $16V$

5.	In the circuit shown below, if $V_o = 4V$ , then $R = \dots$	
a.	$R = 12\Omega$	b. $R = 1\Omega$
c.	$R = 2.4\Omega$	d. $R = 4\Omega$

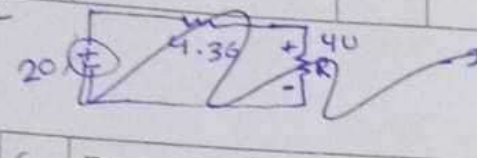

6.	For the circuit below, the equivalent resistance $R_{eq}$ is ....	
a.	$R_{eq} = 14.4\Omega$	b. $R_{eq} = 22\Omega$
c.	$R_{eq} = 2.4\Omega$	d. $R_{eq} = 10\Omega$

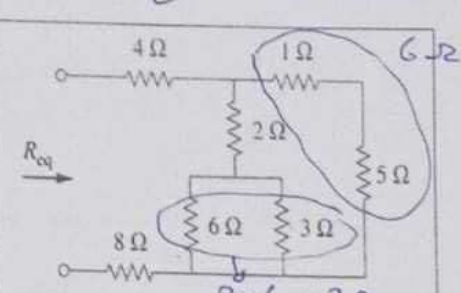

$R_1 = 5 + 1 = 6\Omega$


$R_2 = 2\Omega$

$R_3 = 4\Omega$

$R_4 = \frac{4 \times 6}{6 + 4} = 2.4$

$R_5 = 2.4 + 8 + 4 = 14.4$

7.	For the circuit shown below, the power dissipated in the $3\Omega$ resistor is .....	
a.	$P_{3\Omega} = 8W$	b. $P_{3\Omega} = 5.33W$
c.	$P_{3\Omega} = 48W$	d. $P_{3\Omega} = 1.33W$

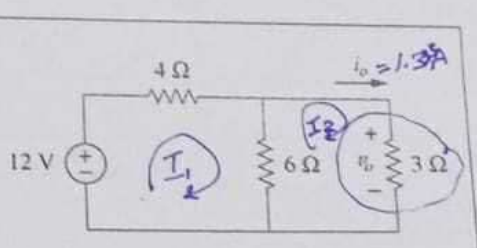

KVL mesh ①:

$-12 + 4I_1 + 6(I_1 - I_2) = 0$

$10I_1 - 6I_2 = 12 \quad (1)$

KVL mesh ②:

$6(I_2 - I_1) + 3I_2 = 0$


$-6I_1 + 9I_2 = 0 \quad (2)$

$I_1 = 2A$

$I_2 = 1.33A$


$I_o = 1.33 \times 3 = 3.99$

8.	For the circuit below, the power supplied/consumed by the $15V$ - and $6V$ -voltage sources are .....	
a.	$P_{15V} = 30W$ supplied $P_{6V} = 3W$ consumed	b. $P_{15V} = 15W$ consumed $P_{6V} = 6W$ supplied
c.	$P_{15V} = 15W$ supplied $P_{6V} = 6W$ consumed	d. $P_{15V} = 30W$ consumed $P_{6V} = 3W$ supplied

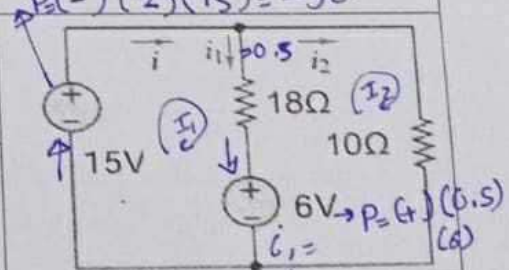

$15 + 0.75 + \frac{0-0}{18} + \frac{0-0}{10} = 0$

$\rightarrow 101.25$

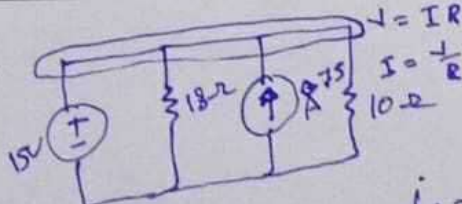

$15 + 18(I_1 - I_2) + 6 = 0$

$18I_1 - 18I_2 = 9 \quad (1)$

$-6 + 18(I_2 - I_1) + 10I_2 = 0$


$-18I_1 + 28I_2 = 6 \quad (2)$

$I_1 = 2$

$I_2 = 1.5$



9.	Using the nodal analysis, the node voltage $V_1$ and $V_2$ are .....
a.	$V_1 = -6$ V and $V_2 = 84$ V
b.	$V_1 = 6$ V and $V_2 = 42$ V
<input checked="" type="radio"/> c.	$V_1 = -6$ V and $V_2 = -42$ V
d.	$V_1 = 6$ V and $V_2 = -84$ V

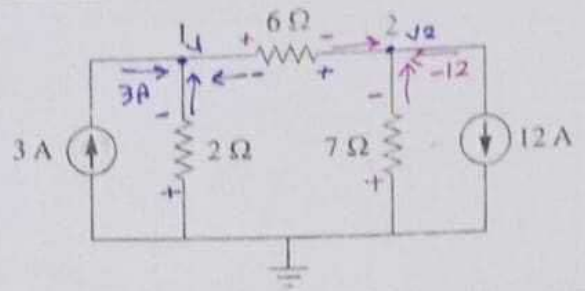


node ①:  $3 + \frac{0 - V_1}{2} + \frac{V_2 - V_1}{6} = 0 \times 6$   
 $-3V_1 + V_2 - V_1 = -18$   
 $-4V_1 + V_2 = -18 \quad \text{--- (1)}$

node ②:  $(-12 + \frac{0 - V_2}{7} + \frac{V_1 - V_2}{6} = 0) \times 42 \rightarrow \frac{V_1}{6} - \frac{13}{42}V_2 = 2$   
 $-6V_2 + 7V_1 - 7V_2 = 504$   
 $7V_1 - 13V_2 = 504 \quad \text{--- (2)}$

$-\frac{2V_1 + V_2}{3} = -3$

10.	Using the node voltage analysis method in the circuit shown below, the current $i$ through the 10 V-voltage source is .....
<input checked="" type="radio"/> a.	$i = 2.5$ A
b.	$i = 1.5$ A
c.	$i = -2.5$ A
d.	$i = 3$ A

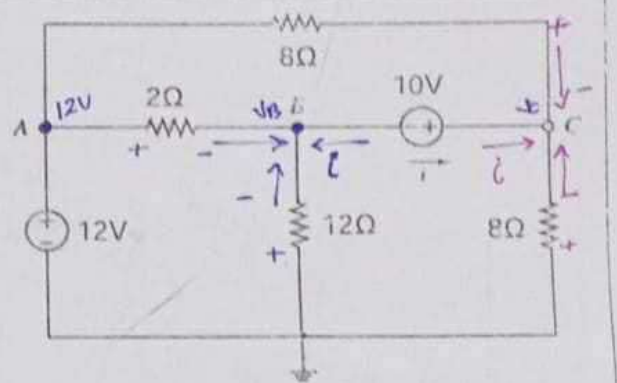

node B  $\rightarrow \frac{12 - V_B}{2} + \frac{0 - V_B}{12} + i = 0 \rightarrow \frac{-7}{12}V_B + i = 6 \quad \text{--- (1)}$


node C  $\rightarrow \frac{12 - V_C}{8} + \frac{0 - V_C}{8} + i = 0$   
 $-\frac{1}{4}V_C + i = -\frac{12}{8} \rightarrow 1 + 2 = \frac{-7}{12}V_B - \frac{1}{4}V_C = -\frac{15}{2} \quad \text{--- (2)}$

$V_C - V_B = 10 \quad \text{--- (3)}$

$V_B = 6$  volt.  
 $V_C = 16$  volt.


$\frac{12-6}{2} - \frac{6}{12} - i = 0$   
 $i = 2.5$

11.	For the circuit shown below, using mesh analysis, the mesh currents $i_1$ and $i_2$ are .....
a.	$i_1 = 2$ A and $i_2 = 5$ A
<input checked="" type="radio"/> b.	$i_1 = -2$ A and $i_2 = -5$ A
c.	$i_1 = 2$ A and $i_2 = -5$ A
d.	$i_1 = -2$ A and $i_2 = 5$ A

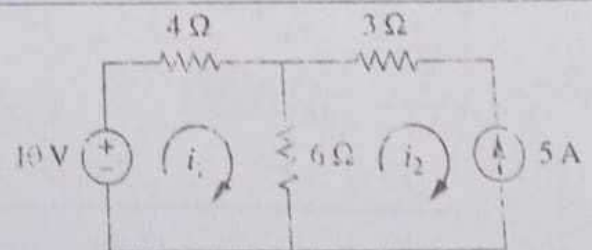

KVL at mesh ①:  
 $-10 + 4I_1 + 6(I_1 - I_2) = 0 \rightarrow I_1 = -2$  A.

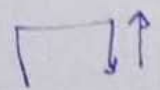KVL at mesh ②:  
 $I_2 = -5 \rightarrow$  by inspection.



12.	Using mesh analysis in the circuit shown below, the power supplied/absorbed by the 2-A current source is ....		
a.	$P_{2A} = 30 \text{ W}$ absorbed	b.	$P_{2A} = 50 \text{ W}$ supplied
c.	$P_{2A} = 30 \text{ W}$ supplied	d.	$P_{2A} = 6 \text{ W}$ absorbed

$$I_2 - I_1 = 2$$

$I_2 - I_1 = 2 \sim \text{①} \rightarrow -I_1 + I_2 = 2 \sim \text{①}$   
 Super mesh:  
 $-20 + 2I_1 + 1I_2 + 4I_2 + 3I_1 = 0$   
 $5I_1 + 5I_2 = 20 \sim \text{②}$   
 $+ \rightarrow ab$

$I_1 = 1A$   
 $I_2 = 3A$

KVL:  
 $-20 + 2 + V + 3 = 0$   
 $V = 20 - 3 - 2$   
 $= 15V$   
 $P = I V = 15 \times 2$   
 $= 30 \text{ watt.}$


$$P = (+) (-2) I (5) V$$

13.	Using source transformation, the current $I$ and the voltage $V$ are ....		
a.	$I = -1 \text{ A}, V = 18 \text{ V.}$	b.	$I = 3 \text{ A}, V = 12 \text{ V.}$
c.	$I = -1 \text{ A}, V = 20 \text{ V.}$	d.	$I = 3 \text{ A}, V = 20 \text{ V.}$

(20V) (15V)  
  
 KVL  $\rightarrow -15 + 3I + 2I + 20 = 0$   
 $5I + 5 = 0$   
 $I = -1A$

$-45 + 20(I_1 - I_2) + 10(I_1 - I_2) = 0$   
 $30I_1 - 30I_2 = 45 \sim \text{①}$   
 $10(I_2 - I_1) + 20(I_2 - I_1) + 3I_2 + 45(I_2 + 2) = 0$   
~~10I\_2 - 10I\_1 + 20I\_2 - 20I\_1 + 3I\_2 + 45I\_2 + 90 = 0~~  
~~33I\_2 - 30I\_1 + 90 = 0~~  
~~33I\_2 - 30I\_1 = -90~~  
~~11I\_2 - 10I\_1 = -30~~  
~~11I\_2 - 10I\_1 = -30~~

14.	Using superposition principle, the contribution of the 45 V-voltage source to the current $i$ through the 60 Ω resistor is ....		
a.	$i_{45V} = -0.6 \text{ A.}$	b.	$i_{45V} = 0.6 \text{ A.}$
c.	$i_{45V} = 1.5 \text{ A.}$	d.	$i_{45V} = -1.2 \text{ A.}$

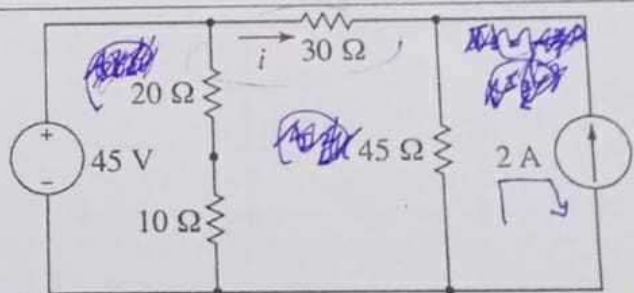

$i_{20} = \frac{45}{20} = 2.25A$   
 $V = \frac{12.86 \times 20}{30} = 8.57V$   
 $V = \frac{45 \times 30}{75 + 30} = 12.86$   
 $I = \frac{12.86}{30} = 0.4A$



$V = \frac{45 \times 75}{75 + 30} = 32.14$

$I = \frac{V}{R} = \frac{32.14}{75} = 0.4A$

$I_{30} = \frac{32.14 \times 30}{75} = 12.86A$   
 $I = \frac{V}{R}$



(13)

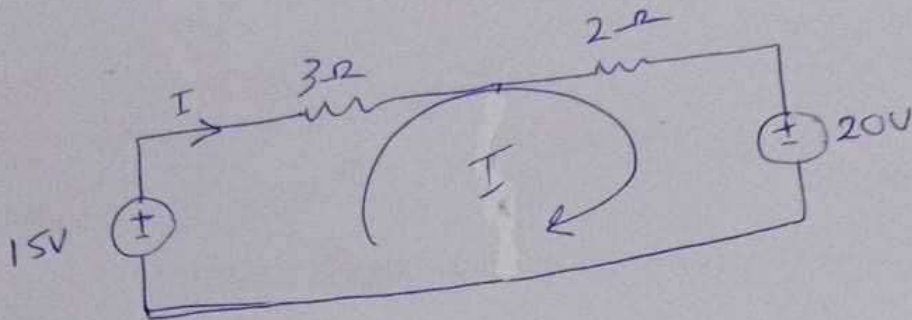
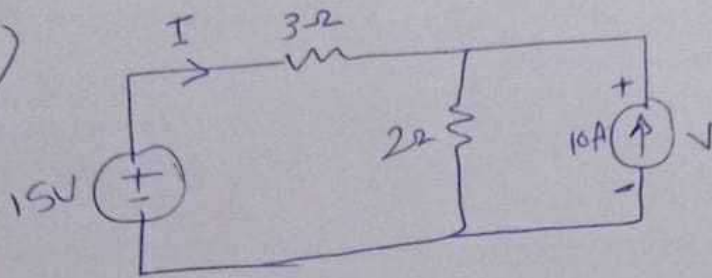


KVL :

$$-15 + 3I + 2I + 20 = 0$$




$$5I = 5$$

$$I = 1A \rightarrow I = -1A$$

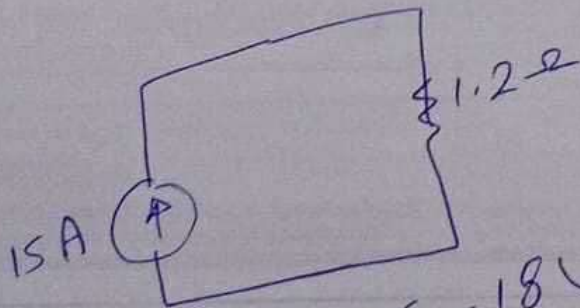
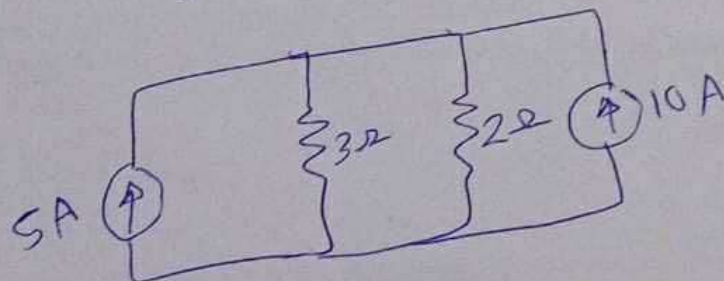


$$V = 1.2 \times 15 = 18V$$

15. For the circuit below, the Thevenin's equivalent seen between the terminals $ab$ is given as ..	
a.	
b.	
c.	
d.	

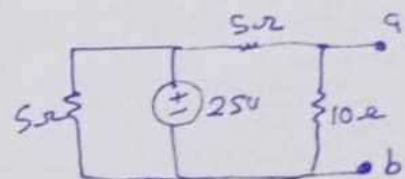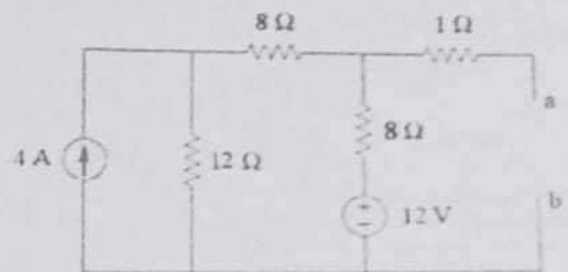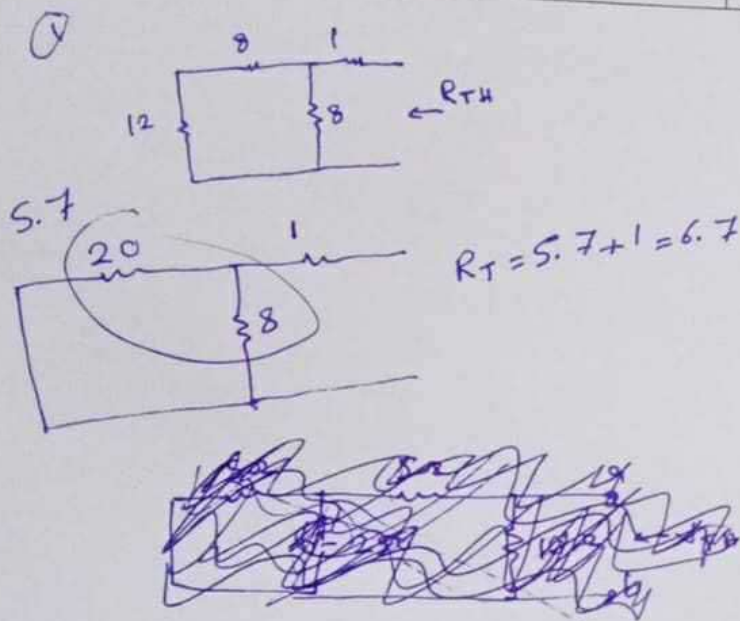

16. For the circuit shown below, what is the value of the resistor load to be connected between terminal $ab$ to transfer a maximum power? what is the maximum power?	
a.	$R_L = 5 \Omega$ , $P_{max} = 125 \text{ W}$
b.	$R_L = 20 \Omega$ , $P_{max} = 31.3 \text{ W}$
c.	$R_L = 5 \Omega$ , $P_{max} = 7.8 \text{ W}$
d.	$R_L = 20 \Omega$ , $P_{max} = 62.5 \text{ W}$

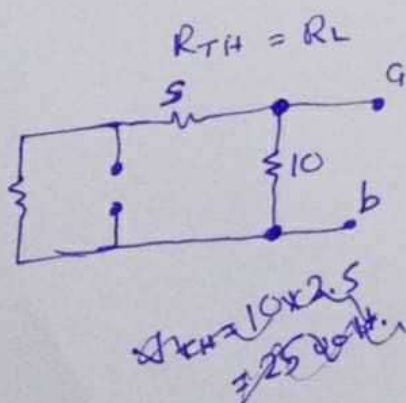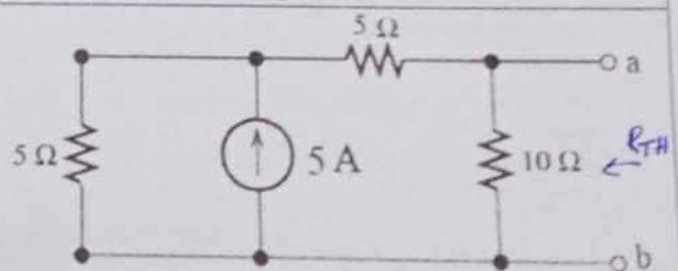


$$R_1 = 10 \Omega$$

$$R_2 = \frac{10 \times 10}{10 + 10} = 5 \Omega$$

~~$R_{TH} = 5 + 10 = 15 \Omega$~~

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$
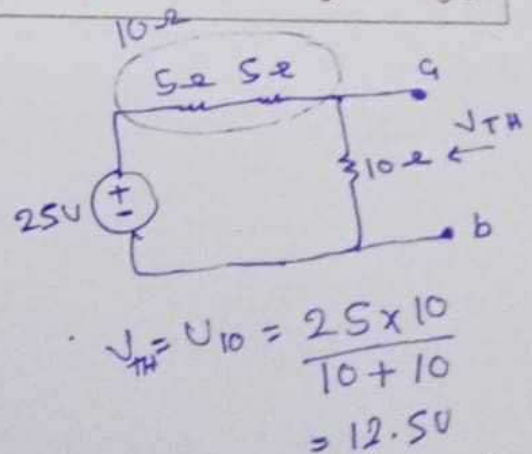
$$= \frac{(25)^2}{4 \times 20} = (2.5)^2$$








### Question # 1 (6 points)

For the circuit shown below, use the **principle of superposition** to find the current  $i$ . Draw the corresponding circuit diagrams

a.	Find the current $i_1$ due to the 6-V voltage source.	$i_1 =$	<b>3.5</b>	A
b.	Find the current $i_2$ due to the 2-A current source.	$i_2 =$	<b>1</b>	A
c.	Find the total current $i$ due to both sources.	$i =$	<b>4.5</b>	A

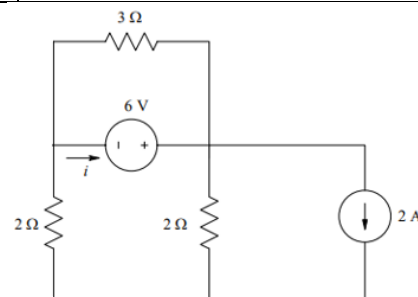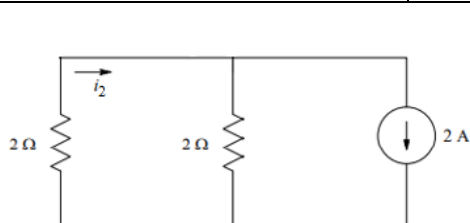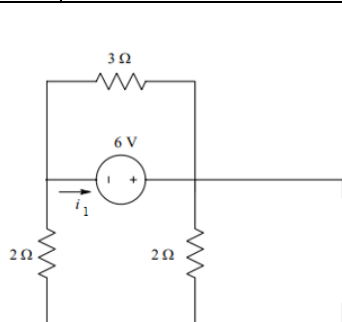

### Solution:

$$i_1 = 6/3 + 6/4 = 3.5 \text{ A}$$



$$i_2 = 2 \times 2/(2+2) = 1 \text{ A}$$

$$i = i_1 + i_2 = 3.5 + 1 = 4.5 \text{ A}$$

### Question # 2 (6 points)

For the circuit shown below, find


a.	the load resistance $R_L$ for maximum power transfer	$R_L =$	<b>6</b>	$\Omega$
b.	the Thevenin equivalent voltage using source transformation technique.	$V_{th} =$	<b>36</b>	V
c.	the maximum power absorbed by the load $R_L$ .	$P_{max} =$	<b>54</b>	W

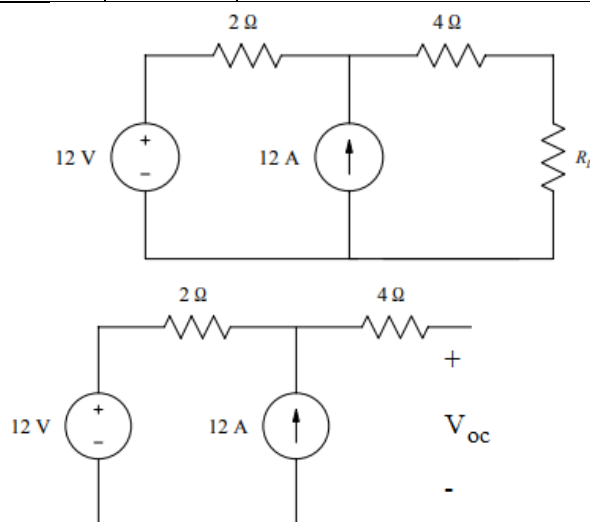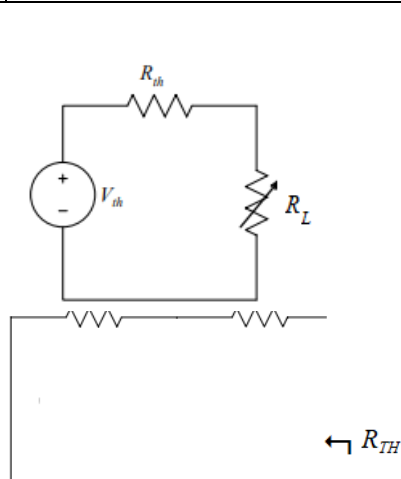
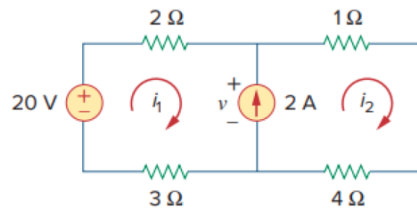
### Solution:

$$R_{th} = 2 + 4 = 6 \Omega \quad V_{th} = V_{oc} = 12 \times 2 + 12 = 36 \text{ V}$$

$$P_{max} = V_{th}^2 / (4 \times R_{th}) = (36 \times 36) / (4 \times 6) = 54 \text{ W}$$



**a) Mesh Equations**

From Mesh 1:

$$5i_1 + 5(i_1 + 2) = 20$$

Simplifying:

$$5i_1 + 5i_1 + 10 = 20 \Rightarrow 10i_1 = 10 \Rightarrow i_1 = \boxed{1 \text{ A}}$$

From the current source constraint:

$$i_2 = i_1 + 2 = 1 + 2 = \boxed{3 \text{ A}}$$

**b) Voltage across the current source**

Method 1:

$$v = 5i_2 = 5 \cdot 3 = \boxed{15 \text{ V}}$$


Method 2:

$$v = 20 - 5i_1 = 20 - 5 \cdot 1 = \boxed{15 \text{ V}}$$

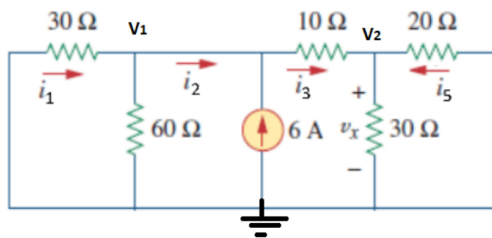**Final Answers:**

$$i_1 = 1 \text{ A}, \quad i_2 = 3 \text{ A}, \quad v = 15 \text{ V}$$





**Nodal Equations:**

$$\left( \frac{1}{60} + \frac{1}{30} + \frac{1}{10} \right) V_1 - \frac{1}{10} V_2 = 6$$

$$-\frac{1}{10} V_1 + \left( \frac{1}{10} + \frac{1}{30} + \frac{1}{20} \right) V_2 = 0$$

**Simplified Form:**

$$\frac{3}{20} V_1 - \frac{1}{10} V_2 = 6$$

$$-\frac{1}{10} V_1 + \frac{11}{60} V_2 = 0$$

**Cleared of Fractions:**  $3V_1 - 2V_2 = 120, \quad -6V_1 + 11V_2 = 0$

**Solutions:**

$$V_1 = \frac{440}{7} = 62.86 \text{ V}, \quad V_2 = \frac{240}{7} = 34.29 \text{ V}$$


**Current through the 10 Ω resistor:**

$$I_3 = \frac{V_1 - V_2}{10} = \frac{62.86 - 34.29}{10} = \frac{28.57}{10} = 2.857 \text{ A}$$

**Power supplied by the 6A current source:**

$$P_{6A} = -V_1 \cdot 6 = -62.86 \cdot 6 = \frac{-2640}{7} = -377.14 \text{ W}$$
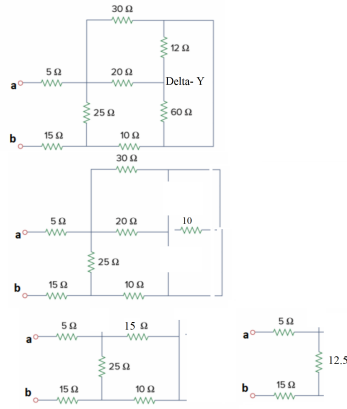
## Equivalent Resistance and Circuit Analysis Questions



To find the equivalent resistance between terminals  $a$  and  $b$ , we simplify the network step by step using series-parallel combinations and an effective transformation based on recognizing a short circuit.

The triangle formed by  $12\ \Omega$ ,  $60\ \Omega$ , and a short circuit ( $0\ \Omega$ ) can be replaced by:

$$R = \frac{12 \cdot 60}{12 + 60 + 0} = \frac{720}{72} = 10\ \Omega$$

This  $10\ \Omega$  resistor is in series with a  $20\ \Omega$  resistor:

$$R_1 = 10 + 20 = 30\ \Omega$$

The result is in parallel with a  $30\ \Omega$  resistor:

$$R_2 = \frac{30 \cdot 30}{30 + 30} = \frac{900}{60} = 15\ \Omega$$

Adding  $10\ \Omega$  in series:

$$R_3 = 15 + 10 = 25\ \Omega$$

Now this is in parallel with a  $25\ \Omega$  resistor:


$$R_4 = \frac{25 \cdot 25}{25 + 25} = \frac{625}{50} = 12.5\ \Omega$$

Adding the final series resistors  $5\ \Omega$  and  $15\ \Omega$ :

$$R_{\text{eq}} = 12.5 + 5 + 15 = \boxed{32.5\ \Omega}$$




### Current Divider (Q2\_B)

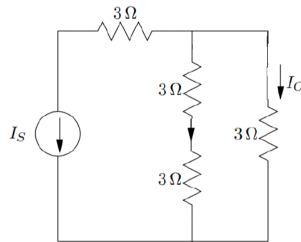

In this circuit, the total current  $I_s$  splits between two branches:  
 - Left branch: two  $3\Omega$  resistors in series  $\rightarrow R_1 = 6\Omega$  - Right branch: one  $3\Omega$  resistor  $\rightarrow R_2 = 3\Omega$   
 Using the current divider rule:

$$\frac{I_o}{I_s} = \frac{R_1}{R_1 + R_2} = -\frac{6}{6 + 3} = -\frac{6}{9} = -\boxed{\frac{2}{3}}$$


### Voltage Calculation (Figure 4)

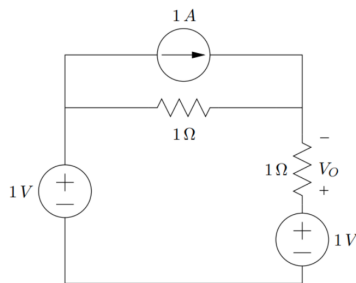

Walking through the loop clockwise:  
 - Bottom voltage source:  $+1\text{ V}$  - Middle resistor:  $1\text{ A} \cdot 1\Omega = +1\text{ V}$  - Top voltage source:  $-1\text{ V}$   
 Using KVL or voltage division:

$$V_o = (1\text{ V} - 1\text{ V} - 1\text{ A} \cdot 1\Omega) \cdot \frac{1}{1 + 1} = -1 \cdot \frac{1}{2} = -\boxed{0.5\text{ V}}$$

### Question 3: Mesh Analysis

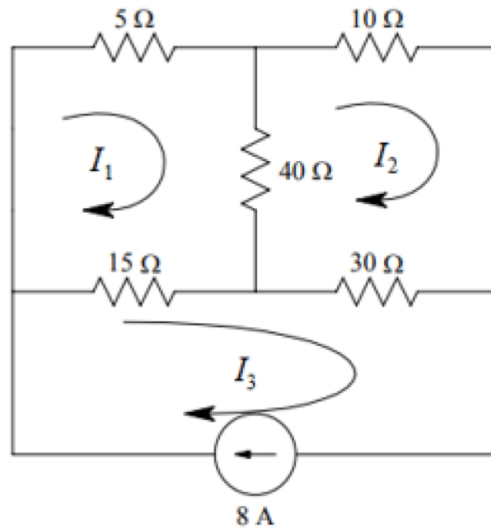

a) Mesh Equations:

$$\begin{aligned} 60i_1 - 40i_2 - 15 \cdot 8 &= 0 \\ -40i_1 + 80i_2 - 30 \cdot 8 &= 0 \end{aligned}$$

Answer:

$$i_1 = 6 \text{ A}, \quad i_2 = 6 \text{ A}, \quad i_3 = 8 \text{ A}$$

b) Current through the  $30 \Omega$  resistor:

$$i_{30\Omega} = i_2 - i_3 = -2 \text{ A}$$

c) Power dissipated by the  $15 \Omega$  resistor:

$$P_{15\Omega} = (i_1 - i_3)^2 \cdot 15 = (-2)^2 \cdot 15 = 60 \text{ W}$$

d) Power balance check:

Voltage across the  $8 \text{ A}$  current source:

$$V_{\text{source}} = \frac{P_{\text{absorbed}}}{I} = \frac{2340}{8} = 292.5 \text{ V}$$

Power supplied by the current source:

$$P_{\text{source}} = V \cdot I = 292.5 \cdot 8 = 2340 \text{ W}$$

Total power absorbed by resistors:

$$P_{15\Omega} + P_{60\Omega} + P_{30\Omega} = 60 + 2160 + 120 = 2340 \text{ W}$$

**Conclusion:** Power supplied equals power absorbed.  $\sum P = 0$  is satisfied.



# *Chapter 6*

# DC-CIRCUIT

30/7/2025

[1] Capacitors and inductors are called energy storage elements.

[2] A capacitor is a passive element designed to store energy in its electric field.

[3] A capacitor consists of two conducting plates separated by an insulator (or dielectric).


[4] Capacitance  $C$  is the ratio of the charge  $q$  on one plate of a capacitor to the voltage difference  $V$  between the two plates, measured in farads (F).

$$q = CV \quad C = \frac{\epsilon A}{d} \quad \epsilon \text{ permittivity}$$

[5] If  $i$  is flowing into the +ve terminal of  $C$

\* Charging  $\Rightarrow i$  is (+ve)

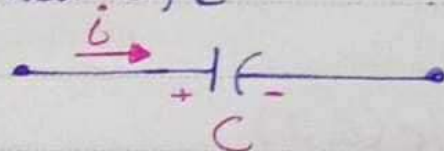\* Discharging  $\Rightarrow i$  is (-ve)



[6] The current-voltage relationship of capacitor according to above convention is

$$i = C \frac{dV}{dt} \quad V = \frac{1}{C} \int_{t_0}^t i \, dt + V_0(t_0)$$

[7] The energy,  $w$ , stored in the capacitor is:


$$W = \frac{1}{2} CV^2$$

[8] A capacitor is

\* an open circuit to dc ( $dV/dt = 0$ ).

\* its voltage cannot change abruptly

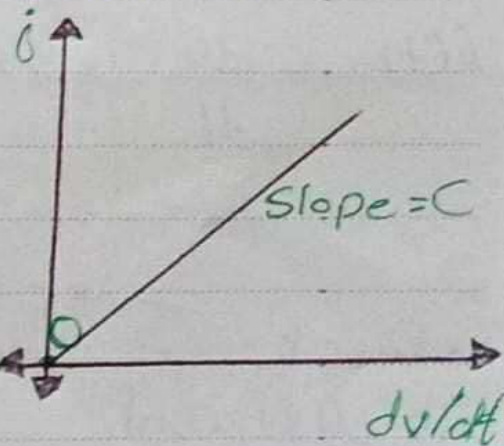Units: F, pF ( $10^{-12}$ ), nF ( $10^{-9}$ ),  $\mu$ F ( $10^{-6}$ )





### Example (6.1)

- a) Calculate the charge stored on 3 PF capacitor with 20V across it.  
b) Find the energy stored in the capacitor.

Sol:

a)  $q = CV = 3 \times 10^{-12} \times 20 = 60 \text{ PC}$

b)  $w = \frac{1}{2} CV^2 = \frac{1}{2} \times 3 \times 10^{-12} \times (20)^2 = 600 \text{ PJ}$

\* What is the Power?  $P = \frac{dw}{dt} = 0$

$P = Vi = (20) \left( C \frac{dv}{dt} \right) = 0$  →  $\frac{dw}{dt} = 0$

### Example (6.2)

The voltage across a 5-MF capacitor is

$v(t) = 10 \cos 6000t \text{ V}$  →  $\omega = 2\pi f$

Calculate the current through it.  $f = \frac{1}{T}$

Sol:-

$i(t) = C \frac{dv}{dt} = 5 \times 10^{-6} \times \frac{d(10 \cos 6000t)}{dt}$

$= -5 \times 10^{-6} \times 6000 \times 10 \sin 6000t$

$= -0.3 \sin 6000t \text{ A}$

\* Discharge capacitor because the sign of  $v$  &  $i$  is different.



### Example (6.3)s

Determine the voltage across 2- $\mu$ F capacitor if the current through is

$$i(t) = 6e^{-3000t} \text{ mA}$$


Assume that the initial capacitor voltage is zero.

$$v = \frac{1}{C} \int_0^t i \, dt + v(0)$$

$$v = \frac{1}{2} \int_0^t 6e^{-3000t} \, dt \cdot 10^{-3}$$

$$= \frac{3 \times 10^3}{-3000} e^{-3000t} \Big|_0^t = (1 - e^{-3000t}) \text{ V}$$

### Example (6.4)s

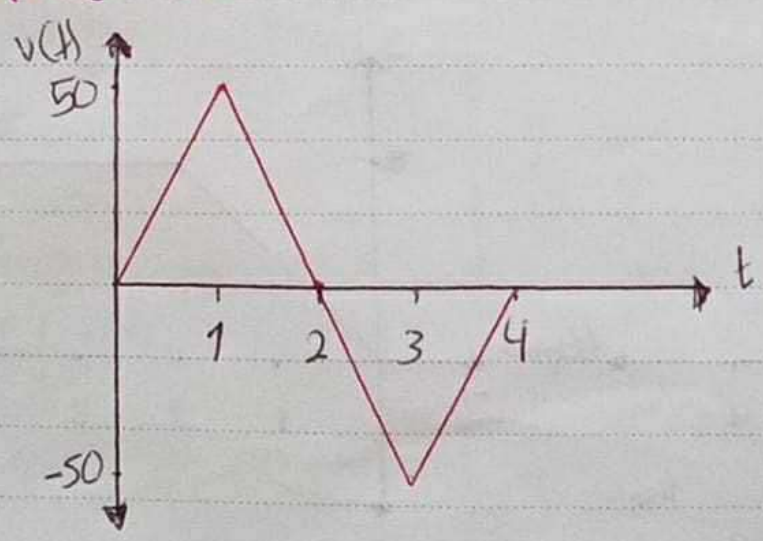


Determine the current through 200- $\mu$ F capacitor.

$$v(t) = \begin{cases} 50t, & 0 \leq t < 1 \\ 100 - 50t, & 1 \leq t < 2 \\ -200 + 50t, & 2 \leq t < 4 \\ 0, & \text{otherwise} \end{cases}$$



$$i = C \, dv/dt, \quad C = 200 \, \mu\text{F}$$
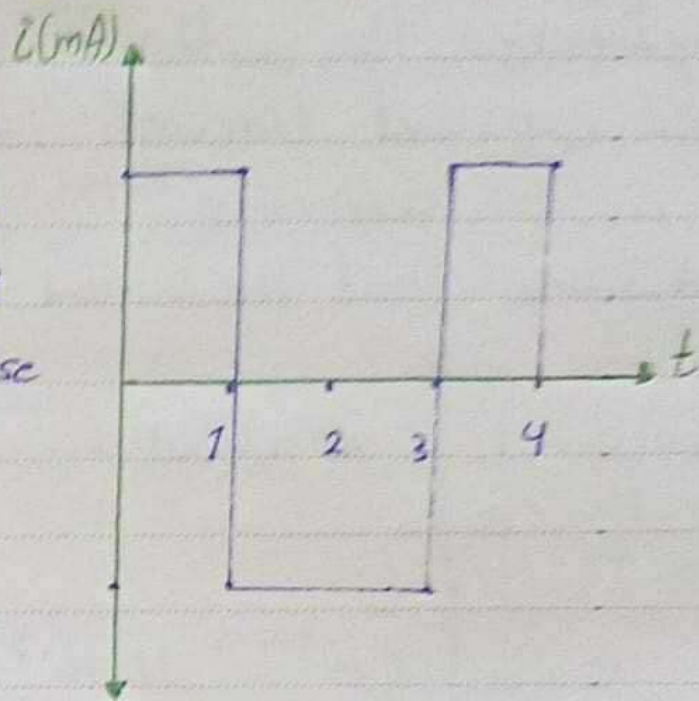
$$i(t) = 200 \times 10^{-6} \times \begin{cases} 50 & 0 < t < 1 \\ -50 & 1 < t < 3 \\ 50 & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$





$$= \begin{cases} 10 \, \text{mA} & 0 < t < 1 \\ -10 \, \text{mA} & 1 < t < 3 \\ 10 \, \text{mA} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

Exit Example:

Find the capacitor voltage that is associated with the current shown graphically. The value of the cap. is  $5 \, \mu\text{F}$ .
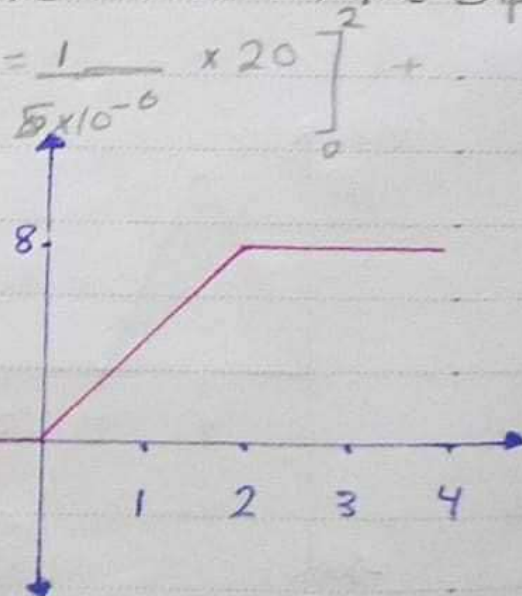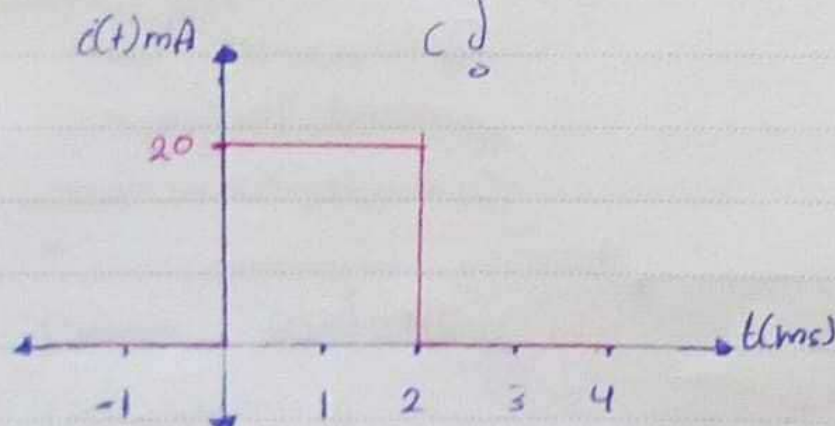
$$v = \frac{1}{C} \int_0^t i(t) \, dt + v(0) = \frac{1}{5 \times 10^{-6}} \times 20 \int_0^2 +$$




$$\begin{aligned} i &= C \, dv/dt \\ dv &= \frac{i}{C} \, dt \\ v &= \frac{i}{C} t \end{aligned} \quad \begin{cases} v(t) = 0 & t \leq 0 \\ = 1000t & 0 \leq t \leq 2 \, \text{ms} \\ = 8 & t \geq 2 \, \text{ms} \end{cases}$$

$\hookrightarrow \frac{1}{5 \times 10^{-6}} (0) + 8000 \times 10^{-3}$



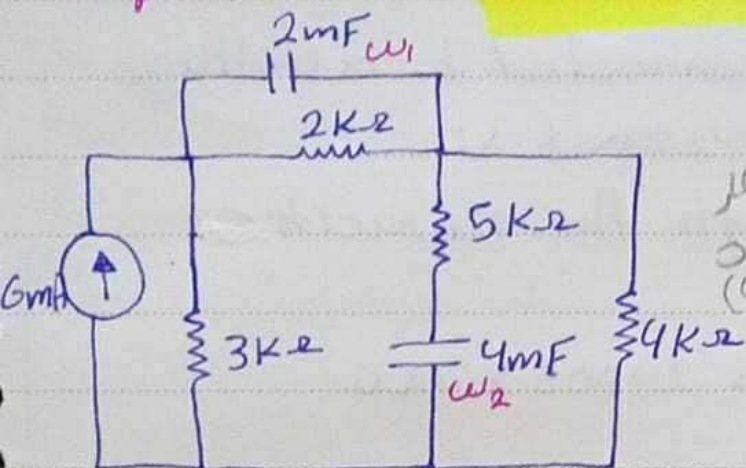Example (6.5):

In DC circuit each capacitor replace O.C.




$$w = \frac{1}{2} C V^2$$

الشارة بالدارت (4+2)  $i = \frac{3}{3+2+4} (6mA) = 2mA$

$$V_1 = 2000 i = 4V$$

$$V_2 = 4000 i = 8V$$
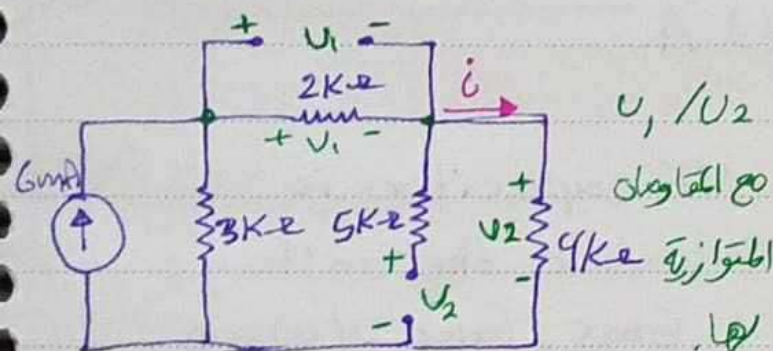
$$w_1 = \frac{1}{2} C_1 V_1^2 = \frac{1}{2} (2 \times 10^{-3}) (4)^2 = 16mJ$$



$$w_2 = \frac{1}{2} C_2 V_2^2 = \frac{1}{2} (4 \times 10^{-3}) (8)^2 = 128mJ$$

Practice Problem (6.1)

What is the voltage across a 4.5-μF capacitor if the charge on one plate is 0.12mC? How much energy is stored?

$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_{t_0}^t i(t) dt + v(0)$$

$$q = CV$$

$$V = \frac{q}{C} = \frac{0.12 \times 10^{-3}}{4.5 \times 10^{-6}} = 26.67 \text{ volt}$$

$$w = \frac{1}{2} C V^2 = \frac{1}{2} \times 4.5 \times 10^{-6} \times (26.67)^2 = 1.6mJ$$



### Practice Problem 6.2:

If a 10- $\mu$ F capacitor is connected to a voltage source with  $v(t) = 75 \sin 2000t$  V determine the current through the capacitor.

$$i = C \frac{dv}{dt} = 10 \times 10^{-6} \times 75 \times \cos 2000t \times 2000$$

$$= 1.5 \cos(2000t) \text{ A.}$$

### Practice Problem 6.3:

The current through a 100- $\mu$ F capacitor is  $i(t) = 50 \sin(120\pi t)$  mA. Calculate the voltage across it at  $t = 1$  ms and  $t = 5$  ms. Take  $v(0) = 0$ .


$$v = \frac{1}{C} \int_0^t 50 \sin(120\pi t) dt + 0$$

$$= \frac{1}{100 \times 10^{-6}} \times 50 \times \frac{\cos(120\pi t)}{120\pi}$$

$$v(1) = \frac{1}{100 \times 10^{-6}} \times 50 \times \frac{\cos(120\pi \times 1 \times 10^{-3})}{120\pi}$$



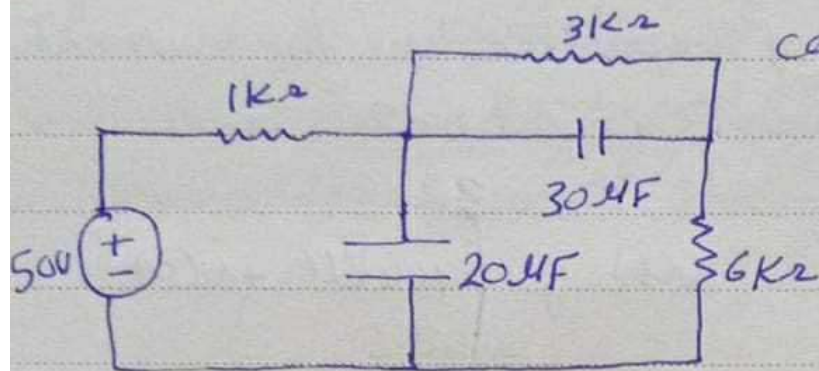Practice Problem 6.5: Find the energy stored in the capacitor.




$$i = \frac{50}{1+3+6} = 5 \text{ mA}$$

$$V_1 = 6 \times 10^3 \times 5 \times 10^{-3} = 30 \text{ volt}$$

$$V_2 = 3 \times 10^3 \times 5 \times 10^{-3} = 15 \text{ volt}$$
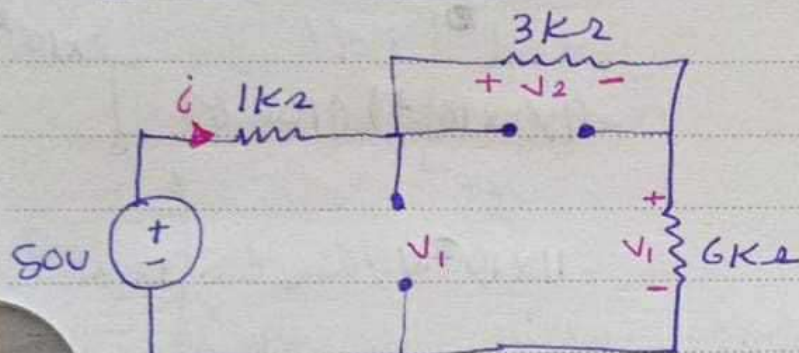
$$W = \frac{1}{2} C V^2 = \frac{1}{2} \times 20 \times 10^{-6} \times (50)^2 = 0.025 \text{ J}$$




$$W = \frac{1}{2} \times 3 \times 10^3 \times (15)^2 = 3.375 \text{ mJ}$$

### Exercise:


The voltage across a 5-μF capacitor is given.

$v(t)$  (V)

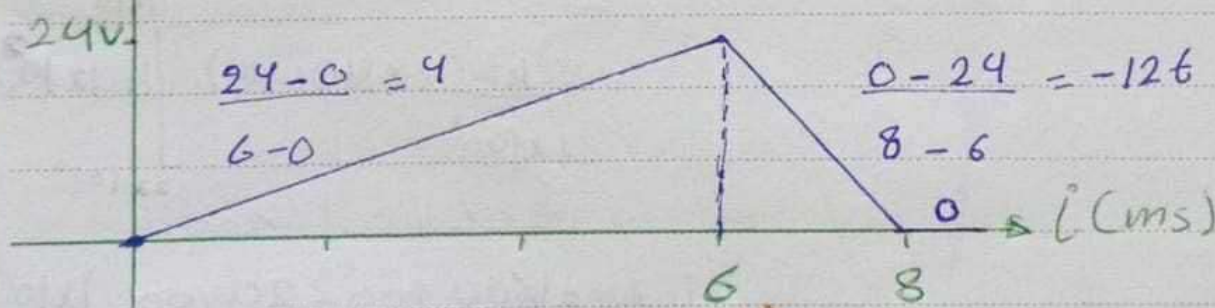

$$i = C \frac{dv}{dt}$$
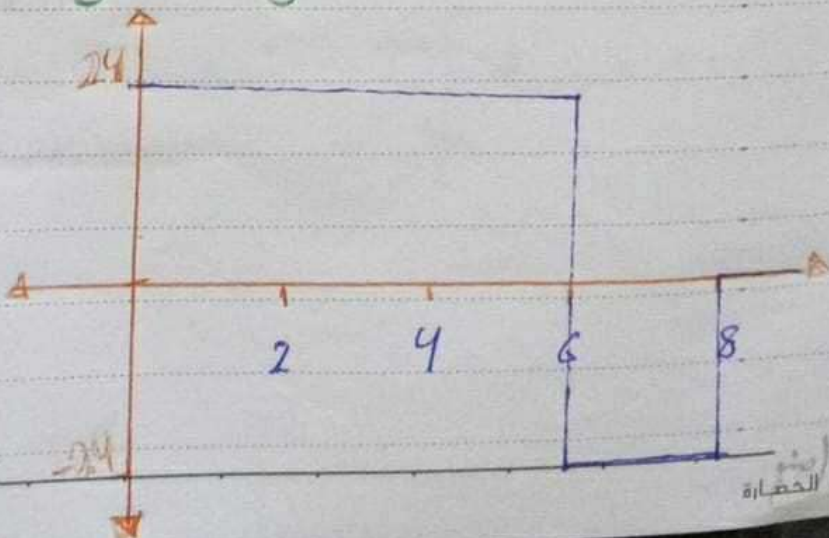
$$i(t) = \begin{cases} 4t, & 0 \leq t \leq 6 \\ -12t, & 6 \leq t \leq 8 \\ 0, & t > 8 \end{cases}$$






# Series and Parallel Capacitors.

## \* Capacitors in Parallel:

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$


Proof:

$$i = i_1 + i_2 + i_3 + \dots + i_N$$

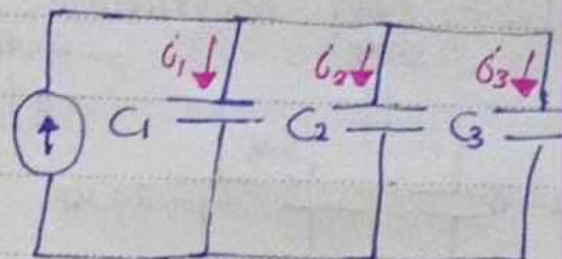



$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$
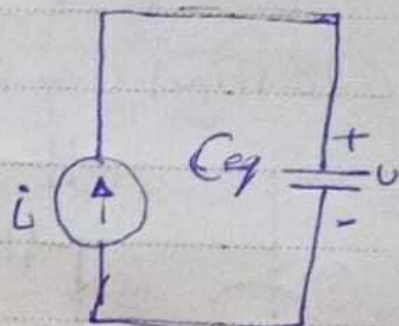
$$= \sum_{k=1}^N C_k \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$


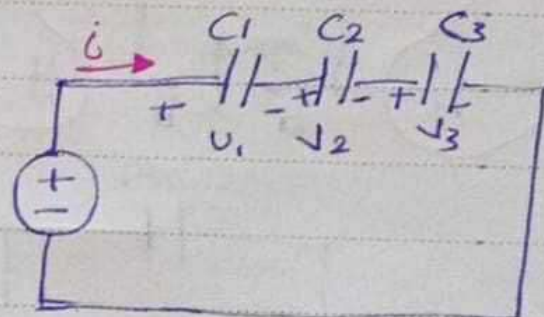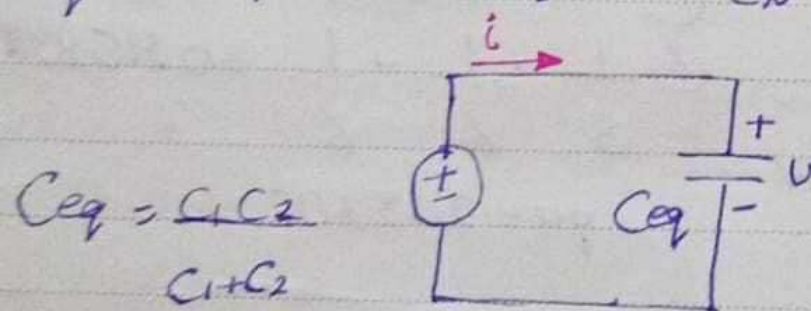
## \* Capacitors in series:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$



Proof:


$$v = v_1 + v_2 + v_3 + \dots + v_N$$

$$v = \frac{1}{C_1} \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(\tau) d\tau + v_2(t_0) + \dots$$

$$= \left( \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + v_2(t_0) = \frac{1}{C_{eq}} \int_{t_0}^t i(\tau) d\tau + v_0$$



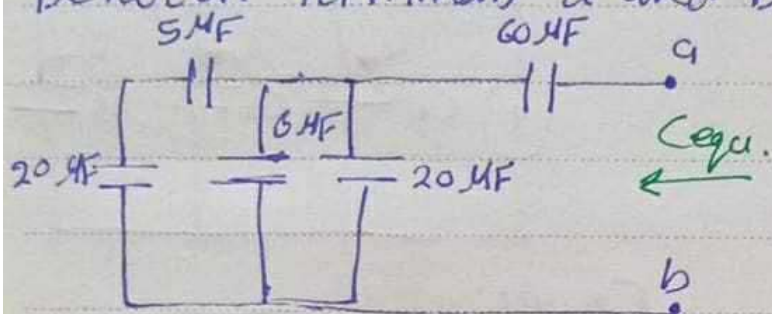Example (6.6): Find the equivalent capacitance seen between terminals a and b.




$$20 \times 5 = 4 \mu F$$

$$20 + 5$$

$$4 + 6 + 20 = 30$$

$$C_{eq} = (30 \times 60) / (30 + 60) = 20 \mu F$$

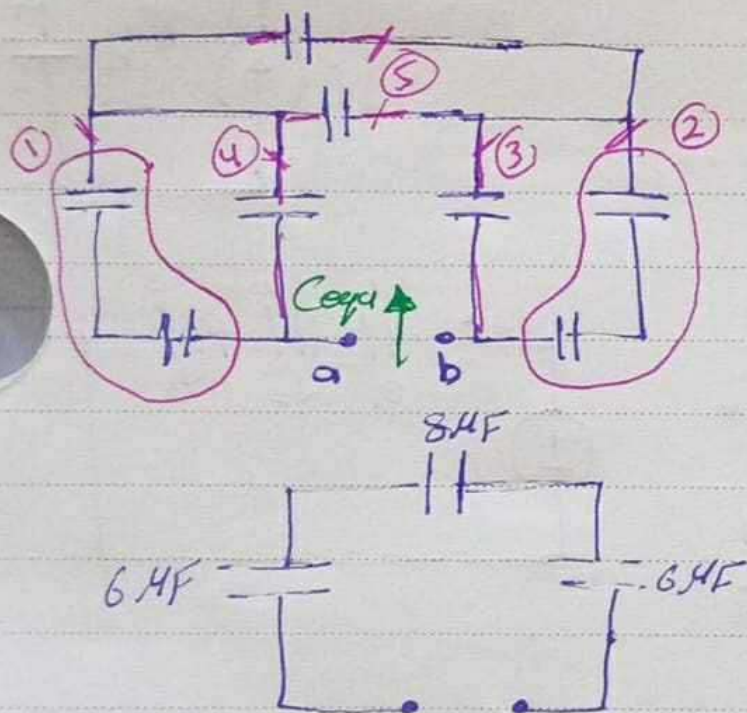6.18 Find  $C_{eq}$  in the circuit if all capacitors are  $4 \mu F$



$$\textcircled{1} 4 \times 4 = 2 \mu F$$

$$4 + 4$$

$$\textcircled{2} 2 \mu F$$

$$\textcircled{3} 2 + 4 = 6 \mu F$$


$$\textcircled{4} 2 + 4 = 6 \mu F$$

$$\textcircled{5} 4 + 4 = 8 \mu F$$

$$\textcircled{6} \frac{1}{8} + \frac{1}{6} + \frac{1}{6} = 0.4583 \mu F$$

$$C_{eq} = 2.18 \mu F$$

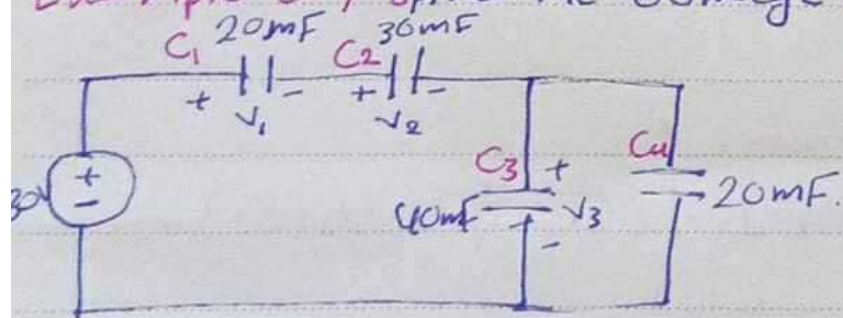Example 6.7: Find the voltage across each capacitor.



$V_3 \rightarrow$  is the same as  $C_3$  &  $C_4$  because it's parallel


$$C_{eq} = \frac{1}{20} + \frac{1}{30} + \frac{1}{60} = 10 \text{ mF}$$

$$q_{\text{total}} = C_{eq}(30) = 0.3C, \text{ charge acts like current, } q_1 = q_2 = q_{\text{total}}$$

$$V_1 = \frac{q_1}{C_1} = 15V, V_2 = \frac{q_2}{C_2} = 10V, V_3 = 30 - V_1 - V_2 = 5V$$



### Practice Problem 6.6:

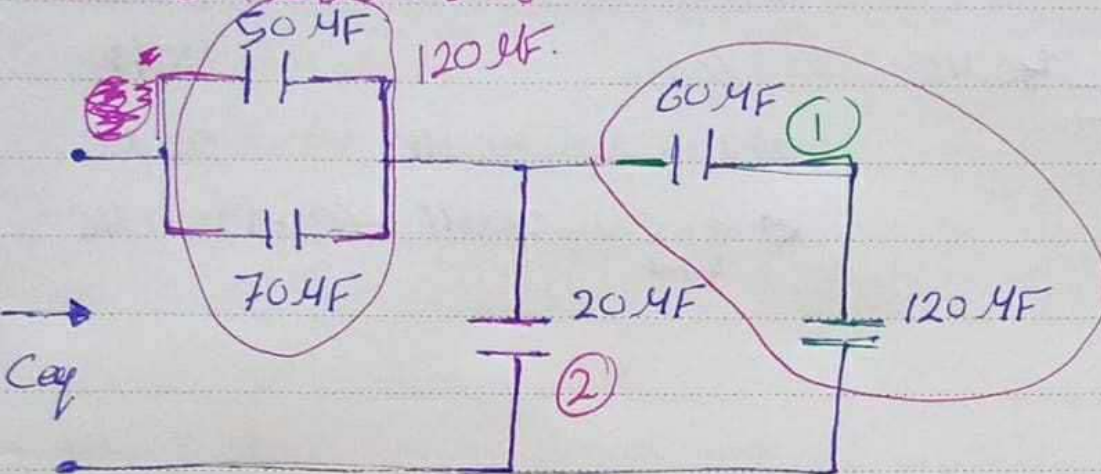


$$C_1 = \frac{60 \times 120}{60 + 120} = 40 \mu F$$

$$C_2 = 40 + 20 = 60 \mu F$$

$$C_3 = \frac{60 \times 120}{60 + 120} = 40 \mu F$$
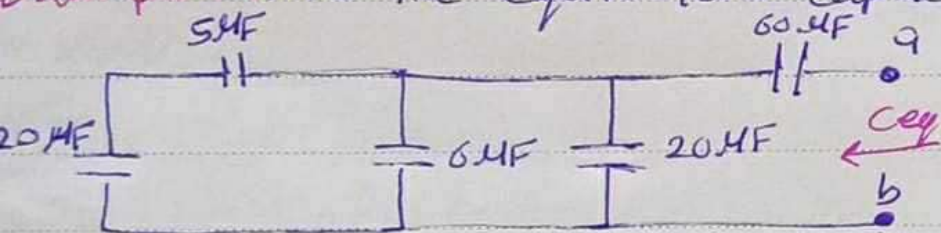
### Example 7: Find the equivalent capacitance between a and b.



$$C_{eq} = 15 \mu F$$

### Exercise: Compute the equivalent capacitance.


$$1) 2 + 4 = 6 \mu F$$

$$2) 6 \times 3 = 2 \mu F$$


$$6 + 3$$


$$3) 2 + 2 = 4 \mu F$$
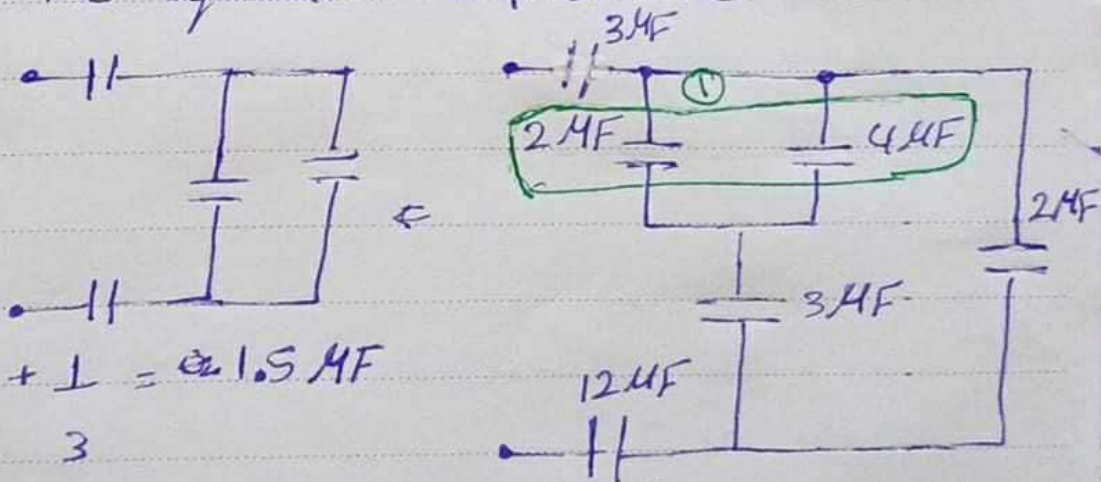
$$4) C_{eq} = \frac{1}{4} + \frac{1}{12} + \frac{1}{3} = 1.5 \mu F$$


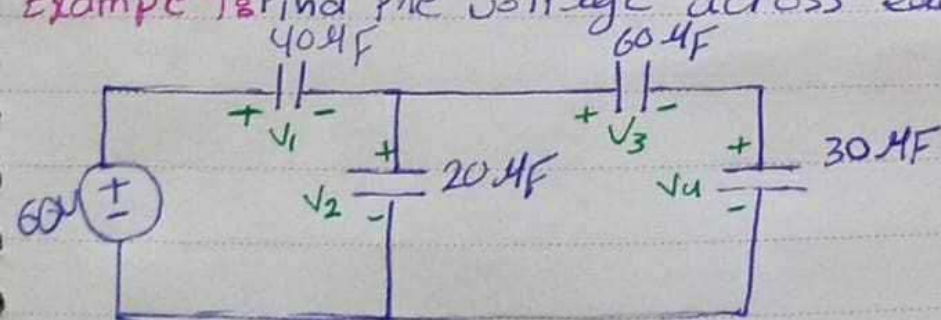
### Example 9: Find the voltage across each of the



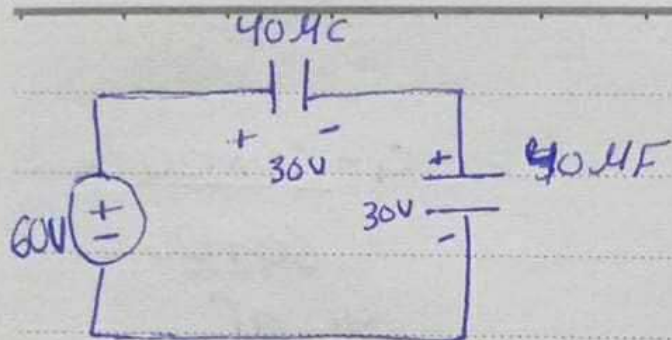

$$1) 60 \times 30 = 20 \mu F$$

$$3) 40 \times 30$$

$$60 + 30$$

$$40 + 30$$

$$2) 20 + 20 = 40 \mu F$$

$$= 20 \mu C$$

$$q_{total} = CV = 20 \mu F \times 60 = 1200 \mu C$$



# Inductors

- ① passive element designed to store energy in its magnetic field.
  - ② An inductor consists of a coil of conducting wire.
  - ③ Inductance is the property where by an inductor exhibits opposition to the change of current flowing through it.
- \* Measured in henrys (H).

$$V = L \frac{di}{dt} \quad \text{and} \quad L = \frac{N^2 \mu A}{l}$$

$N \rightarrow$  number of turns

$l \rightarrow$  length

$$\mu = \mu_r \mu_0$$

$A \rightarrow$  cross-section area.


$$\mu_0 = 4\pi \times 10^{-7} \text{ (H/m)}$$

$\mu \rightarrow$  permeability of the

\* The unit of inductors (mH) and (kH). core.

\* The current-voltage relationship of an inductor:
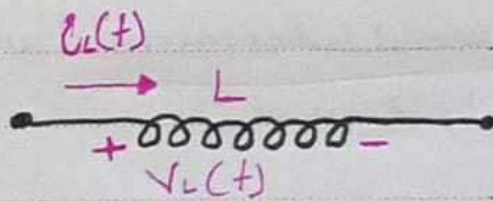
$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$



\* The energy stored by an inductor is  $W = \frac{1}{2} L i^2$

\* An inductor acts like a short circuit to dc ( $di/dt = 0$ ) and its current cannot change abruptly.

$$* V = L \frac{di}{dt}$$



**Example 6.8:** The current through a  $0.1 \text{ H}$  inductor is  $i(t) = 10e^{-5t}$ . Find the voltage across the inductor and the energy stored.

$$V = L \frac{di}{dt}$$


$$L = 0.1 \text{ H}$$

$$v = 0.1 \frac{d(10te^{-5t})}{dt} = e^{-5t} + t(-5)e^{-5t} = e^{-5t}(1-5t) \text{ V}$$

\* The energy stored is:-

$$w = \frac{1}{2} Li^2 = \frac{1}{2} (0.1)(100)t^2 e^{-10t} = 5t^2 e^{-10t} \text{ J}$$

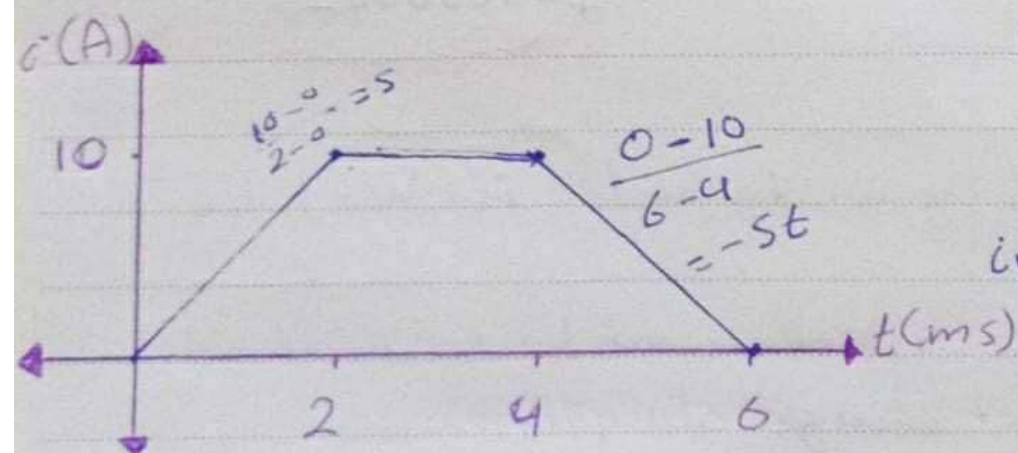**6.40:** The current through a  $5 \text{ mH}$  inductor is shown in Figure. Determine the voltage across the inductor at  $t = 1, 3$  and  $5$ .




$$v(t) = L \frac{di}{dt}$$

$$i(t) = \begin{cases} 5t, & 0 < t < 2 \text{ ms} \\ 10, & 2 < t < 4 \text{ ms} \\ 30-5t, & 4 < t < 6 \text{ ms} \end{cases}$$

$$v = L \frac{di}{dt} = \frac{5 \times 10^{-3}}{10^{-3}} \begin{cases} 5, & 0 < t < 2 \text{ ms} \\ 0, & 2 < t < 4 \text{ ms} \\ -5, & 4 < t < 6 \text{ ms} \end{cases}$$


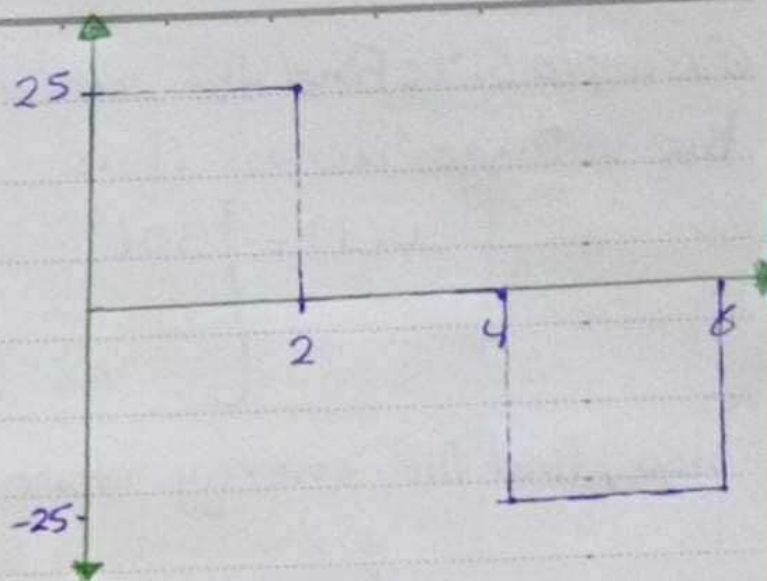
$$v = \begin{cases} 25, & 0 \leq t \leq 2 \text{ ms} \\ 0, & 2 \leq t \leq 4 \text{ ms} \\ -25, & 4 \leq t \leq 6 \text{ ms} \end{cases}$$




At  $t = 1 \text{ ms}$ ,  $v = 25 \text{ V}$

At  $t = 3 \text{ ms}$ ,  $v = 0 \text{ V}$

At  $t = 5 \text{ ms}$ ,  $v = -25 \text{ V}$

6.42: If the voltage is applied across the terminals of 5-H inductor, calculate the current through the inductor.

Assume  $i(0) = -1 \text{ A}$ .

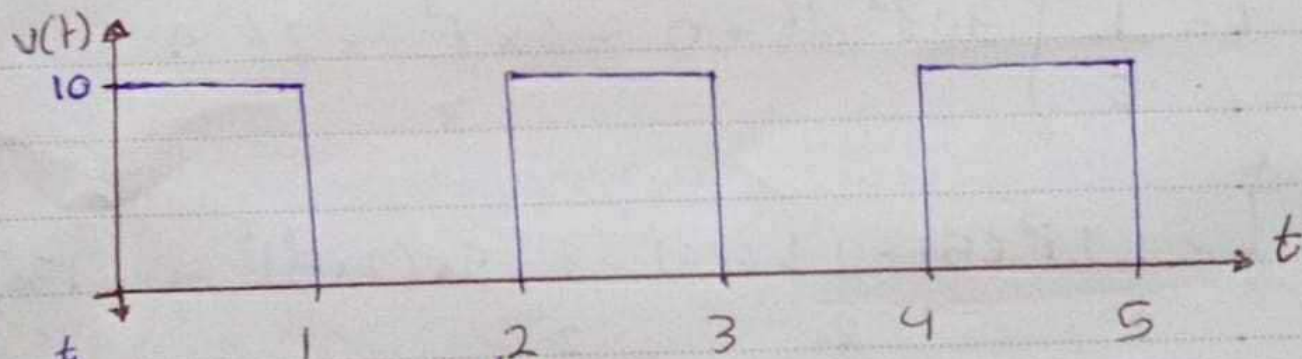

$$i = \frac{1}{L} \int_0^t v dt + i(0) = \frac{1}{5} \int_0^t v dt - 1$$

$$\text{For } 0 \leq t < 1, i = \frac{10}{5} \int_0^t t dt - 1 = 2t - 1 \text{ A}$$

$$\text{For } 1 \leq t < 2, i = 0 + i(1) = 1 \text{ A}$$

$$\text{For } 2 \leq t < 3, i = \frac{1}{5} \int_2^t 10 dt + i(2) = 2t \Big|_2^t + 1 = 3 \text{ A}$$

$$\text{For } 3 \leq t < 4, i = 0 + i(3) = 3 \text{ A}$$

$$\text{For } 4 \leq t < 5, i = \frac{1}{5} \int_4^t 10 dt + i(4) = 2t \Big|_4^t + 3 = 2t - 5 \text{ A}$$



Example 6.9: Find the current through a 5-H inductor if the voltage across it is

$$v(t) = \begin{cases} 30t^2 & , t > 0 \\ 0 & , t < 0 \end{cases}$$

Also, find the energy stored at  $t = 5$  s. Assume  $i(0) = 0$ .


Since  $i = \frac{1}{L} \int_0^t v(t) dt + i(t_0)$  and  $L = 5$  H.

$$i = \frac{1}{5} \int_0^t 30t^2 dt + 0 = 6 \times \frac{t^3}{3} = 2t^3 \text{ A.}$$

$$w = \int_0^5 \frac{1}{2} L i^2(5) - \frac{1}{2} L i(0) = \frac{1}{2} \times 5 \times (2 \times 5^3)^2 - 0 = 156.25 \text{ kJ}$$



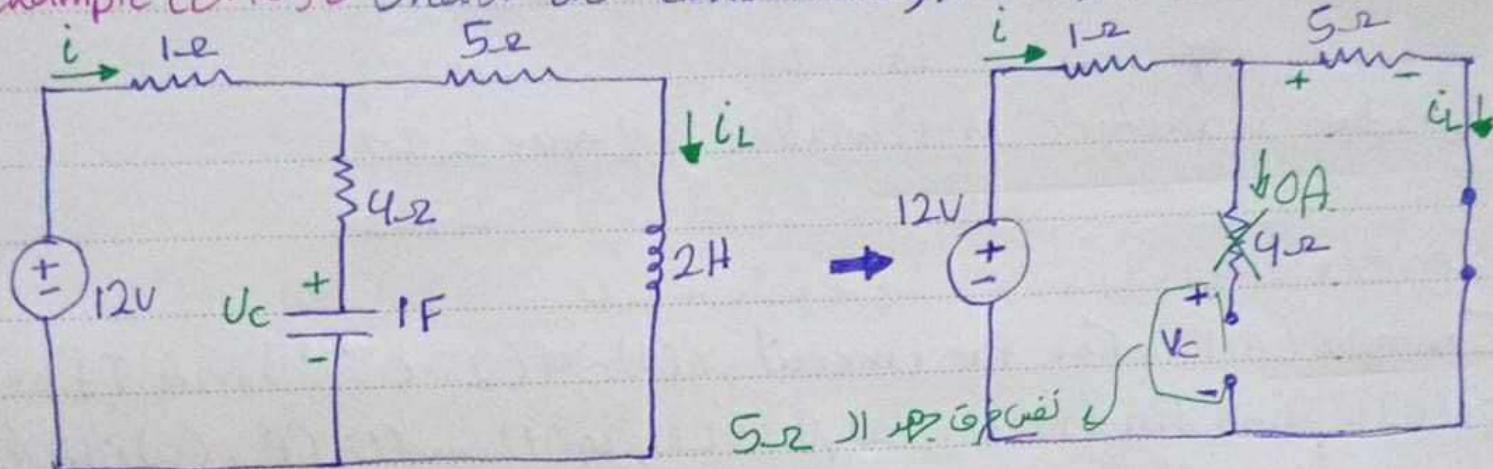Example (6.10): Under dc conditions, find a)  $i$ ,  $V_C$  and  $i_L$ .



$$i = i_L = \frac{12}{5+1} = 2A$$

$$V_C = 5i = 10V$$

$$W_C = \frac{1}{2} C V^2 = \frac{1}{2} (1) (10^2) = 50J$$

$$W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (2) (2^2) = 4J$$




# Series and Parallel Inductors.

Parallel:  $\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$

For two inductors in Parallel:  $L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$

Series:  $L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$

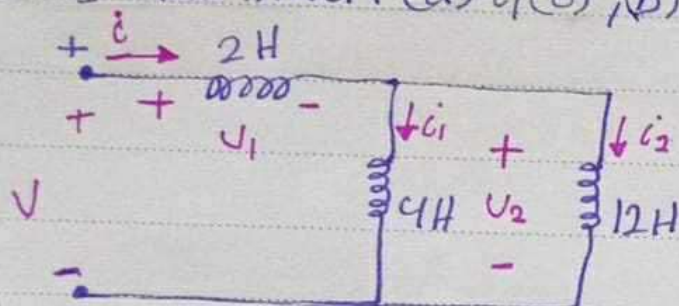
Example (6.12): For the circuit,  $i(t) = 4(2 - e^{-10t})$  mA. If  $i_2(0) = -1$  mA. Find: (a)  $i_1(0)$ , (b)  $v(t)$ ,  $v_1(t)$  and  $v_2(t)$ , (c)  $i_1(t)/i_2(t)$



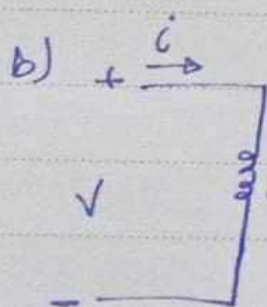a)  $i = i_1 + i_2$

$i(0) = i_1(0) + i_2(0)$

$4 = i_1(0) + -1 \Rightarrow i_1(0) = 5$  mA.



$v = L_{eq} \frac{di}{dt} = (5)(4)(-10)e^{-10t} = -200e^{-10t}$  mV

$v_1 = 2 \frac{di}{dt} = 2(4)(-10)e^{-10t}$


$v_2 = V - v_1 =$



$$c) i_1(t) = \frac{1}{L} \int_0^t v_2(t') dt' = \frac{1}{4} \int_0^t$$

$$i_2(t) = i(t) - i_1(t)$$

Example (6.11):

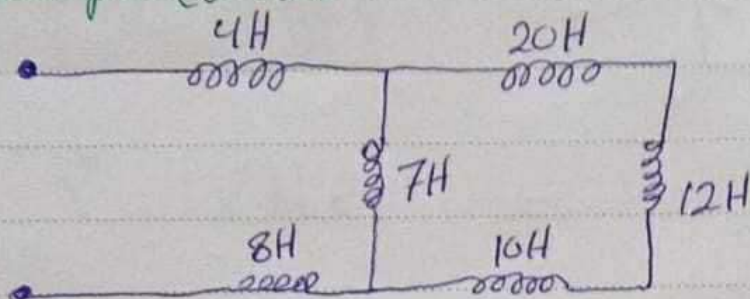


$$R(1) = 20 + 12 + 10 = 42 \text{ H}$$

$$L(2) = \frac{42 \times 7}{42 + 7} = 6 \text{ H}$$

$$L(3) = 4 + 6 + 8 = 18 \text{ H}$$

Practice Problem 6.11:

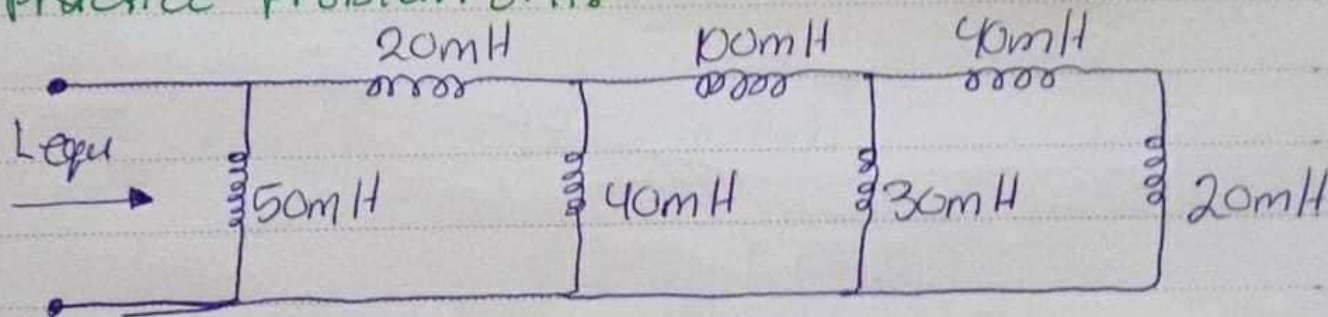

$$L(1) = 20 + 40 = 60 \text{ mH}$$

$$L(2) = \frac{60 \times 30}{60 + 30} = 20 \text{ mH}$$


$$L(3) = 20 + 100 = 120 \text{ mH}$$

$$L(4) = \frac{40 \times 120}{40 + 120} = 30 \text{ mH}$$

$$L(5) = 30 + 20 = 50 \text{ mH}$$

$$L(6) = \frac{50 \times 50}{50 + 50} = 25 \text{ mH}$$

# Particle Problem 6.128

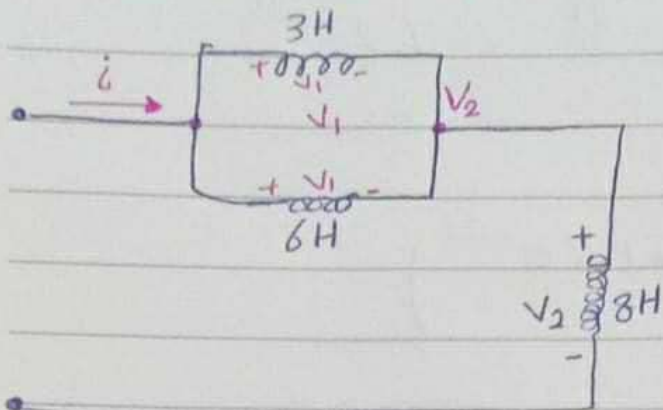

$$i_1(t) = 0.6e^{-2t}$$

$$i(0) = 1.4A$$

a) Find  $i_2(0)$ .

b) Find  $i_2(t)$  and  $i(t)$ .

c) Find  $V_1(t)$ ,  $V_2(t)$  and  $V(t)$ .

$$\begin{aligned} \text{a) } i_2(0) &= i(0) - i_1(0) \rightarrow i_1(0) = 0.6e^{-2 \times 0} = 0.6 \\ &= 1.4 - 0.6 \\ &= 0.8A \end{aligned}$$

$$\text{b) } i_2 = \frac{1}{L_2} \int V_1 dt$$

$$\begin{aligned} \text{For } 6H \Rightarrow (3H, 6H) \text{ لولتان متساويتان} \\ V_1(t) = L \frac{di}{dt} \\ = 6 \times -2 \times 0.6e^{-2t} \\ = -7.2e^{-2t} \end{aligned}$$

$$\begin{aligned} \text{For } 3H \Rightarrow \\ -7.2e^{-2t} = 3 \frac{di_2(t)}{dt} \end{aligned}$$

$$\begin{aligned} \frac{di_2(t)}{dt} &= \frac{-7.2e^{-2t}}{3} \\ &= -2.4e^{-2t} \end{aligned}$$

$$\begin{aligned} i_2(t) &= \int -2.4e^{-2t} dt \\ &= -\frac{2.4e^{-2t}}{-2} + C \end{aligned}$$

$$= +1.2e^{-2t} + C$$

$$i_2(0) = 0.8$$

$$i_2(0) = +1.2e^{-2 \times 0} + C = 0.8$$

$$C = 0.8 - 1.2 = -0.4$$

$$i_2(t) = 1.2e^{-2t} - 0.4$$

$$i(t) = i_1(t) + i_2(t)$$

$$= 0.6e^{-2t} + (-0.4 + 1.2e^{-2t})$$

$$= -0.4 + (0.6 + 0.4)e^{-2t}$$

$$= -0.4 + 1.8e^{-2t}$$

$$i(t) = 1.8e^{-2t} - 0.4$$



c)

$$v_1(t) = L \frac{di}{dt} = 6 \times 0.6 \times -2 \times e^{-2t} = -7.2 e^{-2t}$$

$$v_2(t) = L \frac{di}{dt} = 8 \frac{d}{dt} (-0.4 + 1.8 e^{-2t})$$

$$= 8(0 + 1.8 \times -2 \times e^{-2t})$$

$$= 8 \times (-3.6 e^{-2t})$$

$$= -28.8 e^{-2t} \text{ V}$$

$$v(t) = v_1(t) + v_2(t)$$

$$= (-7.2 e^{-2t}) + (-28.8 e^{-2t})$$

$$= (-7.2 - 28.8) e^{-2t}$$

$$= -36 e^{-2t} \text{ V}$$

*Chapters-*

*9 + 10*



# AC circuits Analysis.


## \* Complex numbers:

$$\vec{X} = a + j^{\rightarrow} b \quad (\text{rectangular form})$$

$$a = \text{Re} \{ \vec{X} \}$$

$$b = \text{Im} \{ \vec{X} \}$$

$$\vec{X} = |\vec{X}| \angle \theta \quad (\text{Polar form}).$$

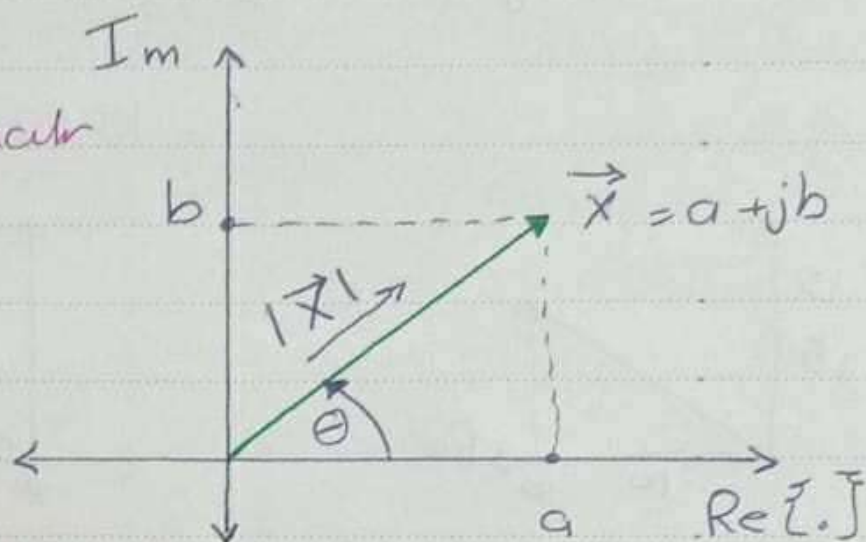

## \* Convert from rectangular form to polar form:

$$\vec{X} = a + jb, \quad |\vec{X}| = \sqrt{a^2 + b^2}$$



$$\theta = \tan^{-1}(b/a)$$

## \* Convert from polar form to rectangular form:


$$\vec{X} = |\vec{X}| \angle \theta \Rightarrow a = |\vec{X}| \cos \theta$$

$$b = |\vec{X}| \sin \theta$$

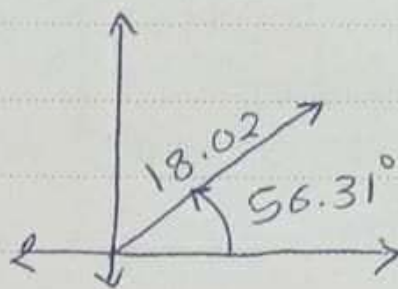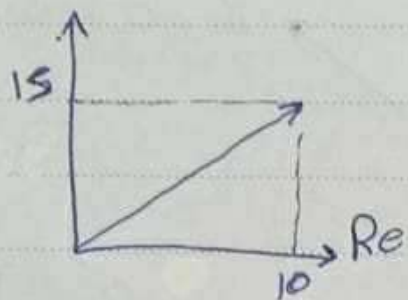
Ex:  $\vec{X} = 10 + j15$  ,  $\triangleq \sqrt{10^2 + 15^2} \angle \tan^{-1}(15/10)$   
 $= 18.02 \angle 56.31^\circ$



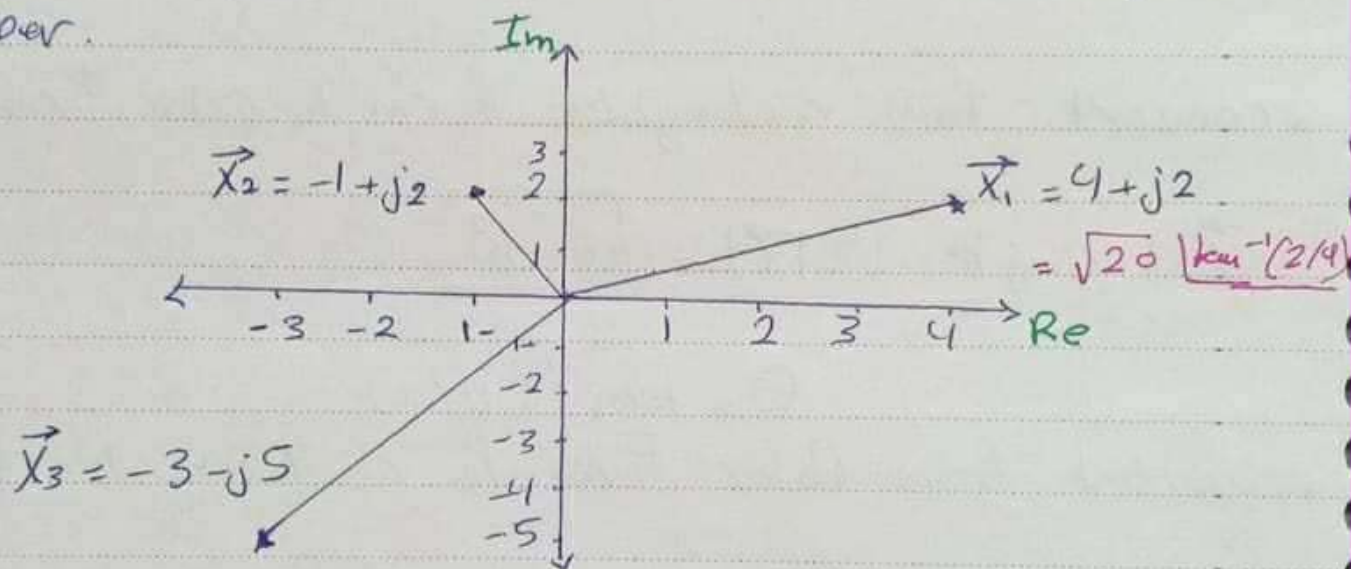Ex: Find the polar form for each of the complex number.



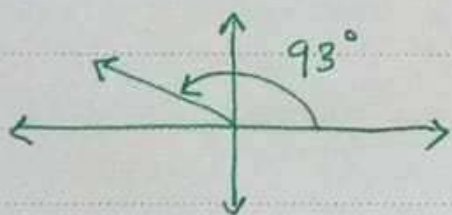Ex:  $\vec{Y} = 110 \angle 93^\circ \Rightarrow \vec{Y} = 110 \cos(93^\circ) + j110 \sin(93^\circ)$




$= -5.76 + j109.849$




Ex:  $\vec{X} = 12 \angle 43^\circ \triangleq 12 \angle 43 + 360 = 12 \angle 403^\circ = 12 \angle -317^\circ$

أو ٣ مقاديرين  
في القيمة

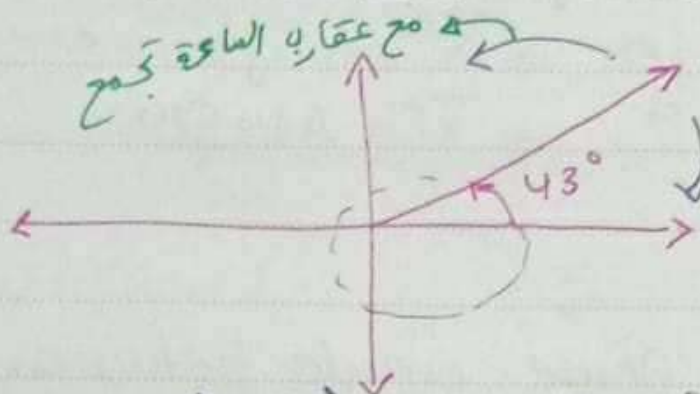

الزاوية ملا تزيد 360  
ترجع نفسها  
عكس عقارب  
الساعة تدور

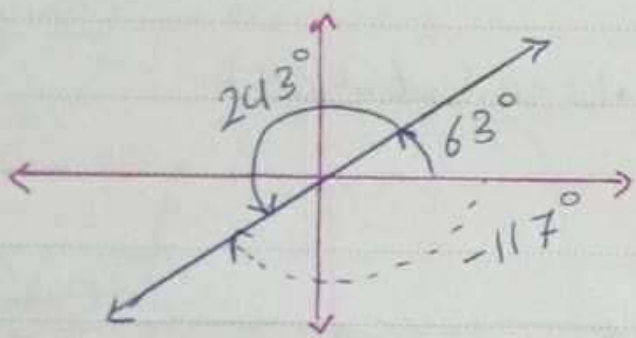Ex:  $\vec{X}_1 = 5 \angle 63^\circ \Rightarrow \vec{X}_2 - \vec{X}_1 = 5 \angle 63^\circ + 180^\circ$   
 $= 5 \angle 243^\circ$   
 $= 5 \angle -117^\circ$



Sum & subtraction of two complex number (Preferred in the rectangular form).

الترتيب المفضل

Ex:  $\vec{X}_1 = 3 + j4$  ,  $\vec{X}_2 = -9 + j2$  form

$\vec{X}_1 + \vec{X}_2 = (3 + (-9)) + j(4 + 2) = -6 + j6$

$\vec{X}_1 - \vec{X}_2 = (3 - (-9)) + j(4 - 2) = 12 + j2$

Multiplication & division (Preferred in Polar form).


Ex:  $\vec{X}_1 = 120 \angle -89^\circ$  ,  $\vec{X}_2 = 60 \angle 112^\circ$

$\vec{X}_1 \vec{X}_2 = (120)(60) \angle -89^\circ + 112^\circ = 7200 \angle 23^\circ$

$\frac{\vec{X}_1}{\vec{X}_2} = \frac{120 \angle -89^\circ}{60 \angle 112^\circ} = \frac{120}{60} \angle (-89^\circ - 112^\circ) = 2 \angle -201^\circ$

Conject for complex number:

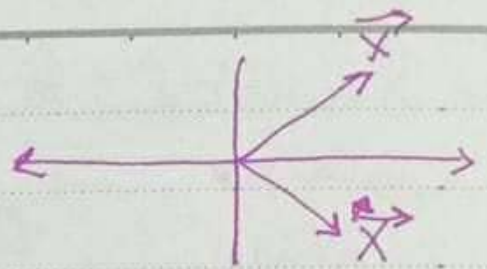$\vec{X} = a + jb \Rightarrow \vec{X}^* = a - jb$   
 $\vec{X} = A \angle \theta \Rightarrow \vec{X}^* = A \angle -\theta$



Sinusoidal:


Example: (9.2)

Calculate the phase angle between  $v_1 = -10 \cos(\omega t + 50^\circ)$  and  $v_2 = 12 \sin(\omega t - 10^\circ)$ .

$$v_1 = +10 \sin(\omega t + 50 - 90) = +10 \sin(\omega t - 40^\circ)$$

$$v_2 = 12 \sin(\omega t - 10^\circ)$$

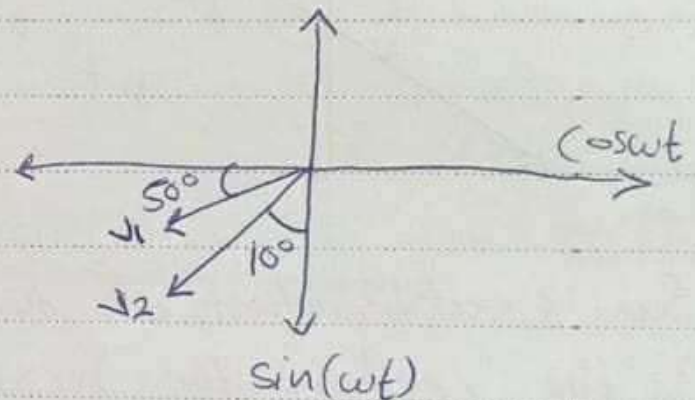$v_2$  leads  $v_1$  by  $30^\circ$   
 $90 - 10 - 50^\circ$



Particle Problem (9.2)

Find the phase angle between


$$i_1 = -4 \sin(377t + 55^\circ)$$

$$i_2 = 5 \cos(377t - 65^\circ)$$

$$i_1 = -4 \cos(377t + 55 - 90)$$

$$= -4 \cos(377t - 35) = -4 \cos(377t + 145^\circ)$$

Does  $i_1$  lead or lag  $i_2$ ?

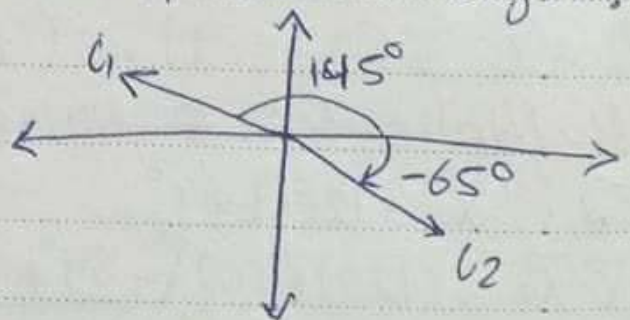



Sinusoidal characteristics.  $\left\{ \begin{array}{l} \sin( ) \\ \cos( ) \end{array} \right.$


$$v(t) = V_m \sin(\omega t)$$

$V_m \Rightarrow$  Peak value (amplitude)


$\omega t \Rightarrow$  argument [rad]

$\omega \Rightarrow$  radian frequency [rad/sec]

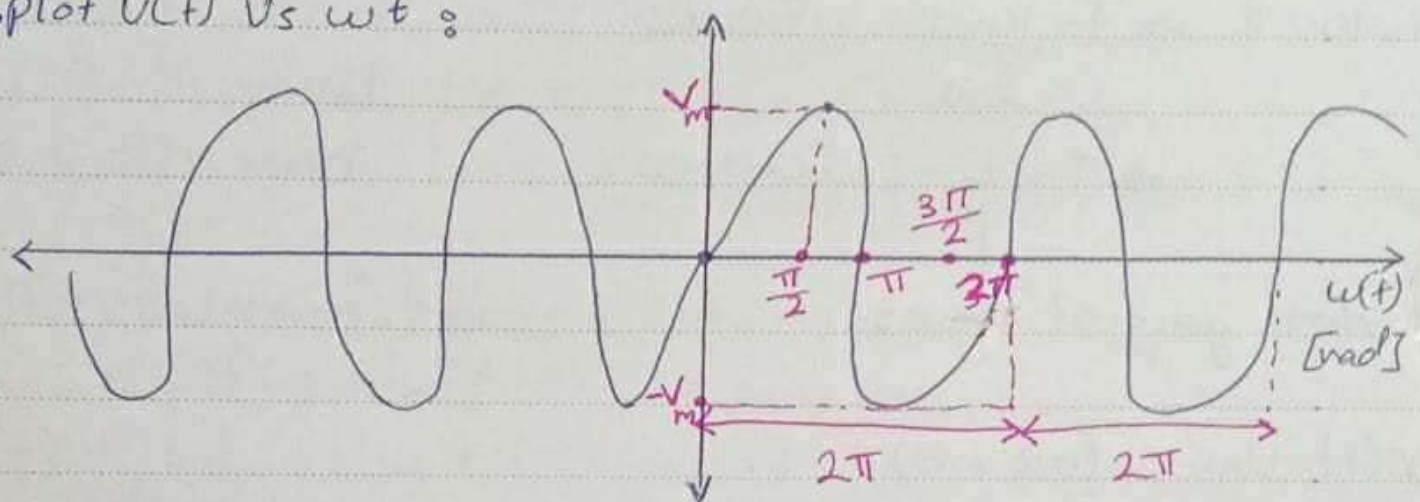$\rightarrow$  plot  $v(t)$  vs  $\omega t$  :



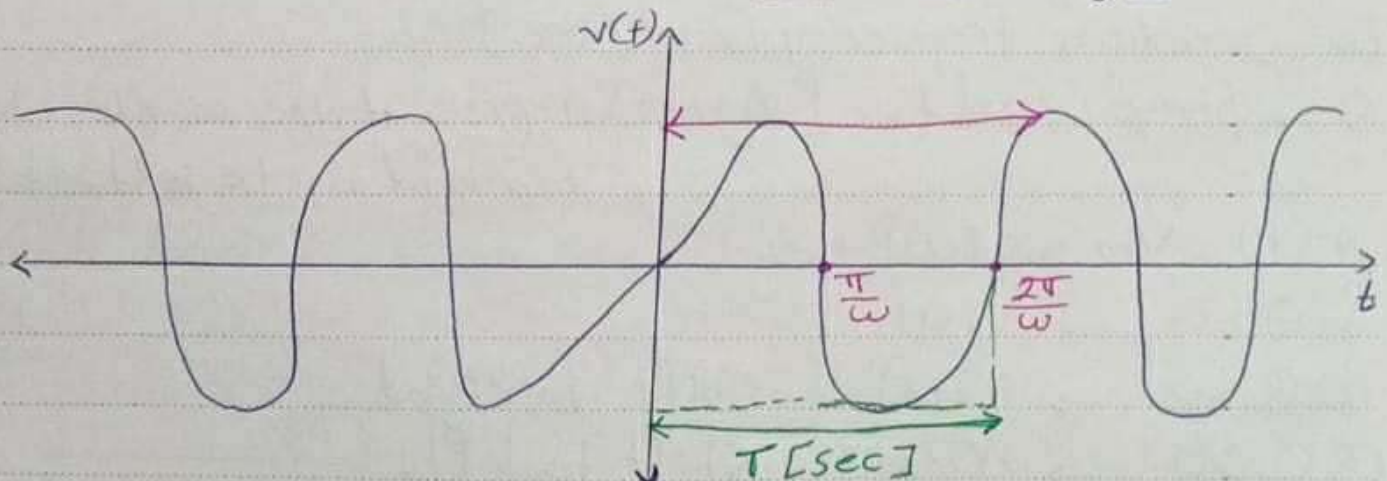$\rightarrow$  Plot  $v(t)$  vs  $t$  & divide the  $(\omega t)$ -axis by  $\omega$  :



$$f = \frac{1}{T} \text{ (Hz)} \rightarrow \text{Frequency} \Rightarrow T = \frac{2\pi}{\omega} \Rightarrow \omega = \frac{2\pi}{T} = 2\pi f$$

Ex:  $v(t) = 20 \sin(1000t)$ , find  $f$  &  $T$ .

frequency

sol:  $\omega = 1000 \Rightarrow f = \frac{\omega}{2\pi} = \frac{1000}{2\pi} = 159.15 \text{ Hz}$

Period.  $\Rightarrow T = \frac{1}{f} = 6.283 \text{ msec}$

Ex:  $i(t) = 10 \cos(100\pi t) \text{ [A]}$

$\omega = 100\pi \Rightarrow f = \frac{100\pi}{2\pi} = 50 \text{ Hz}$

$\Rightarrow T = \frac{1}{f} = 20 \text{ msec.}$

More general cases:

$v(t) = V_m \sin(\omega t + \theta)$

$V_m \rightarrow$  Peak value or amplitude

$\omega t + \theta \rightarrow$  argument [rad] / [degree]

$\omega \rightarrow$  radian frequency [rad/sec]

$\theta \rightarrow$  phase [rad] or [degree]  $\rightarrow$  represent, the single shift to right or to left  $\theta(+)$

$v(t) = V_m \sin(\omega t + \theta)$

①  $\theta = 0 \rightarrow v_1(t)$

②  $\theta < 0 \rightarrow v_2(t)$  shift to right

③  $\theta > 0 \rightarrow v_3(t)$  shift to left.



(متأخر) ← (متقدم)

lagging & leading

$v_1(t)$  leads  $v_2(t)$  by  $\theta$

OR  $v_2(t)$  lags  $v_1(t)$  by  $\theta$

OR  $v_1(t)$  lags  $v_2(t)$  by  $-\theta = 360^\circ - \theta$

OR  $v_2(t)$  leads  $v_1(t)$  by  $-\theta = 360^\circ - \theta$

لا تعكس ال lag


to be

الزاوية

leads

تغير

بمقابل

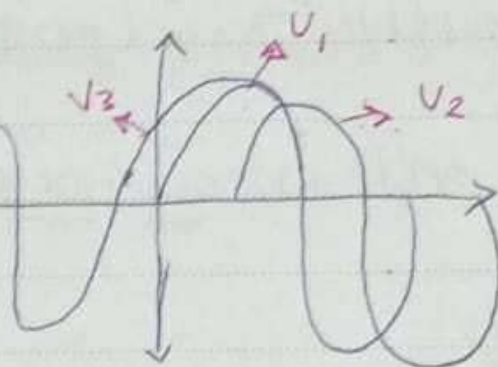

\* Two compare two sinusoids:

① Both must have same  $\omega$ .

② Both must be "cosine" or "sine".

③ Both must have +ve amplitude.

The conversion between them is:

$$-\sin(\omega t) = \sin(\omega t \pm 180^\circ) \quad \text{إشارة ال sin/cos}$$

$$-\cos(\omega t) = \cos(\omega t \pm 180^\circ) \quad \text{مع إشارة الزاوية}$$

$$\mp \cos(\omega t) = \sin(\omega t \mp 90^\circ) \quad \text{نفس الترتيب}$$


$$\mp \sin(\omega t) = \cos(\omega t \pm 90^\circ)$$

Ex:  $v_1(t) = +10 \overset{\text{amplitude}}{\cos}(1000\pi t^\circ \overset{\text{to the right}}{-10^\circ})$

$v_2(t) = +2 \cos(1000\pi t^\circ \overset{\text{to the left}}{+40^\circ})$

which leads? which lags?

Sol:

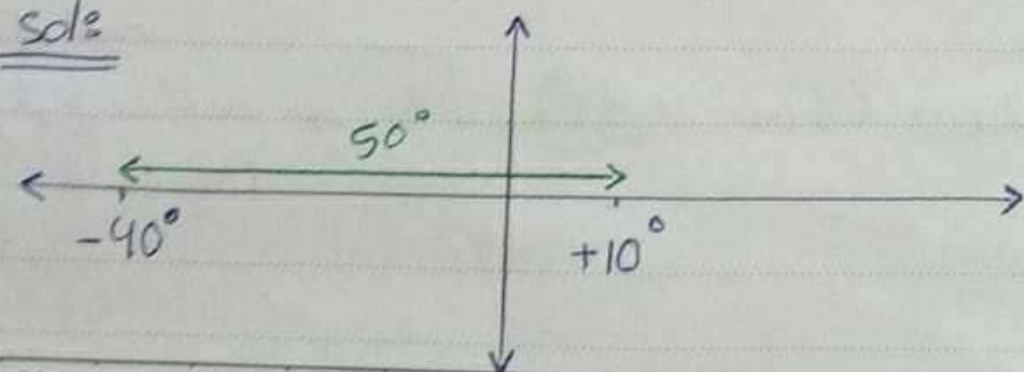

$v_1$  lags  $v_2$  by  $50^\circ$

$v_2$  leads  $v_1$  by  $50^\circ$


$v_1$  leads  $v_2$  by  $-50^\circ = 310^\circ$

$$\text{Ex: } i(t) = \hat{2} \cos(100\pi t + 20^\circ) \text{ [A]}$$

$$v(t) = \hat{12} \sin(100\pi t - 40^\circ) \text{ [V]}$$

Sol:
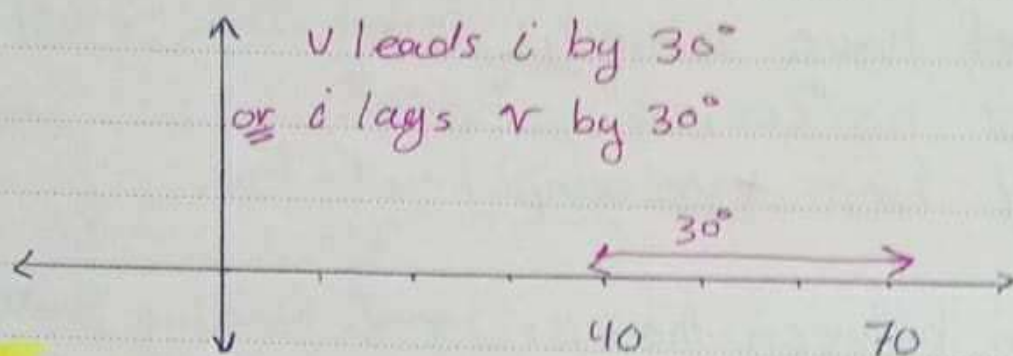
$$\begin{aligned} i(t) &= 2 \sin(100\pi t + 20^\circ - 90^\circ) \\ &= 2 \sin(100\pi t - 70^\circ) \end{aligned}$$



Ex:  $v(t) = 2 \cos(200\pi t + 30^\circ)$

Find  $v(0.01)$ ?

Sol:

$$v(0.01) = 2 \cos(200 \times \overset{\text{rad}}{\pi} \times 0.01 + \overset{\text{degree}}{30^\circ})$$


your calculator  $\rightarrow \Delta = 2 \cos(2\pi + 30 \times \frac{\pi}{180}) = \sqrt{3} \rightarrow$  درجہ میں  
on rad Degree

your calculator  $\Delta = 2 \cos(360^\circ + 30^\circ) = \sqrt{3} \rightarrow$  درجہ میں  
on degree. Degree


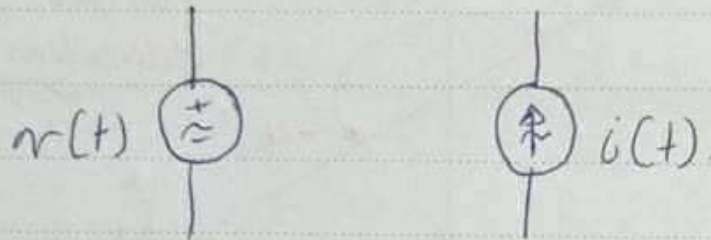
## AC - circuits.

\* Electric circuits that are driven by AC (sinusoidal)



### \* Phasors:

Defn a phasor is a complex number that represent the amplitude and phase of a sinusoid.

(the sinusoid has to be written as cosine with the amplitude).

$$\text{let's } v(t) = V_m \cos(\omega t + \theta_v)$$

Time do. لتحويل من

$$= \text{Re} \left[ V_m \angle \omega t + \theta_v \right]$$

إلى phasor

①  $\cos$  لازم

$$= \text{Re} \left[ V_m \angle \theta_v \cdot 1 \angle \omega t \right]$$

② amplitude (+)

③ تحويل إلى phasor

this is the phasor  $\vec{V} = V_m \angle \theta_v$

$$v(t) = V_m \cos(\omega t + \theta_v) \Leftrightarrow \vec{V} = V_m \angle \theta_v$$


the same of currents

$$i(t) = I_m \cos(\omega t + \theta_i) \Leftrightarrow \vec{I} = I_m \angle \theta_i$$

Ex:  $i_1(t) = 6 \cos(50t - 40^\circ) \text{ A}$   $\vec{I}_1$

$$\vec{I} = 6 \angle -40^\circ \text{ A}$$

$$= 6 \angle 320^\circ \text{ A}$$

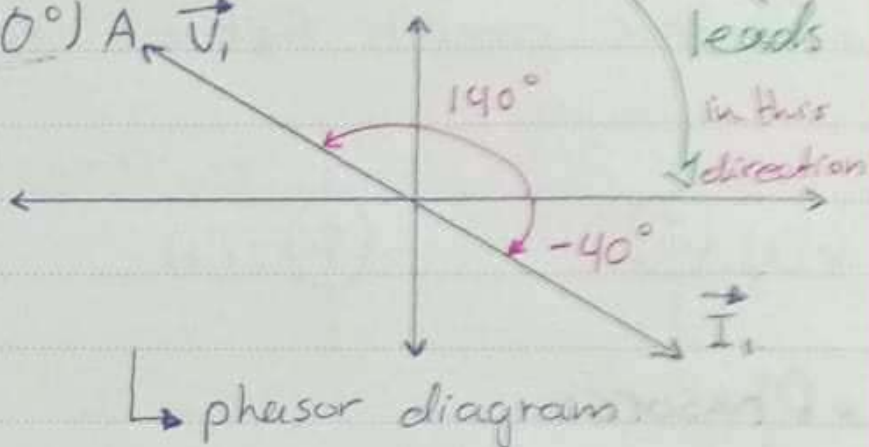

$$v_1(t) = -4 \sin(30t + 50^\circ)$$

$$= 4 \cos(30t + 50^\circ + 90^\circ)$$

$$= 4 \cos(30t + 140^\circ)$$

$$\vec{v}_1 = 4 \angle 140^\circ \Rightarrow v_1(t) \text{ leads } i_1(t) \text{ by } 180^\circ.$$

Ex:  $\vec{I} = 30 \angle -20^\circ \text{ mA}$

sol:  $i(t) = 30 \cos(\omega t - 20^\circ) \text{ mA}$

Ex:  $\vec{V} = -3 + j4 \text{ V}$ , Find  $v(t)$ .

sol:  $\vec{V} = \sqrt{9+16} \angle \tan^{-1}(4/-3) = 5 \angle \overset{-53.1^\circ}{\cancel{126.87^\circ}}$

$$v(t) = 5 \cos(\omega t + \overset{-53.1^\circ}{\cancel{126.87^\circ}})$$



Ex 1 Find  $i(t) = 4 \cos(\omega t + 30^\circ) + 5 \sin(\omega t - 20^\circ)$ .

Solr  $i(t) = i_1(t) + i_2(t)$

$$i_1(t) = 4 \cos(\omega t + 30^\circ) \Rightarrow I_1 = 4 \angle 30^\circ$$

$$i_2(t) = 5 \sin(\omega t - 20^\circ)$$

$$= 5 \cos(\omega t - 11^\circ) \Rightarrow I_2 = 5 \angle 11^\circ$$

$$i(t) = \vec{I} = \vec{I}_1 + \vec{I}_2$$

$$= 4 \angle 30^\circ + 5 \angle -11^\circ$$

$$= 3.218 \angle -56.97^\circ$$

$$i(t) = 3.218 \cos(\omega t - 56.97^\circ)$$

# Impedance

\* What is Impedance? can be delt as complex number.

$$\begin{array}{lcl} \text{---} \overline{\text{R}} \text{---} & \Rightarrow & \text{---} \overline{Z_R} \text{---}, \vec{Z} = \text{number such as } 2 \\ \text{---} \overline{\text{C}} \text{---} & \Rightarrow & \text{---} \overline{Z_C} \text{---}, \vec{Z} = \text{complex and number (+)} \rightarrow j2 \\ \text{---} \overline{\text{L}} \text{---} & \Rightarrow & \text{---} \overline{Z_L} \text{---}, \vec{Z} = \text{complex (-)} \rightarrow -j2 \end{array}$$

$$\vec{Z} = R + j[X] = |\vec{Z}| \angle \theta \quad [r]$$

resistance (dissipate energy), originally

Reactance (stores energy)

--- R ---

originally --- ~~C~~  $\overline{R}$  ---


\* Ohm's law directly applied:

$$\vec{V} = \vec{Z} \vec{I}$$

$$V_m \angle \theta_v = (|\vec{Z}| \angle \theta_z)(I_m \angle \theta_i)$$

$$V_m = |\vec{Z}| I_m$$

$$\theta_v = \theta_i + \theta_z$$

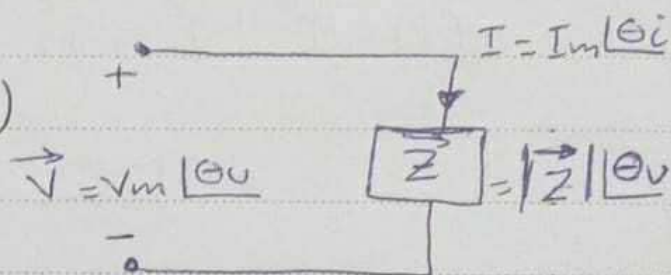

time domain

R

L

C






complex domain

$$R = Z_R = R \angle 0^\circ$$


$$j\omega L = \vec{Z}_L = \omega L \angle 90^\circ$$

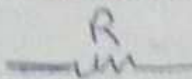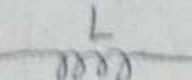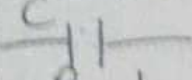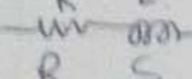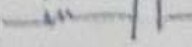
$$\frac{-j}{\omega C} = Z_C = \frac{1}{\omega C} = \frac{1}{\omega C} \angle 90^\circ$$




Time	$\vec{Z}$	load typical	$\Theta_z$	$\vec{I}$ & $\vec{V}$
	$R \angle 0^\circ$	pure resistance	0	In phase
	$j\omega L = jX_L$	pure inductive	$90^\circ$	$\vec{I}$ lags $\vec{V}$ by $90^\circ$
	$-j/\omega C = -jX_C$	pure capacitive	$-90^\circ$	$\vec{I}$ leads $\vec{V}$ by $90^\circ$
	$R + jX_L$	inductive (not pure)	+ve	$\vec{I}$ lags $\vec{V}$ by $\Theta_z$
	$R - jX_C$	capacitive (not pure)	-ve	$\vec{I}$ leads $\vec{V}$ by $\Theta_z$

Ex: If  $\omega = 10 \text{ rad/sec}$ , specify the equivalent load for each of the following impedances:


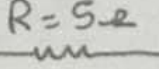
①  $\vec{Z} = 5 \Omega$  (Pure resistance)  $\Rightarrow R = 5 \Omega$ , 

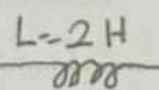②  $\vec{Z} = j20 \Omega$  (Pure inductive)  $\Rightarrow L = 2 \text{ H}$ , 



$$j20 = j\omega L \Rightarrow L = 20/\omega = 2 \text{ H}$$

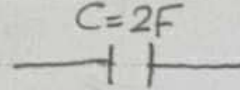③  $\vec{Z} = \frac{1}{j20} \Omega \Rightarrow Z = -j \frac{1}{20} \Rightarrow$  pure capacitive,   $C = 2 \text{ F}$

$$-j \frac{1}{20} = -j \frac{1}{\omega C} \Rightarrow \omega C = 20 \rightarrow C = 2 \text{ F}$$

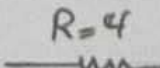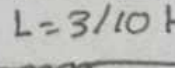④  $\vec{Z} = 4 + j3 \Rightarrow$  inductive load   $R = 4$    $L = 3/10 \text{ H}$


$$\omega L = 3 \Rightarrow L = 3/10 \text{ H}$$

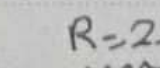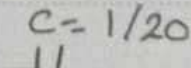⑤  $\vec{Z} = 2 - j2 \Omega \Rightarrow$  capacitive load   $R = 2$    $C = 1/20 \text{ F}$

$$-j2 = -j \frac{1}{\omega C}$$


$$2 = \frac{1}{\omega C} \Rightarrow \frac{1}{20} = C$$

Impedances in series & voltage division:
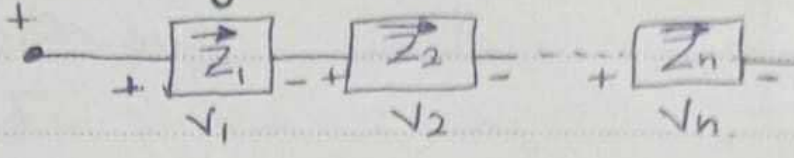
$$\vec{Z}_{equ} = \vec{Z}_1 + \vec{Z}_2 + \vec{Z}_3 + \dots + \vec{Z}_N$$

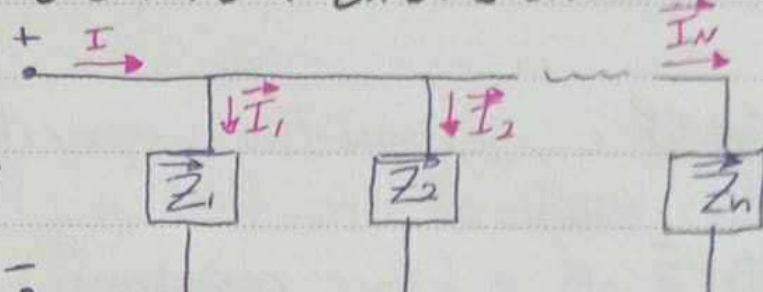
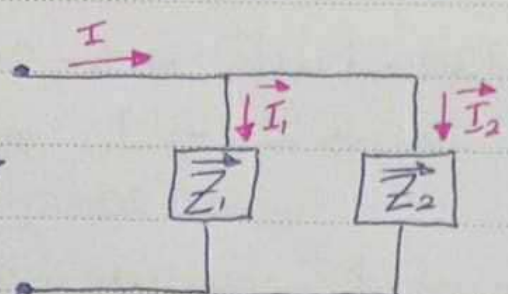
$$\vec{V}_n = \frac{\vec{Z}_n}{\vec{Z}_1 + \vec{Z}_2 + \dots + \vec{Z}_N} \vec{V}$$

Impedances in Parallel & current divisions:

$$\vec{Z}_{equ} = \frac{1}{\frac{1}{\vec{Z}_1} + \frac{1}{\vec{Z}_2} + \dots + \frac{1}{\vec{Z}_N}}$$


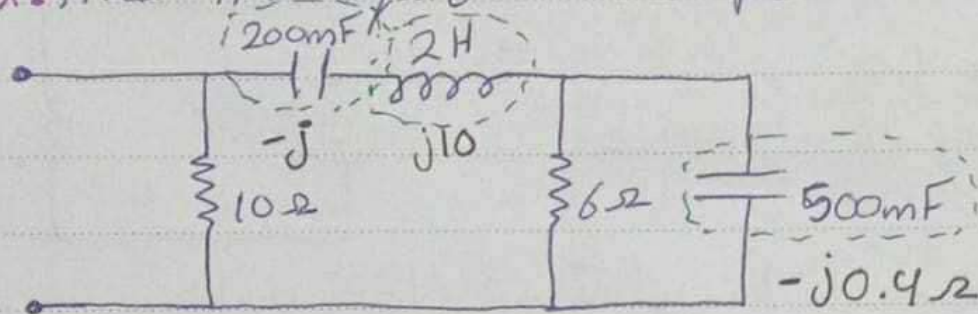
$$I_N = \frac{1/\vec{Z}_N}{1/\vec{Z}_{equ}} I \quad (\text{current division})$$

$$\vec{Z}_{equ} = \frac{\vec{Z}_1 \vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2}$$

$$I_1 = \frac{\vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2} \vec{I} \quad \left\{ \quad I_2 = \frac{\vec{Z}_1}{\vec{Z}_1 + \vec{Z}_2} \vec{I} \right.$$




Ex: Find the equivalent impedance:



$R \rightarrow R$

$H \rightarrow j\omega L$


$C \rightarrow \frac{-j}{\omega C}$

$\omega = 5 \text{ rad/sec}$

$$\textcircled{1} 6 \parallel -j0.4 = \frac{(6)(-j0.4)}{6 - j0.4} = 0.3991 \angle -86.18^\circ$$

$$\textcircled{2} 0.3991 \angle -86.18^\circ + j10 - j = 8.602 \angle 89.823^\circ$$
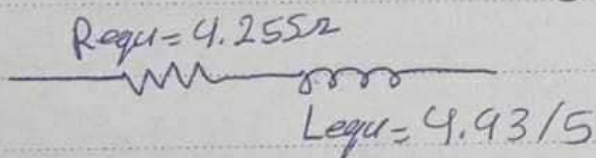
$$\textcircled{3} 8.602 \angle 89.823^\circ \parallel 10 = 6.511 \angle 49.19^\circ = 4.255 + j4.93 \Omega$$




→ lagging impedance

لأن إشارة الـ (j) موجبة دائماً نسحبها هكذا

Ex: Find  $i(t)$

(a) using time-domain

(b) using complex-domain

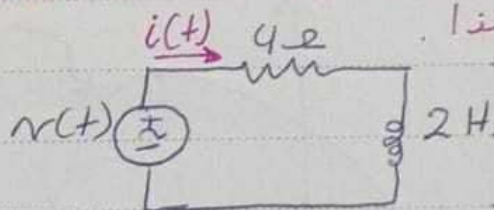

$$v(t) = 10 \cos(50t + 20^\circ)$$

$$\textcircled{a} \text{ KVL } \Rightarrow -v(t) + 4i(t) + 2 \frac{di}{dt} = 0$$

$$2 \frac{di}{dt} + 4i(t) = 10 \cos(50t + 20^\circ)$$

\* we need to solve 1st order diff-equation!

يحل كل ركن ليس ضروري لا نستطيع


الطريقة الثانية: في المجال المعقد

⑥ using complex domain:

$$R = 4\Omega \rightarrow Z_R = 4\Omega$$

$$L = 2H \rightarrow Z_L = j\omega L = j100\Omega$$

$$\vec{V} = 10 \angle 20^\circ$$


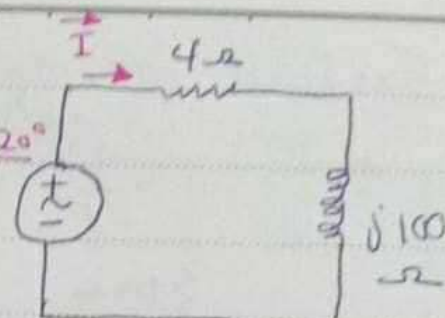


$$v(t) = 10 \cos(50t + 20^\circ) \rightarrow \vec{V} = 10 \angle 20^\circ \text{ volt.}$$


$$\vec{I} = \frac{10 \angle 20^\circ}{4 + j100}$$

$$= 0.1 \angle -67.7^\circ$$
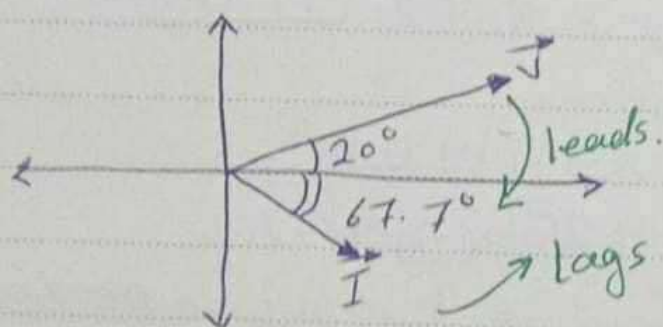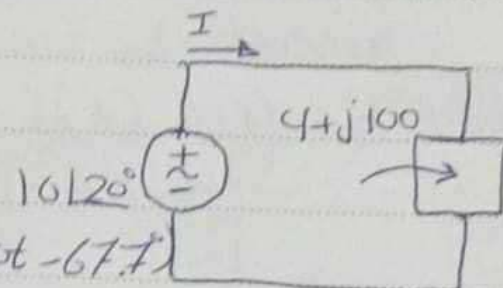
$$\Rightarrow i(t) = 0.1 \cos(50t - 67.7^\circ)$$




$i$  lag  $v$  by  $87.7^\circ$

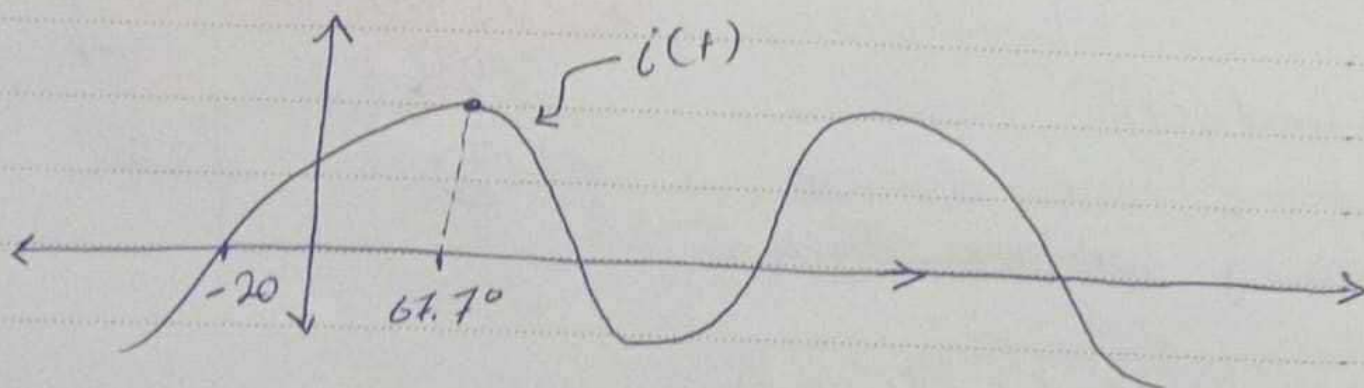



Ex: Find  $\vec{V}_2$ ?

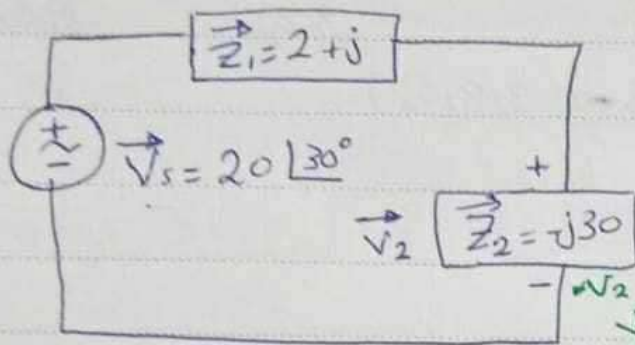

By voltage divisions

$$\vec{V}_2 = \frac{\vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2} \vec{V}_s = \frac{-j30}{2 + j - j30} 20 \angle 30^\circ$$


$$= \frac{-j30}{2 - j28} 20 \angle 30^\circ$$

$$= \frac{-j30}{25.91 \angle -86.42^\circ} 20 \angle 30^\circ$$

$$= 19.244 + j9.34$$

$$= 21.374 \angle 25.91^\circ$$

Exs. Find  $i_s(t)$ ?

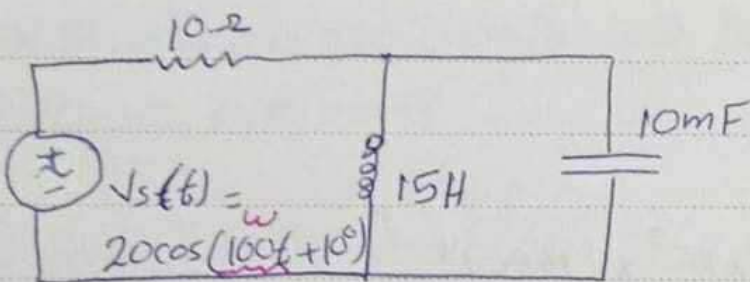

$$Z_L = j\omega L$$

$$= j \times 100 \times 15 = j1500$$

$$Z_C = -j = -j$$

$$\text{or } 100 \times 10 \times 10^{-3}$$

$$= -j$$

$$Z_{\text{equ}} = (-j \parallel j1500) + 10$$

$$= \frac{(-j)(j1500)}{-j + j1500} + 10$$

$$= \frac{1500}{1499} + 10$$

$$= 10.05$$

$$= 10.05 \angle -5.71^\circ$$

$$i_s(t) = 10.05 \cos(100t - 5.71^\circ)$$

$$I_s = 20 \angle 10^\circ$$

$$10.05 \angle -5.71^\circ$$

$$\approx 2 \angle 15.71^\circ$$

$$i_s(t) = 2 \cos(100t + 15.71^\circ)$$

10.7

Ex: Nodal analysis, Find  $\vec{V}_1$  &  $\vec{V}_2$ 

① at node ①:

$$20\text{mA} = \frac{\vec{V}_1 - 0}{-j20} + \frac{\vec{V}_1 - \vec{V}_2}{j4} + 50\angle -90^\circ \text{ mA}$$

$$\left( \frac{1}{-j20} + \frac{1}{j4} \right) \vec{V}_1 - \frac{1}{j4} \vec{V}_2 = 20\text{mA} - 50\angle -90^\circ \text{ mA}$$

$$20\text{mA} - 50\angle -90^\circ \text{ mA}$$

$$\left( \frac{1}{j4} - j\frac{1}{5} \right) \vec{V}_1 - \frac{1}{j4} \vec{V}_2 = 20\text{mA} - 50\angle -90^\circ \text{ mA}$$

$$-j\frac{1}{5} \vec{V}_1 - \frac{1}{j4} \vec{V}_2 = 53.85\angle 68.19^\circ \text{ mA} \quad \text{--- (1)}$$

② at node ②:

$$50\angle -90^\circ \text{ mA} = \frac{\vec{V}_2 - \vec{V}_1}{j4} + \frac{\vec{V}_2 - 0}{25}$$

$$j0.25\vec{V}_1 + 0.253\angle -80.91^\circ \vec{V}_2 = +50\angle -90^\circ \text{ mA} \quad \text{--- (2)}$$

$$\begin{bmatrix} -j/5 & -1/j4 \\ j0.25 & 0.253\angle -80.91^\circ \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} = \begin{bmatrix} 53.85\angle 68.19^\circ \\ -50\angle -90^\circ \end{bmatrix}$$

$$\Delta = (-j/5) \times (0.253\angle -80.91^\circ) - (j0.25 \times -1/j4) = 0.15\angle -96.98^\circ$$

$$\begin{bmatrix} 53.85\angle 68.19^\circ & -1/j4 \\ -50\angle -90^\circ & 0.253\angle -80.91^\circ \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} = \begin{bmatrix} -j/5 \\ j0.25 \end{bmatrix}$$

$$\vec{V}_1 = (53.85\angle 68.19^\circ) \times 0.253\angle -80.91^\circ = 13.62\angle -12.72^\circ$$

$$= 206.8\angle -42.7^\circ$$



$$V_2 = \frac{\begin{vmatrix} A & E \\ B & F \end{vmatrix}}{\Delta} = \frac{5.59 \angle -63.45^\circ}{0.015 \angle -32.53^\circ} = 372.66 \angle -30.92^\circ$$

Cramer's rule

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} E \\ F \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} E & B \\ F & D \end{vmatrix}}{\begin{vmatrix} A & B \\ C & D \end{vmatrix}} = \frac{(E \cdot D) - (B \cdot F)}{(A \cdot D) - (B \cdot C)}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} A & E \\ C & F \end{vmatrix}}{\begin{vmatrix} A & B \\ C & D \end{vmatrix}} = \frac{(A \cdot F) - (E \cdot C)}{(A \cdot D) - (B \cdot C)}$$

① تفعيل complex mode على الآلة الحاسبة


② إدخال الـ complex number وتخزينها على الآلة الحاسبة بـ (Shift + RCL)

STO ↓

③ تطبيق على قانون  $V_1$  و  $V_2$  عند طريق الضغط على RCL وضئهم الحرف المطلوب.

→ 10.3

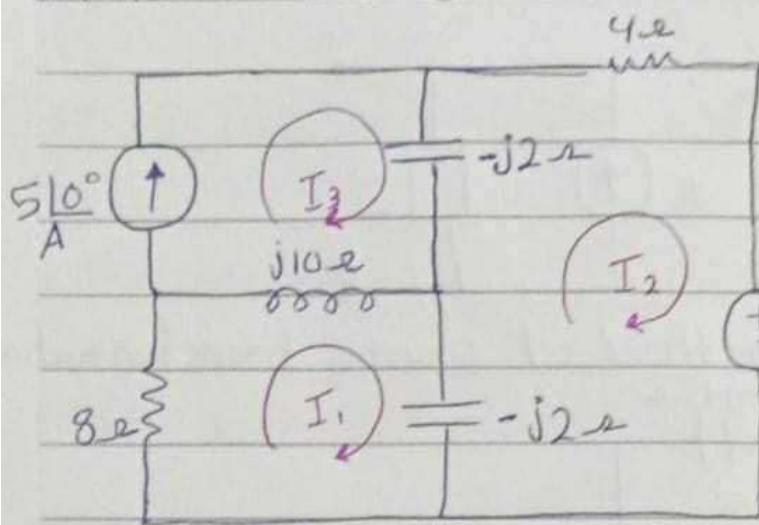Ex: Determine current  $I_0$  using mesh analysis



Apply KVL at mesh (1):

$$8I_1 + j10(I_1 - I_2) -$$

$$j2(I_1 - I_2) = 0$$

$$(8 + j10 - j2)I_1 - j2I_2$$

$$-j10I_3 = 0$$

$$(8 + j8)I_1 - (-j2)I_2 - j10I_3 = 0 \quad (1)$$

KVL at mesh (2):

$$-j2(I_2 - I_1) - (-j2)(I_2 - I_3) + 4I_2 + 20\angle 90^\circ = 0$$

$$-(-j2)I_1 - (4 - j2 - j2)I_2 - (-j2)I_3 + 20\angle 90^\circ = 0 \quad (2)$$

KVL at mesh (3):

by inspection  $\rightarrow I_3 = 5 \rightarrow$  نصف الخارطة 1 و 2

$$(8 + j8)I_1 + j2I_2 = j50 \quad (1)$$

$$j2I_1 + (4 - j4)I_2 = -j10 - j20 \quad (2)$$

$$\begin{bmatrix} \overset{A}{8+j8} & \overset{B}{2j} \\ \overset{C}{j2} & \overset{D}{(4-j4)} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \overset{E}{j50} \\ \overset{F}{-j30} \end{bmatrix}$$

$$\Delta = (AD) - (BC)$$

$$= (8+j8)(4-j4) - (2j \times 2j)$$

$$= 68$$

$$I_1 = \frac{\begin{bmatrix} E & B \\ F & D \end{bmatrix}}{\Delta}$$

$$= \frac{-160}{68} = -2.35$$

$$I_2 = \frac{\begin{bmatrix} A & E \\ C & F \end{bmatrix}}{\Delta}$$

$$= \frac{416.17\angle -35.2^\circ}{68}$$

$$= 6.12 \angle +144.78^\circ$$

$$= 6.12 \angle -35.22^\circ \rightarrow \text{Answer}$$




10.4 ←

Ex: Find  $\vec{V}_1$  using superposition →

$$\vec{V}_1 = \vec{V}_1 + \vec{V}_2''$$


$$= 589.336 \angle -70.66^\circ + 151.99 \angle -61.45^\circ$$

قيمة (w)

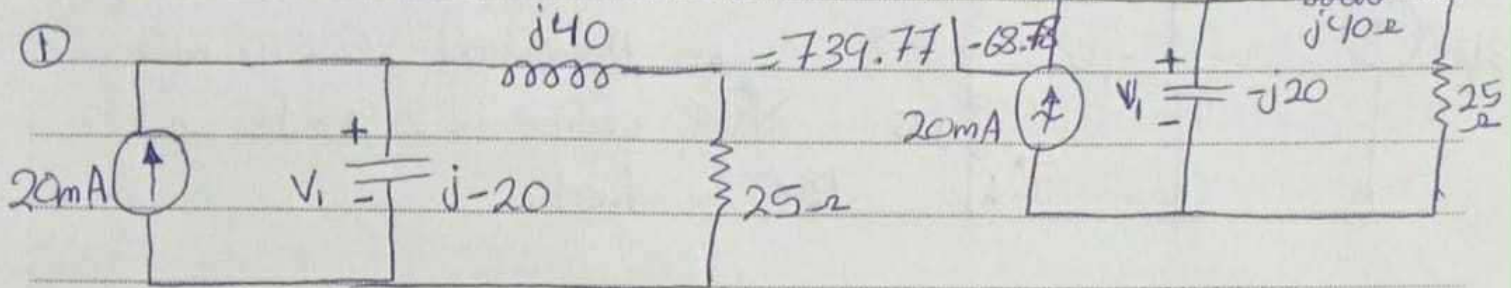

$$\vec{I}_c = \frac{25 + j40}{(25 + j40) - j20} \times 20 \text{ mA} = 29.467 \angle 19.334^\circ \text{ mA}$$
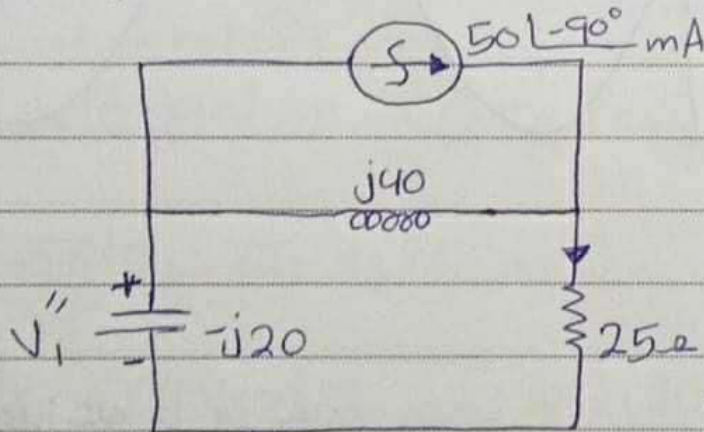
$$\vec{V}_1' = (-j20) \vec{I}_c = 589.336 \angle -70.66^\circ \text{ mA}$$




$$\vec{I} = \frac{(j40)(50 \angle -90^\circ)}{j40 + (25 - j20)} = 6.738 \angle -147.38^\circ$$



$$\vec{V}_1'' = (-j20) \vec{I}_x$$

$$\vec{V}_1'' = (-j20) \times (1 - 6.738 \angle -147.38^\circ)$$

## 10.5: Source Transformation.

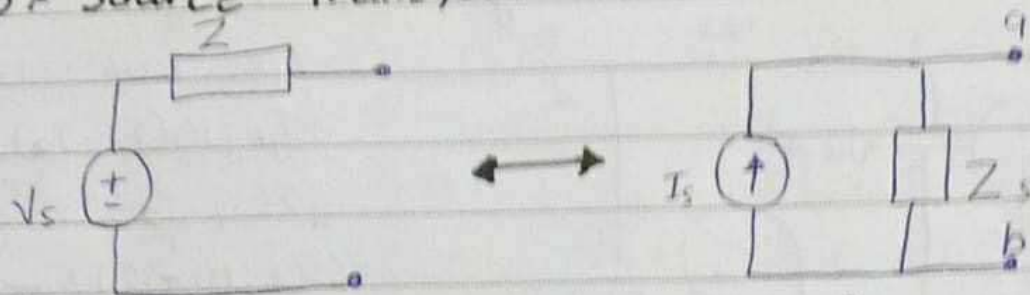

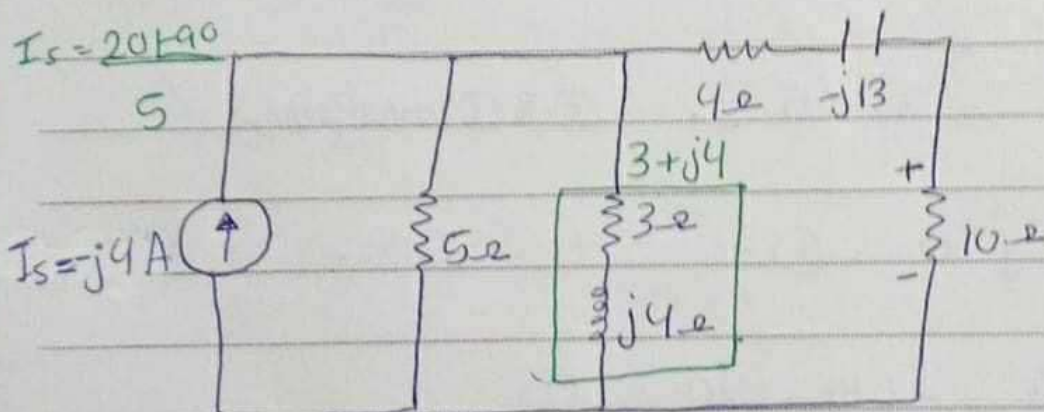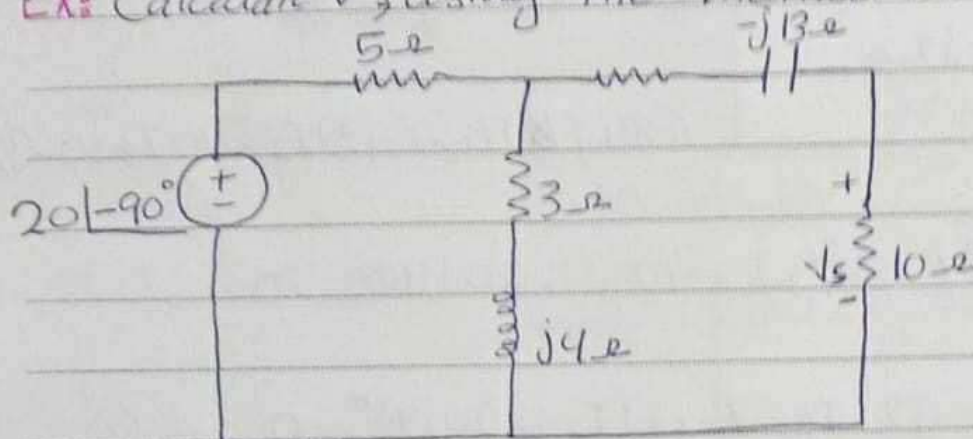Ex: Calculate  $V_x$  using the method of source transformation




$$Z_{eq1} = 5 \times (3 + j4)$$

$$5 + 3 + j4$$

$$= 2.795\angle 26.565^\circ$$

$$= 2.5 + 1.25j\Omega$$

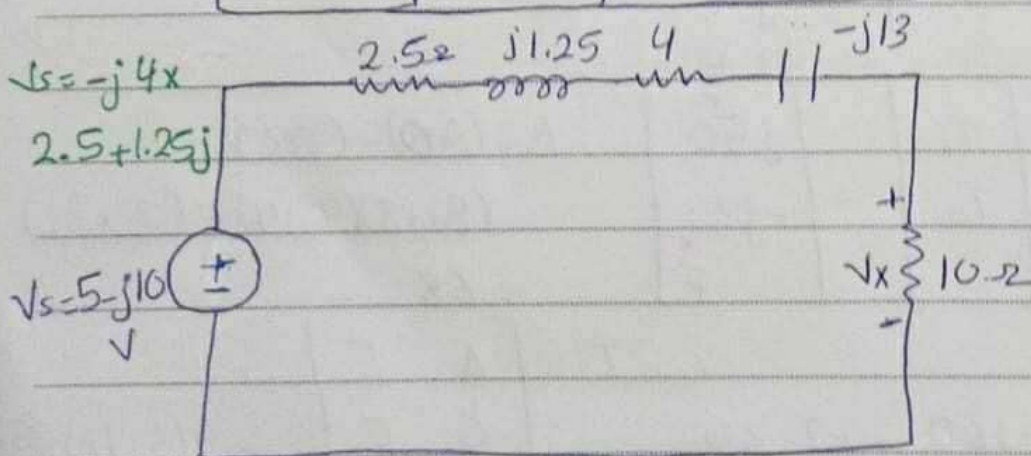


$$V_x = \frac{(5 - j10)(10)}{10 + 4 + 2.5 + j1.25 - j13} = 5.519\angle -28^\circ \text{ V}$$

$$10 + 4 + 2.5 + j1.25 - j13$$



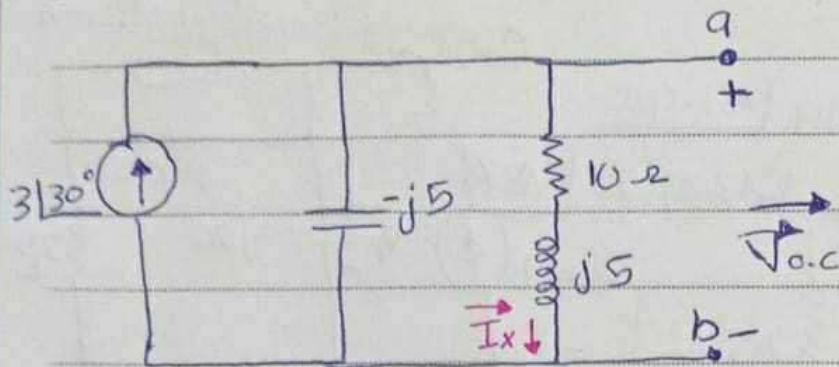Ex: For the circuit shown find the Thevenin equivalent




$$Z_{th} = (-j5) \parallel (10 + j5)$$

$$\text{Kill } \downarrow = (-j5)(10 + j5)$$

the current  $-j5 + 10 + j5$   
source =  $2.5 - j5 \Omega$   
first.

$$\vec{V}_{th} = \vec{V}_{oc} = (10 + j5) \left[ \frac{-j5}{-j5 + 10 + j5} \right] 3 \angle 30^\circ = 16.72 \angle 33.43^\circ \text{ V}$$
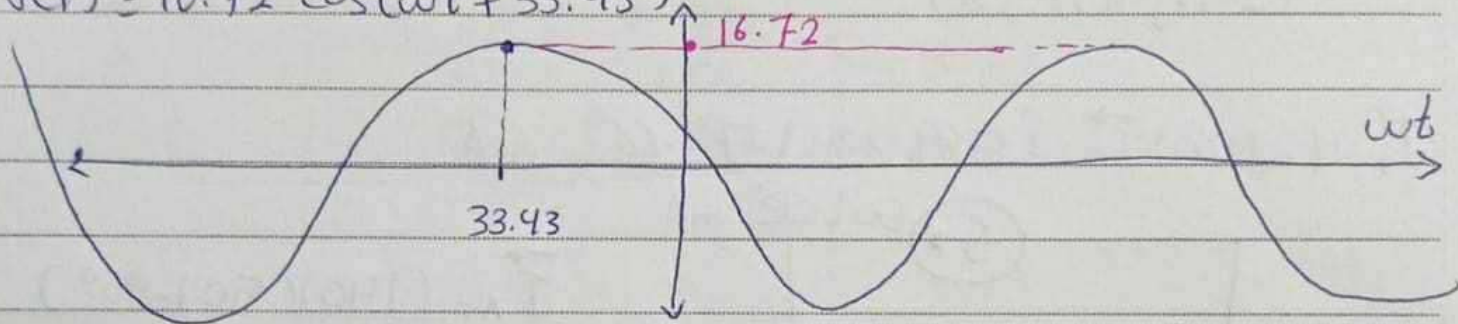
$$v(t) = 16.72 \cos(\omega t + 33.43^\circ)$$



$$\vec{Y} = \frac{1}{\vec{Z}} \text{ (admittance)}$$

حل أسئلة قدر الإمكان

تحويل من AC → Time domain ونطبق طرق اكل القدرة


نعرف lead & lag

تحويل إلى phasor

حساب I, V, Z

Solve for  $V_o$  in the circuit of Fig. 10.9 using mesh analysis.

### Example 10.4

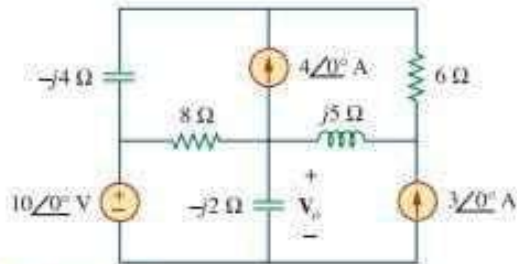

**Figure 10.9**  
For Example 10.4.

#### Solution:

As shown in Fig. 10.10, meshes 3 and 4 form a supermesh due to the current source between the meshes. For mesh 1, KVL gives

$$-10 + (8 - j2)I_1 - (-j2)I_2 - 8I_3 = 0$$

or

$$(8 - j2)I_1 + j2I_2 - 8I_3 = 10 \quad (10.4.1)$$

For mesh 2,

$$I_2 = -3 \quad (10.4.2)$$

For the supermesh,

$$(8 - j4)I_3 - 8I_1 + (6 + j5)I_4 - j5I_2 = 0 \quad (10.4.3)$$

Due to the current source between meshes 3 and 4, at node A,

$$I_4 = I_3 + 4 \quad (10.4.4)$$


**METHOD 1** Instead of solving the above four equations, we reduce them to two by elimination.

Combining Eqs. (10.4.1) and (10.4.2),

$$(8 - j2)I_1 - 8I_3 = 10 + j6 \quad (10.4.5)$$

Combining Eqs. (10.4.2) to (10.4.4),

$$-8I_1 + (14 + j)I_3 = -24 - j35 \quad (10.4.6)$$

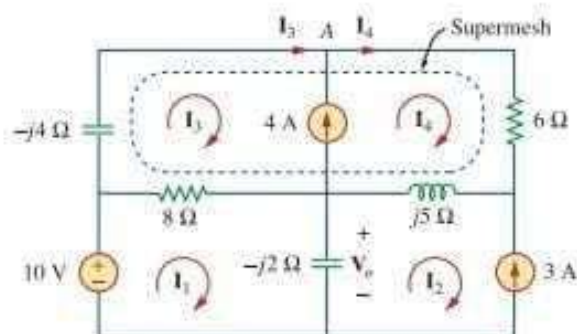

**Figure 10.10**  
Analysis of the circuit in Fig. 10.9.



From Eqs. (10.4.5) and (10.4.6), we obtain the matrix equation

$$\begin{bmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 10 + j6 \\ -24 - j35 \end{bmatrix}$$

We obtain the following determinants

$$\begin{aligned} \Delta &= \begin{vmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{vmatrix} = 112 + j8 - j28 + 2 - 64 = 50 - j20 \\ \Delta_1 &= \begin{vmatrix} 10 + j6 & -8 \\ -24 - j35 & 14 + j \end{vmatrix} = 140 + j10 + j84 - 6 - 192 - j280 \\ &= -58 - j186 \end{aligned}$$

Current  $\mathbf{I}_1$  is obtained as

$$\mathbf{I}_1 = \frac{\Delta_1}{\Delta} = \frac{-58 - j186}{50 - j20} = 3.618 \angle 274.5^\circ \text{ A}$$

The required voltage  $\mathbf{V}_o$  is

$$\begin{aligned} \mathbf{V}_o &= -j2(\mathbf{I}_1 - \mathbf{I}_2) = -j2(3.618 \angle 274.5^\circ + 3) \\ &= -7.2134 - j6.568 = 9.756 \angle 222.32^\circ \text{ V} \end{aligned}$$

**METHOD 2** We can use *MATLAB* to solve Eqs. (10.4.1) to (10.4.4). We first cast the equations as

$$\begin{bmatrix} 8 - j2 & j2 & -8 & 0 \\ 0 & 1 & 0 & 0 \\ -8 & -j5 & 8 - j4 & 6 + j5 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \\ \mathbf{I}_4 \end{bmatrix} = \begin{bmatrix} 10 \\ -3 \\ 0 \\ 4 \end{bmatrix} \quad (10.4.7a)$$

or

$$\mathbf{A}\mathbf{I} = \mathbf{B}$$

By inverting  $\mathbf{A}$ , we can obtain  $\mathbf{I}$  as

$$\mathbf{I} = \mathbf{A}^{-1}\mathbf{B} \quad (10.4.7b)$$

We now apply *MATLAB* as follows:

```
>> A = [(8-j*2) j*2 -8 0;
        0 1 0 0;
        -8 -j*5 (8-j*4) (6+j*5);
        0 0 -1 1];
```

```
>> B = [10 -3 0 4]';
```


```
>> I = inv(A)*B
```

```
I =
    0.2828 - 3.6069i
   -3.0000
   -1.8690 - 4.4276i
    2.1310 - 4.4276i
```

```
>> Vo = -2*j*(I(1) - I(2))
```

```
Vo =
   -7.2138 - 6.5655i
```

as obtained previously.

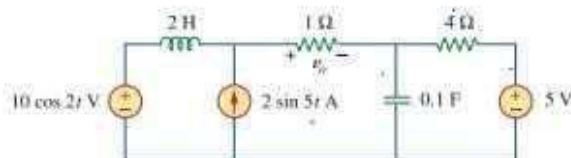

**Figure 10.13**  
For Example 10.6.

**Solution:**

Since the circuit operates at three different frequencies ( $\omega = 0$  for the dc voltage source), one way to obtain a solution is to use superposition, which breaks the problem into single-frequency problems. So we let

$$v_o = v_1 + v_2 + v_3 \quad (10.6.1)$$

where  $v_1$  is due to the 5-V dc voltage source,  $v_2$  is due to the  $10 \cos 2t$  V voltage source, and  $v_3$  is due to the  $2 \sin 5t$  A current source.

To find  $v_1$ , we set to zero all sources except the 5-V dc source. We recall that at steady state, a capacitor is an open circuit to dc while an inductor is a short circuit to dc. There is an alternative way of looking at this. Since  $\omega = 0$ ,  $j\omega L = 0$ ,  $1/j\omega C = \infty$ . Either way, the equivalent circuit is as shown in Fig. 10.14(a). By voltage division,


$$-v_1 = \frac{1}{1+4}(5) = 1 \text{ V} \quad (10.6.2)$$

To find  $v_2$ , we set to zero both the 5-V source and the  $2 \sin 5t$  current source and transform the circuit to the frequency domain.

$$\begin{aligned} 10 \cos 2t &\Rightarrow 10 \angle 0^\circ, & \omega &= 2 \text{ rad/s} \\ 2 \text{ H} &\Rightarrow j\omega L = j4 \Omega \\ 0.1 \text{ F} &\Rightarrow \frac{1}{j\omega C} = -j5 \Omega \end{aligned}$$

The equivalent circuit is now as shown in Fig. 10.14(b). Let

$$\mathbf{Z} = -j5 \parallel 4 = \frac{-j5 \times 4}{4 - j5} = 2.439 - j1.951$$

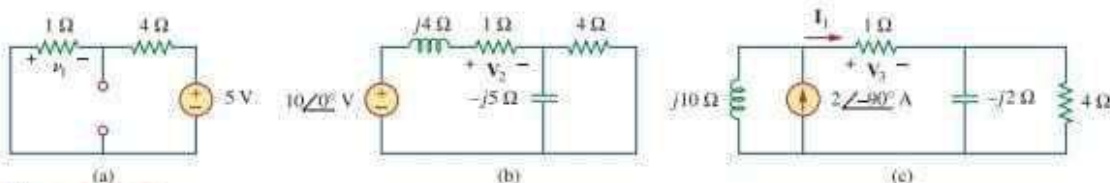

**Figure 10.14**

Solution of Example 10.6: (a) setting all sources to zero except the 5-V dc source, (b) setting all sources to zero except the ac voltage source, (c) setting all sources to zero except the ac current source.

By voltage division,

$$\mathbf{V}_2 = \frac{1}{1 + j4 + \mathbf{Z}}(10 \angle 0^\circ) = \frac{10}{3.439 + j2.049} = 2.498 \angle -30.79^\circ$$


In the time domain,

$$v_2 = 2.498 \cos(2t - 30.79^\circ) \quad (10.6.3)$$

To obtain  $v_3$ , we set the voltage sources to zero and transform what is left to the frequency domain.

$$\begin{aligned} 2 \sin 5t &\Rightarrow 2 \angle -90^\circ, & \omega &= 5 \text{ rad/s} \\ 2 \text{ H} &\Rightarrow j\omega L = j10 \Omega \end{aligned}$$



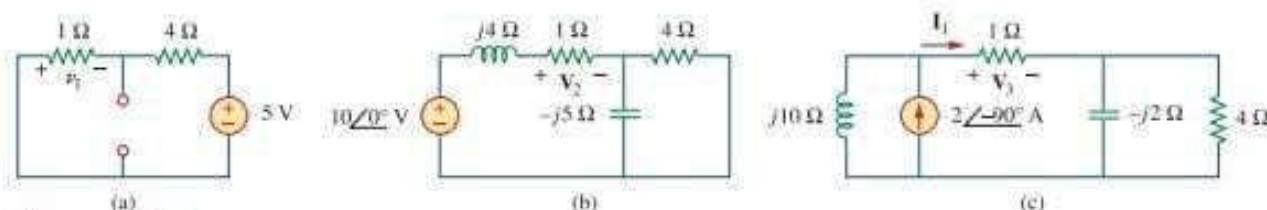

**Figure 10.14**

Solution of Example 10.6: (a) setting all sources to zero except the 5-V dc source, (b) setting all sources to zero except the ac voltage source, (c) setting all sources to zero except the ac current source.

By voltage division,

$$\mathbf{V}_2 = \frac{1}{1 + j4 + \mathbf{Z}} (10 \angle 0^\circ) = \frac{10}{3.439 + j2.049} = 2.498 \angle -30.79^\circ$$

In the time domain,

$$v_2 = 2.498 \cos(2t - 30.79^\circ) \quad (10.6.3)$$

To obtain  $v_3$ , we set the voltage sources to zero and transform what is left to the frequency domain.

$$\begin{aligned} 2 \sin 5t &\Rightarrow 2 \angle -90^\circ, \quad \omega = 5 \text{ rad/s} \\ 2 \text{ H} &\Rightarrow j\omega L = j10 \, \Omega \\ 0.1 \text{ F} &\Rightarrow \frac{1}{j\omega C} = -j2 \, \Omega \end{aligned}$$

The equivalent circuit is in Fig. 10.14(c). Let

$$\mathbf{Z}_1 = -j2 \parallel 4 = \frac{-j2 \times 4}{4 - j2} = 0.8 - j1.6 \, \Omega$$

By current division,


$$\begin{aligned} \mathbf{I}_1 &= \frac{j10}{j10 + 1 + \mathbf{Z}_1} (2 \angle -90^\circ) \text{ A} \\ \mathbf{V}_3 &= \mathbf{I}_1 \times 1 = \frac{j10}{1.8 + j8.4} (-j2) = 2.328 \angle -80^\circ \text{ V} \end{aligned}$$

In the time domain,

$$v_3 = 2.33 \cos(5t - 80^\circ) = 2.33 \sin(5t + 10^\circ) \text{ V} \quad (10.6.4)$$

Substituting Eqs. (10.6.2) to (10.6.4) into Eq. (10.6.1), we have

$$v_o(t) = -1 + 2.498 \cos(2t - 30.79^\circ) + 2.33 \sin(5t + 10^\circ) \text{ V}$$

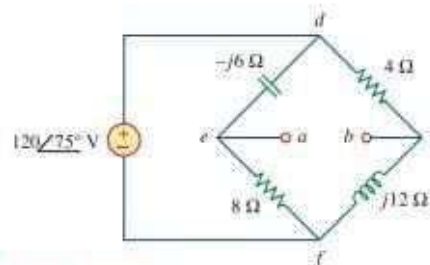

**Figure 10.22**  
For Example 10.8.


**Solution:**

We find  $Z_{Th}$  by setting the voltage source to zero. As shown in Fig. 10.23(a), the  $8\text{-}\Omega$  resistance is now in parallel with the  $-j6$  reactance, so that their combination gives

$$Z_1 = -j6 \parallel 8 = \frac{-j6 \times 8}{8 - j6} = 2.88 - j3.84 \text{ }\Omega$$

Similarly, the  $4\text{-}\Omega$  resistance is in parallel with the  $j12$  reactance, and their combination gives

$$Z_2 = 4 \parallel j12 = \frac{j12 \times 4}{4 + j12} = 3.6 + j1.2 \text{ }\Omega$$

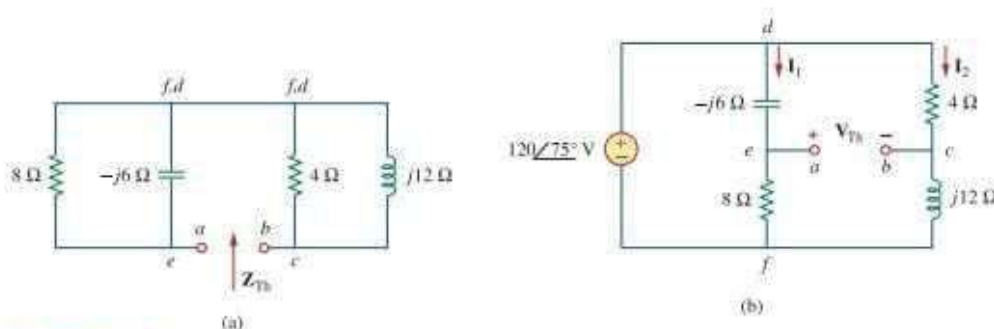

**Figure 10.23**  
Solution of the circuit in Fig. 10.22: (a) finding  $Z_{Th}$ , (b) finding  $V_{Th}$ .

The Thevenin impedance is the series combination of  $Z_1$  and  $Z_2$ ; that is,

$$Z_{Th} = Z_1 + Z_2 = 6.48 - j2.64 \text{ }\Omega$$

To find  $V_{Th}$ , consider the circuit in Fig. 10.23(b). Currents  $I_1$  and  $I_2$  are obtained as

$$I_1 = \frac{120\angle 75^\circ}{8 - j6} \text{ A}, \quad I_2 = \frac{120\angle 75^\circ}{4 + j12} \text{ A}$$


Applying KVL around loop  $bcd eab$  in Fig. 10.23(b) gives

$$V_{Th} - 4I_2 + (-j6)I_1 = 0$$

or

$$\begin{aligned} V_{Th} = 4I_2 + j6I_1 &= \frac{480\angle 75^\circ}{4 + j12} + \frac{720\angle 75^\circ + 90^\circ}{8 - j6} \\ &= 37.95\angle 3.43^\circ + 72\angle 201.87^\circ \\ &= -28.936 - j24.55 = 37.95\angle 220.31^\circ \text{ V} \end{aligned}$$



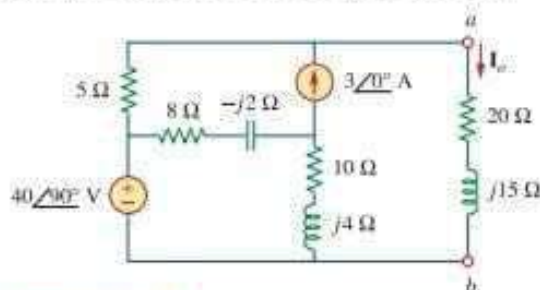

**Figure 10.28**  
For Example 10.10.


**Solution:**

Our first objective is to find the Norton equivalent at terminals  $a$ - $b$ .  $\mathbf{Z}_N$  is found in the same way as  $\mathbf{Z}_{Th}$ . We set the sources to zero as shown in Fig. 10.29(a). As evident from the figure, the  $(8 - j2)$  and  $(10 + j4)$  impedances are short-circuited, so that

$$\mathbf{Z}_N = 5 \Omega$$

To get  $\mathbf{I}_N$ , we short-circuit terminals  $a$ - $b$  as in Fig. 10.29(b) and apply mesh analysis. Notice that meshes 2 and 3 form a supermesh because of the current source linking them. For mesh 1,

$$-j40 + (18 + j2)\mathbf{I}_1 - (8 - j2)\mathbf{I}_2 - (10 + j4)\mathbf{I}_3 = 0 \quad (10.10.1)$$

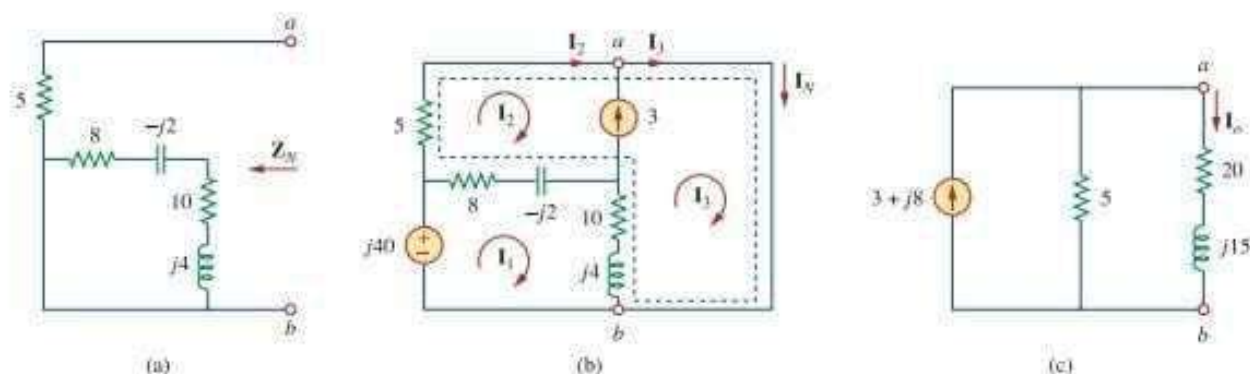

**Figure 10.29**

Solution of the circuit in Fig. 10.28: (a) finding  $\mathbf{Z}_N$ , (b) finding  $\mathbf{V}_N$ , (c) calculating  $\mathbf{I}_o$ .

For the supermesh,

$$(13 - j2)\mathbf{I}_2 + (10 + j4)\mathbf{I}_3 - (18 + j2)\mathbf{I}_1 = 0 \quad (10.10.2)$$

At node  $a$ , due to the current source between meshes 2 and 3,

$$\mathbf{I}_3 = \mathbf{I}_2 + 3 \quad (10.10.3)$$

Adding Eqs. (10.10.1) and (10.10.2) gives

$$-j40 + 5\mathbf{I}_2 = 0 \quad \Rightarrow \quad \mathbf{I}_2 = j8$$

From Eq. (10.10.3),

$$\mathbf{I}_3 = \mathbf{I}_2 + 3 = 3 + j8$$

The Norton current is

$$\mathbf{I}_N = \mathbf{I}_3 = (3 + j8) \text{ A}$$

Figure 10.29(c) shows the Norton equivalent circuit along with the impedance at terminals  $a$ - $b$ . By current division,

$$\mathbf{I}_o = \frac{5}{5 + 20 + j15} \mathbf{I}_N = \frac{3 + j8}{5 + j3} = 1.465 \angle 38.48^\circ \text{ A}$$



Question #3 (7 points)

- a. For the circuit shown below, find the equivalent capacitance  $C_{eq}$  seen between terminal A-B.

$$C_{eq(1)} = \frac{12 \times 6}{12 + 6} = 4 \mu F$$

$$C_{eq(2)} = 12 + 4 = 16 \mu F$$
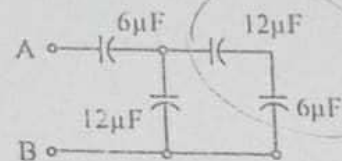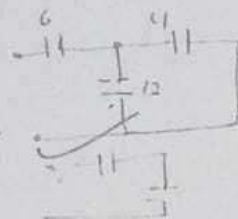
$$C_{eq(3)} = \frac{16 \times 6}{16 + 6} = 4.4 \mu F$$




- b. For the circuit shown below, determine  $C_x$  if the equivalent capacitance is  $20 \mu F$ .

$$C_{eq(1)} = \frac{10 \times 40}{10 + 40} = 8 \mu F$$

$$20 = 8 + C_x$$


$$C_x = 12 \mu F$$

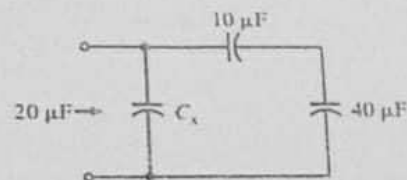

- c. For the circuit shown below, find the equivalent inductance  $L_T$ .

$$L_{eq(1)} = \frac{18 \times 9}{18 + 9} = 6 H$$

$$L_{eq(2)} = 14 + 6 = 20 H$$

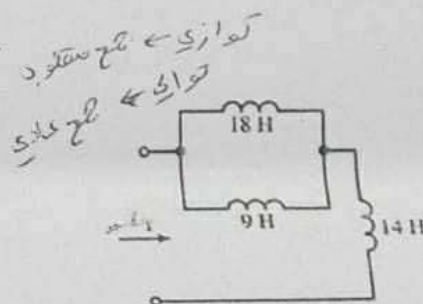



- d. If the voltage  $v_c(t)$  across a  $2F$  capacitor is shown below, draw the waveform for the capacitor current  $i_c(t)$ .

$$I = C \cdot V$$

current  $i_c(t)$ .

$0 < t < 2 \rightarrow v_c = 1 \text{ volt} \rightarrow i_c(t) = 2 \text{ A}$   
 $2 < t < 4 \rightarrow v_c = 0 \text{ volt} \rightarrow i_c = 0$   
 $4 < t < 6 \rightarrow v_c = 1 \text{ volt} \rightarrow i_c = 2 \text{ A}$   
 $6 < t < 8 \rightarrow v_c = -2 \text{ volt} \rightarrow i_c = -4 \text{ A}$

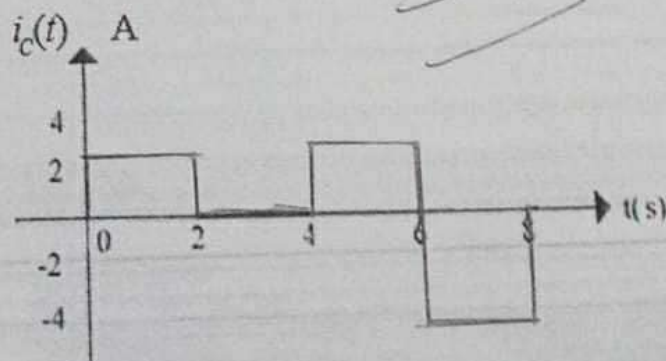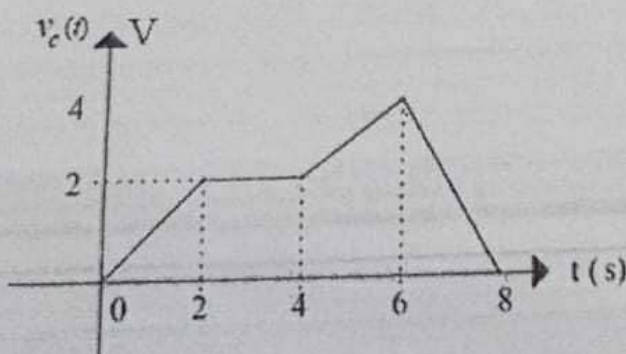
$0 < t < 2 \rightarrow v_c = 1 \text{ volt} \rightarrow i_c = 2 \text{ A}$   
 $2 < t < 4 \rightarrow v_c = 0 \text{ volt} \rightarrow i_c = 0$   
 $4 < t < 6 \rightarrow v_c = 1 \text{ volt} \rightarrow i_c = 2 \text{ A}$   
 $6 < t < 8 \rightarrow v_c = -2 \text{ volt} \rightarrow i_c = -4 \text{ A}$





For the circuit shown below, the sources have been connected for very long time. Find under this condition:

a.	the current through the inductor.	$I_L =$	A
b.	the voltage across the capacitor.	$v_C =$	V
c.	the energy stored in the inductor.	$W_L =$	J
d.	the energy stored in the capacitor.	$W_C =$	J

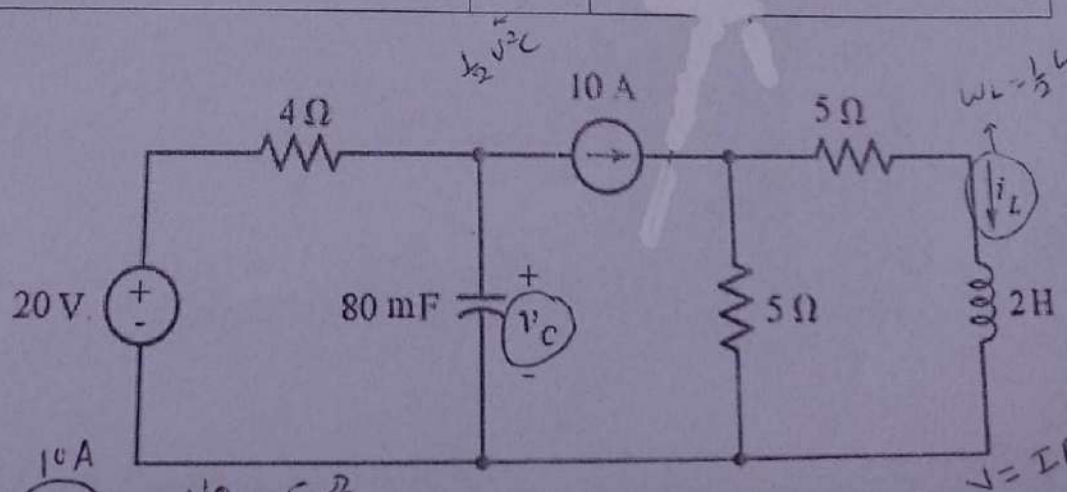

Question # 5 (6 points)

- a. In a linear circuit, if the voltage source is  $v_s(t) = 12\sin(314t + 30^\circ)$  V, find the frequency  $f$  and the period  $T$  of the voltage waveform.

$$\omega = 2\pi f$$


$$314 = 2\pi f \rightarrow f = \frac{314}{2\pi} = 49.97 \approx 50$$

$$T = \frac{1}{f} = 0.02 \text{ s}$$

- b. Write the equation of the sinusoidal current waveform  $i(t)$  shown below with the phase angle  $\theta$  expressed in degrees.

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{100 \times 10^{-3}} = 62.8$$

$$i(t) = 20 \sin(62.8t + 34/2)$$

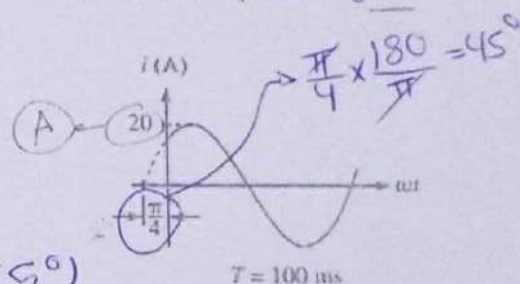

$$i(t) = 20 \sin(\omega t + \frac{\pi}{4}) = 20 \sin(\omega t + 45^\circ)$$

- c. Obtain the sinusoidal waveforms corresponding to each of the following phasors:

i.  $\bar{V}_1 = 60 \angle 15^\circ$  V,  $\omega = 10$  rad/s

$$v(t) = 60 \sin(10t - 75^\circ)$$

$$60 \cos(10t + 15^\circ)$$

ii.  $\bar{V}_2 = 6 + j8$  V,  $\omega = 40$  rad/s

$$V = \sqrt{6^2 + 8^2} = 10$$

$$v(t) = 10 \cos(40t + 53.1^\circ)$$

$$\theta = \tan^{-1}\left(\frac{8}{6}\right) = 53.1$$

- d. Given  $v(t) = 20\sin(\omega t + 60^\circ)$  V and  $i(t) = 60\cos(\omega t - 10^\circ)$ , determine the phase angle  $\theta$



# *Chapter 11*

# CH(11): AC POWER Analysis

## 11.2: Instantaneous and average Power

\* The instantaneous Power:  $P(t)$  → تتغير قيمتها بتغير الزمن



$$P(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$v(t) = V_m \cos(\omega t + \theta_v)$$

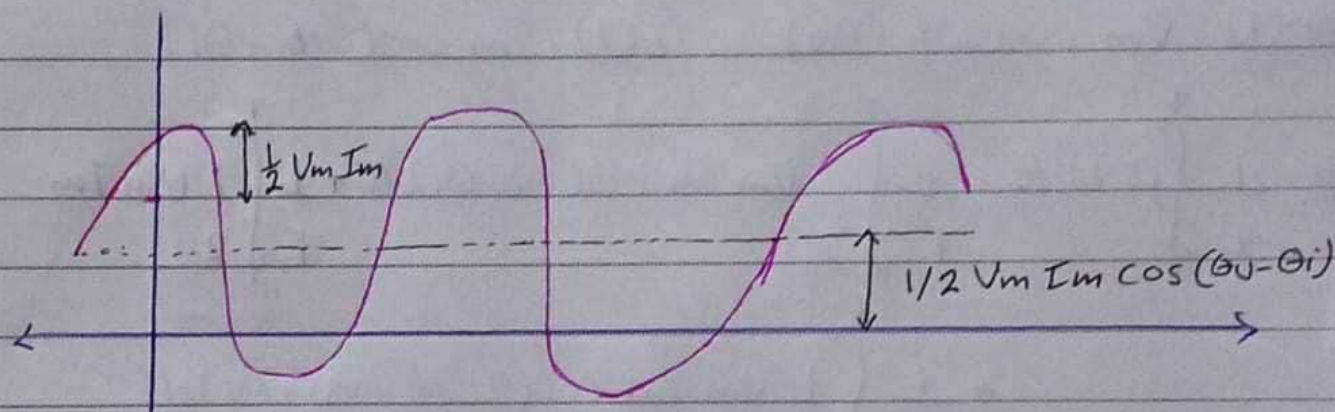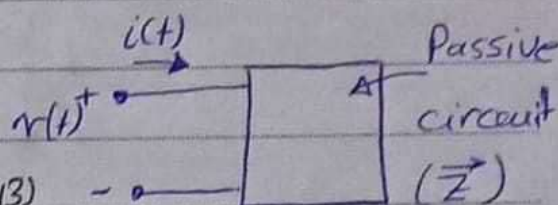
$$\cos(A) \cos(B) = \frac{1}{2} \cos(A-B) + \frac{1}{2} \cos(A+B)$$



التمثيل البياني للـ Instantaneous Power عبارة عن  $\cos$  (المتذبذبة) و  $\cos$  مع Peak value)  $\theta_v - \theta_i$  (shift)

\* Average Powers
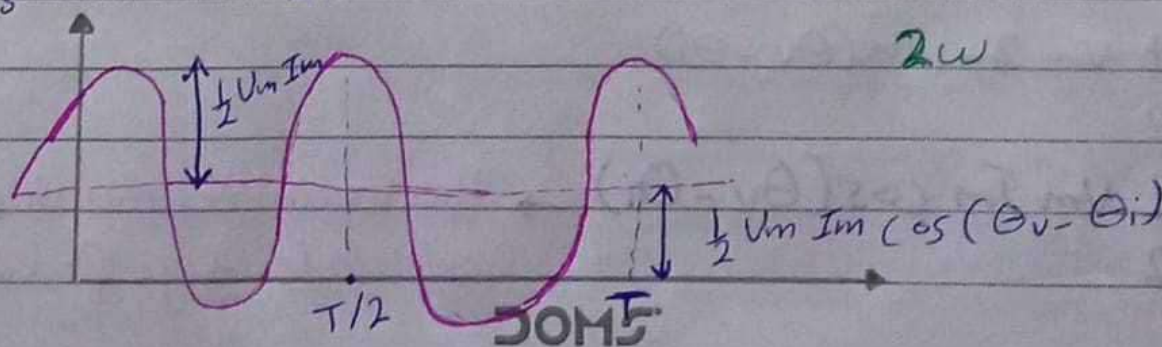
$$P = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$





NOTE:

- ①  $P$  is not time dependent
- ② When  $\theta_v = \theta_i$ , it is a purely resistive load case.
- ③ When  $\theta_v - \theta_i = \pm 90^\circ$ , it is a purely reactive load case.
- ④  $P=0$  means that the circuit absorbs no average power.

The average Power  $P$  is the average of the instantaneous power over one period.

$$p(t) = v(t)i(t) \rightarrow \text{Instantaneous Power}$$

$$P = \frac{1}{T} \int_0^T p(t) dt \rightarrow \text{Average Power}$$

$$v(t) = V_m \cos(\omega t + \theta_v) \quad i(t) = I_m \cos(\omega t + \theta_i)$$

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt$$

$$+ \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt + \frac{1}{2} V_m I_m \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt$$

Integral of sinusoidal = 0

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \rightarrow \text{The main relationship to calculate Avg. Power}$$




• If I have impedance with value of  $I$  8V will be 3 cases:

① If Impedance Pure resistor:

$$\vec{Z} = R, \theta_v - \theta_i = 0$$

$$P_{avg} = \frac{1}{2} V_m I_m$$

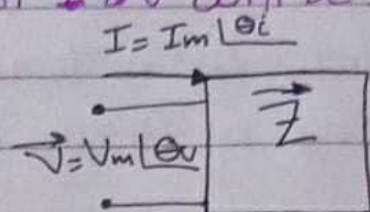

②  $\vec{Z} = j\omega L = \omega L \angle 90^\circ, \theta_v - \theta_i = 90^\circ$


$P_{avg} = 0 \rightarrow$  Don't have inductor Power.

③  $\vec{Z} = -j = 1 \angle -90^\circ$

$\omega C \quad \omega C$

$P = 0$

Ex:

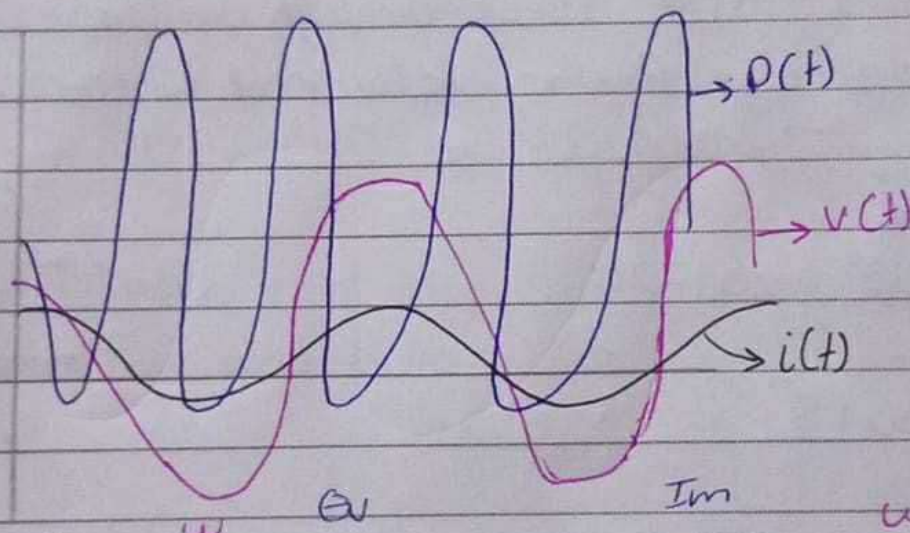

$$v(t) = 120\sqrt{2} \cos(377t + 60^\circ) \quad i(t) = 24\sqrt{2} \cos(377t + 30^\circ)$$

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} \times 120\sqrt{2} \times 24\sqrt{2} \times \cos(60^\circ - 30^\circ)$$

$$= 2494.2 + \frac{1}{2} \times 120\sqrt{2} \times 24\sqrt{2} \times \cos(754t + 90^\circ)$$

لأنها دورة كاملة فتصبح 2\omega

$$= 2494.2 + 2880 \cos(754t + 90^\circ)$$



### Example:

Calculate the instantaneous Power and average Power absorbed by Passive linear network if:

$$v(t) = 80 \cos(10t + 20^\circ) \quad \text{جیب کوسین}$$

$$i(t) = 15 \sin(10t + 60^\circ) \quad \text{کوسین} \rightarrow 15 \cos(10t + 60^\circ - 90^\circ)$$

$$\sin = \cos - 90$$

$$2\omega \leftarrow$$

$$P(t) = v(t) i(t) = \frac{1}{2} \times 80 \times 15 \cos(50) + \frac{1}{2} \times 80 \times 15 \times \cos(20t - 10^\circ)$$

$$\text{Power} \leftarrow = 385.7 + 600 \cos(20t - 10^\circ) \text{ W}$$

### Example:


A current  $I = 10 \angle 30^\circ$  flows through an impedance. Find the average Power delivered to the impedance.

$$Z = 20 \angle -22^\circ \Omega$$

$$\textcircled{1} \vec{V} = \vec{I} \vec{Z}$$

$$= 10 \angle 30^\circ \times 20 \angle -22^\circ$$

$$= 200 \angle 8^\circ$$

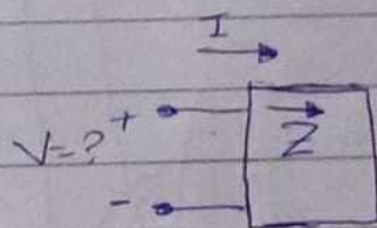

$$\textcircled{2} P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$\frac{1}{2}$$

$$= \frac{1}{2} \times 200 \times 10 \times \cos(8 - 30)$$

$$\frac{1}{2}$$


$$= 927.2 \text{ W}$$

$$\textcircled{3} P(t) = 927.2 + \frac{1}{2} \times 200 \times 10 \times \cos(2\omega t + 38^\circ)$$

$$\frac{1}{2}$$



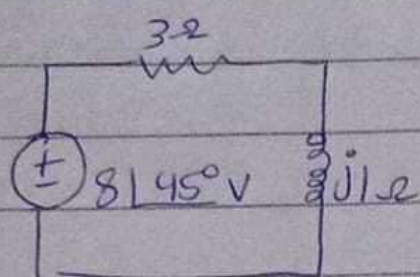Example: Find the average absorbed by resistor and inductor. Find the average power supplied by the source



① For the resistor:  $I = 8∠45^\circ$   
 $I_R = I = 2.53∠26.57^\circ$   
 $V_R = 3I = 7.59∠26.57^\circ$   
 $P_R = \frac{1}{2} V_m I_m = \frac{1}{2} (2.53)(7.59) = 9.6 \text{ W}$

② For the inductor,  $I_L = 2.53∠26.57^\circ$


$$V_L = jI_L = 2.53∠26.57^\circ + 90^\circ = 2.53∠116.57^\circ$$

$$P_L = \frac{1}{2} (2.53)^2 \cos(90^\circ) = 0 \text{ W}$$

③ The average Power supplied is:

$$p = \frac{1}{2} (8)(2.53) \cos(45^\circ - 26.57^\circ) = 9.6 \text{ W}$$

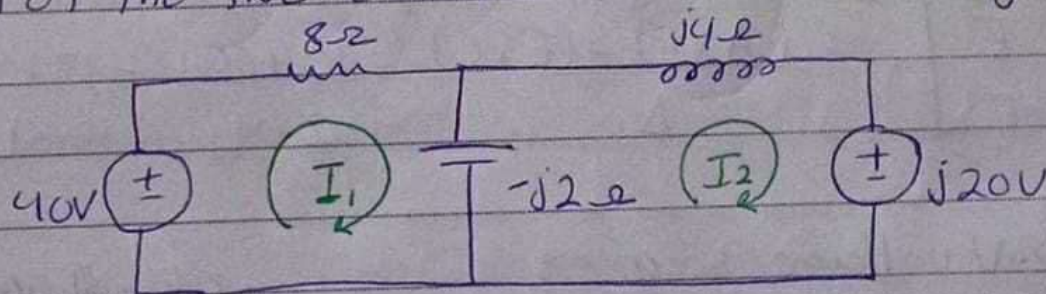Example: Calculate the average Power absorbed by each of the five elements in the circuit given.



For mesh ①:

$$-40 + 8I_1 + -j2(I_1 - I_2) = 0$$

$$-40 + (8 - j2)I_1 + (-j2)I_2 = 0$$

$$((8 - j2)I_1 + (-j2)I_2 = 40) \div 2$$

$$(4 - j)I_1 + (-j)I_2 = 20 \quad \text{--- ①}$$



For mesh ②:

$$-j20 + (j4 - j2)I_2 + (-j2)I_1 = 0$$

$$(j4 - j2)I_2 + (-j2)I_1 = j20 / 2$$

$$-jI_1 + jI_2 = j10$$

In matrix Form:

$$\begin{bmatrix} \overset{A}{4-j} & \overset{B}{-j} \\ \overset{C}{-j} & \overset{D}{j2} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \overset{E}{20} \\ \overset{F}{j10} \end{bmatrix}$$

$$\Delta = (A \times D) - (C \times B) = (1 + 4 \times j) - (-1) = 2 + 4j$$

$$\Delta_1 = \begin{bmatrix} E & B \\ F & C \end{bmatrix} = \frac{(E \times C) - (B \times F)}{\Delta} = \frac{-10 - 20j - (-5 - 6j)}{2 + 4j} = \frac{-10 + 20j}{2 + 4j} = 3 + 4j$$

$$I_1 = \frac{5 \angle 53.14^\circ}{7.8 \angle -129.8^\circ} = \dots$$

الجواب الذي في الأسود هيك طالع  
محي على الآلة الحاسبة

$$\Delta_2 = \begin{bmatrix} A & E \\ C & F \end{bmatrix} = \frac{(A \times F) - (E \times C)}{\Delta} = \frac{10 + 60j}{2 + 4j} = 13 + 4j = 13.6 \angle 17.11^\circ$$

For the 40-V voltage source:

$$V_s = 40 \angle 0^\circ \quad I_1 = 5 \angle 53.14^\circ$$

$$P_s = \frac{-1(-4)(5) \cos(-53.14^\circ)}{2} = -60 \text{ W}$$

For the j20-V voltage source:

$$V_s = 20 \angle 90^\circ \quad I_2 = 13.6 \angle 17.11^\circ$$



$$P_s = \frac{-1 (20)(13.6) \cos(90^\circ - 17.11^\circ)}{2} = -40 \text{ W}$$


For the resistors

$$I = |I_1| = 5 \quad V = 8 |I_1| = 40 \text{ volt}$$

$$P = \frac{1 (40)(5)}{2} = 100 \text{ W}$$

\* The average power absorbed by the inductor and capacitor is zero watts.
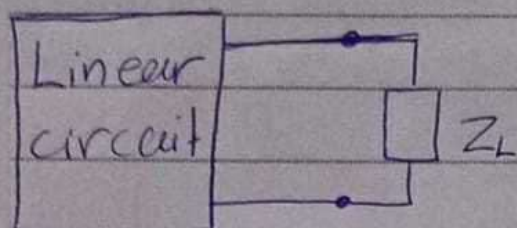
### 11.3 → Maximum Average Power Transfer.



$$Z_{TH} = R_{TH} + jX_{TH}$$


$$* R_L = R_{TH}$$

$$Z_L = R_L + jX_L$$

$$* X_L = -X_{TH}$$

The maximum average power can be transferred to the load if

a) Circuit with a load

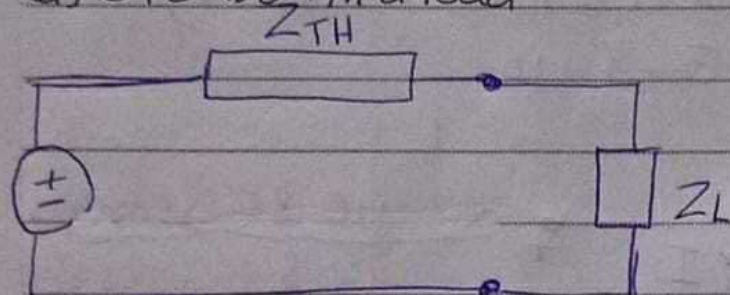

$$X_L = -X_{TH} \text{ and } R_L = R_{TH}$$

$$P_{max} = \frac{|V_{TH}|^2}{8 R_{TH}}$$

\* If the load is purely real, then  $R_L = \sqrt{R_{TH}^2 + X_{TH}^2}$


b) Thevenin Equivalent circuit.

$$= |Z_{TH}|$$


$$Z_L = R_{TH} - jX_{TH} = Z_{TH}^*$$



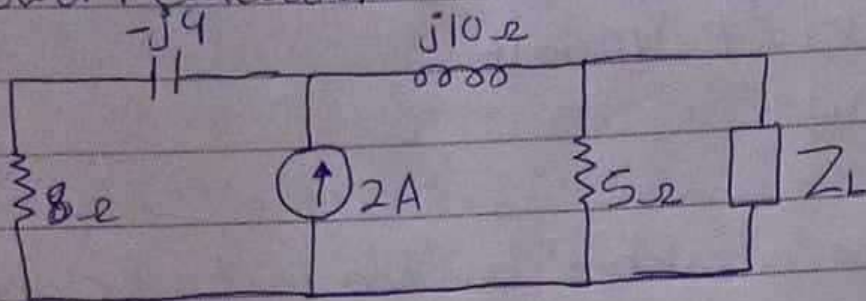**Example:** For the circuit shown below, find the load impedance  $Z_L$  that absorbs the maximum average power. Calculate the maximum average power.




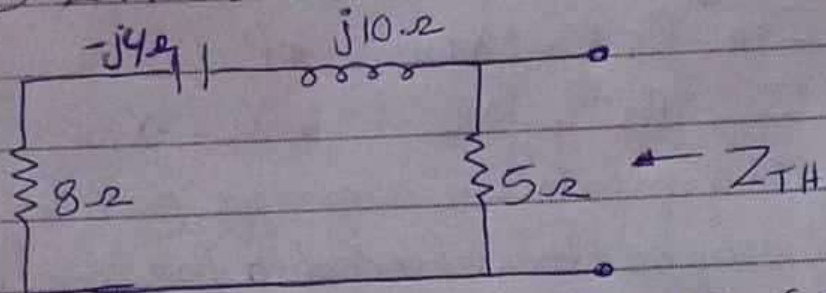①  $Z_{TH} = Z_L$  (We must kill all source and remove  $Z_L$ )



$$Z_{TH} = 5 \parallel (-j4 + j10 + 8) = \frac{5 \times (8 + j6)}{5 + 8 + j6} = 3.415 + j0.7317$$

②  $V_{TH} = ?$

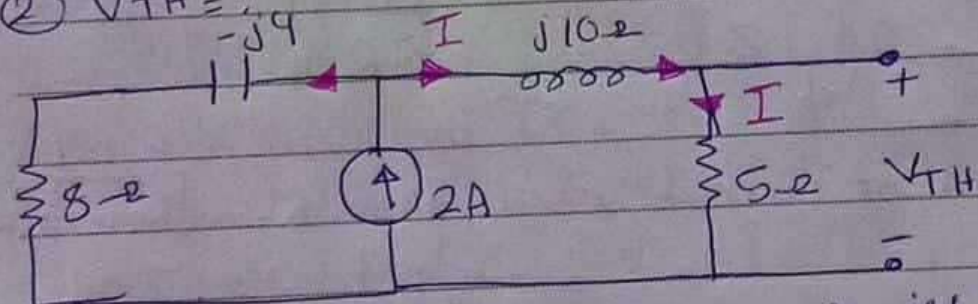

$j10 \ 8 \ 5 \rightarrow$  series  
 $-j4 \ 8 \ 8 \rightarrow$  series

By current division  $\Rightarrow I = \frac{8 - j4}{8 - j4 + j10 + 5} \quad (2)$

$$V_{TH} = 5I = (2)(5)(8 - j4) = 6.25 \angle -51.94^\circ$$

$Z_L = Z_{TH} = 3.415 - j0.7317 \ \Omega$

$R_L = 3.415 \ \Omega$        $X_L = -j0.7317 \ \Omega$

$$P_{max} = \frac{|V_{TH}|^2}{8R_L} = \frac{(6.25)^2}{(8)(3.415)} = 1.429 \text{ W}$$

## Maximum Average Power for Resistive Load.


\* When the load is Purely Resistive, the condition for maximum power transfer is:

$$R_L = \sqrt{R_{TH}^2 + X_{TH}^2} = |Z_{TH}|$$

\* Now the maximum power can not be obtained from  $P_{max}$  formula given before.

$$P = \frac{1}{2} I_L^2 R_L = \frac{1}{2} I_L V_L = \frac{1}{2} \frac{V_L^2}{R_L}$$

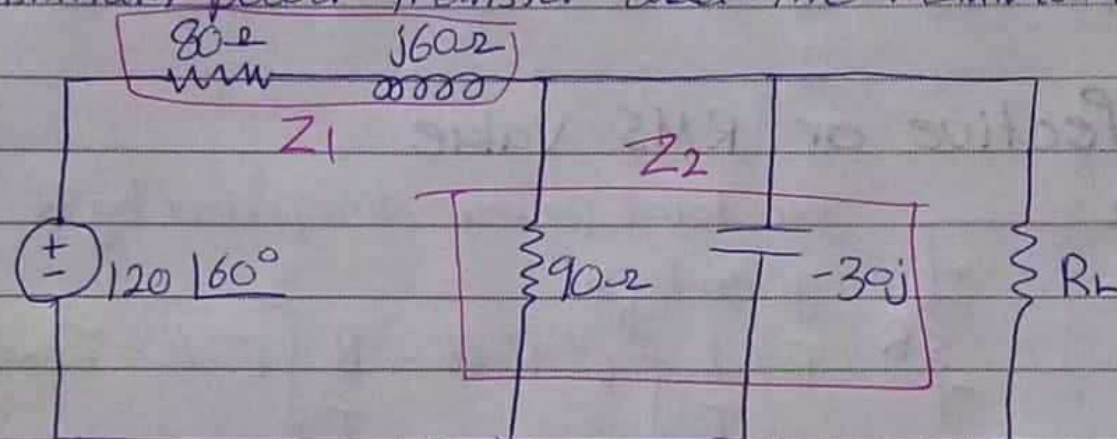**Examples** Calculate the resistive load needed for maximum power transfer and the maximum avg. power




sol: We first find  $Z_{TH}$  and  $V_{TH}$  across  $R_L$

$$\text{Let } Z_1 = 80 + j60 \text{ and } Z_2 = 90 \parallel -j30 = \frac{(90)(-j30)}{90 - j30} = 9(1 - j3)$$

$$Z_{TH} = Z_1 \parallel Z_2 = \frac{(80 + j60)(9 - j27)}{80 + j60 + 9 - j27}$$

$$= 17.181 - j24.57 \Omega$$

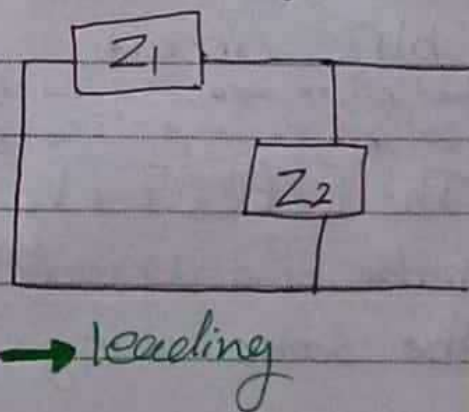$\frac{17.181}{R}$        $\frac{-j24.57}{X_{MS}}$



→ leading




$$V_{TH} = \frac{Z_2}{Z_1 + Z_2} (120 \angle 60^\circ) = \frac{9(1-j3)}{89+j33} (120 \angle 60^\circ)$$

$$= 35.98 \angle -31.91^\circ$$

$$R_L = |Z_{TH}| = 30.2$$

\* The current through the load is

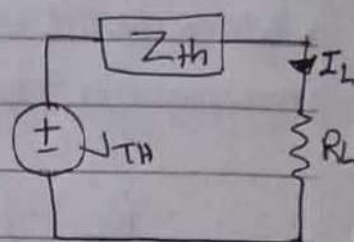
$$I = \frac{V_{TH}}{Z_{TH} + R_L} = \frac{35.98 \angle -31.91^\circ}{47.181 - j24.57} = 0.6764 \angle -4.4^\circ$$



The maximum average Power absorbed by  $R_L$  is

$$P_{max} = \frac{1}{2} |I|^2 R_L = \frac{1}{2} \times (0.6764)^2 (30) = 6.863 \text{ W}$$

## 11.4: Effective or RMS Value

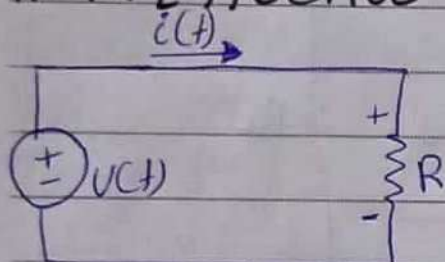


The total power dissipated by  $R$

given by:

$$P = \frac{1}{T} \int_0^T i^2 R dt = R \int_0^T i^2 dt = I_{rms}^2 R$$

a) AC circuit

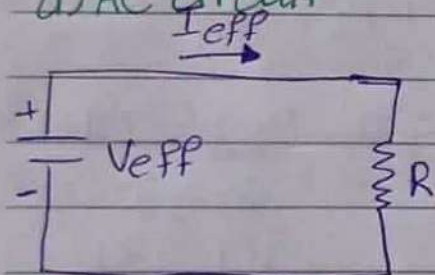

Hence,  $I_{eff}$  is equal to:

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{rms}$$

The rms value is a constant itself which depending on the shape of the function  $i(t)$ .


b) DC circuit

هذا لا سقافة من 2000 فرق الجهد المتغير بطريقة مستقيمة في 2000 فرق الجهد المتغير

The EFFECTIVE Value or the Root Mean Square (RMS) value of a periodic current is the DC value that delivers the same average power to a resistor as the periodic current.



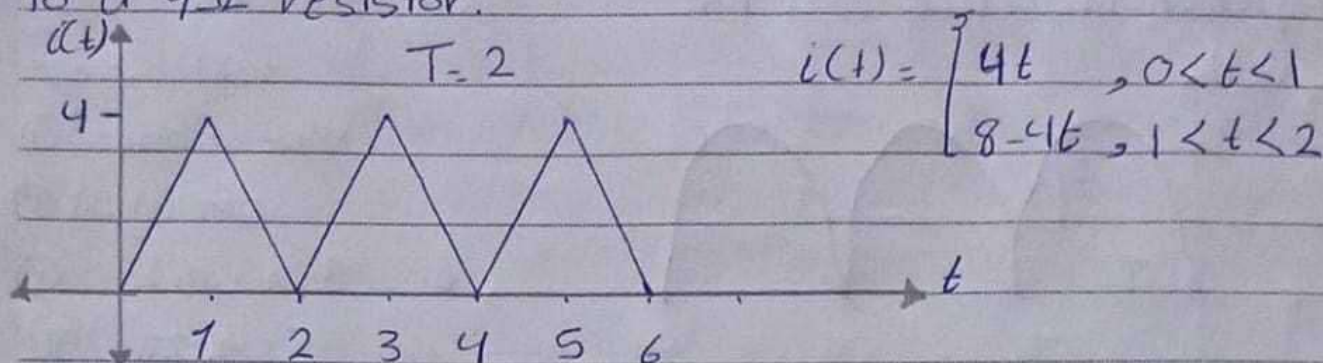Example: Find the RMS value of the current waveform. Calculate the average power if the current is applied to a  $9\Omega$  resistor.



$$I_{rms}^2 = \frac{1}{T} \int_0^T i^2 dt = \frac{1}{2} \left[ \int_0^1 (4t)^2 dt + \int_1^2 (8-4t)^2 dt \right]$$

$$I_{rms}^2 = \frac{16}{2} \left[ \int_0^1 t^2 dt + \int_1^2 (4-4t+t^2) dt \right]$$


$$I_{rms}^2 = 8 \left[ \frac{1}{3} + \left( 4t - 2t^2 + \frac{t^3}{3} \right) \right]_1^2 = \frac{16}{3}$$

$$I_{rms} = \sqrt{\frac{16}{3}} = 2.309 \text{ A}$$

$$P = I_{rms}^2 R = \frac{16}{3} (9) = 48 \text{ W}$$



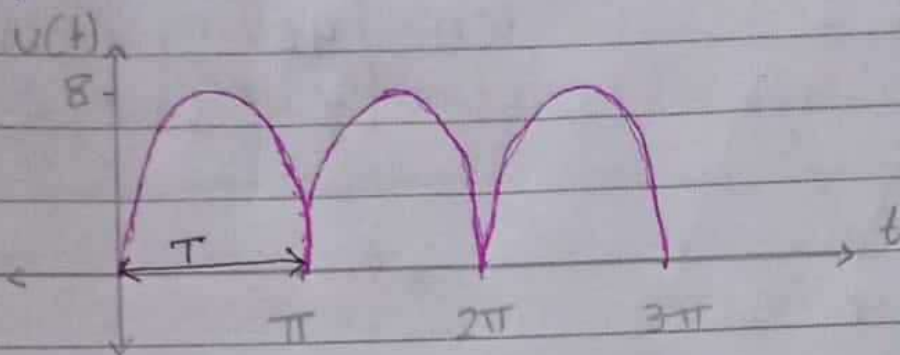Example: Find the RMS value of the full-wave rectified sine wave. Calculate the average power dissipated in a 6  $\Omega$  resistor.



كيف جيبا  $v(t)$  :

Value of peak = 8 ①

② اقتران sin

$8 \sin(\omega t)$  ③

$= 8 \sin(2\pi t / 2\pi)$

الفترة الزمنية Period

للكمال دورة كاملة

$= 8 \sin(t)$

$T = \pi, v(t) = 8 \sin(t), 0 < t < \pi$

$$V_{eff}^2 = \frac{1}{T} \int_0^T v^2 dt = \frac{1}{\pi} \int_0^{\pi} (8 \sin(t))^2 dt$$

$$V_{eff}^2 = \frac{64}{\pi} \int_0^{\pi} \frac{1}{2} [1 - \cos(2t)] dt = 32$$

$$V_{eff} = 5.657V$$

$$P = \frac{V_{eff}^2}{R} = \frac{32}{6} = 5.333W$$

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$\vec{V} = V_m \angle \theta_v [V]$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} [V_{rms}]$$

## 11.5: Apparent Power and Power Factor.

→ Apparent Power,  $S$ , is the product of the r.m.s values of voltage and current.

→ It is measured in volt-amperes or VA

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

Apparent Power  $\downarrow$   $\downarrow$  P.F

مهم الجيد

Purely resistive load (R)	$\theta_v - \theta_i = 0$ $PF = 1$	$P/S = 1$ , all power are consumed
Purely reactive load (L or C)	$\theta_v - \theta_i = \pm 90$ $PF = 0$ $\oplus \rightarrow L$ $\ominus \rightarrow C$	$P = 0$ , no real power consumption
Resistive and reactive load (R and L/C)	$\theta_v - \theta_i > 0$ $\theta_v - \theta_i < 0$	Lagging $\rightarrow$ inductive load leading $\rightarrow$ capacitive load

تأثير العلاقات التالية

$$① P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i) \rightarrow [W]$$

2

$$② PF = \frac{P}{S} = \cos(\theta_v - \theta_i)$$


S

$$③ S = \frac{1}{2} V_m I_m = V_{rms} I_{rms} [VA]$$

2



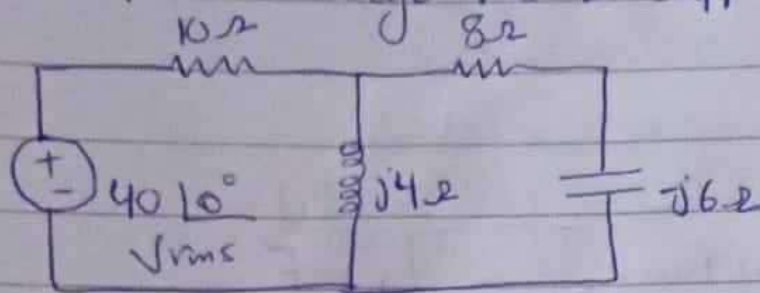Examples Calculate the power factor seen by the source and the average power supplied by the source



$$\begin{aligned} * V_m &= V_{rms} \times \sqrt{2} \\ &= 40 \angle 0^\circ \times \sqrt{2} \\ &= 56.56 \text{ Volt} \end{aligned}$$

The total impedance as seen by the source is

$$Z = 10 + [j4 \parallel (8 - j6)] = 10 + \frac{(j4)(8 - j6)}{8 - j6 + j4} \Rightarrow Z = 12.69 \angle 20.62^\circ$$

$\underbrace{\hspace{1cm}}_{R} \quad \underbrace{\hspace{1cm}}_{L}$

\* The Power Factor

$$PF = \cos(20.62^\circ) = 0.936 \text{ (lagging)} \rightarrow \text{lead/lag} \text{ (تأخر/تقدم)}$$

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{40 \angle 0^\circ}{12.69 \angle 20.62^\circ} = 3.152 \angle -20.62^\circ$$

\* The average power supplied by the source is equal to the power absorbed by the load.

$$P = I_{rms}^2 R = (3.152)^2 (11.88) = 118 \text{ W}$$


or

$$P = V_{rms} I_{rms} \cos \theta = (40)(3.152)(0.936) = 118 \text{ W}$$
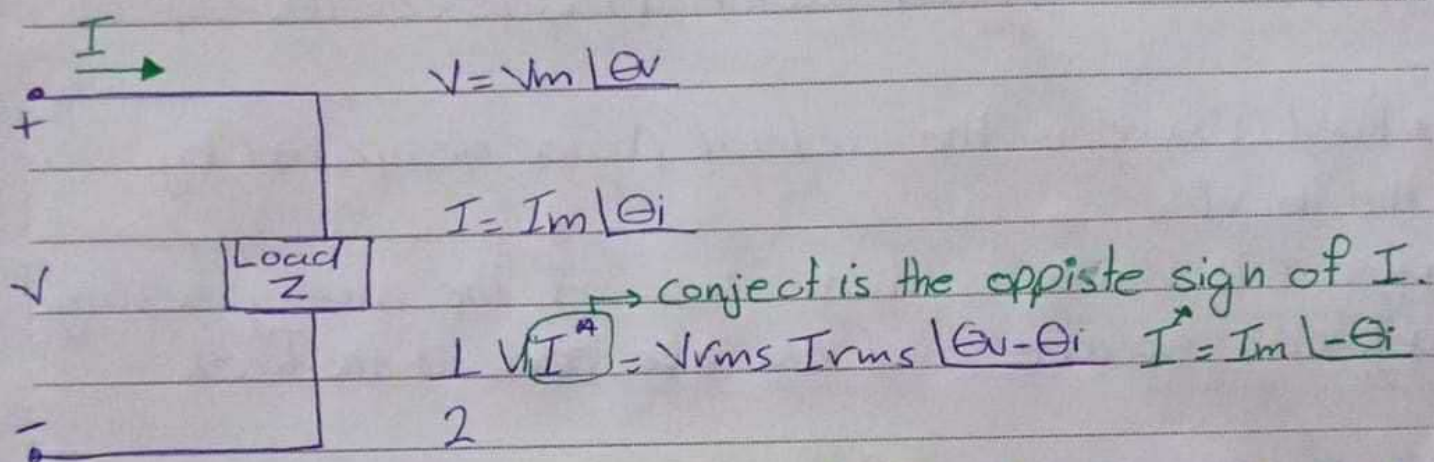
## 11.6: Complex Power

\* The COMPLEX Power ( $S$ ) contains all the information pertaining to the Power absorbed by a given load.

\* Complex power ( $S$ ) is the product of the voltage and the complex conjugate of the current.



\* (نقطة هامة) (complex power) (معامل القدرة) (power factor)

Ex:  $\vec{S} = 2 \angle 30^\circ \rightarrow S = 2, PF = \cos(30^\circ), P = S \times P.F$

$$S = \frac{1}{2} V I^* = \frac{V_{rms} I_{rms}}{2} \angle (\theta_v - \theta_i)$$

$$S = V_{rms} I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

$$S = P + jQ = S \angle \theta_v - \theta_i, S = \sqrt{P^2 + Q^2}$$

$P$  is the average Power in watts.


$Q$  is the reactive Power exchange between the source and the reactive part of the load.

$Q = 0$  (For resistive loads (unity PF)).

$Q < 0$  (For capacitive loads (leading PF)).

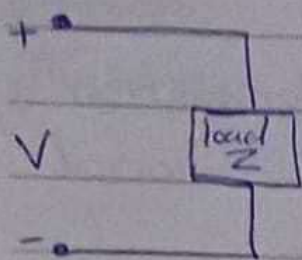$Q > 0$  (For inductive loads (lagging PF)).





$$S = V_{rms} I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

$$S = P + jQ$$

$$\rightarrow \text{Apparent Power } S = |S| = V_{rms} I_{rms} = \sqrt{P^2 + Q^2}$$

$$\rightarrow \text{Real Power, } P = \text{Re}(S) = S \cos(\theta_v - \theta_i)$$


$$\rightarrow \text{Reactive Power, } Q = \text{Im}(S) = S \sin(\theta_v - \theta_i)$$

$$\rightarrow \text{Power Factor, } PF = P/S = \cos(\theta_v - \theta_i)$$

\* Real Power is the actual power dissipated by the load.


\* Reactive Power is a measure of the energy exchange between source and reactive part of the load.

## Power Triangle

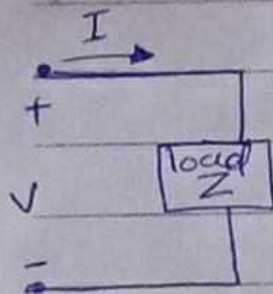


$$S = V_{rms} I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$


$$S = P + jQ$$

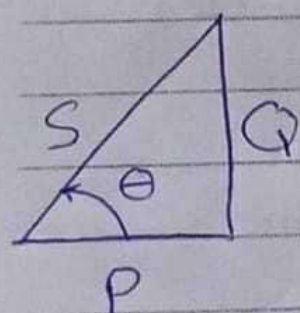

Power Triangle

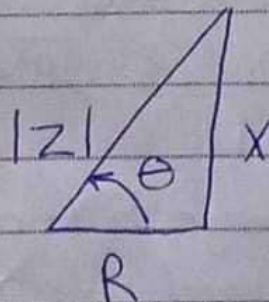

Impedance Triangle

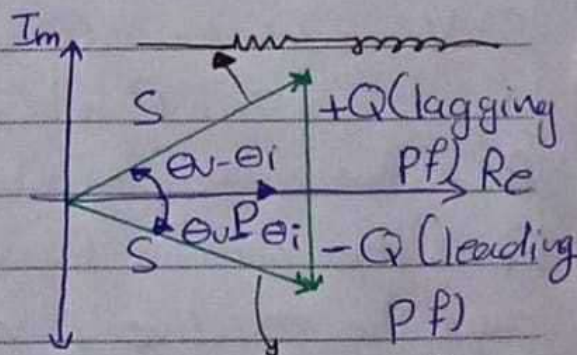

Power Factor



# Real and Reactive Powers

\* The unit of  $Q$  is volt-ampere reactive (VAR)

$$S = P + jQ = \text{Re}(S) + j\text{Im}(S)$$

= Real Power + Reactive Power


$$S = I_{\text{RMS}}^2 Z = I_{\text{RMS}}^2 (R + jX) = P + jQ$$

$$P = V_{\text{RMS}} I_{\text{RMS}} \cos(\theta_v - \theta_i) = \text{Re}\{S\} = I_{\text{RMS}}^2 R$$

$$Q = V_{\text{RMS}} I_{\text{RMS}} \sin(\theta_v - \theta_i) = \text{Im}\{S\} = I_{\text{RMS}}^2 X$$

Unit:  $P$  [W] /  $\vec{S}$  [VA] /  $Q$  [VAR]


## Use of Power Triangles

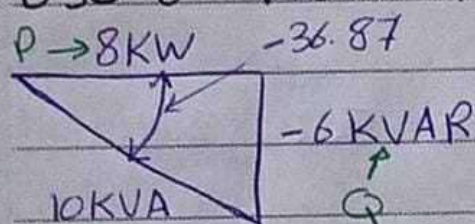

$$\vec{S}_1 = 10 \angle -36.87^\circ$$

$$= P + jQ$$

leading

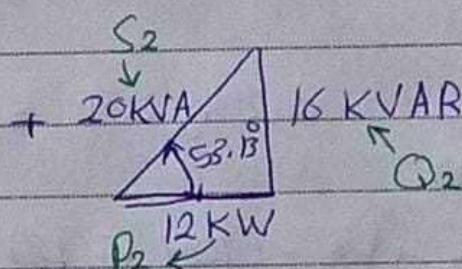


$$\vec{S}_2 = 20 \angle 53.13^\circ$$

$$* S_{\text{Total}} = P + jQ = S_1 + S_2$$

$$= (P_1 + P_2) + j(Q_1 + Q_2)$$

$$= (8 + 12) + j(-6 + 16)$$

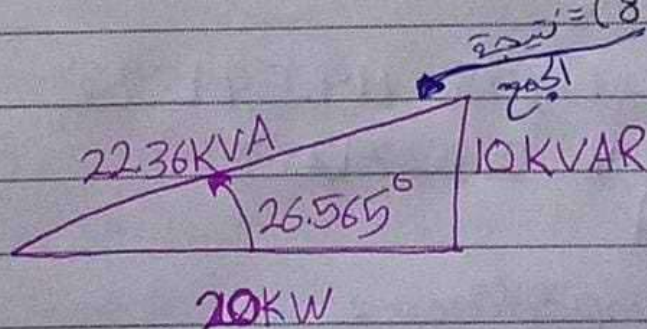

Power (W) ← قاطعة المثلث


Q (VAR) ← الضلع

$\vec{S}$  (VA) ← الوتر


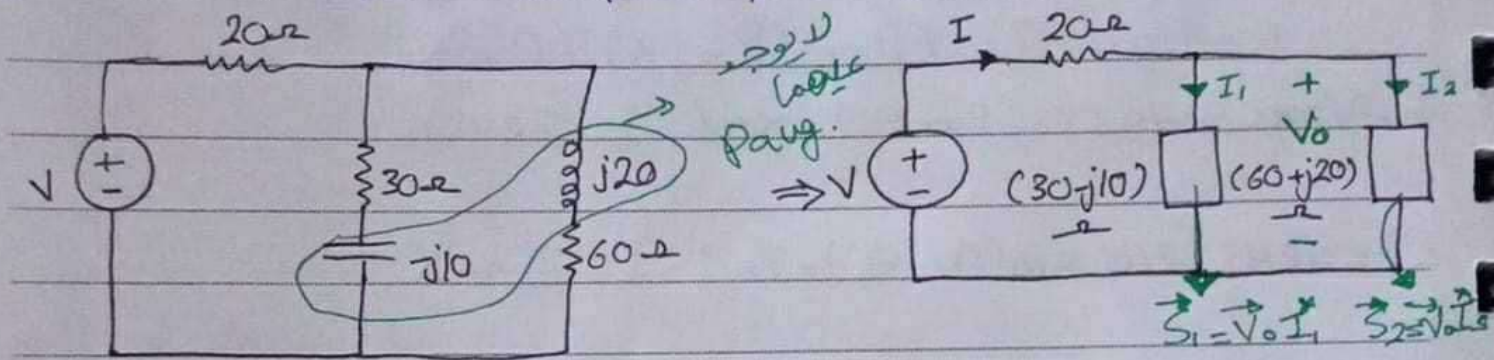
# Example:

The  $60\Omega$  resistor absorbs 240 Watt of average Power. Calculate  $V$  and the complex power of each branch. What is the total complex power?



$$P = I_2^2 R \Rightarrow I_2^2 = \frac{P}{R} = \frac{240}{60} = 4 \Rightarrow I_2 = 2 \angle 0^\circ \text{ (rms)}$$

$$V_0 = I_2(60 + j20) = 120 + j40 \rightarrow V_{rms}$$

$$I = \frac{V_0}{30 - j10} = 3.2 + j2.4 \Rightarrow I = I_1 + I_2 = 5.2 + j2.4$$

$$V = 20I + V_0 = (104 + j48) + (120 + j40) = 224 + j88$$

$$= 240.67 \angle 21.45^\circ \text{ (rms)}$$

For the  $20\Omega$  resistor:

$$V = 20I = 204 + j48 = 114.54 \angle 24.8^\circ$$

$$I = 5.2 + j2.4 = 5.727 \angle 24.8^\circ$$

$$S = 656 \text{ VA}$$

For the  $(30 - j10)\Omega$  impedance:

$$V_0 = 120 + j40 = 126.5 \angle 18.43^\circ$$

$$I_1 = 3.2 + j2.4 = 4 \angle 36.87^\circ$$

$$S_1 = V_0 I_1^* = (126.5 \angle 18.43^\circ)(4 \angle -36.87^\circ)$$



$S_1 = 506 \angle -18.44^\circ = 480 - j160 \text{ VA}$

*Annotations:  $P_{avg}$  points to 480,  $Q = -160$  points to -j160*

For the  $(60 + j20) \Omega$  impedance:

$I_2 = 2 \angle 0^\circ$

$S_2 = V_o I_2^* = (126.5 \angle 18.43^\circ)(2 \angle 0^\circ)$   
 $= 253 \angle 18.43^\circ$   
 $= 240 + j80 \text{ VA}$

The overall complex power supplied by the source is

$S_T = V I^* = (240.67 \angle 21.45^\circ)(5.727 \angle -24.8^\circ)$   
 $= 1378.31 \angle -3.35^\circ$   
 $= 1376 - j80 \text{ VA}$

**Example:** Two loads are connected in Parallel. Load 1 has 2 KW,  $PF = 0.75$  leading and Load 2 has 4 KW,  $PF = 0.95$  lagging. Calculate the PF of two loads and the complex power supplied by the source.

Load (1)  $\Rightarrow P_1 = 2000$

$P_1 = S_1 \cos \theta_1$

$S_1 = \frac{P_1}{\cos \theta_1}$

$= \frac{2000}{\cos \theta_1}$

$= \frac{2000}{0.75}$

$= 2666.67$

$PF = 0.75 = \cos \theta_1$

$\theta_1 = \cos^{-1}(0.75) = -41.41^\circ$

$Q_1 = S_1 \sin \theta_1 = -176.85$

$S_1 = P_1 + jQ_1$

$= 2000 - j176.85 \text{ (leading)}$

Load (2)  $\Rightarrow P_2 = 4000$

$S_2 = \frac{P_2}{\cos \theta_2}$

$= \frac{4000}{\cos \theta_2}$

$= \frac{4000}{0.95}$

$= 4210.53$

$PF = 0.95 = \cos \theta_2$

$\theta_2 = \cos^{-1}(0.95) = 18.19^\circ$

$Q_2 = S_2 \sin \theta_2 = 1314.4$

$S_2 = P_2 + jQ_2$

$= 4000 + j1314.4 \text{ (lagging)}$




The total complex Power is

$$S = S_1 + S_2$$

$$= 6 - j0.4495 \text{ kVA}$$

$$PF = \frac{P}{|S|} = \frac{6000}{6016.18} = 0.9972 \text{ (leading)}$$


Example:

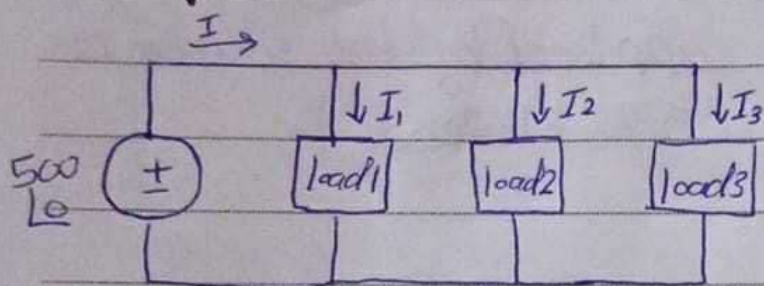

load 1


load 2

load 3

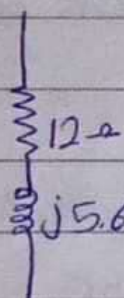


$$Z_1 = 12 + j5.65$$

$$= 13.26 \angle 25.21^\circ \Omega$$

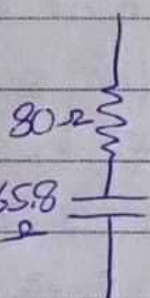

$$Z_2 = 80 - j165.8$$

$$= 184.1 \angle -64.2^\circ \Omega$$

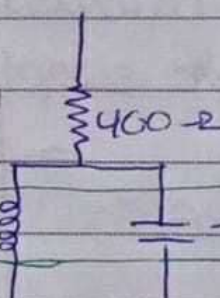

$$Z_3 = 400 - j571$$

$$= 697 \angle -55^\circ \Omega$$

$$Z_{\text{equ}} = \frac{(j7540)(-j530.5)}{j7540 - j530.5} = -570.6 \approx 571 \Omega$$

$$PF_1 = \cos(25.21)$$

$$= 0.9 \text{ lag}$$

$$PF_2 = \cos(-64.2)$$

$$= 0.43 \text{ lead}$$

$$PF_3 = \cos(-55)$$

$$= 0.571 \text{ lead}$$

$$I_1 = \frac{500 \angle 0^\circ}{13.26 \angle 25.21^\circ} = 37.7 \angle -25.21^\circ = 34.11 - j16.06$$



$$I_2 = \frac{500 \angle 0^\circ}{184.11 \angle -64.2^\circ} = 2.72 \angle 64.2^\circ = 1.18 + j2.45$$

$$I_3 = \frac{500 \angle 0^\circ}{697 \angle -55^\circ} = 0.72 \angle 55^\circ = 0.41 + j0.59$$

$$I = I_1 + I_2 + I_3 = 35.7 - j13.02 = 38 \angle -20^\circ \text{ A}$$

$$\text{Combined PF} = \cos(20) = 0.94 \text{ lag}$$

$$S_1 = \hat{V} I_1^* = 500 \times 37.7 \angle 25.21^\circ = 18850 \angle 25.21^\circ = 17055 + j8029 \text{ VA}$$

$$S_2 = \hat{V} I_2^* = 500 \times 2.72 \angle -64.2^\circ = 1360 \angle -64.2^\circ = 592 - j1224 \text{ VA}$$

$$S_3 = \hat{V} I_3^* = 500 \times 0.72 \angle -55^\circ = 360 \angle -55^\circ = 207 - j295 \text{ VA}$$



$$S = S_1 + S_2 + S_3 = 17854 - j6510 = 19000 \angle -20^\circ \text{ VA}$$

$$\text{Check: } S = \hat{V} I^* = 500 \times 38 \angle -20^\circ = 19000 \angle -20^\circ \text{ VA}$$


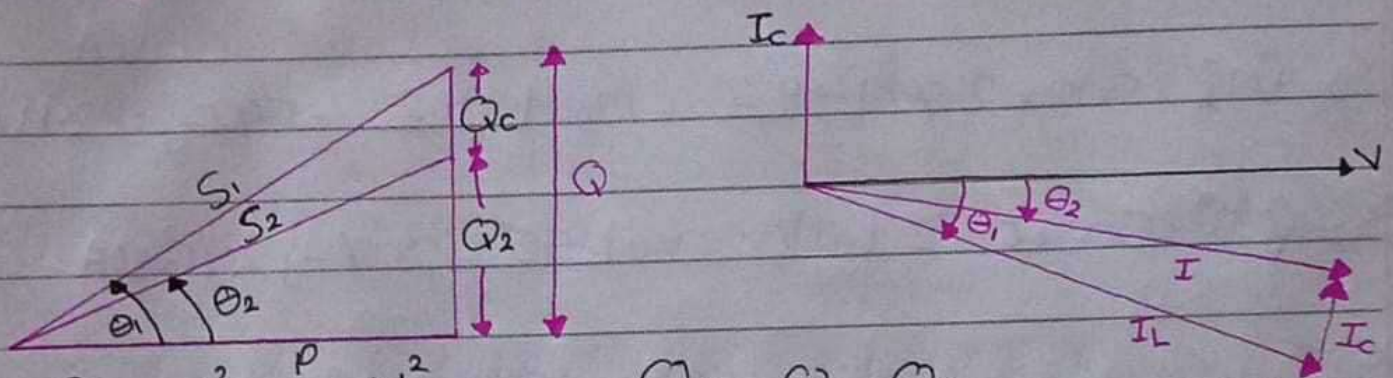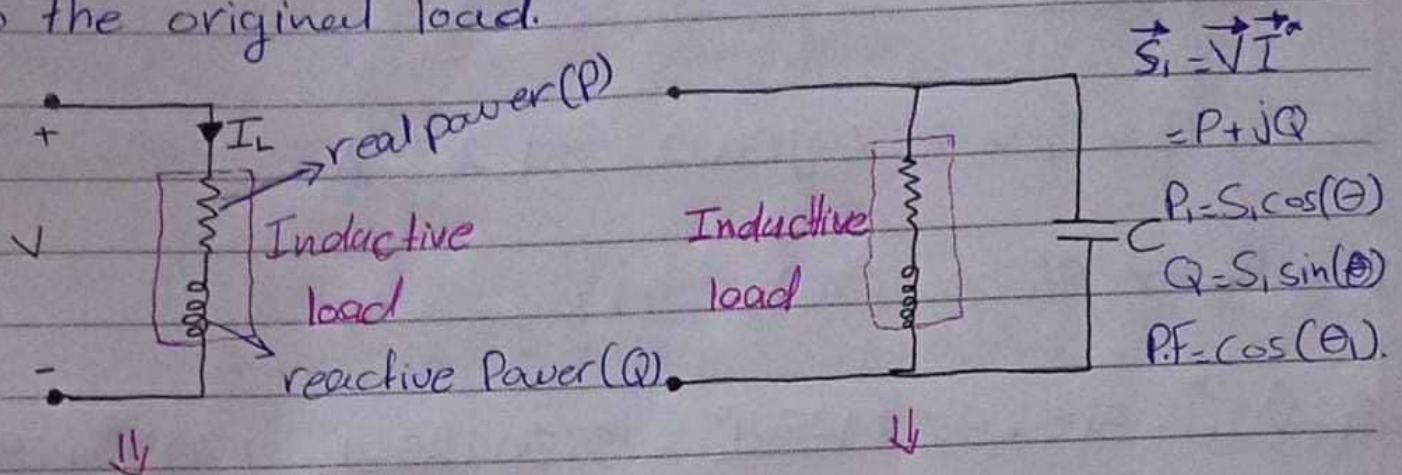
# Power Factor Correction

Power factor correction is the process of increasing the Power factor without altering the voltage or current to the original load.



$$Q_c = \frac{V_{rms}^2 P}{X_c} = \frac{V_{rms}^2}{1/\omega C}$$

$$Q_c = Q_1 - Q_2$$

$$= P(\tan \theta_1 - \tan \theta_2)$$

$$= \omega C V_{rms}^2$$

$$Q_2 = Q_1 + Q_c$$

$$Q_2 < Q_1$$

$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V_{rms}^2}$$

↑ P.F. ↓  $\theta$  ، لترفع قيمة (P) وتنزل قيمة الزاوية  $\theta$  .



11

Examples Find the value of the capacitance needed to correct a load of 140 KVAR at 0.85 lagging PF to unity PF. The load is supplied by 110 V (rms), 60 Hz line

$$PF = 0.85 = \cos \theta \rightarrow \theta = 31.79^\circ$$

$$Q = S \sin \theta \rightarrow S = \frac{Q}{\sin \theta} = \frac{140}{\sin(31.79^\circ)} = 265.8 \text{ KVA}$$

$$P = S \cos \theta = 225.93 \text{ KW}$$

\*For  $PF = 1 = \cos \theta \rightarrow \theta = 0^\circ$

Since  $P$  remains the same

$$P = P_1 = S_1 \cos \theta_1 \rightarrow S_1 = \frac{P_1}{\cos \theta_1} = 225.93$$

$$Q_1 = S_1 \sin \theta_1 = 0$$

The different between the new  $Q$  and the old  $Q$  is  $Q_c$ .


$$Q_c = 140 \text{ KVAR} = \omega C V_{rms}^2$$

$$C = \frac{140 \times 10^3}{(2\pi)(60)(110)^2} = 30.69 \mu\text{F}$$



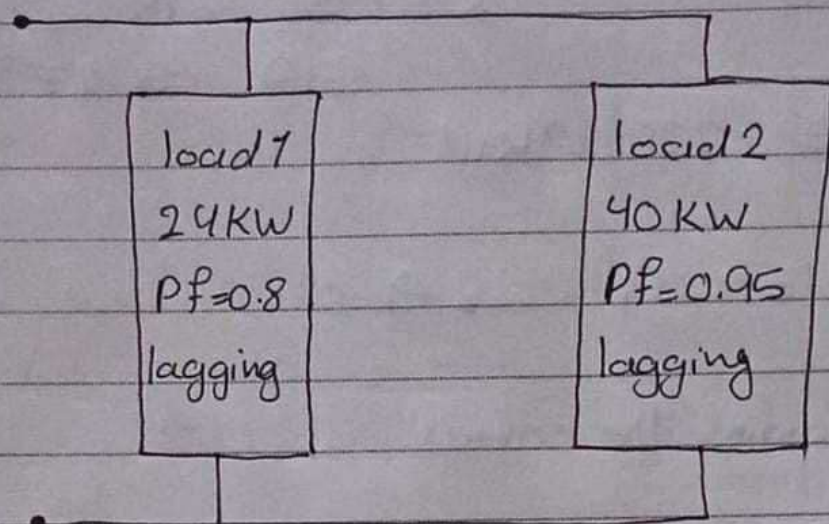Example 3 A 120-Vrms, 60 Hz source supplies two loads connected in parallel.

- Find the power Factor of the Parallel combination.
- calculate the value of the capacitance connected in Parallel that will raise the Power factor to unity.



$$a) \theta_1 = \cos^{-1}(0.8) = 36.87^\circ, S_1 = \frac{P_1}{\cos \theta_1} = \frac{24}{0.8} = 30 \text{ KVA}$$

$$Q_1 = S_1 \sin(\theta) = (30)(0.6) = 18 \text{ KVAR}, \vec{S}_1 = 24 + j18 \text{ KVA}$$

$$\theta_2 = \cos^{-1}(0.95) = 18.19^\circ, S_2 = \frac{P_2}{\cos \theta_2} = \frac{40}{0.95} = 42.105 \text{ KVA}$$

$$Q_2 = S_2 \sin(\theta) = 13.144 \text{ KVAR}, \vec{S}_2 = 40 + j13.144 \text{ KVA}$$

$$S = S_1 + S_2 = 64 + j31.144 \text{ KVA}$$

$$\theta = \tan^{-1}(31.144/64) = 25.95^\circ, \text{PF} = \cos \theta = 0.8992 (\text{lag})$$

$$b) \theta_2 = 25.95^\circ, \theta_1 = 0^\circ$$

$$Q_c = P[\tan \theta_2 - \tan \theta_1] = 64[\tan(25.95^\circ) - 0] = 31.144 \text{ KVAR}$$

$$C = \frac{Q_c}{\omega V_{\text{rms}}^2} = \frac{31.144}{(2\pi)(60)(120^2)} = 5.79 \text{ mF}$$



11

**Problem (1):** The heating element in a soldering iron has a resistance of  $30\ \Omega$ . Find the average power dissipated in the soldering iron if it is connected to a voltage source of  $117\text{ Vrms}$ .

$$P_{\text{avg}} = \frac{V_{\text{rms}}^2}{R} = \frac{(117)^2}{30} = 456.3\text{ W}$$

**Problem (2):**

A current of  $4\text{ A}$  flows when a neon light advertisement is supplied a  $110\text{ Vrms}$  power system. The current lags the voltage by  $60^\circ$ . Find the power dissipated by the circuit and the power factor.

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}} = \frac{4}{\sqrt{2}} = 2.82 \quad \text{or} \quad V_m = V_{\text{rms}} \times \sqrt{2} = 110 \times \sqrt{2} = 155.56$$

$$P = I_{\text{rms}} V_{\text{rms}} \cos(\theta_v - \theta_i) = 2.82 \times 110 \times \cos(-60) = 155.1\text{ W}$$

$$P.F. = \cos(60) = 0.5, \quad P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = 155.56\text{ W}$$

**Problem (3):**

A current of  $10\text{ Arms}$  flow when a single-phase circuit is placed across a  $220\text{ Vrms}$  source. The current lags the voltage by  $60^\circ$ . Find the power dissipated by the circuit and the Power Factor.

$$\begin{aligned} P &= V_{\text{rms}} I_{\text{rms}} \cos(-60) \\ &= 10 \times 220 \times \cos(-60) \\ &= 1100\text{ W} \end{aligned}$$

$$P.F. = \cos(-60) = 0.5$$



Problem: A current source  $i(t)$  is connected to a  $50\text{-}\Omega$  resistor. Find the average Power delivered to the resistor that  $i(t)$  is:

a.  $5 \cos(50t) \text{ A}$ .  $I_{\text{rms}} = I_m / \sqrt{2}$

$i = 5 \angle 0^\circ \rightarrow P_{\text{avg}} = I_{\text{rms}}^2 \times R = (5/\sqrt{2})^2 \times 50 = 625 \text{ W}$

b.  $5 \cos(5t - 45) \text{ A}$ .

$i = 5 \angle -45 \rightarrow P_{\text{avg}} = (5 \angle -45 / \sqrt{2})^2 \times 50 = 625 \text{ W}$

c.  $5 \cos(50t) - 2 \cos(50t - 0.873)$

$5 \angle 0 - 2 \angle -0.873 = 3 \angle 0.582$

$I_{\text{rms}} = \frac{3 \angle 0.582}{\sqrt{2}} = 2.12 \angle 0.582$ ,  $P_{\text{avg}} = (2.12 \angle 0.582)^2 \times 50 = 225 \text{ W}$

d.  $5 \cos(50t) - 2 \text{ A}$ .

DC  $\rightarrow -2 \text{ A}$

AC  $\rightarrow 5 \angle 0^\circ$

$P_{\text{total}} = P_{\text{AC}} + P_{\text{DC}}$

$= (-2)^2 \times 50 + (5/\sqrt{2})^2 \times 50 = 200 + 625 = 825 \text{ W}$

Problem: Find the rms value of each of the following:

a.  $i(t) = \cos(450t) + 2 \cos(450t) \text{ A}$ .

$= 3 \cos(450t)$

$I_{\text{rms}} = 3/\sqrt{2} = 2.12 \text{ A}$

b.  $i(t) = \cos(5t) + \sin(5t)$

$= \cos(5t) + \cos(5t - 90)$

$= 1 \angle 0^\circ + 1 \angle -90^\circ$

$= \sqrt{2} \angle -45^\circ$

$I_{\text{rms}} = \sqrt{2} \angle -45^\circ / \sqrt{2} = 1 \angle -45^\circ$



$$c. i(t) = \cos(450t) + 2$$
$$= 1 \angle 0^\circ + 2$$

$$I_{rms} = \sqrt{(2)^2 + \left(\frac{1}{\sqrt{2}}\right)^2} = \sqrt{4 + 0.5} = 2.12 \text{ A}$$

$$d. i(t) = \cos(5t) + \cos(5t + \pi/3)$$

$$= 1 \angle 0^\circ + 1 \angle 60^\circ$$

$$= 1 + 0.5 + j0.866$$

$$= 1.5 + j0.866$$

$$\text{value} = \sqrt{(1.5)^2 + (0.866)^2} = \sqrt{3}$$

$$I_{rms} = \frac{\sqrt{3}}{\sqrt{2}} = 1.22 \text{ A}$$

$$e. i(t) = \cos(200t) + \cos(400t)$$

$$I_{rms} = \sqrt{\left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2} = \sqrt{0.5 + 0.5} = 1 \text{ Arms}$$

**Problem 8** A residential electric power monitoring system rated for 120V rms, 60 Hz, source registers power consumption of 1.2 kW, with P.F = 0.8. Find:-

①  $I_{rms} = ?$       ② The phase angle      ③ The system impedance

④ The system resistance.

$$② \theta = \cos^{-1}(0.8) = 38.87^\circ$$

$$① I_{rms} = \frac{P}{V \cos \theta}$$

$$S = \frac{P}{\cos \theta} = \frac{1.2}{0.8} = 1.5 \text{ kVA}$$

$$V \cos \theta$$

$$= \frac{1200}{0.8}$$

$$Q = S \sin \theta = 1.5 \times \sin(38.87^\circ) = 0.9413 \text{ kVAR}$$

$$120 \times 0.8$$

$$\vec{S} = 1.2 + j0.9413$$

$$= 12.5 \text{ Arms}$$

$$③ |Z| = \frac{V}{I} = 120 / 12.5 = 9.6 \Omega$$


$$④ R = |Z| \cos \theta = 9.6 \times 0.8 = 7.68 \Omega$$


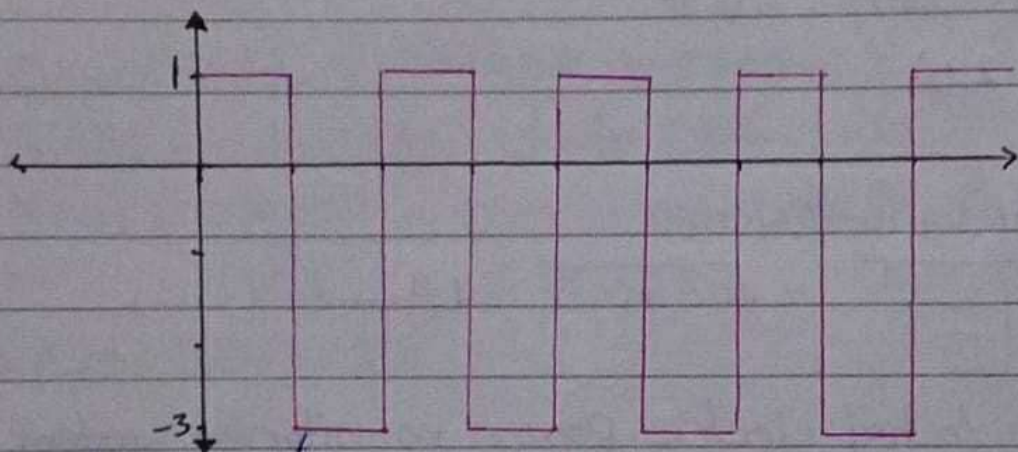
### Problem #7.8:

Given the waveform of a voltage source shown below, find:

- The steady DC voltage that would cause the same heating effect across a resistance.
- The average current supplied to a  $10\text{-}\Omega$  resistor connected across the voltage source.
- The average power supplied to a  $1\text{-}\Omega$  resistor across the voltage source.



$$a) V_{rms}^2 = \frac{1}{T} \int_0^T v(t)^2 dt$$

$$V_{rms}^2 = \frac{1}{2} \left[ \int_0^1 (1)^2 dt + \int_1^2 (-3)^2 dt \right]$$

$$= \frac{1}{2} (1 + 9)$$

$$V_{rms}^2 = 5$$

$$V_{rms} = 2.24\text{ V}$$

$$b) V_{avg} = \frac{1}{T} \int_0^T V(t) dt$$

$$V_{avg} = \frac{1}{2} \left[ \int_0^1 (1) dt + \int_1^2 (-3) dt \right]$$

$$= \frac{1}{2} (1 - 3)$$

$$= -1$$

$$= -1V$$

$$I_{avg} = \frac{V_{avg}}{R} = \frac{-1}{10} = -0.1A$$

$$c) P_{avg} = \frac{V_{rms}^2}{R}$$

$$= \frac{5}{1.5}$$

$$= 3.33W$$

$$= 3.33W$$

Problem: For the circuit shown below, determine the power factor for the load and state whether it is leading or lagging for the following conditions:


$$a. V_s(t) = 540 \cos(\omega t + 15^\circ) V$$

$$i_L(t) = 20 \cos(\omega t + 47^\circ) A$$

$$V = 540 \angle 15^\circ, Z = \frac{V}{I} = \frac{540 \angle 15^\circ}{20 \angle 47^\circ} = 27 \angle -32^\circ$$

$$I = 20 \angle 47^\circ$$
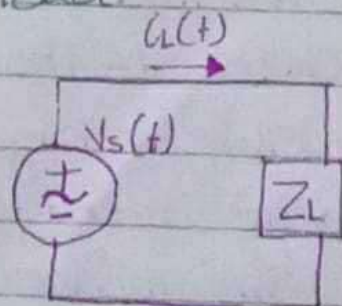
$$P.F. = \cos(1-32) = \cos(32) = 0.848 \text{ leading}$$





b)  $V_s(t) = 155 \cos(\omega t - 15^\circ)$

$i_L(t) = 20 \cos(\omega t - 22^\circ)$

Phase difference  $\phi = -15 - (-22) = 7$ , P.F. =  $\cos(7^\circ) = 0.993$  lagging

c)  $V_s(t) = 208 \cos(\omega t)$

$i_L(t) = 1.7 \sin(\omega t + 175^\circ) = 1.7 \cos(\omega t + 175 - 90^\circ) = \cos(\omega t + 85^\circ)$

Phase difference:  $\phi = 0 - 85^\circ = -85^\circ$ , P.F. =  $\cos(-85^\circ) = 0.087$  leading

d)  $Z_L = (48 + j16) \Omega = 50.6 \angle 18.4^\circ$ ,  $G > 0$ .

P.F. =  $\cos(18.4^\circ) = 0.949$ , lagging.

**Problem:** For the circuit shown below, determine whether the load is capacitive or inductive for the circuit shown

a) PF = 0.87 (leading), b) PF = 0.42 (leading).

leading power factor means current leads voltage, which indicates a capacitive load. a & b ✓ same answer.

c)  $V_s(t) = 42 \cos(\omega t) V$

$i_L(t) = 4.2 \sin(\omega t) A \Rightarrow i_L(t) = 4.2 \cos(\omega t - 90^\circ)$

current leads voltages by  $90^\circ$ , indicating a capacitive load.

d)  $V_s(t) = 10.4 \cos(\omega t - 12^\circ) V$

$i_L(t) = 0.4 \cos(\omega t - 12^\circ) A$  No phase change means (neither capacitive nor ind.)

### Problem 8

A load impedance,  $Z_L = 10 + j3 \Omega$ , is connected to a source with line resistance equal  $1 \Omega$ , as shown below.

Calculate the following values:

a) The average Power delivered to the total.

b) The average Power absorbed by the line.

c) The apparent power supplied by the generator.


d) The Power Factor to the load.

e) The power factor of line plus load.

$$Z_{total} = 1 + j0 + j3 = 1 + j3 = 11.4 \angle 15.26^\circ$$

$$I = \frac{V_s}{Z_{total}} = \frac{230 \angle 0^\circ}{11.4 \angle 15.26^\circ} = 20.18 \angle -15.26^\circ$$

$$Z_{total} = 11.4 \angle 15.26^\circ$$

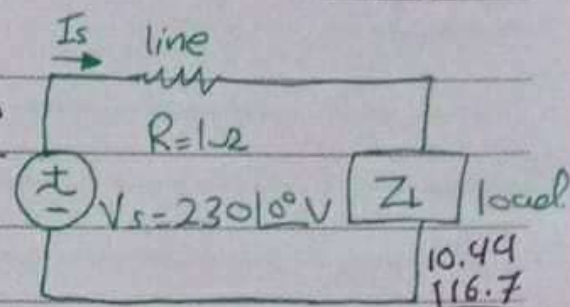

$$a) P_{load} = I^2 R = (20.18)^2 \times 10.44 = 4251.51$$

$$b) P_{line} = I^2 R = (20.18)^2 \times 1 = 407.23$$

$$c) S = VI = 230 \times 20.18 = 4641 \text{ VA}$$


$$d) P.F. = \cos(16.7) = 0.958, \text{ lagging}$$

$$e) P.F. = \cos(15.26^\circ) = 0.965, \text{ lagging}$$


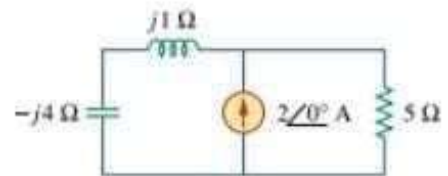
### 11. Problem # 11

Given the circuit shown below, find the average power supplied or absorbed by each element.




3
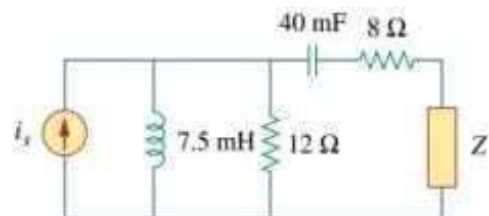
### 12. Problem # 12

It is desired to transfer maximum power to the load  $\mathbf{Z}$  in the circuit shown below. If the source current,  $i_s(t) = 5\cos 40t\text{ A}$ , find:


- the load impedance  $\mathbf{Z}$  for maximum power transfer.
- the maximum average power.


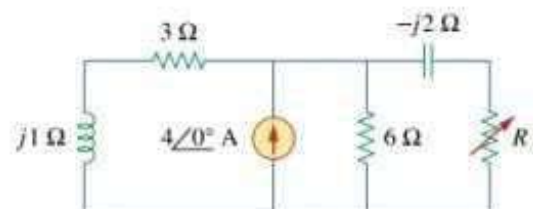
### 13. Problem # 13


The variable resistor  $R$  in the circuit shown below is adjusted until it absorbs the maximum average power. Find:

- the load resistance  $R$  for maximum power transfer.
- the maximum average power.



### Chapter 11, Problem 19.

The variable resistor  $R$  in the circuit of Fig. 11.50 is adjusted until it absorbs the maximum average power. Find  $R$  and the maximum average power absorbed.

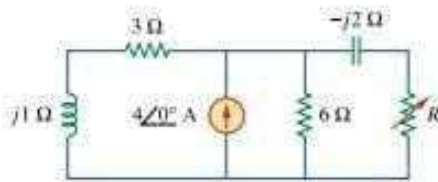

**Figure 11.50**  
For Prob. 11.19.

### Chapter 11, Solution 19.

At the load terminals,

$$Z_{Th} = -j2 + 6 \parallel (3 + j) = -j2 + \frac{(6)(3 + j)}{9 + j}$$

$$Z_{Th} = 2.049 - j1.561$$

$$R_L = |Z_{Th}| = \underline{2.576 \Omega}$$

To get  $V_{Th}$ , let  $Z = 6 \parallel (3 + j) = 2.049 + j0.439$ .

By transforming the current sources, we obtain


$$V_{Th} = (4 \angle 0^\circ) Z = 8.196 + j1.756$$

$$P_{max} = \left| \frac{8.382}{2.049 - j1.561 + 2.576} \right|^2 \frac{2.576}{2} = \underline{3.798 \text{ W}}$$



### Chapter 11, Problem 14.

It is desired to transfer maximum power to the load  $\mathbf{Z}$  in the circuit of Fig. 11.45. Find  $\mathbf{Z}$  and the maximum power. Let  $i_s = 5\cos 40t$  A.

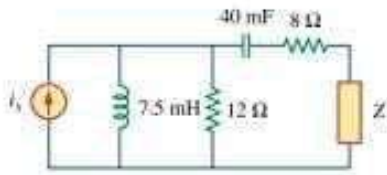


**Figure 11.45**  
For Prob. 11.14.

### Chapter 11, Solution 14.

We find the Thevenin equivalent at the terminals of  $\mathbf{Z}$ .

$$\begin{aligned} 40 \text{ mF} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j40 \times 40 \times 10^{-3}} = -j0.625 \\ 7.5 \text{ mH} &\longrightarrow j\omega L = j40 \times 7.5 \times 10^{-3} = j0.3 \end{aligned}$$

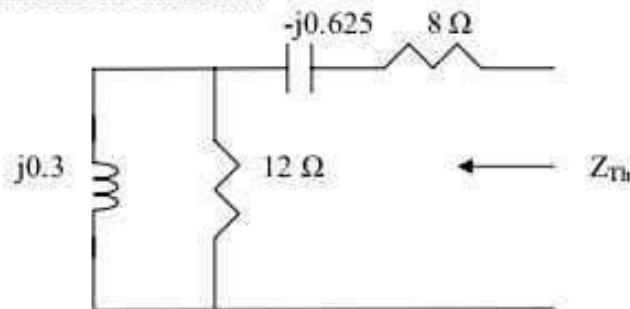To find  $\mathbf{Z}_{Th}$ , consider the circuit below.




$$\mathbf{Z}_{Th} = 8 - j0.625 + 12 // j0.3 = 8 - j0.625 + \frac{12 \times j0.3}{12 + j0.3} = 8.0075 - j0.3252$$

$$\mathbf{Z}_L = (\mathbf{Z}_{Th})^* = \underline{\underline{8.008 + j0.3252 \Omega}}$$

### Chapter 11, Problem 19.

The variable resistor  $R$  in the circuit of Fig. 11.50 is adjusted until it absorbs the maximum average power. Find  $R$  and the maximum average power absorbed.

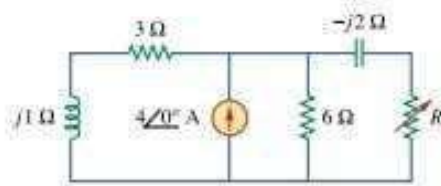

**Figure 11.50**  
For Prob. 11.19.

### Chapter 11, Solution 19.

At the load terminals,

$$Z_{Th} = -j2 + 6 \parallel (3 + j) = -j2 + \frac{(6)(3 + j)}{9 + j}$$

$$Z_{Th} = 2.049 - j1.561$$

$$R_L = |Z_{Th}| = \underline{2.576\Omega}$$

To get  $V_{Th}$ , let  $Z = 6 \parallel (3 + j) = 2.049 + j0.439$ .

By transforming the current sources, we obtain

$$V_{Th} = (4\angle 0^\circ)Z = 8.196 + j1.756$$

$$P_{max} = \left| \frac{8.382}{2.049 - j1.561 + 2.576} \right|^2 \frac{2.576}{2} = \underline{3.798 \text{ W}}$$